


Final Exam

(December 12th @ 7:00 pm)

Presentation and clarity are very important! Show your procedure!

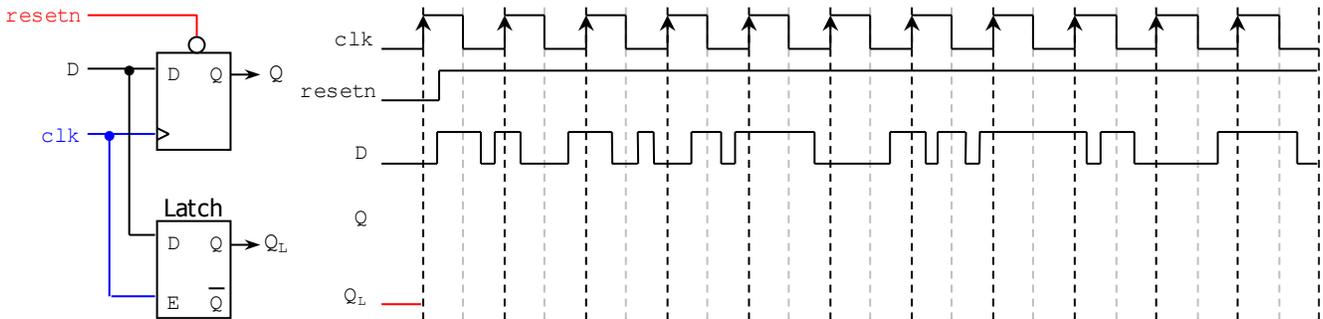
PROBLEM 1 (18 PTS)

- Complete the timing diagram of the circuit shown below. (8 pts)




- Complete the timing diagram of the following bit-serial adder. $DX=1001$, $DY=1110$. (10 pts)

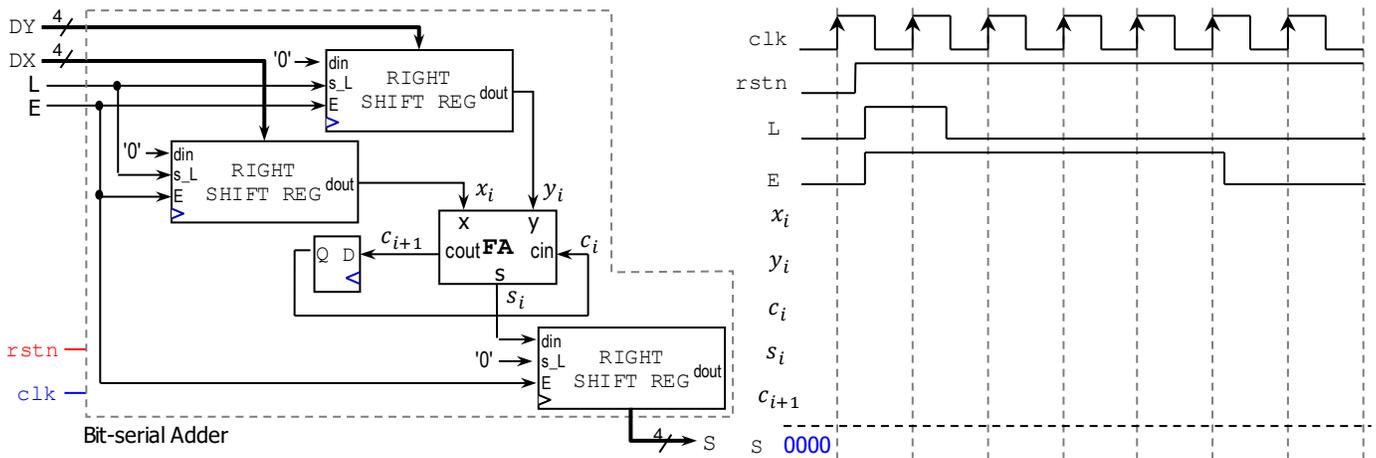✓ This circuit includes three 4-bit parallel access shift registers, a flip flop, and a full adder.



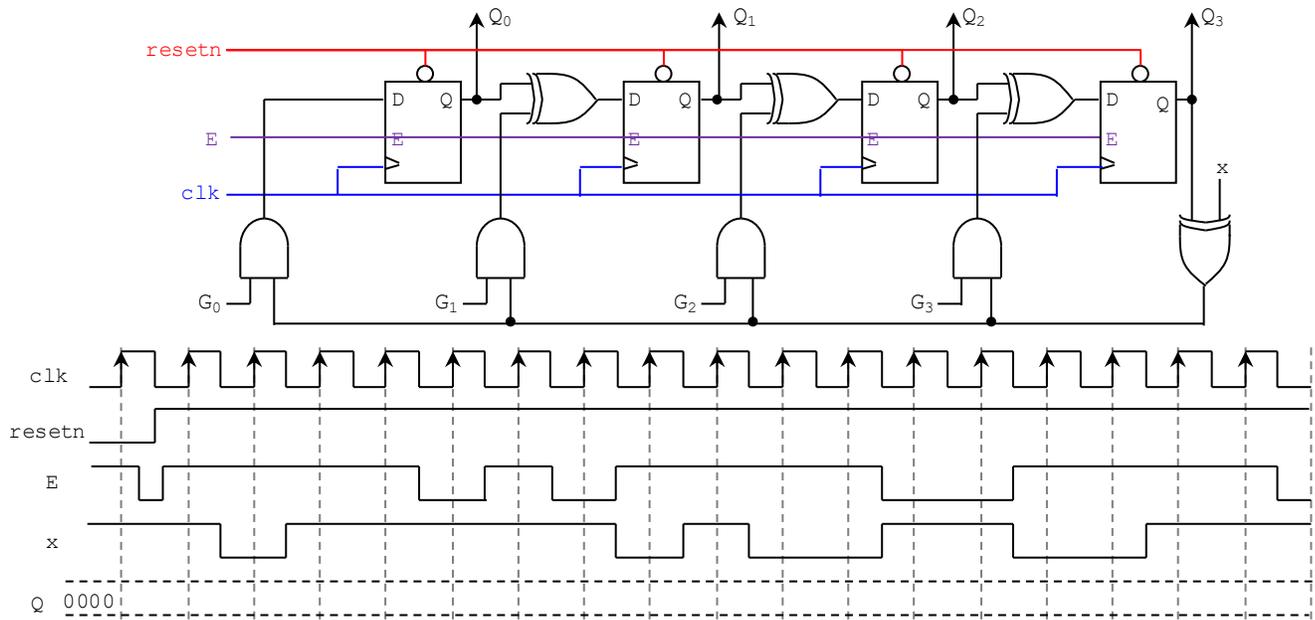
PROBLEM 2 (13 PTS)

- Complete the timing diagram of the following circuit. $G = G_3G_2G_1G_0 = 1001$, $Q = Q_3Q_2Q_1Q_0$



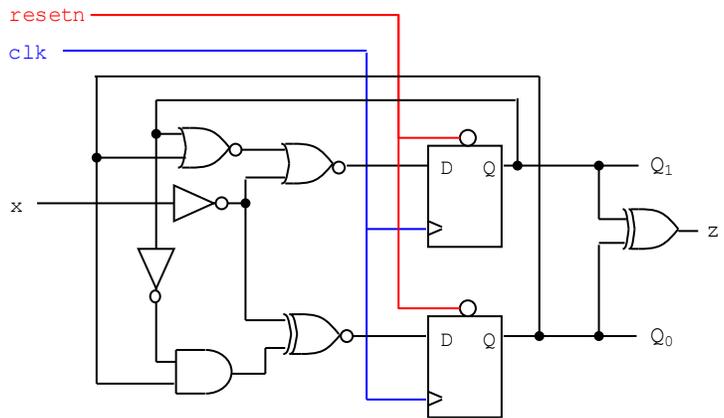
PROBLEM 3 (13 PTS)

- Given the following circuit that represents a Finite State Machine, provide: (12 pts)
 - ✓ Excitation equations and output Boolean equation.
 - ✓ Excitation Table, State Table.
 - ✓ State Diagram (any representation).
- Is this a Mealy or a Moore Machine? (1 pt.)



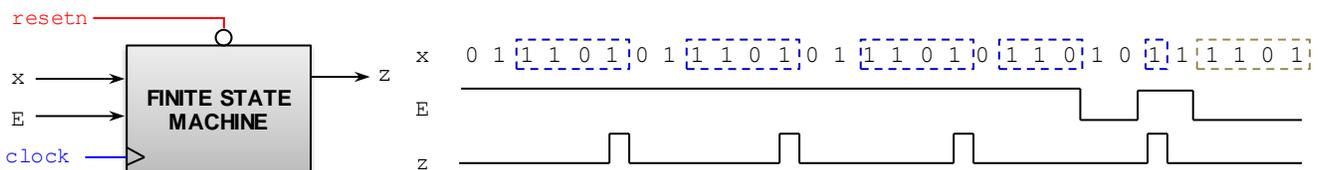PROBLEM 4 (16 PTS)

- Sequence detector: The machine generates $z = 1$ when it detects the sequence 1101. Once the sequence is detected, the circuit looks for a new sequence.
- The signal E is an input enable: It validates the input x , i.e., if $E=1$, x is valid, otherwise x is not valid.



- Draw the State Diagram (any representation) of this circuit with inputs E and x and output z . (7 pts.)
- Complete the State Table and the Excitation Table. (8 pts.)
- Is this a Mealy or a Moore machine? Why?

PROBLEM 5 (18 PTS)

- “Counting 0’s” Circuit: It counts the number of bits in register *A* that has the value of ‘0’.
- ✓ Example: for $n = 8$: if $A = 00110010$, then $C = 0101$.
- ✓ The behavior (on the clock tick) of the generic components is as follows:

m-bit counter (modulo- $n+1$): If $E=0$, the count stays.

```




if E = 1 then
  if sclr = 1 then
    Q ← 0
  else
    Q ← Q+1
  end if;
end if;
    
```

n-bit Parallel access shift register: If $E=0$, the output is kept.

```

if E = 1 then
  if s_l = '1' then
    Q ← D
  else
    Q ← shift in 'din' (to the right)
  end if;
end if;
    
```

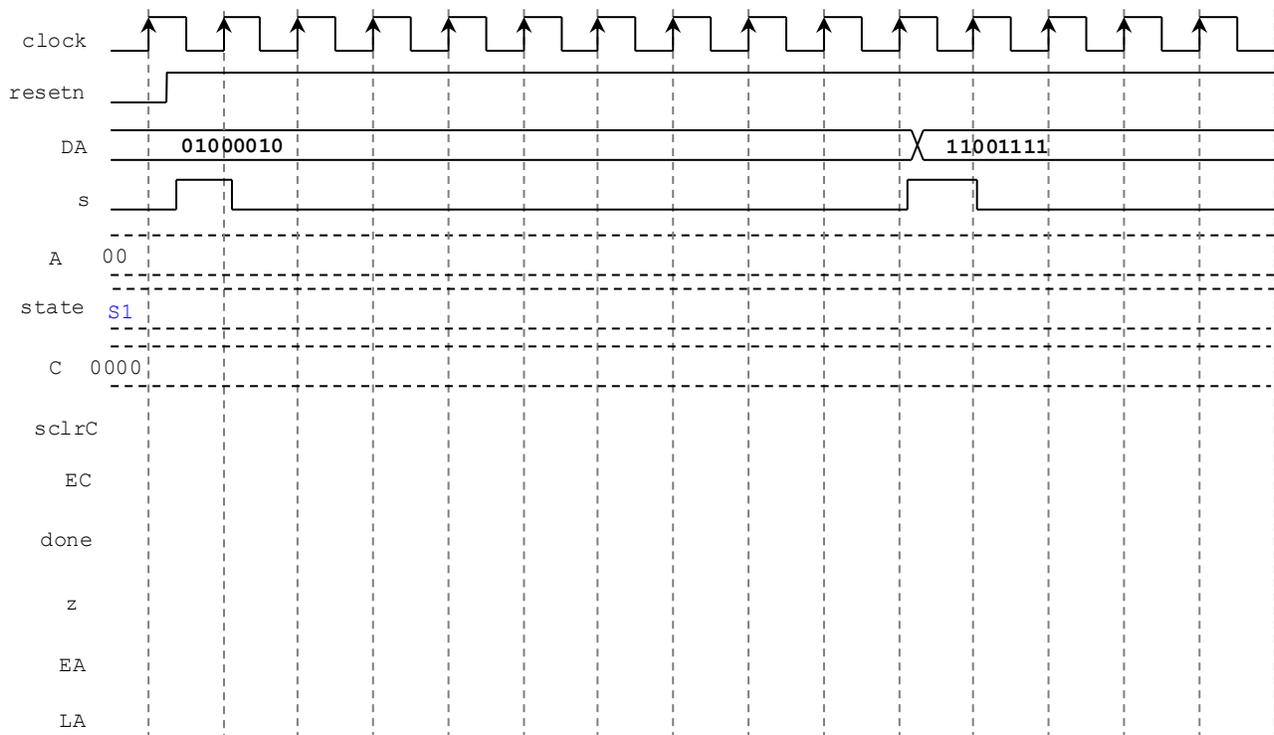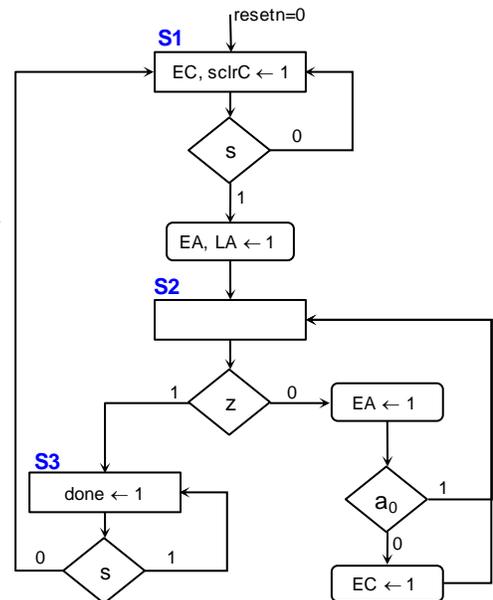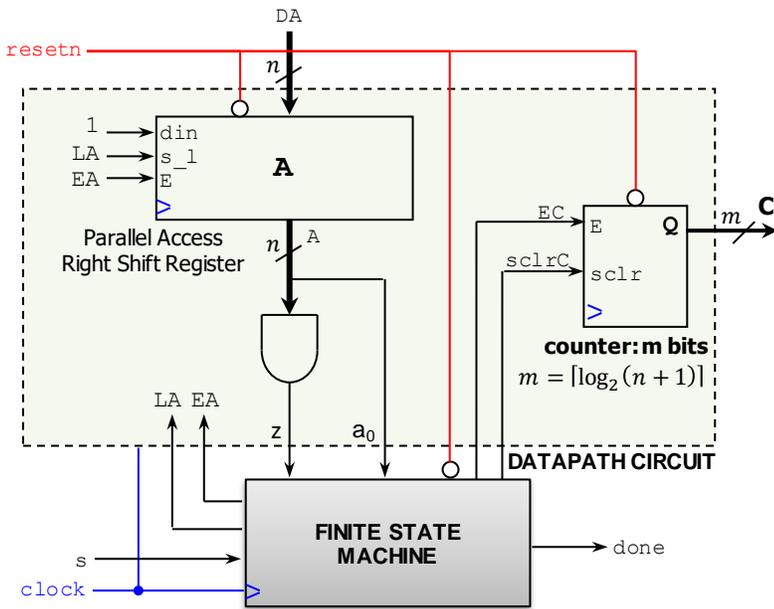- Complete the timing diagram where $n = 8, m = 4$. *A* is represented in hexadecimal format, while *C* is in binary format.



PROBLEM 6 (22 PTS)

- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. (6 pts)
- Provide the State Table and the Excitation Table. Is it a Mealy or a Moore FSM? (6 pts).
- Provide the excitation equations and the Boolean output equations (simplify your circuit: K-maps or Quine-McCluskey).
- Sketch the circuit. (3 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
    port ( clk, rstn: in std_logic;
          a, b: in std_logic;
          x, z: out std_logic);
end circ;
```

```
architecture behavioral of circ is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (rstn, clk, a, b)
    begin
        if rstn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if a = '1' then
                        y <= S2;
                    else
                        if b = '1' then y <= S3; else y <= S1; end if;
                    end if;
                when S2 =>
                    if b = '1' then y <= S2; else y <= S1; end if;
                when S3 =>
                    if b = '1' then y <= S3; else y <= S1; end if;
            end case;
        end if;
    end process;

    Outputs: process (y, a, b)
    begin
        x <= '0'; z <= '0';
        case y is
            when S1 => if a = '0' then z <= '1'; end if;
            when S2 => x <= '1';
            when S3 => if a = '0' then x <= '1'; end if;
        end case;
    end process;
end behavioral;
```