



5 DIGIT LOCK SAFE

KARAMA ALKEILANI

HEELOS ALMOOSAWI

KYLE BUDZYNOWSKI


DEREK SMITH

OUR CIRCUIT & SPECS

- The circuit created here can store a 5 digit 4 bit integer in 5 separate register locations that are combined into one RAM module.
- After the code is stored the circuit will display either a U on the 7 segment display if the correct code is input, or an E if the incorrect code is input.
- One of the RGB LEDs also displays green or red depending on if the correct code is input.


COMPONENTS

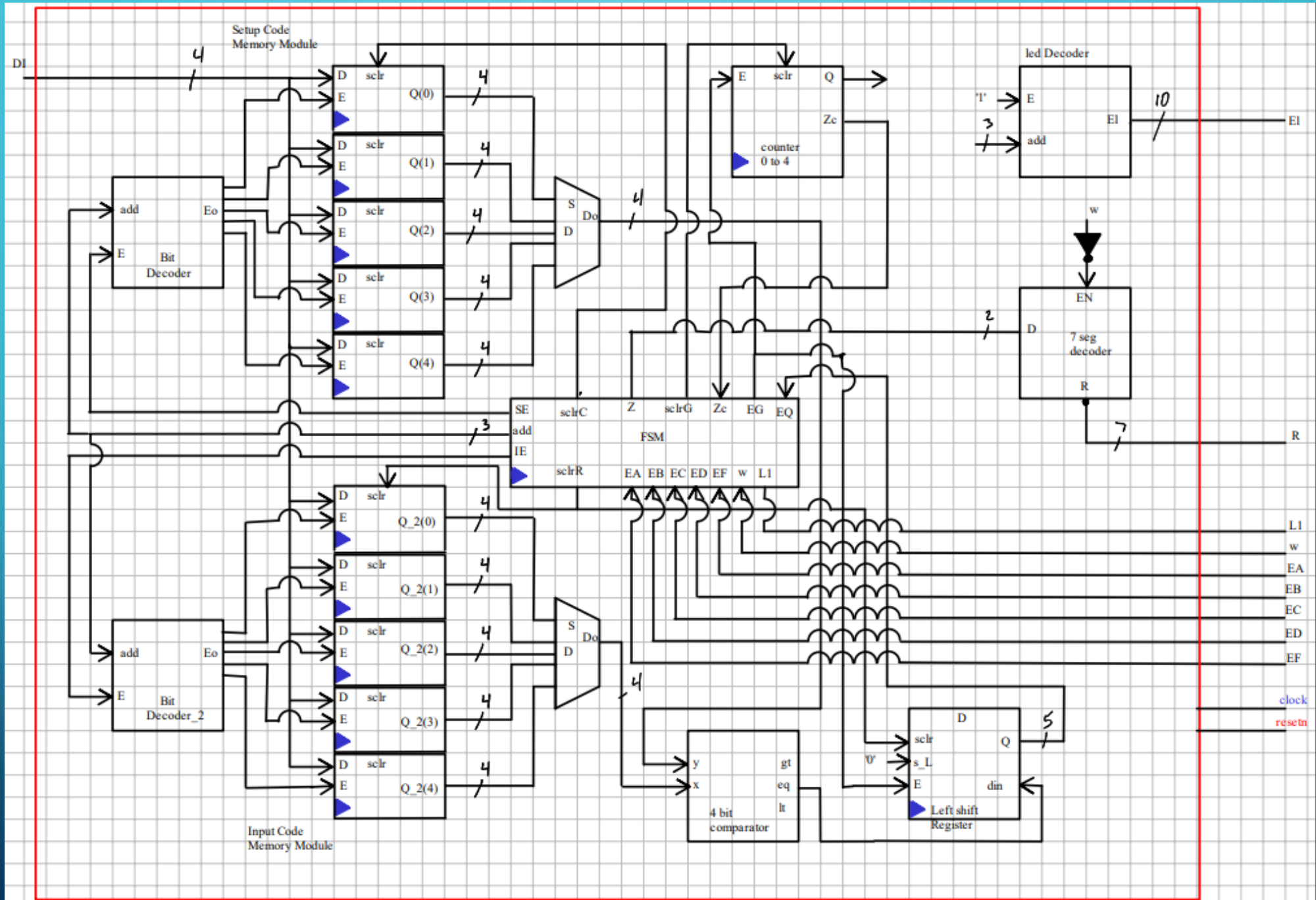- Decoders x 3
- FSM
- 5 Location 4 bit RAM Modules x 2
- Multiplexer x 3
- 7-SEG Decoder
- Left Shift Register
- 4 Bit Comparator




5 LOCATION 4 BIT RAM MODULES

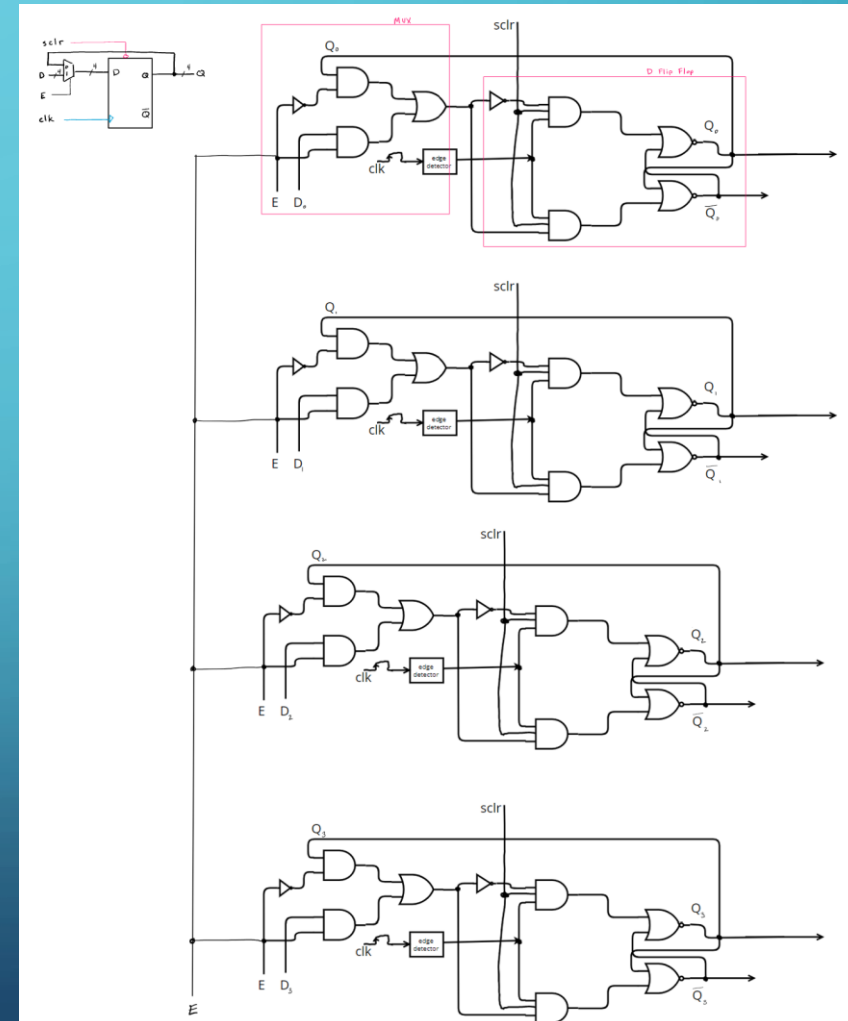- Inputs:
 - D (4 bits) DATA IN
 - E
 - Resetn
 - Sclr
 - clock
- Outputs:
 - Q(n)



DECODER

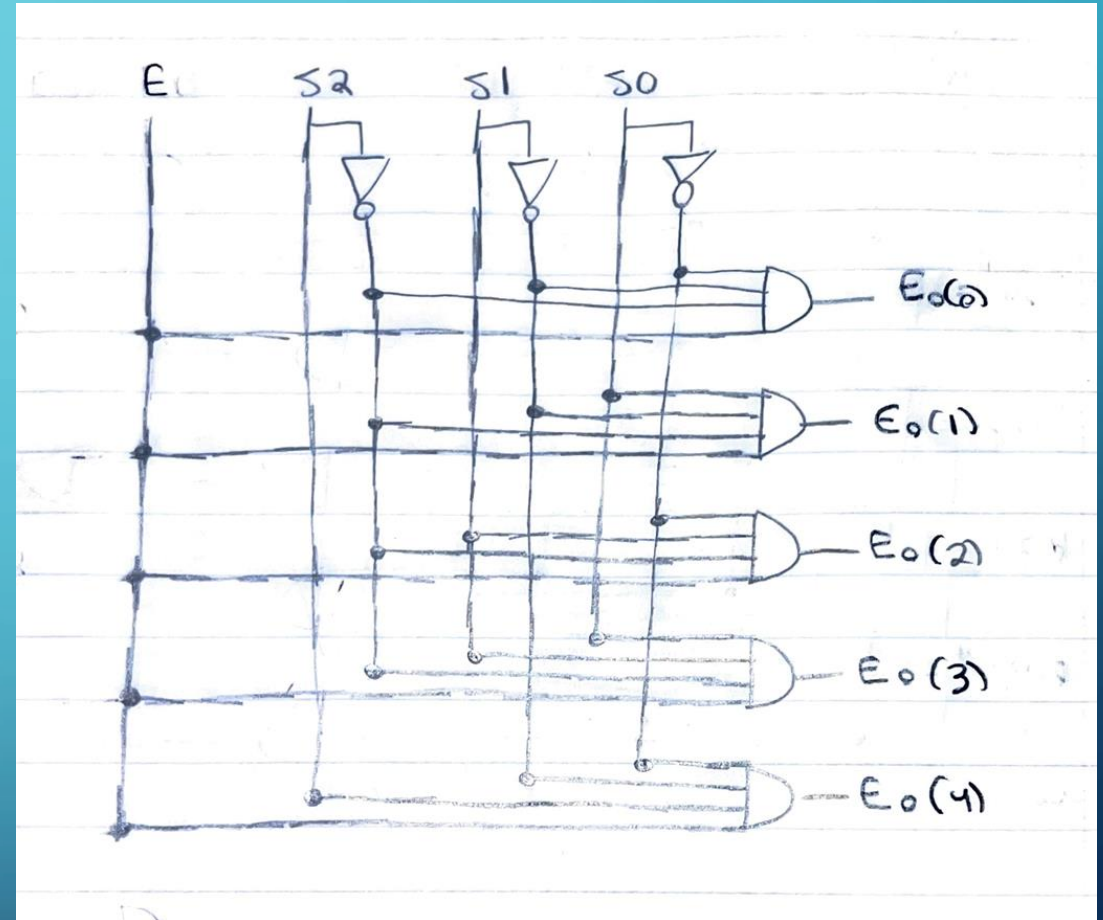- Inputs:
 - Add (3 bits)
 - E (w)
- Outputs:
 - E_o (input E for register enable, 5 bits)






4 BIT COMPARATOR


- Inputs:

- X (Combination Code)
- Y (Unlocking Code)
- G_{in} , L_{in}

- Outputs:

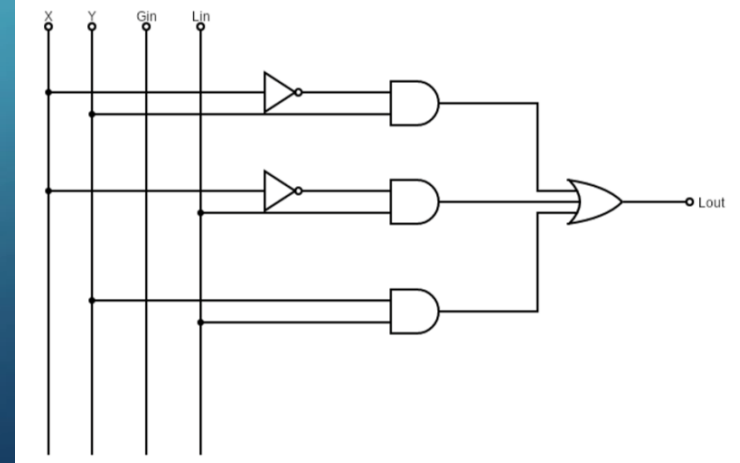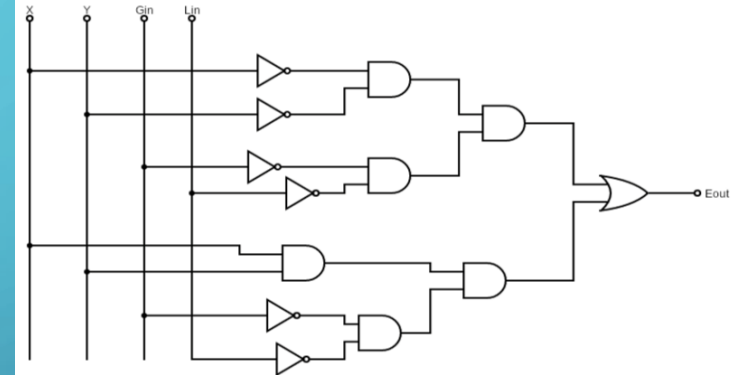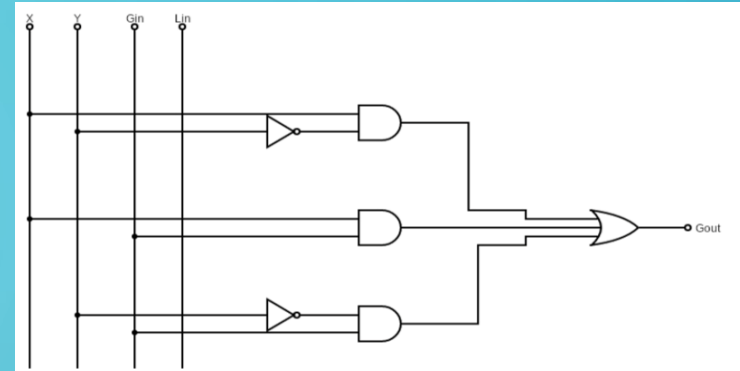
- G_{out} , L_{out}
- E_{out} (indicates matching code)



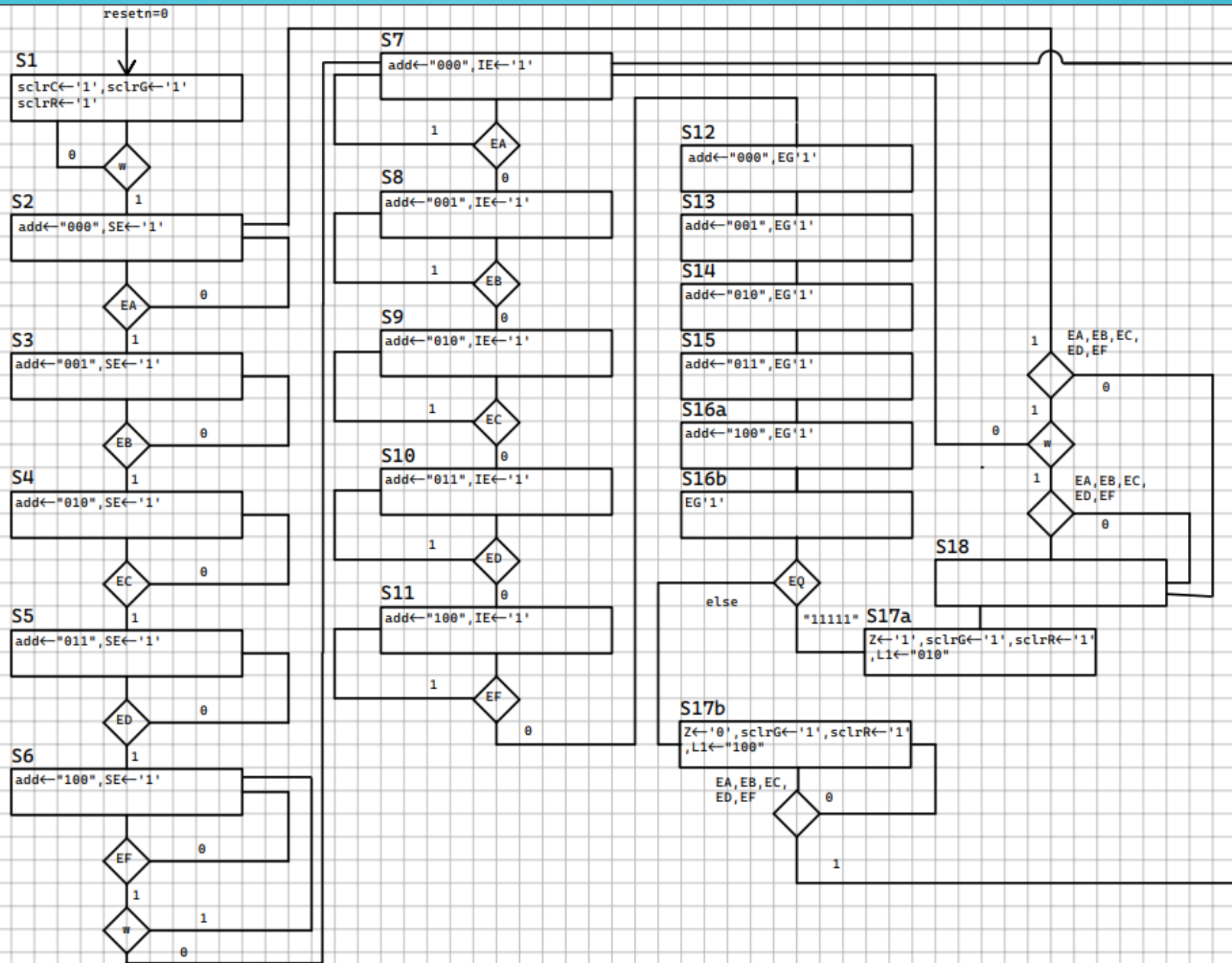


MULTIPLEXER

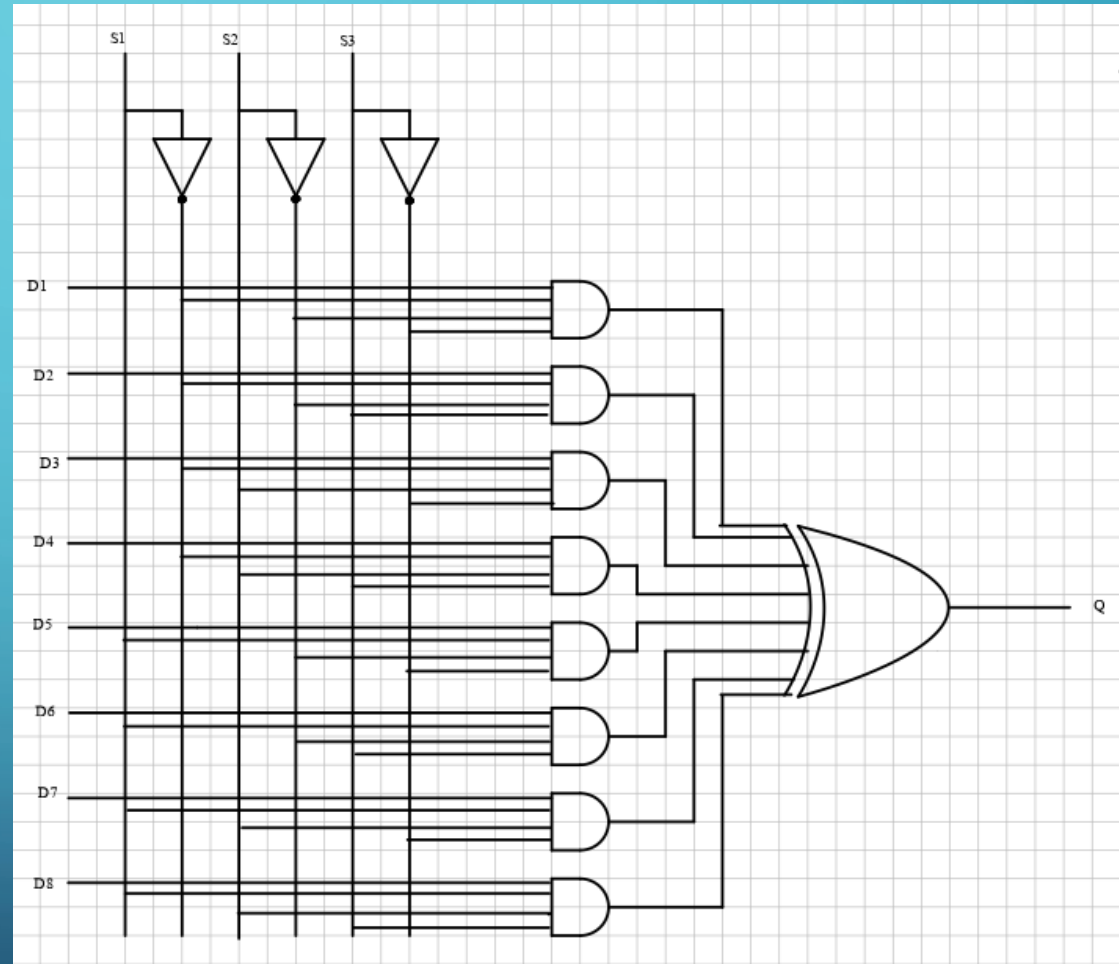- Inputs:
 - E (AKA W)
 - D (from Q(n) from register)
- Outputs:
 - Q




LEFT SHIFT REGISTER

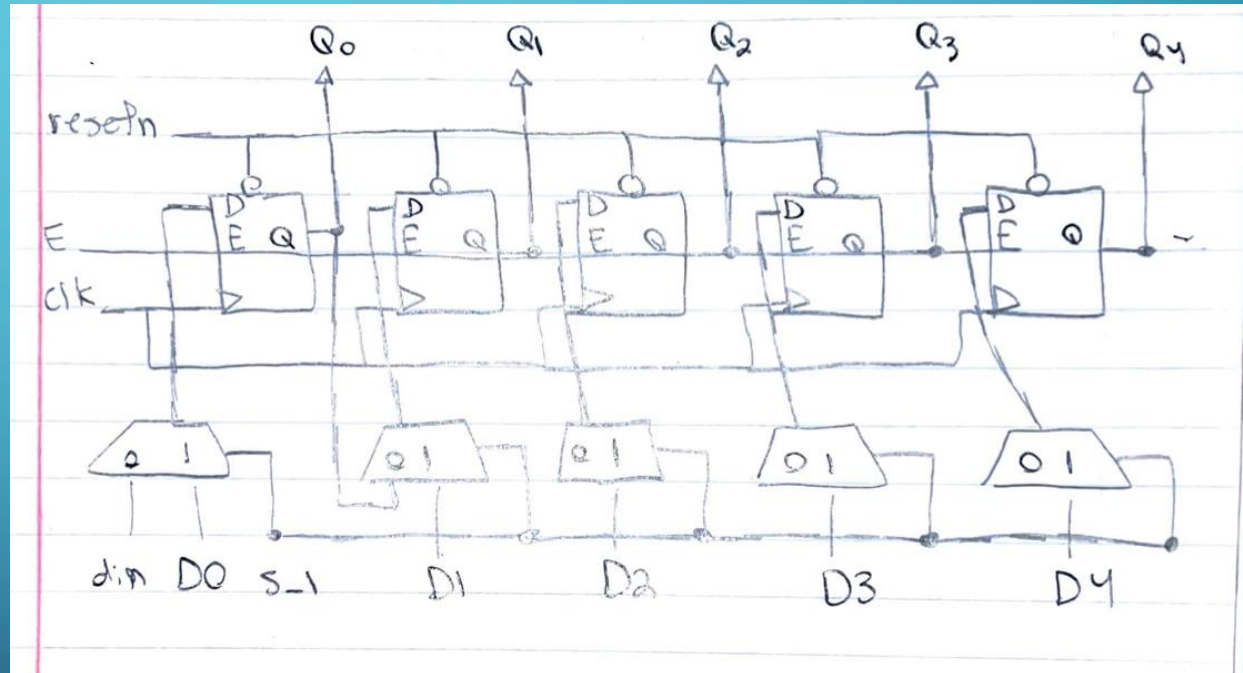- Inputs:
 - Clock
 - Resetn
 - Din, E, sclr, s_l
 - D
- Outputs:
 - Qpss
 - Shiftout




7 SEG DECODER

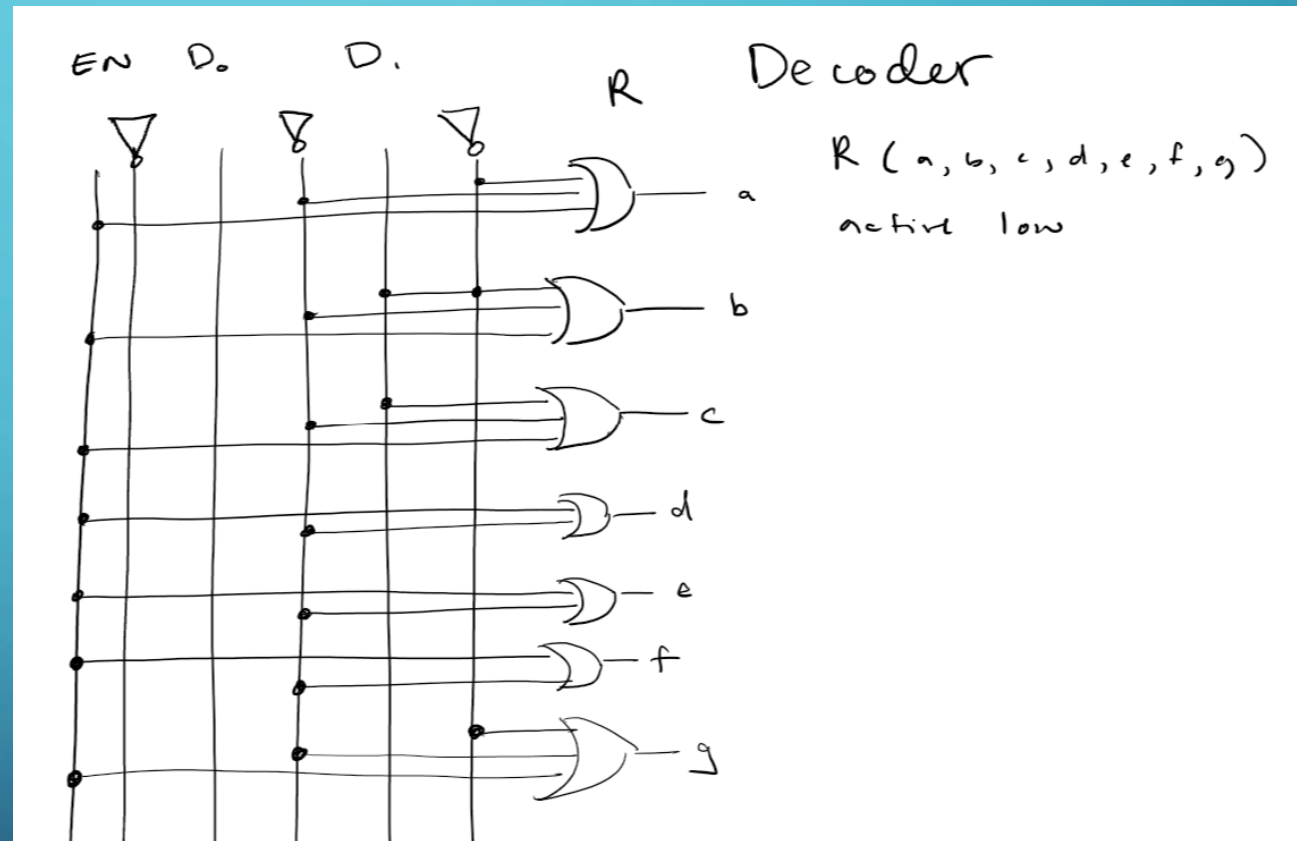- Inputs:
 - EN (Not w)
 - D
- Outputs:
 - R



SIMULATION

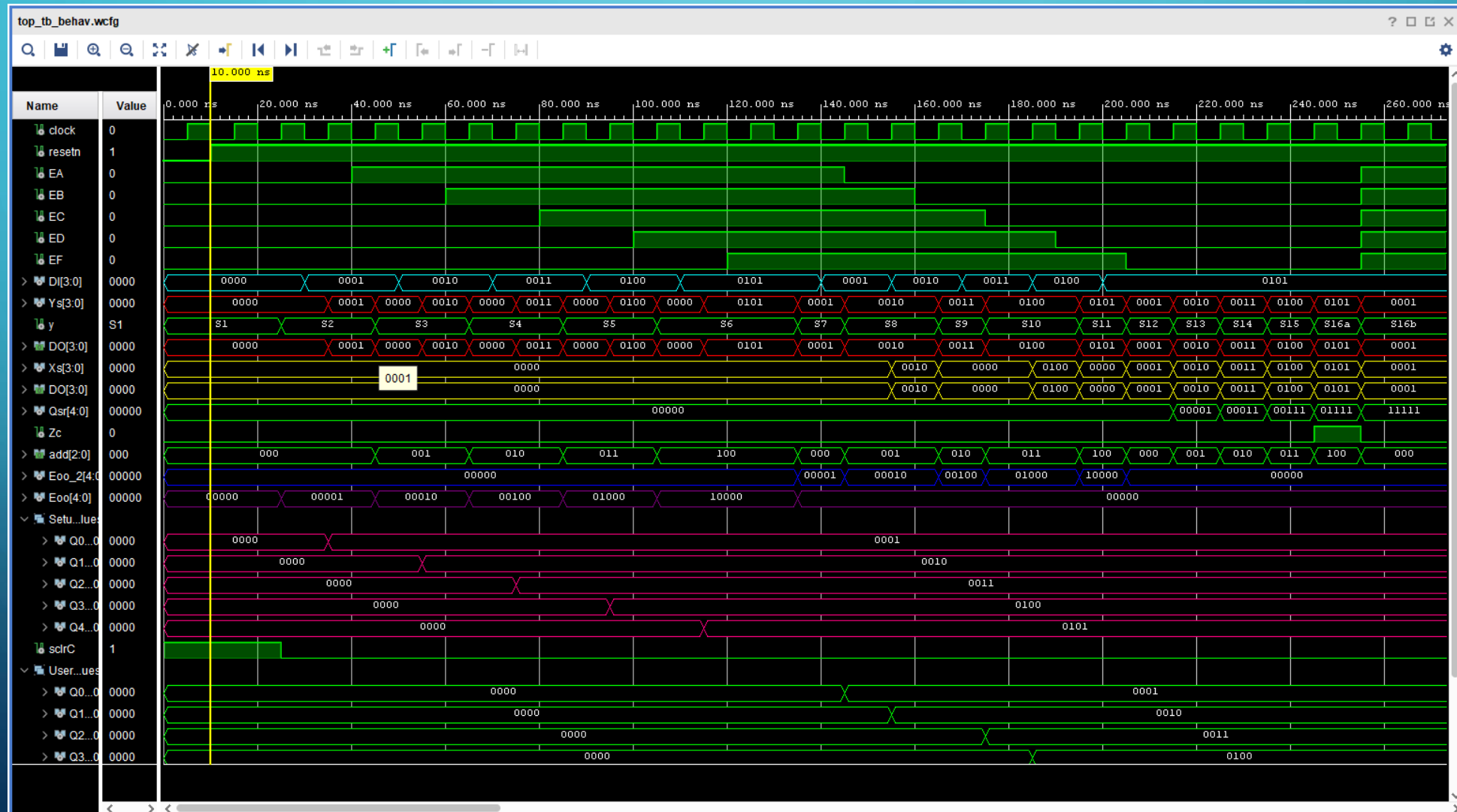

DEMO

