


# Homework 3

(Due date: November 2<sup>nd</sup> @ 11:59 pm)


Presentation and clarity are very important! Show your procedure!
 
## PROBLEM 1 (12 PTS)

- Complete the timing diagram of the circuit shown below. (7 pts)




 - Complete the timing diagram of the circuit shown below: (5 pts)



 
## PROBLEM 2 (16 PTS)

- Complete the timing diagram of the circuit shown below. Get the excitation equation for Q. (6 pts)



 
- Complete the timing diagram of the circuit shown below: (10 pts)



 **PROBLEM 3 (16 PTS)**

- With a D flip flop and logic gates, sketch the circuit whose excitation equation is given by:  
 $Q(t+1) \leftarrow \bar{y}Q(t) + x\bar{Q}(t)$  (4 pts)

- Given the following circuit, get the excitation equations for each flip flop output  $Q = Q_3Q_2Q_1Q_0$  (6 pts)



- Complete the timing diagram of the circuit whose VHDL description is shown below. Also, get the excitation equation for  $q$ .


```

library ieee;
use ieee.std_logic_1164.all;

entity circ is
port (clrn, clk,x,a: in std_logic;
      q: out std_logic);
end circ;

architecture t of circ is
    signal qt: std_logic;
begin
    process (clrn, clk, x, a)
    begin
        if clrn = '0' then
            qt <= '0';
        else
            if (clk'event and clk = '1') then
                if x = '1' then
                    qt <= a xnor qt;
                end if;
            end if;
        end process;
        q <= qt;
    end t;


```

 

$q(t+1) \leftarrow$

 
**PROBLEM 4 (15 PTS)**

- Given the following circuit, complete the timing diagram (signals  $DO$ ,  $Q$  and  $DATA$ ).  
 The LUT 6-to-6 implements the following function:  $OLUT = [ILUT^{0.85}]$ , where  $ILUT$  is an unsigned number.  
 For example:  $ILUT = 35 (100011_2) \rightarrow OLUT = [35^{0.85}] = 21 (010101_2)$



 
**PROBLEM 5 (10 PTS)**

- Complete the timing diagram of the following 4-bit parallel access shift register with enable input. When  $E=1$ : If  $s\_1=0$  (shifting operation). If  $s\_1=1$  (parallel load). Note that  $Q = Q_3Q_2Q_1Q_0$ .  $D = D_3D_2D_1D_0$



 **PROBLEM 6 (23 PTS)**

- For the following circuit, we have  $Q = Q_3Q_2Q_1Q_0$ .  $P = P_3P_2P_1P_0$ 
  - Write structural VHDL code. Create two files: i) flip flop, ii) top file (where you will interconnect the flip flops and the logic gates). (10 pts)
  - Write a VHDL testbench according to the timing diagram shown below. Complete the timing diagram by simulating your circuit (Behavioral Simulation). The clock frequency must be 50 MHz with 50% duty cycle. (13 pts)
- Upload (as a .zip file) the following files to Moodle (an assignment will be created):
  - VHDL code files and testbench.
  - A screenshot of your simulation showing the results for Q (this is on top of you completing the timing diagram below).



### PROBLEM 7 (8 PTS)

- Attach your Project Status Report (no more than 1 page, single-spaced, 2 columns, only one submission per group). This report should contain the initial status of your project. For formatting, use the provided template (Final Project - Report Template.docx). The sections included in the template are the ones required in your Final Report. At this stage, you are only required to:
  - ✓ Include a (draft) project description and title.
  - ✓ Include a draft Block Diagram of your hardware architecture.
  
- As a guideline, the figure shows a simple Block Diagram. There are input and output signals, as well as internal components along with their interconnection.
  - ✓ At this stage, only a rough draft is required. There is no need to go into details: it is enough to show the tentative top-level components that would constitute your system as well as the tentative inputs and outputs.
  
- Only student is needed to attach the report (make sure to indicate all the team members).

