

Solutions - Homework 1

(Due date: September 21st @ 11:59 pm)

Presentation and clarity are very important! Show your procedure!

PROBLEM 1 (31 PTS)


- a) Simplify the following functions using ONLY Boolean Algebra Theorems. For each resulting simplified function, sketch the logic circuit using AND, OR, XOR, and NOT gates. (15 pts)

✓ $F = \overline{x} + x(y + \overline{z})$


✓ $F(x, y, z) = \prod(M_2, M_4, M_6, M_7)$

✓ $F = (z + \overline{y})(\overline{z} + x)(\overline{y} + x)$

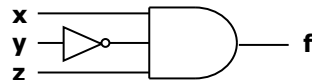
✓ $F = \overline{x(y + \overline{z})} + \overline{x} = \overline{x(y + \overline{z})}.x = (\overline{x} + \overline{y + \overline{z}}).x = (\overline{y + \overline{z}}).x = x\overline{y}z$



✓ $F(X, Y, Z) = \prod(M_2, M_4, M_6, M_7) = \sum(m_0, m_1, m_3, m_5) = \overline{X}\overline{Y}\overline{Z} + \overline{X}\overline{Y}Z + \overline{X}YZ + X\overline{Y}Z = \overline{X}\overline{Y} + \overline{X}YZ + X\overline{Y}Z$
 $F(X, Y, Z) = \overline{X}\overline{Y} + \overline{X}YZ + X\overline{Y}Z = \overline{X}(\overline{Y} + YZ) + X\overline{Y}Z = \overline{X}(\overline{Y} + Z) + X\overline{Y}Z = \overline{X}\overline{Y} + \overline{X}Z + X\overline{Y}Z$
 $F(X, Y, Z) = \overline{X}\overline{Y} + \overline{X}Z + X\overline{Y}Z = \overline{X}\overline{Y} + Z(\overline{X} + X\overline{Y}) = \overline{X}\overline{Y} + Z(\overline{X} + \overline{Y}) = \overline{X}\overline{Y} + Z\overline{X} + Z\overline{Y}$

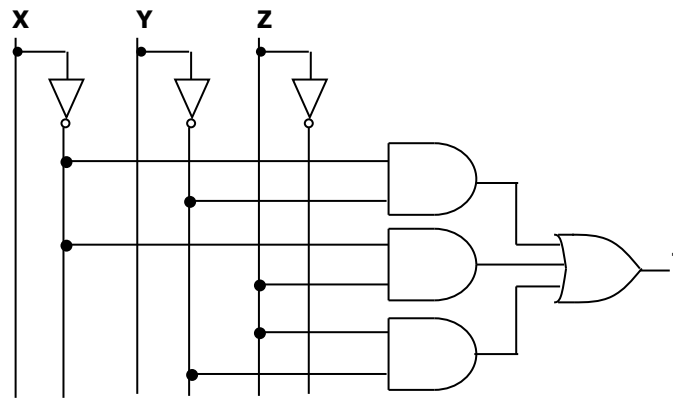

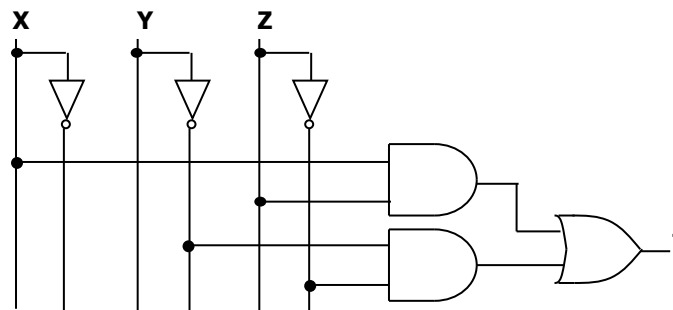✓ $F = (Z + \overline{Y})(\overline{Z} + X)(\overline{Y} + X) = (Z + \overline{Y})(\overline{Z} + X)$ (Consensus Theorem)
 $(Z + \overline{Y})(\overline{Z} + X) = \overline{Z}X + Z\overline{Y} + X\overline{Y} = Z\overline{Y} + X\overline{Y}$ (Consensus Theorem)



- b) Using Boolean Algebra Theorems, prove that: $x(y \oplus z) = (xy) \oplus (xz)$ (6 pts)

$x(y \oplus z) = x(\overline{y}z + y\overline{z}) = x\overline{y}z + xy\overline{z}$

$(xy) \oplus (xz) = \overline{xy}xz + xy\overline{xz} = (\overline{x} + \overline{y})xz + xy(\overline{x} + \overline{z}) = \overline{x}xz + \overline{y}xz + xy\overline{x} + xy\overline{z} = x\overline{y}z + xy\overline{z}$

$\therefore x(y \oplus z) = (xy) \oplus (xz)$

c) For the following Truth table with two outputs: (10 pts)

- Provide the Boolean functions using the Canonical Sum of Products (SOP), and Product of Sums (POS). (4 pts)
- Express the Boolean functions using the minterms and maxterms representations.
- Sketch the logic circuits as Canonical Sum of Products and Product of Sums. (4 pts)

x	y	z	f ₁	f ₂
0	0	0	1	1
0	0	1	0	0
0	1	0	1	0
0	1	1	1	1
1	0	0	1	0
1	0	1	0	1
1	1	0	1	1
1	1	1	0	1

Sum of Products

$$f_1 = \bar{x}\bar{y}\bar{z} + \bar{x}y\bar{z} + \bar{x}yz + x\bar{y}\bar{z} + xy\bar{z}$$



$$f_2 = \bar{x}\bar{y}\bar{z} + \bar{x}yz + x\bar{y}z + xy\bar{z} + xyz$$

Product of Sums

$$f_1 = (X + Y + \bar{Z})(\bar{X} + Y + \bar{Z})(\bar{X} + \bar{Y} + \bar{Z})$$

$$f_2 = (X + Y + \bar{Z})(X + \bar{Y} + Z)(\bar{X} + Y + Z)$$

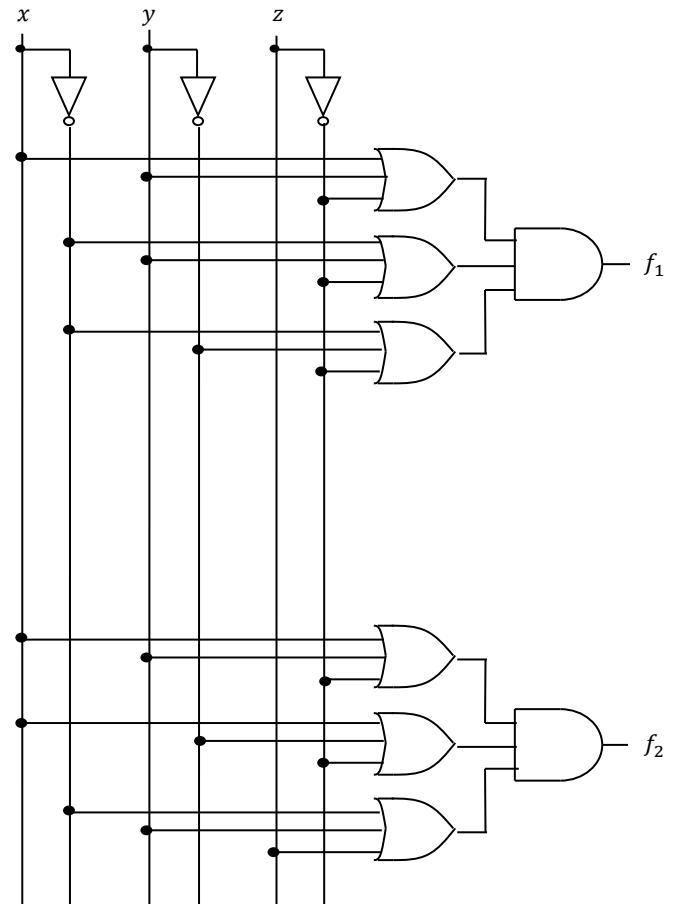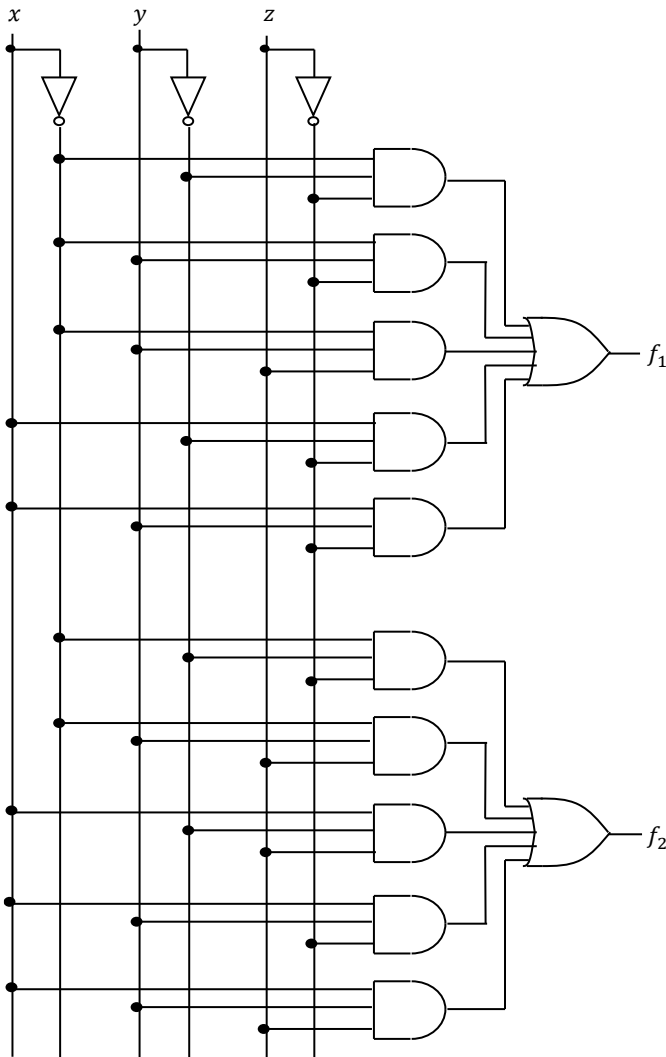Minterms and maxterms: $f_1 = \sum(m_0, m_2, m_3, m_4, m_6) = \prod(M_1, M_5, M_7).$
 $f_2 = \sum(m_0, m_3, m_5, m_6, m_7) = \prod(M_1, M_2, M_4).$



PROBLEM 2 (24 PTS)

- a) The following is the timing diagram of a logic circuit with 3 inputs. Sketch the logic circuit that generates this waveform. Then, complete the VHDL code. (8 pts)

```
library ieee;
use ieee.std_logic_1164.all;



entity wave is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end wave;

architecture struct of wave is
  signal x: std_logic;
begin
  x <= not(c) and a;
  f <= (b and c) or x;
end struct;
```

a	b	c	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

c	ab			
	00	01	11	10
0	0	0	1	1
1	0	1	1	0

$f = bc + a\bar{c}$

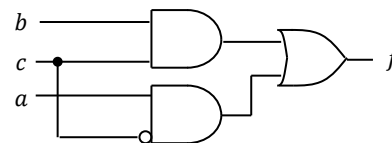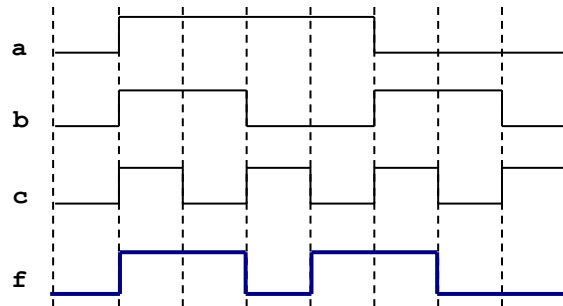


- b) Complete the timing diagram of the logic circuit whose VHDL description is shown below: (5 pts)



```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end circ;

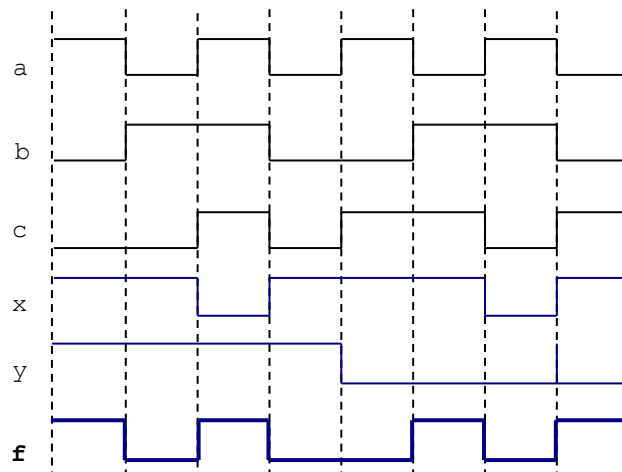
architecture struct of circ is
  signal x, y: std_logic;
begin
  f <= y xor (not a);
  x <= a nand b;
  y <= x xnor (not c);
end struct;
```



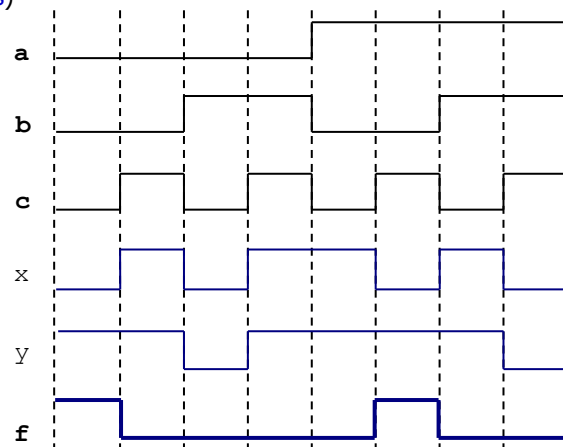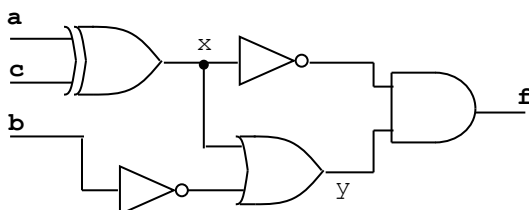- c) Complete the timing diagram of the following circuit: (5 pts)



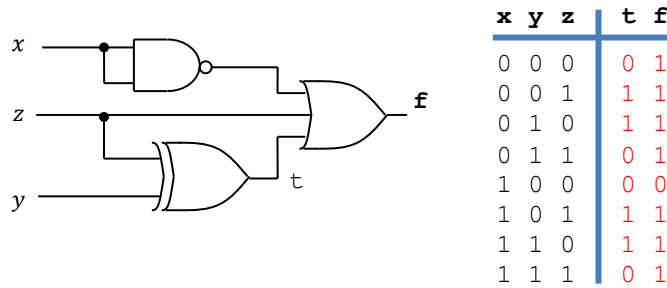
d) Complete the truth table describing the output of the following circuit and write the simplified Boolean equation (6 pts).



$$f = \bar{x} + y + z$$


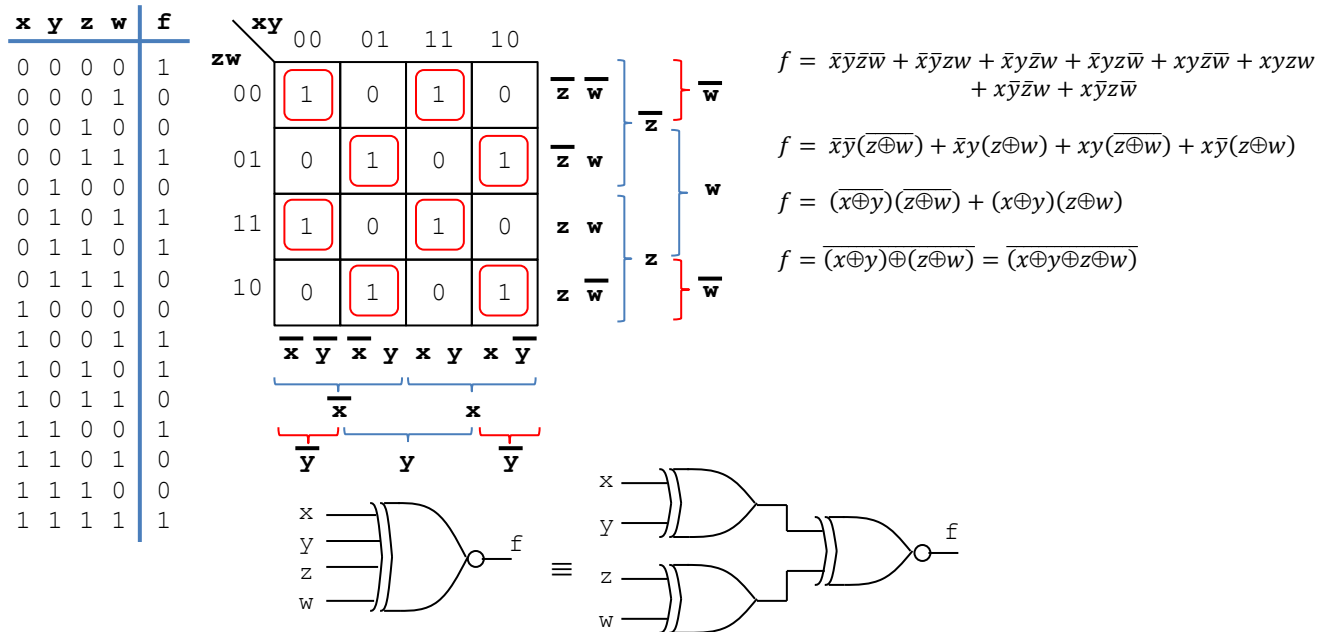
PROBLEM 3 (10 PTS)

- Complete the truth table for a circuit with 4 inputs x, y, z, w that activates an output ($f = 1$) when the number of 1's in the inputs is even. For example: If $xyzw = 1100 \rightarrow f = 1$. If $xyzw = 1011 \rightarrow f = 0$.
- Design (provide the simplified Boolean equation for f and sketch the logic circuit).




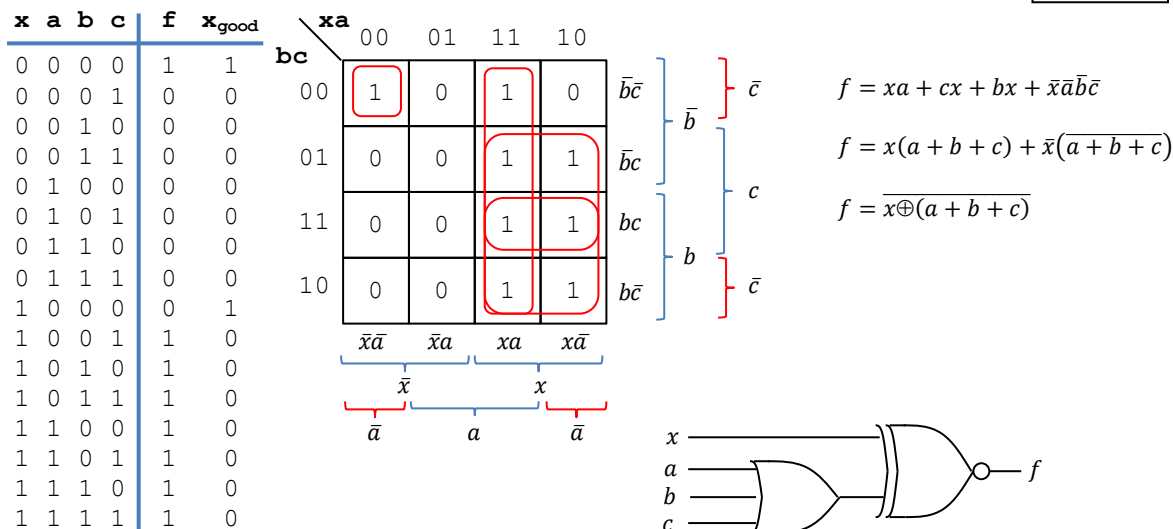
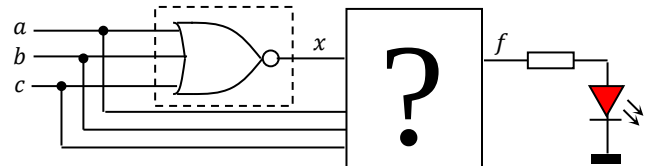
PROBLEM 4 (11 PTS)

- Design a circuit (simplify your circuit) that verifies the logical operation of a 3-input NOR gate. $f = '1'$ (LED ON) if the NOR gate does NOT work properly. Assumption: when the NOR gate is not working, it generates 1's instead of 0's and vice versa.



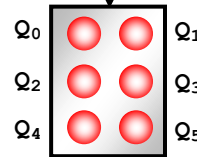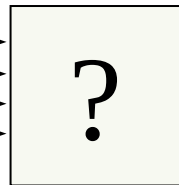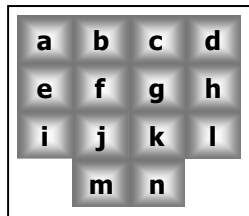PROBLEM 5 (25 PTS)

- A 14-letter keypad produces a 4-bit code as shown in the table. We want to design a logic circuit that converts those 4-bit codes to Braille code, where the 6 dots are represented by LEDs. A raised (or embossed) dot is represented by an LED ON (logic value of '1'). A missing dot is represented by a LED off (logic value of '0').
- ✓ Complete the truth table for each output (Q_0 - Q_5). (4 pts)
- ✓ Provide the simplified expression for each output (Q_0 - Q_5). Use Karnaugh maps for Q_3 , Q_2 , Q_0 and the Quine-McCluskey algorithm for Q_5 , Q_4 , Q_1 . Note it is safe to assume that the codes 1110 and 1111 will not be produced by the keypad.



x	y	z	w	Letter
0	0	0	0	a
0	0	0	1	b
0	0	1	0	c
0	0	1	1	d
0	1	0	0	e
0	1	0	1	f
0	1	1	0	g
0	1	1	1	h
1	0	0	0	i
1	0	0	1	j
1	0	1	0	k
1	0	1	1	l
1	1	0	0	m
1	1	0	1	n
1	1	1	0	
1	1	1	1	

a	b	c	d	e	f	g	h	i	j	k	l	m	n
● ○	● ○	● ●	● ●	● ○	● ●	● ●	● ○	○ ●	○ ●	● ○	● ○	● ●	● ●
○ ○	● ○	○ ○	○ ●	○ ●	● ○	● ●	● ●	● ○	● ●	○ ○	● ○	○ ○	○ ●
○ ○	○ ○	○ ○	○ ○	○ ○	○ ○	○ ○	○ ○	○ ○	○ ○	● ○	● ○	● ○	● ○

x	y	z	w	Q_5	Q_4	Q_3	Q_2	Q_1	Q_0	Letter
0	0	0	0	0	0	0	0	0	1	a
0	0	0	1	0	0	0	1	0	1	b
0	0	1	0	0	0	0	0	1	1	c
0	0	1	1	0	0	1	0	1	1	d
0	1	0	0	0	0	1	0	0	1	e
0	1	0	1	0	0	0	1	1	1	f
0	1	1	0	0	0	1	1	1	1	g
0	1	1	1	0	0	1	1	0	1	h
1	0	0	0	0	0	0	1	1	0	i
1	0	0	1	0	0	1	1	1	0	j
1	0	1	0	0	1	0	0	0	1	k
1	0	1	1	0	1	0	1	0	1	l
1	1	0	0	0	1	0	0	1	1	m
1	1	0	1	0	1	1	0	1	1	n
1	1	1	0	X	X	X	X	X	X	
1	1	1	1	X	X	X	X	X	X	

Q_3	xy	00	01	11	10
zw	00	0	1	0	0
	01	0	0	1	1
	11	1	1	X	0
	10	0	1	X	0

Q_2	xy	00	01	11	10
zw	00	0	0	0	1
	01	1	1	0	1
	11	0	1	X	1
	10	0	1	X	0

Q_0	xy	00	01	11	10
zw					
00		1	1	1	0
01		1	1	1	0
11		0	1	X	1
10		1	1	X	1

$$\begin{aligned}
 Q_5 &= 0 \\
 Q_4 &= xz + xy \\
 Q_3 &= \bar{x}y\bar{w} + \bar{x}zw + x\bar{z}w \\
 Q_2 &= yz + \bar{x}\bar{z}w + x\bar{y}\bar{z} + x\bar{y}w \\
 Q_1 &= \bar{x}\bar{y}z + y\bar{z}w + \bar{x}z\bar{w} + x\bar{z} \\
 Q_0 &= \bar{x} + y + z
 \end{aligned}$$

▪ $Q_4 = \sum m(10,11,12,13) + \sum d(14,15).$

Number of ones	4-literal implicants	3-literal implicants	2-literal implicants	1-literal implicant
2	$m_{10} = 1010 \checkmark$ $m_{12} = 1100 \checkmark$	$m_{10,11} = 101- \checkmark$ $m_{10,14} = 1-10 \checkmark$ $m_{12,13} = 110- \checkmark$ $m_{12,14} = 11-0 \checkmark$	$m_{10,11,14,15} = 1-1-$ $m_{10,14,11,15} = 1-1-$ $m_{12,13,14,15} = 11--$ $m_{12,14,13,15} = 11--$	We can't combine any further, so we stop here
3	$m_{11} = 1011 \checkmark$ $m_{13} = 1101 \checkmark$ $m_{14} = 1110 \checkmark$	$m_{11,15} = 1-11 \checkmark$ $m_{13,15} = 11-1 \checkmark$ $m_{14,15} = 111- \checkmark$		
4	$m_{15} = 1111 \checkmark$			

Prime Implicants		Minterms			
		10	11	12	13
$m_{10,11,14,15}$	xz	X	X		
$m_{12,13,14,15}$	xy			X	X

$\rightarrow Q_4 = xz + xy$

▪ $Q_1 = \sum m(2,3,5,6,8,9,12,13) + \sum d(14,15).$

Number of ones	4-literal implicants	3-literal implicants	2-literal implicants	1-literal implicant
1	$m_2 = 0010 \checkmark$ $m_8 = 1000 \checkmark$	$m_{2,3} = 001-$ $m_{2,6} = 0-10$ $m_{8,9} = 100- \checkmark$ $m_{8,12} = 1-00 \checkmark$	$m_{8,9,12,13} = 1-0-$ $m_{8,12,9,13} = 1-0-$ $m_{12,14,13,15} = 11--$ $m_{12,13,14,15} = 11--$	We can't combine any further, so we stop here
2	$m_3 = 0011 \checkmark$ $m_5 = 0101 \checkmark$ $m_6 = 0110 \checkmark$ $m_9 = 1001 \checkmark$ $m_{12} = 1100 \checkmark$	$m_{5,13} = -101$ $m_{6,14} = -110$ $m_{9,13} = 1-01 \checkmark$ $m_{12,13} = 110- \checkmark$ $m_{12,14} = 11-0 \checkmark$		
3	$m_{13} = 1101 \checkmark$ $m_{14} = 1110 \checkmark$	$m_{13,15} = 11-1 \checkmark$ $m_{14,15} = 111- \checkmark$		
4	$m_{15} = 1111 \checkmark$			

$Q_1 = \bar{x}\bar{y}z + \bar{x}z\bar{w} + y\bar{z}w + yz\bar{w} + x\bar{z} + xy$

Prime Implicants		Minterms							
		2	3	5	6	8	9	12	13
$m_{2,3}$	$\bar{x}\bar{y}z$	X	X						
$m_{2,6}$	$\bar{x}z\bar{w}$	X			X				
$m_{5,13}$	$y\bar{z}w$			X					X
$m_{6,14}$	$yz\bar{w}$				X				
$m_{8,9,12,13}$	$x\bar{z}$					X	X	X	X
$m_{12,14,13,15}$	xy							X	X

$\rightarrow Q_1 = \bar{x}\bar{y}z + y\bar{z}w + x\bar{z} + \bar{x}z\bar{w}$