






- b) Perform the binary operation of these numbers, where numbers are represented in 2's complement. Indicate every carry from  $c_0$  to  $c_n$ . Use the fewest number of bits to represent the summands and the result so that overflow is avoided. (8 pts)

✓  $30 - 47$

n = 7 bits

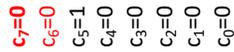

$c_7 \oplus c_6 = 0$

No Overflow


$$\begin{array}{r} 30 = 0011110 + \\ -47 = 1010001 \\ \hline \end{array}$$

$$-17 = 1101111$$

$30 - 47 = -17 \in [-2^6, 2^6-1] \rightarrow$  no overflow

- c) Perform binary multiplication of the following numbers that are represented in 2's complement arithmetic. (4 pts)


✓  $-9 \times 12$

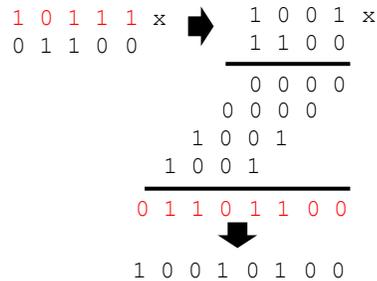


**PROBLEM 6 (17 PTS)**

- Given the following Boolean function:  $f(x, y, z) = \prod M(3,4)$ 
  - Provide the simplified expression for  $f$  and sketch this circuit using logic gates. (4 pts)

x	y	z	f
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

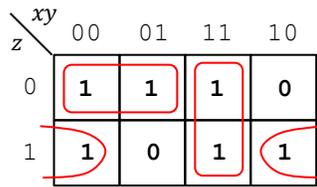

$f = xy + \bar{y}z + \bar{x}z$

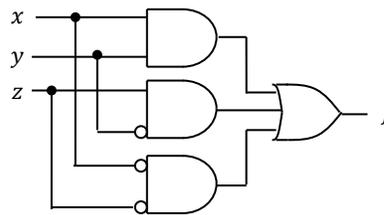

- Implement the previous circuit using ONLY 2-to-1 MUXs (AND, OR, NOT, XOR gates are not allowed). (13 pts)

$f(x, y, z) = \bar{x}f(0, y, z) + xf(1, y, z) = \bar{x}(\bar{y}z + \bar{z}) + x(y + \bar{y}z) = \bar{x}g(y, z) + xh(y, z)$

$g(y, z) = \bar{y}g(0, z) + yg(1, z) = \bar{y}(1) + y(\bar{z})$

$h(y, z) = \bar{y}h(0, z) + yh(1, z) = \bar{y}(z) + y(1)$

Also:  $\bar{z} = \bar{z}(1) + z(0)$

