

# Solutions - Quiz 1

(September 26<sup>th</sup> @ 5:30 pm)

## PROBLEM 1 (35 PTS)


- Complete the timing diagram of the logic circuit whose VHDL description is shown below:

```

library ieee;
use ieee.std_logic_1164.all;


entity test is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end test;

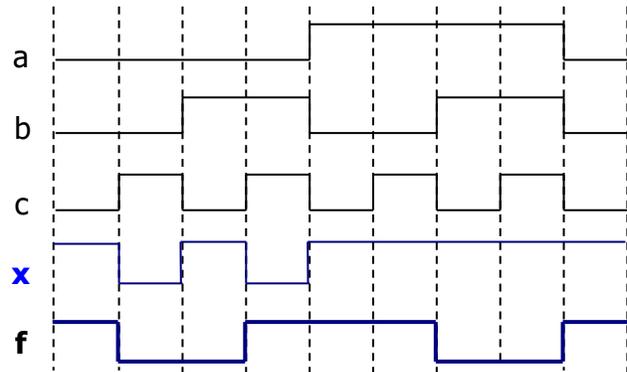architecture struct of test is
  signal x: std_logic;
begin
  f <= x xnor (not (b));
  x <= a or (not (c));
end struct;
    
```



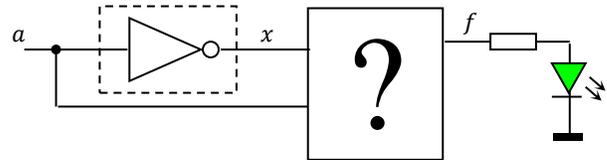
## PROBLEM 2 (30 PTS)

- Design a circuit that verifies the logical operation of a NOT gate.  $f=1$  (LED ON) if the NOT gate does not work properly. Assumption: when the NOT gate is not working, it generates 1's instead of 0's and vice versa.




a	x	f
0	0	1
0	1	0
1	0	0
1	1	1

$$f = \bar{a}x + ax$$

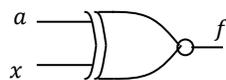
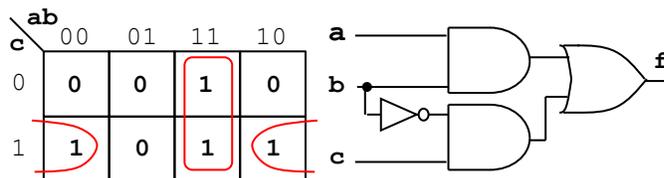
## PROBLEM 3 (35 PTS)

- The following is the timing diagram of a logic circuit with three inputs. Simplify the Boolean expression of the circuit and sketch the minimized circuit.



$$f = ab + \bar{b}c$$

