

# Homework 1

(Due date: January 18<sup>th</sup> @ 5:30 pm)  
Presentation and clarity are very important!

## PROBLEM 1 (27 PTS)

a) Simplify the following functions using ONLY Boolean Algebra Theorems. For each resulting simplified function, sketch the logic circuit using AND, OR, XOR, and NOT gates. (14 pts)

✓  $F = \overline{Y(Z + \overline{X})} + \overline{X}Y$

✓  $F = \prod(M_1, M_4, M_5, M_7)$

✓  $F(A, B, C) = \overline{ABC} + \overline{(A \oplus C)}B$

✓  $F = \overline{XYZ} + \overline{X}(Y \oplus Z)$

b) Demonstrate the following Theorem: (5 pts)

$$(X + Y)(\overline{X} + Z)(Y + Z) = (X + Y)(\overline{X} + Z)$$


c) For the following Truth table with two outputs: (8 pts)

- Provide the Boolean functions using the Canonical Sum of Products (SOP), and Product of Sums (POS).
- Express the Boolean functions using the minterms and maxterms representations.
- Sketch the logic circuits as Canonical Sum of Products and Product of Sums.

| x | y | z | f <sub>1</sub> | f <sub>2</sub> |
|---|---|---|----------------|----------------|
| 0 | 0 | 0 | 1              | 0              |
| 0 | 0 | 1 | 0              | 1              |
| 0 | 1 | 0 | 0              | 1              |
| 0 | 1 | 1 | 0              | 0              |
| 1 | 0 | 0 | 0              | 1              |
| 1 | 0 | 1 | 1              | 1              |
| 1 | 1 | 0 | 0              | 0              |
| 1 | 1 | 1 | 1              | 1              |

## PROBLEM 2 (26 PTS)

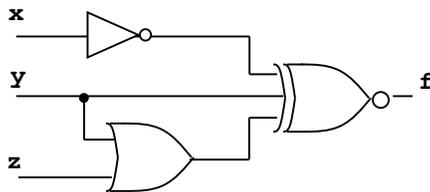a) Construct the truth table describing the output of the following circuit and write the simplified Boolean equation (8 pts).  
Note that  $a \oplus b \oplus c = (a \oplus b) \oplus c = a \oplus (b \oplus c) = b \oplus (a \oplus c)$



| x | y | z | f |
|---|---|---|---|
| 0 | 0 | 0 |   |
| 0 | 0 | 1 |   |
| 0 | 1 | 0 |   |
| 0 | 1 | 1 |   |
| 1 | 0 | 0 |   |
| 1 | 0 | 1 |   |
| 1 | 1 | 0 |   |
| 1 | 1 | 1 |   |

f =

b) The following is the timing diagram of a logic circuit with 3 inputs. Sketch the logic circuit that generates this waveform. Then, complete the VHDL code. (8 pts)


```

library ieee;
use ieee.std_logic_1164.all;


entity circ is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end circ;

architecture st of circ is
-- ???
begin
-- ???
end st;

```

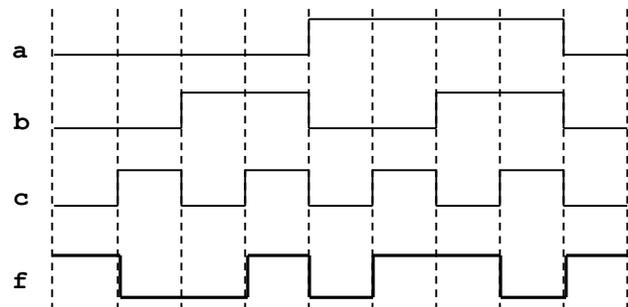

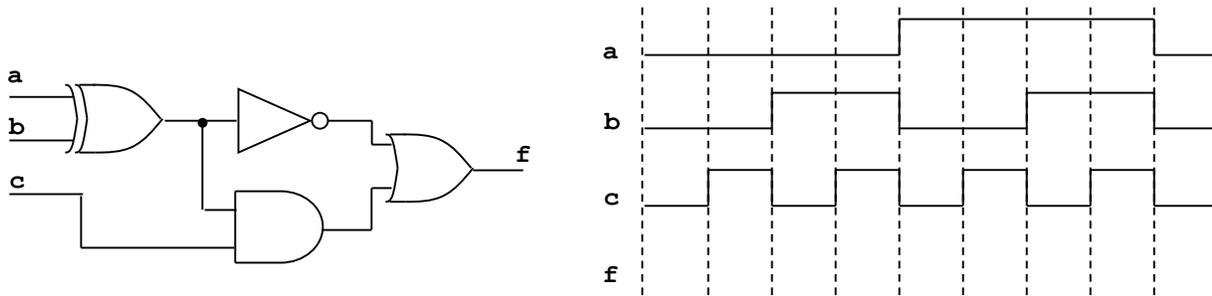c) Complete the timing diagram of the following circuit: (5 pts)




d) Complete the timing diagram of the logic circuit whose VHDL description is shown below: (5 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end circ;

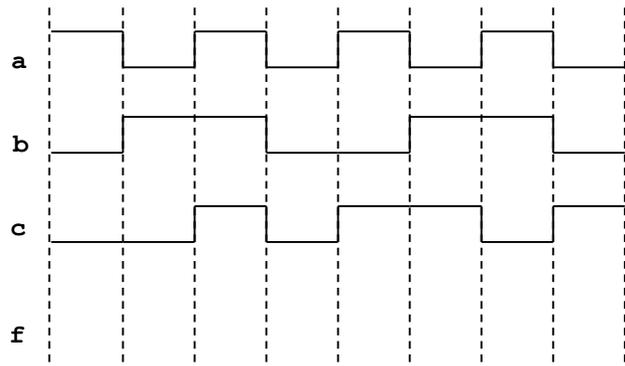architecture st of circ is
  signal x, y: std_logic;
begin
  x <= a nor b;
  y <= x xor c;
  f <= y xnor (not a);
end st;
```




**PROBLEM 3 (11 PTS)**

- Complete the truth table for a circuit with 4 inputs  $x, y, z, w$  that activates an output ( $f = 1$ ) when the number of 1's in the inputs is equal than the number of 0's. For example: If  $xyzw = 1001 \rightarrow f = 1$ . If  $xyzw = 1011 \rightarrow f = 0$ .
- Provide the Boolean equation for the output  $f$  and sketch the logic circuit.

**PROBLEM 4 (11 PTS)**

- Tic-tac-toe game: It is played on a 3-by-3 grid of squares: The players alternate turns. Each player chooses a square and places a mark in a square (one player uses  $x$  and the other  $o$ ). The first player with three marks in a row, column, or diagonal wins the game.
- A logical circuit is to be designed for an electronic tic-tac-toe that indicates the presence of a winning pattern for a player. The circuit has 9 inputs ( $x_1$  to  $x_9$ ) and an output  $F$ .  $F$  is '1' if a winning pattern is present and a 0 otherwise.
  - Provide the Boolean expression for  $F$ . The 9 inputs ( $x_1$  to  $x_9$ ) are arranged in the following pattern:


|       |       |       |
|-------|-------|-------|
| $x_1$ | $x_2$ | $x_3$ |
| $x_4$ | $x_5$ | $x_6$ |
| $x_7$ | $x_8$ | $x_9$ |

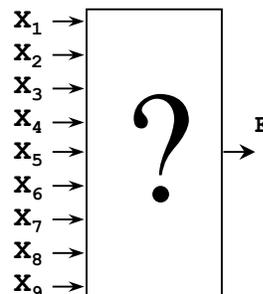

- Sketch the logical circuit resulting from the Boolean equation for  $F$ .

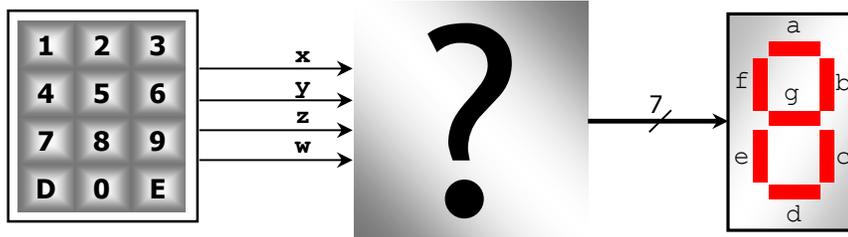**PROBLEM 5 (25 PTS)**

- A numeric keypad produces a 4-bit code as shown below. We want to design a logic circuit that converts each 4-bit code to a 7-segment code, where each segment is an LED. The LEDs are lit with a logical '0' (negative logic). The inputs are active high (or in positive logic).
- ✓ Complete the truth table for each output ( $a, b, c, d, e, f, g$ ).
- ✓ Provide the simplified expression for each output ( $a, b, c, d, e, f, g$ ). Use Karnaugh maps for  $a, b, c, d, e$  and the Quine-McCluskey algorithm for  $f, g$ . Note that it is safe to assume that the codes 1100 to 1111 will not be produced by the keypad.



| Value | X | Y | Z | W | a | b | c | d | e | f | g |
|-------|---|---|---|---|---|---|---|---|---|---|---|
| 0     | 0 | 0 | 0 | 0 |   |   |   |   |   |   |   |
| 1     | 0 | 0 | 0 | 1 |   |   |   |   |   |   |   |
| 2     | 0 | 0 | 1 | 0 |   |   |   |   |   |   |   |
| 3     | 0 | 0 | 1 | 1 |   |   |   |   |   |   |   |
| 4     | 0 | 1 | 0 | 0 |   |   |   |   |   |   |   |
| 5     | 0 | 1 | 0 | 1 |   |   |   |   |   |   |   |
| 6     | 0 | 1 | 1 | 0 |   |   |   |   |   |   |   |
| 7     | 0 | 1 | 1 | 1 |   |   |   |   |   |   |   |
| 8     | 1 | 0 | 0 | 0 |   |   |   |   |   |   |   |
| 9     | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| E     | 1 | 0 | 1 | 0 |   |   |   |   |   |   |   |
| D     | 1 | 0 | 1 | 1 |   |   |   |   |   |   |   |
|       | 1 | 1 | 0 | 0 |   |   |   |   |   |   |   |
|       | 1 | 1 | 0 | 1 |   |   |   |   |   |   |   |
|       | 1 | 1 | 1 | 0 |   |   |   |   |   |   |   |
|       | 1 | 1 | 1 | 1 |   |   |   |   |   |   |   |

