


# Homework 4

(Due date: March 29<sup>th</sup> @ 5:30 pm)

Presentation and clarity are very important! Show your procedure!
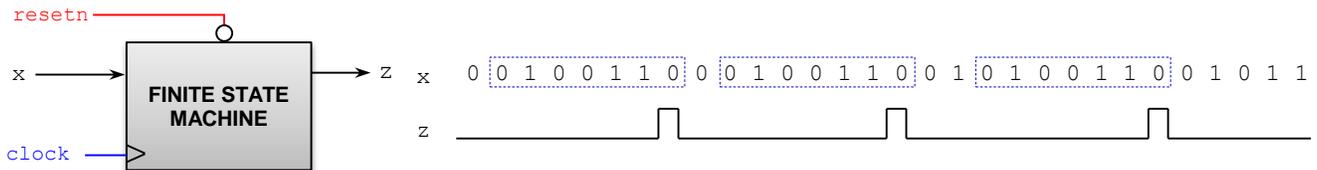
## PROBLEM 1 (23 PTS)


- Sequence Detector: The machine has to generate  $z=1$  when it detects the sequence 0100110. Once the sequence is detected, the circuit looks for a new sequence.



- Draw the State Diagram (any representation), State Table, and Excitation Table. Is this a Mealy or a Moore machine? Why?
- Provide the excitation equations (simplify your circuit using K-maps or the Quine-McCluskey algorithm) (5 pts)
- Sketch the circuit. (3 pts)
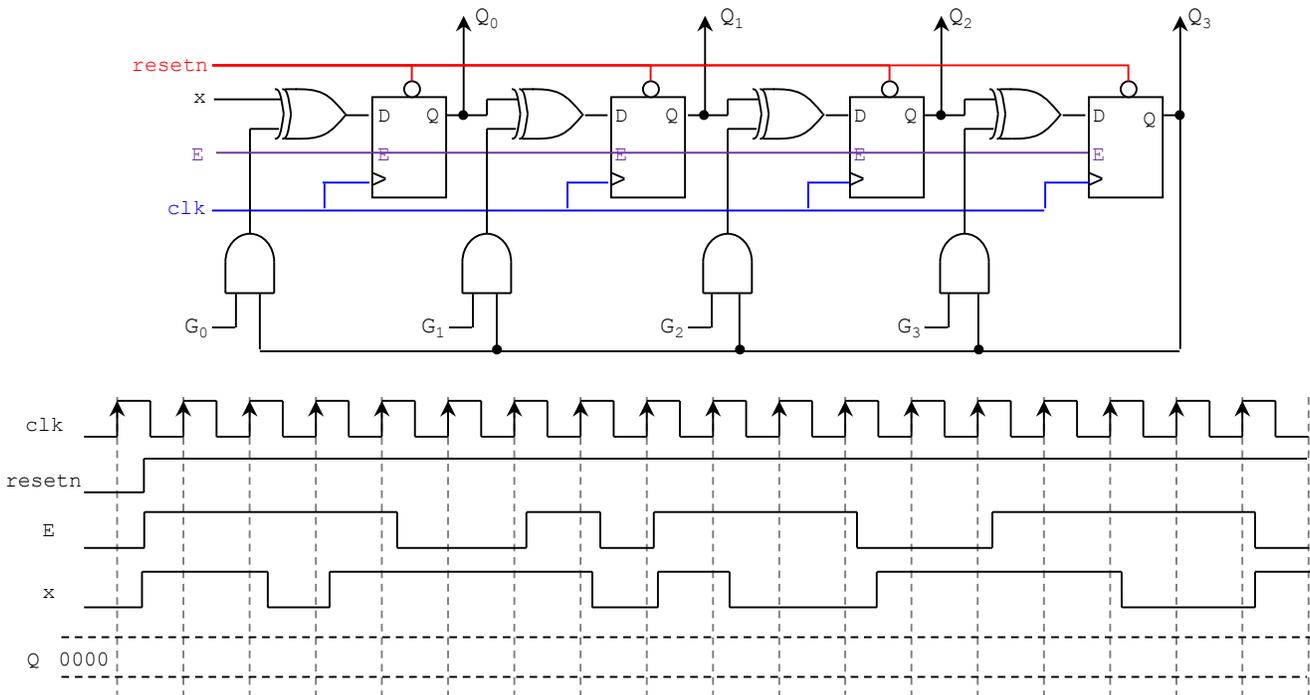
## PROBLEM 2 (15 PTS)


- Complete the timing diagram of the following circuit.  $G = G_3G_2G_1G_0 = 1101$ ,  $Q = Q_3Q_2Q_1Q_0$


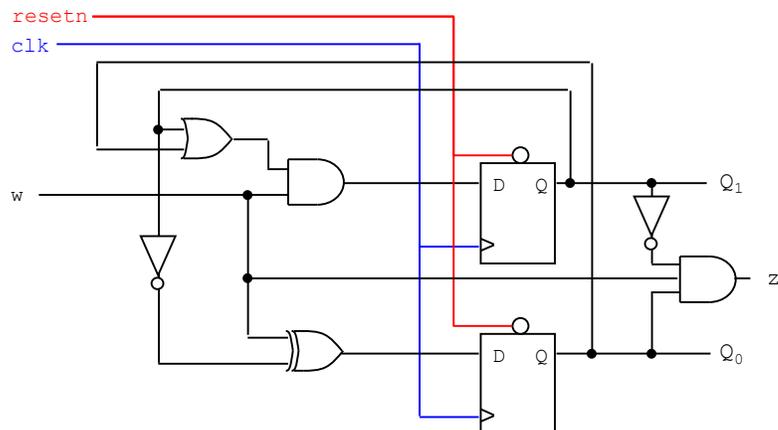
## PROBLEM 3 (12 PTS)

- Provide the State Diagram (any representation), the Excitation Table, and the Excitation equations of the following FSM.

$w$ : input,  $z$ : output,  $Q_1Q_0$ : state.



PROBLEM 4 (17 PTS)

- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. Is it a Mealy or a Moore FSM?
- Complete the Timing Diagram.

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
    port ( clk, resetn: in std_logic;
          r, p, q: in std_logic;
          x, w, z: out std_logic);
end circ;
```

```
architecture behavioral of circ is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (resetn, clk, r, p, q)
    begin
        if resetn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if r = '1' then
                        y <= S2;
                    else
                        if p = '1' then y <= S1; else y <= S3; end if;
                    end if;
                when S2 =>
                    if p = '1' then y <= S1; else y <= S3; end if;
                when S3 =>
                    if q = '1' then y <= S3; else y <= S2; end if;
            end case;
        end if;
    end process;

    Outputs: process (y, r, p, q)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => if r = '0' then
                if p = '1' then
                    w <= '1'; x <= '1';
                end if;
            end if;
            when S2 => if q = '0' then x <= '1'; end if;
                if p = '0' then z <= '1'; end if;
            when S3 => if q = '0' then x <= '1'; end if;
        end case;
    end process;
end behavioral;
```

