


Solutions - Final Exam

(April 19th @ 7:00 pm)

Presentation and clarity are very important! Show your procedure!

 
PROBLEM 1 (12 PTS)

- Complete the timing diagram of the following circuit. $G = G_3G_2G_1G_0 = 1001$, $Q = Q_3Q_2Q_1Q_0$



 
PROBLEM 2 (12 PTS)

- Given the following circuit, complete the timing diagram.
The LUT 6-to-6 implements the following function: $OLUT = \lceil \sqrt{ILUT} \rceil$, where $ILUT$ is a 6-bit unsigned number.
For example $ILUT = 41 (101001_2) \rightarrow OLUT = \lceil \sqrt{41} \rceil = 7 (000111_2)$



 PROBLEM 3 (20 PTS)

- Complete the timing diagram of the circuit shown below: (8 pts)



- Provide the State Diagram (any representation), the Excitation Table, and the Excitation equations of the following Finite State Machine: (12 pts)


$$Q_1(t+1) = \overline{(Q_1 + Q_0) \oplus w}$$

$$Q_0(t+1) = Q_1 Q_0 w$$

$$z = \overline{w} Q_1 Q_0$$

State Assignment:


S1: Q=00 S2: Q=01
S3: Q=10 S4: Q=11

 

PRESENT STATE			NEXTSTATE		
w	Q ₁ Q ₀ (t)		Q ₁ Q ₀ (t+1)	z	
0	0 0	0	1 0	0	
0	0 1	0	0 0	0	
0	1 0	0	0 0	0	
0	1 1	0	0 0	1	
1	0 0	0	0 1	0	
1	0 1	1	1 1	0	
1	1 0	1	1 1	0	
1	1 1	1	1 0	0	




PRESENT STATE			NEXT STATE		
w	STATE		STATE	z	
0	S1		S3	0	
0	S2		S1	0	
0	S3		S1	0	
0	S4		S1	1	
1	S1		S2	0	
1	S2		S4	0	
1	S3		S4	0	
1	S4		S3	0	

 

 
PROBLEM 4 (22 PTS)

- Sequence detector: The machine has to generate $z = 1$ when it detects the sequence 1001. Once the sequence is detected, the circuit looks for a new sequence.
- The signal E is an input enable: It validates the input x , i.e., if $E = 1$, x is valid, otherwise x is not valid.



- Draw the State Diagram (any representation), State Table, and the Excitation Table of this circuit with inputs E and x and output z . Is this a Mealy or a Moore machine? Why? (15 pts)
- Provide the excitation equations (simplify your circuit using K-maps or the Quine-McCluskey algorithm) (4 pts)
- Sketch the circuit. (3 pts)

 State Diagram, State Table, and Excitation Table:



This is a Mealy Machine. The output 'z' depends on the input as well as on the present state.

- Excitation equations, minimization, and circuit implementation:


$$Q_1(t+1) = \bar{E}Q_1 + E\bar{x}Q_1Q_0 + \bar{x}Q_1\bar{Q}_0$$

$$Q_0(t+1) = \bar{E}Q_0 + Ex\bar{Q}_1 + EQ_1\bar{Q}_0$$

$$z = ExQ_1Q_0$$

Q ₁ (t+1)	Ex	00	01	11	10
Q ₁ Q ₀	00	0	0	0	0
01	0	0	0	1	1
11	1	1	0	0	0
10	1	1	0	1	1

Q ₀ (t+1)	Ex	00	01	11	10
Q ₁ Q ₀	00	0	0	1	0
01	1	1	1	1	0
11	1	1	0	0	0
10	0	0	1	1	1

 


PROBLEM 5 (16 PTS)

- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. Is it a Mealy or a Moore FSM?
- Complete the Timing Diagram.

```
library ieee;
use ieee.std_logic_1164.all;

 
entity myfsm is
    port ( clk, resetn: in std_logic;
          r, p, q: in std_logic;
          x, w, z: out std_logic);
end myfsm;
```



```
architecture behavioral of myfsm is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (resetn, clk, r, p, q)
    begin
        if resetn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if r = '1' then
                        y <= S2;
                    else
                        if p = '1' then y <= S3; else y <= S1; end if;
                    end if;
                when S2 =>
                    if p = '1' then y <= S1; else y <= S3; end if;
                when S3 =>
                    if q = '1' then y <= S3; else y <= S2; end if;
            end case;
        end if;
    end process;

    Outputs: process (y, r, p, q)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => if r = '0' then
                            if p = '0' then
                                z <= '1'; x <= '1';
                            end if;
                        end if;
            when S2 => if q = '0' then x <= '1'; end if;
                            if p = '0' then w <= '1'; end if;
            when S3 => if q = '0' then x <= '1'; end if;
        end case;
    end process;
end behavioral;
```

 This is a Mealy Machine. The outputs 'x,w,z' depend on the input as well as on the present state.



PROBLEM 6 (18 PTS)

- “Counting 1’s” Circuit: It counts the number of bits in register A that has the value of ‘1’.
The digital system is depicted below: FSM + Datapath. Example: For $n = 8$: if $A = 00110110$, then $C = 0100$.
✓ m-bit counter: If $E = sclr = 1$, the count is initialized to zero. If $E = 1, sclr = 0$, the count is increased by 1.
✓ Parallel access shift register: If $E = 1: s_l = 1 \rightarrow \text{Load}, s_l = 0 \rightarrow \text{Shift}$.
- Complete the timing diagram (next page) where $n = 8, m = 4$.

