

Solutions - Homework 1

(Due date: January 18th @ 5:30 pm)

Presentation and clarity are very important!

PROBLEM 1 (27 PTS)

- a) Simplify the following functions using ONLY Boolean Algebra Theorems. For each resulting simplified function, sketch the logic circuit using AND, OR, XOR, and NOT gates. (14 pts)


✓ $F = Y(Z + \bar{X}) + \bar{X}\bar{Y}$

✓ $F = \prod(M_1, M_4, M_5, M_7)$


✓ $F(A, B, C) = \overline{ABC} + (\overline{A \oplus C})B$

✓ $F = \overline{XYZ} + \bar{X}(\bar{Y} \oplus \bar{Z})$

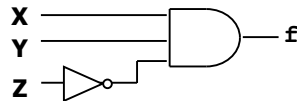
✓ $F(X, Y, Z) = \overline{Y(Z + \bar{X}) + \bar{X}\bar{Y}} = \overline{YZ + Y\bar{X} + \bar{X} + \bar{Y}} = \overline{YZ + \bar{X} + \bar{Y}} = \overline{\bar{X} + (\bar{Y} + Y)(\bar{Y} + Z)} = \overline{\bar{X} + \bar{Y} + Z} = XY\bar{Z}$




✓ $F(X, Y, X) = \prod(M_1, M_4, M_5, M_7) = \sum(m_0, m_2, m_3, m_6) = \bar{X}\bar{Y}\bar{Z} + \bar{X}Y\bar{Z} + \bar{X}YZ + XY\bar{Z} = \bar{X}\bar{Z} + \bar{X}YZ + XY\bar{Z}$
 $= \bar{X}(\bar{Z} + YZ) + XY\bar{Z} = \bar{X}(\bar{Z} + Y) + XY\bar{Z} = \bar{X}\bar{Z} + \bar{X}Y + XY\bar{Z} = \bar{X}Y + \bar{Z}(\bar{X} + XY) = \bar{X}Y + \bar{Z}(\bar{X} + Y)$
 $= \bar{X}Y + \bar{Z}\bar{X} + \bar{Z}Y$

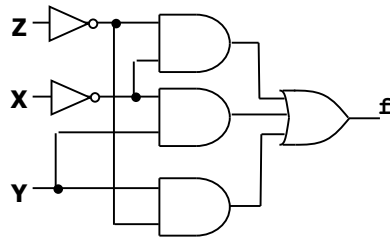

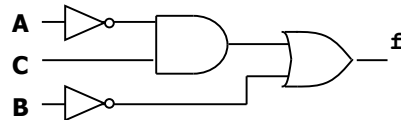✓ $F(A, B, C) = \overline{ABC} + (\overline{A \oplus C})B = \overline{ABC} + (AC + \bar{A}\bar{C})B = \overline{AB(\bar{C} + C)} + \bar{A}\bar{C}B = \overline{AB} + \bar{A}\bar{C}B = \overline{B(A + \bar{A}\bar{C})}$
 $= \overline{B(A + \bar{C})} = \bar{B} + (A + \bar{C}) = \bar{B} + \bar{A}\bar{C}$



✓ $F = \overline{XY\bar{Z} + \bar{X}(\bar{Y} \oplus \bar{Z})} = \overline{XY\bar{Z} + \bar{X}(\bar{Y}Z + Y\bar{Z})} = \overline{XY\bar{Z} + \bar{X}\bar{Y}Z + \bar{X}YZ} = \overline{\bar{X}\bar{Y}Z + Y\bar{Z}(X + \bar{X})} = \overline{\bar{X}\bar{Y}Z + Y\bar{Z}}$
 $= \overline{\bar{X}\bar{Y}Z} \cdot \overline{Y\bar{Z}} = (\bar{Y} + Z)(X + Y + \bar{Z}) = \bar{Y}X + \bar{Y} \cdot \bar{Z} + ZX + ZY = ZX + \bar{Z} \cdot \bar{Y} + ZY$

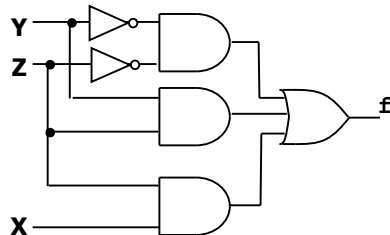

- b) Demonstrate the following Theorem: (5 pts)

$$(X + Y)(\bar{X} + Z)(Y + Z) = (X + Y)(\bar{X} + Z)$$

Note that: $(X + Y)(\bar{X} + Z) = XZ + Y\bar{X} + YZ$

Then: $(X + Y)(\bar{X} + Z)(Y + Z) = (XZ + Y\bar{X} + YZ)(Y + Z) = XZY + Y\bar{X} + YZ + XZ + \bar{X}YZ + YZ = Y\bar{X} + XZ + \bar{X}YZ + XYZ + YZ$
 $= Y\bar{X} + XZ + YZ(\bar{X} + X + 1) = Y\bar{X} + XZ + YZ = XZ + Y\bar{X} + YZ = (X + Y)(\bar{X} + Z)$

c) For the following Truth table with two outputs: (8 pts)

- Provide the Boolean functions using the Canonical Sum of Products (SOP), and Product of Sums (POS).
- Express the Boolean functions using the minterms and maxterms representations.
- Sketch the logic circuits as Canonical Sum of Products and Product of Sums.

x	y	z	f ₁	f ₂
0	0	0	1	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	0
1	0	0	0	1
1	0	1	1	1
1	1	0	0	0
1	1	1	1	1

Sum of Products

$$f_1 = \bar{x}\bar{y}\bar{z} + x\bar{y}z + xyz$$



$$f_2 = \bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}\bar{z} + x\bar{y}z + xyz$$

Product of Sums

$$f_1 = (x + y + \bar{z})(x + \bar{y} + z)(x + \bar{y} + \bar{z})(\bar{x} + y + z)(\bar{x} + \bar{y} + z)$$


$$f_2 = (x + y + z)(x + \bar{y} + \bar{z})(\bar{x} + \bar{y} + z)$$

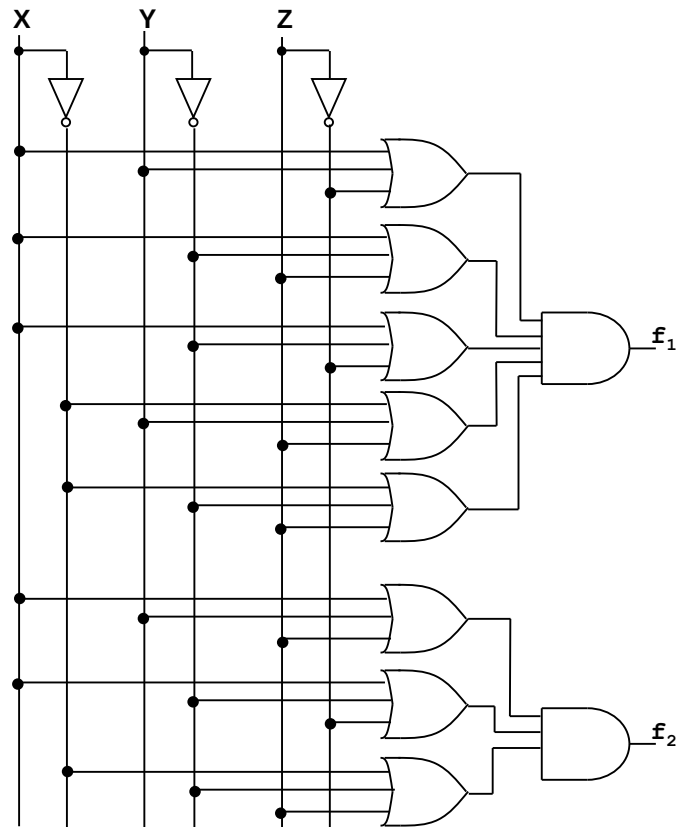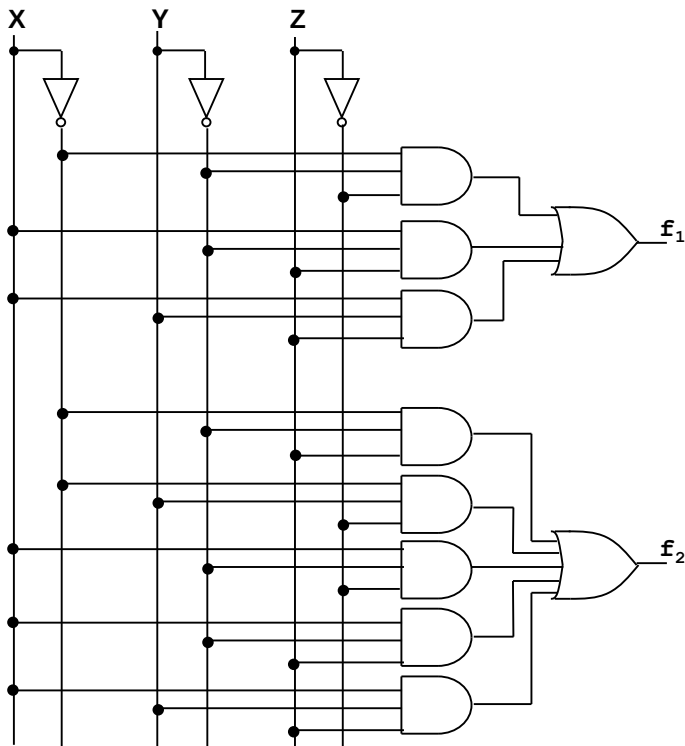Minterms and maxterms: $f_1 = \sum(m_0, m_5, m_7) = \prod(M_1, M_2, M_3, M_4, M_6)$.
 $f_2 = \sum(m_1, m_2, m_4, m_5, m_7) = \prod(M_0, M_3, M_6)$.



PROBLEM 2 (26 PTS)

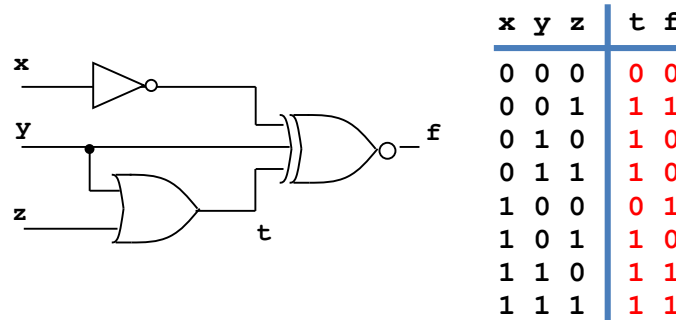- a) Construct the truth table describing the output of the following circuit and write the simplified Boolean equation (8 pts).
Note that $a \oplus b \oplus c = (a \oplus b) \oplus c = a \oplus (b \oplus c) = b \oplus (a \oplus c)$



$$f = \overline{x \oplus y \oplus (y + z)} = \overline{x \oplus (\overline{yz})} = \overline{x \overline{yz}} + \overline{x \overline{yz}} = \overline{x \overline{yz}} + xy + x\overline{z}$$


- b) The following is the timing diagram of a logic circuit with 3 inputs. Sketch the logic circuit that generates this waveform. Then, complete the VHDL code. (8 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end circ;


architecture st of circ is

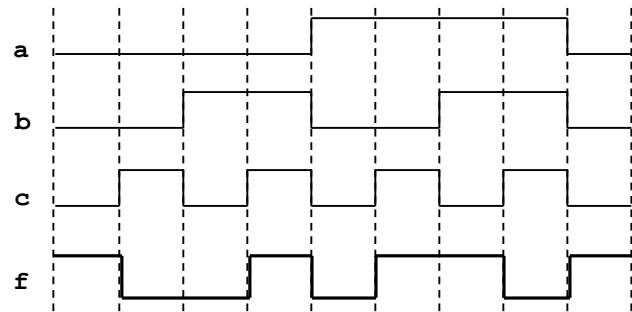begin
  f <= not (a xor b xor c);
end st;
```





a	b	c	f
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

c \ ab	00	01	11	10
0	1	0	1	0
1	0	1	0	1

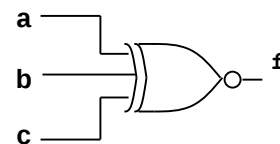

$$f = \overline{a\overline{b}\overline{c}} + \overline{a\overline{b}c} + \overline{ab\overline{c}} + \overline{abc} = \overline{a(\overline{b}\overline{c} + b\overline{c})} + \overline{a(b\overline{c} + \overline{b}c)} = \overline{a(\overline{b \oplus c})} + \overline{a(b \oplus c)} = \overline{a \oplus (b \oplus c)} = \overline{a \oplus b \oplus c}$$

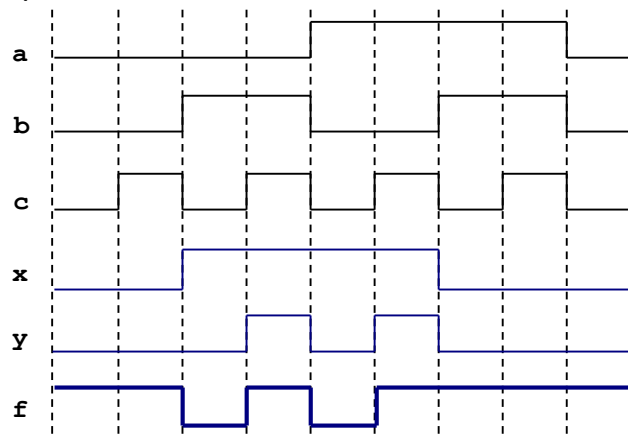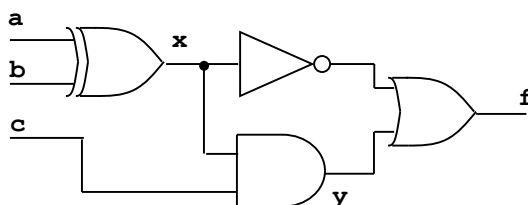- c) Complete the timing diagram of the following circuit: (5 pts)




d) Complete the timing diagram of the logic circuit whose VHDL description is shown below: (5 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
    port ( a, b, c: in std_logic;
          f: out std_logic);
end circ;

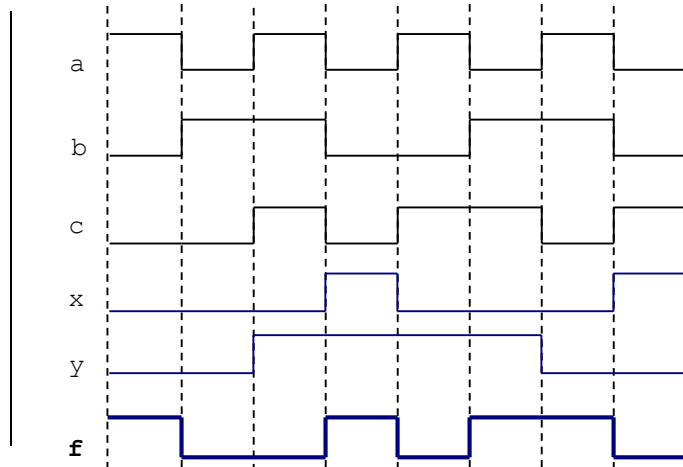architecture st of circ is
    signal x, y: std_logic;
begin
    x <= a nor b;
    y <= x xor c;
    f <= y xnor (not a);
end st;
```



PROBLEM 3 (11 PTS)

- Complete the truth table for a circuit with 4 inputs x, y, z, w that activates an output ($f = 1$) when the number of 1's in the inputs is equal than the number of 0's. For example: If $xyzw = 1001 \rightarrow f = 1$. If $xyzw = 1011 \rightarrow f = 0$.
- Provide the Boolean equation for the output f and sketch the logic circuit.


x	y	z	w	f
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

xy \ zw	00	01	11	10
00	0	0	1	0
01	0	1	0	1
11	1	0	0	0
10	0	1	0	1

$\overline{z} \overline{w}$ } $\overline{z}$ } $\overline{w}$
 $\overline{z} w$ } w
 $z w$ } z } $\overline{w}$
 $z \overline{w}$ } $\overline{z}$ } w


$\overline{x} \overline{y}$ } $\overline{x}$ } $\overline{y}$
 $x y$ } y
 $x \overline{y}$ } x } $\overline{y}$
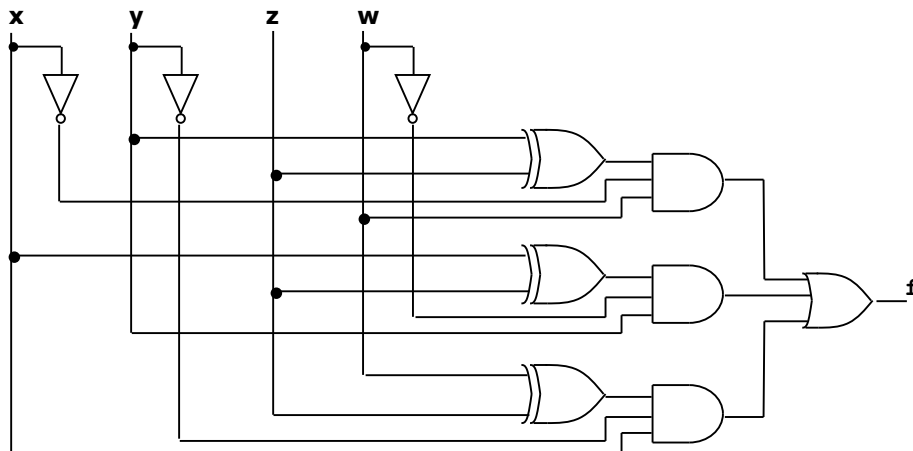
$$f = \overline{x}\overline{y}zw + \overline{x}y\overline{z}w + \overline{x}yz\overline{w} + xy\overline{z}\overline{w} + x\overline{y}\overline{z}w + x\overline{y}z\overline{w} = \overline{x}w(y \oplus z) + y\overline{w}(x \oplus z) + x\overline{y}(z \oplus w)$$



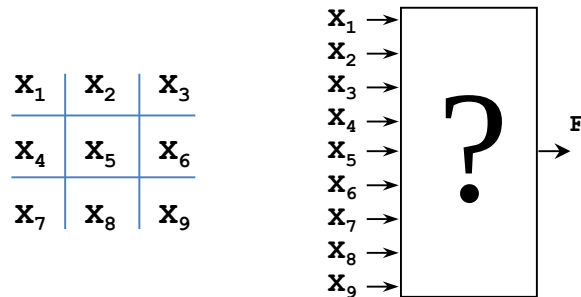PROBLEM 4 (11 PTS)

- Tic-tac-toe game: It is played on a 3-by-3 grid of squares: The players alternate turns. Each player chooses a square and places a mark in a square (one player uses **x** and the other o). The first player with three marks in a row, column, or diagonal wins the game.
- A logical circuit is to be designed for an electronic tic-tac-toe that indicates the presence of a winning pattern for a player. The circuit has 9 inputs (x_1 to x_9) and an output F . F is '1' if a winning pattern is present and a 0 otherwise.
- ✓ Provide the Boolean expression for F . The 9 inputs (x_1 to x_9) are arranged in the following pattern:



$f = 1$ when there are three 1's in a line. Note that there can be more than three 1's before we find three 1's in a line. So, we make $f = 1$ when a winning pattern is present regardless of the values of the remaining variables:

x_1	x_2	x_3	x_4	x_5	x_6	x_7	x_8	x_9	f
1	1	1	X	X	X	X	X	X	1
X	X	X	1	1	1	X	X	X	1
X	X	X	X	X	X	1	1	1	1
1	X	X	1	X	X	1	X	X	1
X	1	X	X	1	X	X	1	X	1
X	X	1	X	X	1	X	X	1	1
1	X	X	X	1	X	X	X	1	1
X	X	1	X	1	X	1	X	X	1
All remaining cases									0

First row: $x_1x_2x_3$. (all permutations for $x_4x_5x_6x_7x_8x_9$) = $x_1x_2x_3 \cdot h(x_4, x_5, x_6, x_7, x_8, x_9)$


Where: $h(x_4, x_5, x_6, x_7, x_8, x_9) = \sum m(0, 1, \dots, 63) = 1$ (the sum of all the minterms of a 6-variable function is always 1).

Thus, Then first row is just: $x_1x_2x_3$

The same technique is applied for every row.


$$\rightarrow f = x_1x_2x_3 + x_4x_5x_6 + x_7x_8x_9 + x_1x_4x_7 + x_2x_5x_8 + x_3x_6x_9 + x_1x_5x_9 + x_3x_5x_7$$

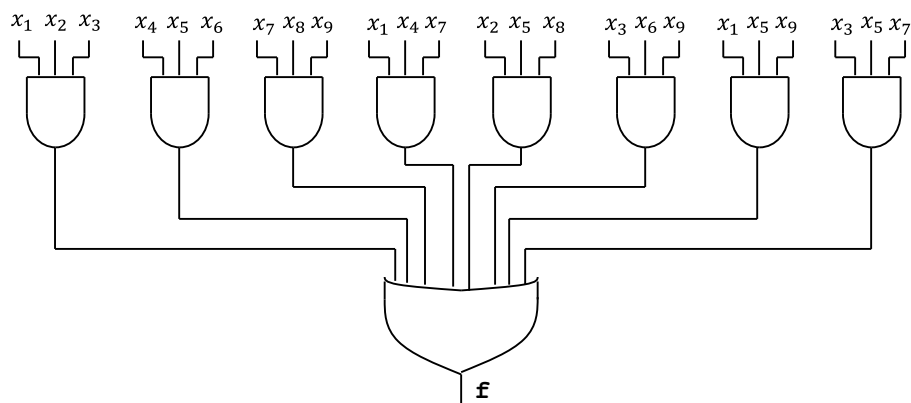- ✓ Sketch the logical circuit resulting from the Boolean equation for F .




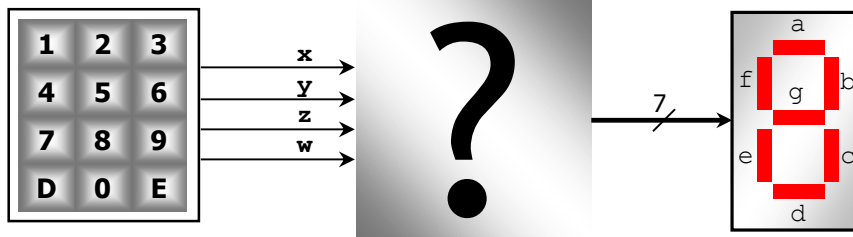PROBLEM 5 (25 PTS)

- A numeric keypad produces a 4-bit code as shown below. We want to design a logic circuit that converts each 4-bit code to a 7-segment code, where each segment is an LED. The LEDs are lit with a logical '0' (negative logic). The inputs are active high (or in positive logic).
- Complete the truth table for each output (a, b, c, d, e, f, g).
- Provide the simplified expression for each output (a, b, c, d, e, f, g). Use Karnaugh maps for a, b, c, d, e and the Quine-McCluskey algorithm for f, g . Note that it is safe to assume that the codes 1100 to 1111 will not be produced by the keypad.



Value	X	Y	Z	W	a	b	c	d	e	f	g
0	0	0	0	0							
1	0	0	0	1							
2	0	0	1	0							
3	0	0	1	1							
4	0	1	0	0							
5	0	1	0	1							
6	0	1	1	0							
7	0	1	1	1							
8	1	0	0	0							
9	1	0	0	1	0	0	0	0	1	0	0
E	1	0	1	0							
D	1	0	1	1							
	1	1	0	0							
	1	1	0	1							
	1	1	1	0							
	1	1	1	1							

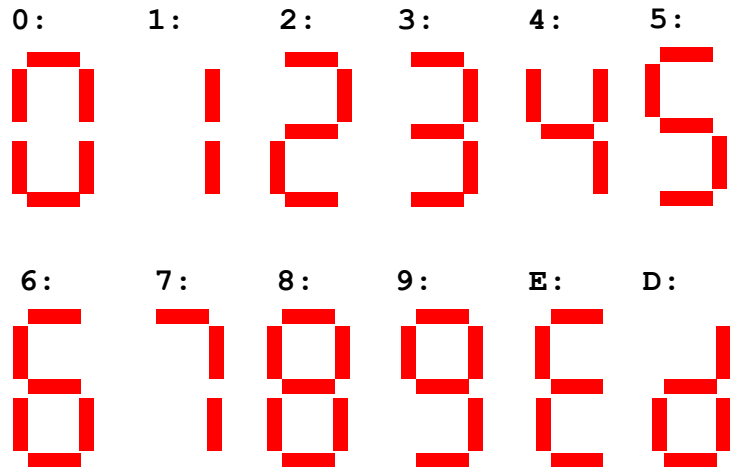

Value	X	Y	Z	W	a	b	c	d	e	f	g
0	0	0	0	0	0	0	0	0	0	0	1
1	0	0	0	1	1	0	0	1	1	1	1
2	0	0	1	0	0	0	1	0	0	1	0
3	0	0	1	1	0	0	0	0	1	1	0
4	0	1	0	0	1	0	0	1	1	0	0
5	0	1	0	1	0	1	0	0	1	0	0
6	0	1	1	0	0	1	0	0	0	0	0
7	0	1	1	1	0	0	0	1	1	1	1
8	1	0	0	0	0	0	0	0	0	0	0
9	1	0	0	1	0	0	0	0	1	0	0
E	1	0	1	0	0	1	1	0	0	0	0
D	1	0	1	1	1	0	0	0	0	1	0
	1	1	0	0	X	X	X	X	X	X	X
	1	1	0	1	X	X	X	X	X	X	X
	1	1	1	0	X	X	X	X	X	X	X
	1	1	1	1	X	X	X	X	X	X	X

$$a = \bar{x}\bar{y}zw + y\bar{z}\bar{w} + xzw$$

$$b = y\bar{z}w + yz\bar{w} + xz\bar{w}$$

$$c = \bar{y}z\bar{w}$$

$$d = \bar{x}\bar{y}zw + y\bar{z}\bar{w} + yzw$$

$$e = y\bar{z} + \bar{z}w + \bar{x}w$$

a	xy \ zw	00	01	11	10
	00	0	1	X	0
	01	1	0	X	0
	11	0	0	X	1
	10	0	0	X	0
b	xy \ zw	00	01	11	10
	00	0	0	X	0
	01	0	1	X	0
	11	0	0	X	0
	10	0	1	X	1
c	xy \ zw	00	01	11	10
	00	0	0	X	0
	01	0	0	X	0
	11	0	0	X	0
	10	1	0	X	1
d	xy \ zw	00	01	11	10
	00	0	1	X	0
	01	1	0	X	0
	11	0	1	X	0
	10	0	0	X	0
e	xy \ zw	00	01	11	10
	00	0	1	X	0
	01	1	1	X	1
	11	1	1	X	0
	10	0	0	X	0

$$f = \sum m(1,2,3,7,11) + \sum d(12,13,14,15)$$

Number of ones	4-literal implicants	3-literal implicants	2-literal implicants	1-literal implicants
1	$m_1 = 0001$ ✓ $m_2 = 0010$ ✓	$m_{1,3} = 00-1$ $m_{2,3} = 001-$		We can't combine any further, so we stop here
2	$m_3 = 0011$ ✓ $m_{12} = 1100$ ✓	$m_{3,7} = 0-11$ ✓ $m_{3,11} = -011$ ✓ $m_{12,13} = 110-$ ✓ $m_{12,14} = 11-0$ ✓	$m_{3,7,11,15} = --11$ $m_{3,11,7,15} = --11$ $m_{14,15,12,13} = 11--$ $m_{12,14,13,15} = 11--$	
3	$m_7 = 0111$ ✓ $m_{11} = 1011$ ✓ $m_{13} = 1101$ ✓ $m_{14} = 1110$ ✓	$m_{7,15} = -111$ ✓ $m_{11,15} = 1-11$ ✓ $m_{13,15} = 11-1$ ✓ $m_{14,15} = 111-$ ✓		
4	$m_{15} = 1111$ ✓			

$$f = \bar{x}\bar{y}w + \bar{x}\bar{y}z + zw + xy$$

Prime Implicants		Minterms				
		1	2	3	7	11
$m_{1,3}$	$\bar{x}\bar{y}w$	X		X		
$m_{2,3}$	$\bar{x}\bar{y}z$		X	X		
$m_{3,7,11,15}$	zw			X	X	X
$m_{14,15,12,13}$	xy					

$$\rightarrow f = \bar{x}\bar{y}w + \bar{x}\bar{y}z + zw$$

▪ $g = \sum m(0,1,7) + \sum d(12,13,14,15).$

Number of ones	4-literal implicants	3-literal implicants	2-literal implicants	1-literal implicants
0	$m_0 = 0000$ ✓	$m_{0,1} = 000-$		
1	$m_1 = 0001$ ✓			We can't combine any further, so we stop here
2	$m_{12} = 1100$ ✓	$m_{12,13} = 110-$ ✓ $m_{12,14} = 11-0$ ✓	$m_{12,13,14,15} = 11--$ $m_{12,14,13,15} = 11--$	
3	$m_7 = 0111$ ✓ $m_{13} = 1101$ ✓ $m_{14} = 1110$ ✓	$m_{7,15} = -111$ ✓ $m_{13,15} = 11-1$ ✓ $m_{14,15} = 111-$ ✓		
4	$m_{15} = 1111$ ✓			

$$g = \bar{x}\bar{y}\bar{z} + yzw + xy$$

Prime Implicants		Minterms		
		0	1	7
$m_{0,1}$	$\bar{x}\bar{y}\bar{z}$	X	X	
$m_{7,15}$	yzw			X
$m_{12,13,14,15}$	xy			

$$\rightarrow g = \bar{x}\bar{y}\bar{z} + yzw$$