


Solutions - Homework 3

(Due date: March 15th @ 5:30 pm)


Presentation and clarity are very important! Show your procedure!

 PROBLEM 1 (12 PTS)

- Complete the timing diagram of the circuit shown below. (5 pts)




 - Complete the timing diagram of the circuits shown below: (7 pts)



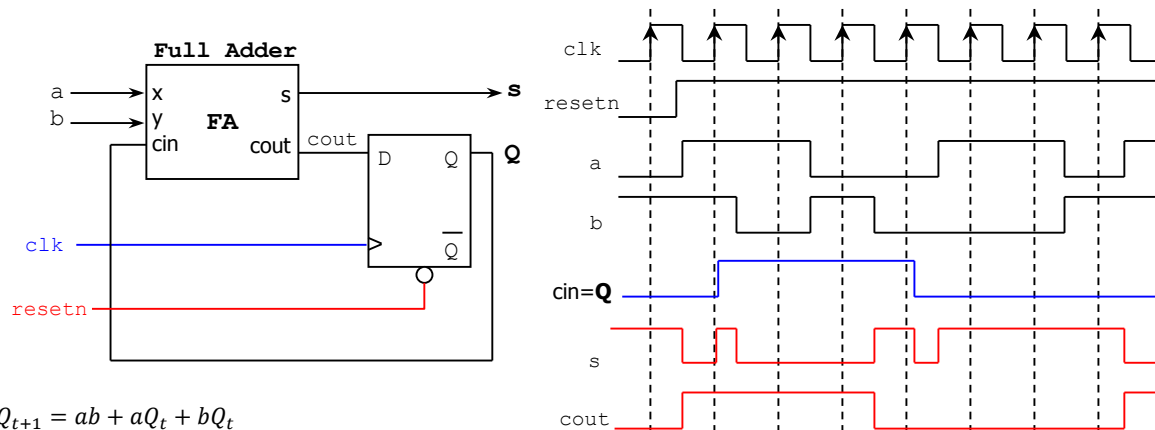
PROBLEM 2 (33 PTS)

- Complete the timing diagram of the circuit shown below: (10 pts)



$$Q_{t+1} = ab + aQ_t + bQ_t$$

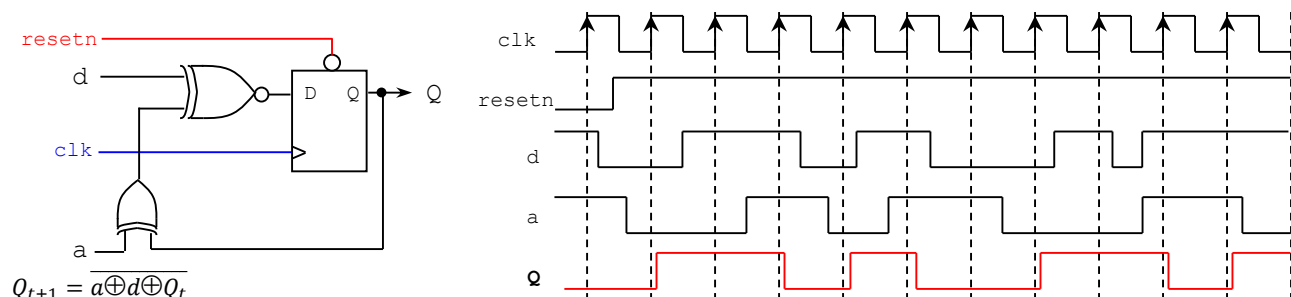- Complete the timing diagram of the circuit shown below: (7 pts)



$$Q_{t+1} = a \oplus d \oplus Q_t$$

- Complete the timing diagram of the circuit whose VHDL description is shown below: (6 pts)


```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( prn, a , clk: in std_logic;
        q: out std_logic);
end circ;


architecture t of circ is
  signal qt: std_logic;

begin
  process (prn, clk, x, a)
  begin
    if prn = '0' then
      qt <= '1';
    end if;
  end process;
```
 
```
    elsif (clk'event and clk = '1') then
      if x = '1' then
        qt <= a xnor qt;
      end if;
    end if;
  end process;
  q <= qt;
end t;
```




 - Complete the timing diagram of the following circuit: $Q = Q_3Q_2Q_1Q_0$ (10 pts)




PROBLEM 3 (18 PTS)

- Given the following circuit, complete the timing diagram (signals *DO* and *DATA*).
The LUT 6-to-6 implements the following function: $OLUT = [ILUT^{0.75}]$, where $ILUT$ is an unsigned number.
For example $ILUT = 35 (100011_2) \rightarrow OLUT = [35^{0.75}] = 14 (001110_2)$
 $ILUT = 51 (110011_2) \rightarrow OLUT = [51^{0.75}] = 20 (010100_2)$ | $ILUT = 23 (010111_2) \rightarrow OLUT = [23^{0.75}] = 11 (001011_2)$
 $ILUT = 61 (111101_2) \rightarrow OLUT = [61^{0.75}] = 22 (010110_2)$ | $ILUT = 46 (101110_2) \rightarrow OLUT = [46^{0.75}] = 18 (010010_2)$

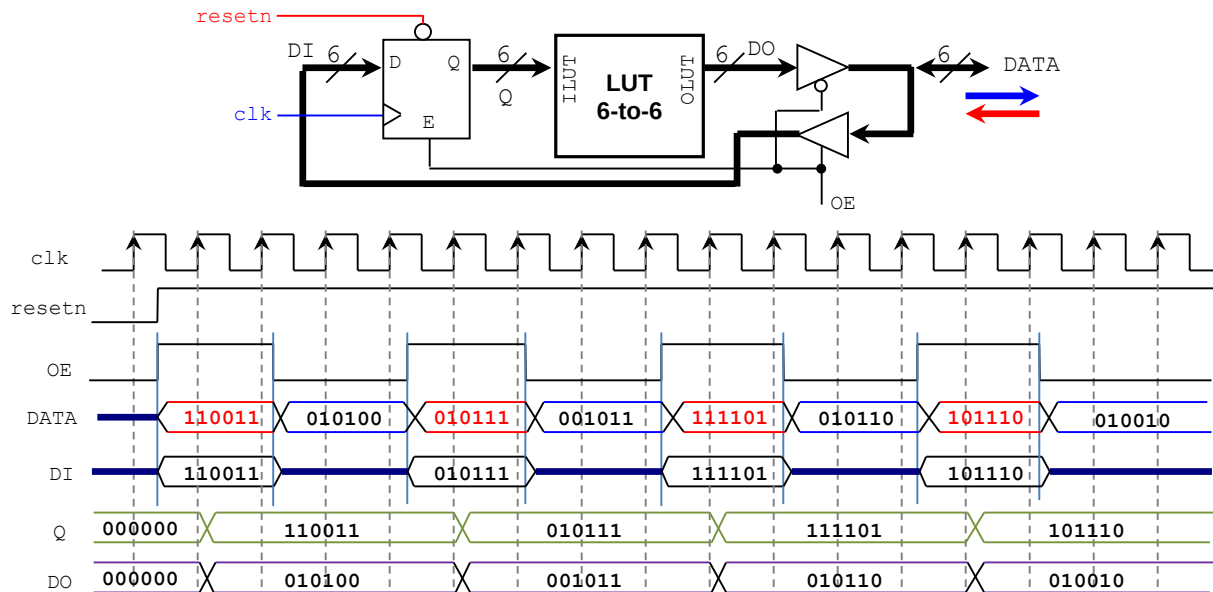

 
PROBLEM 4 (12 PTS)

- Complete the timing diagram of the following 4-bit parallel access shift register with enable input. Shifting operation: $s_1=0$. Parallel load: $s_1=1$. Note that $Q = Q_3Q_2Q_1Q_0$. $D = D_3D_2D_1D_0$



 PROBLEM 5 (25 PTS)

- The following circuit is a multiple-input compressor circuit (MIC), a component in Built-in Self-Test systems. $Q = Q_3Q_2Q_1Q_0$. $P = P_3P_2P_1P_0$
 - Write **structural** VHDL code. Create two files: i) flip flop, ii) top file (where you will interconnect the flip flops and the logic gates). Provide a printout. (10 pts)
 - Write a VHDL testbench according to the timing diagram shown below. Complete the timing diagram by simulating your circuit (Behavioral Simulation). The clock frequency must be 50 MHz with 50% duty cycle. Provide a printout. (15 pts)



✓ **VHDL Code: Top File**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity lfsr_mic is
    generic (N: INTEGER:= 4);
    port ( resetn, clock: in std_logic;
          E: in std_logic;
          P: in std_logic_vector (N-1 downto 0);
          Q: out std_logic_vector (N-1 downto 0));
end lfsr_mic;

architecture structural of lfsr_mic is

    component dffe
    port ( d : in  STD_LOGIC;
          clrn: in std_logic:= '1';
          prn: in std_logic:= '1';
          clk : in  STD_LOGIC;
          ena: in std_logic;
          q : out  STD_LOGIC);
    end component;

    signal D, Qt: std_logic_vector (N-1 downto 0);

begin

    D(N-1) <= Qt(N-1) xor Qt(0) xor P(N-1);

    g0: for i in N-2 downto 0 generate
        D(i) <= Qt(i+1) xor P(i);
    end generate;

    g1: for i in 0 to N-1 generate
        di: dffe port map (d => D(i), clrn => resetn, prn => '1', clk => clock, ena => E, q => Qt(i));
    end generate;

    Q <= Qt;

end structural;
```

✓ **VHDL Code: D-Type flip flop**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity dffe is
    port ( d : in  STD_LOGIC;
          clrn, prn, clk, ena: in std_logic;
          q : out  STD_LOGIC);
end dffe;

architecture behaviour of dffe is

begin
    process (clk, ena, prn, clrn)
    begin
        if clrn = '0' then q <= '0';
        elsif prn = '0' then q <= '1';
        elsif (clk'event and clk='1') then
            if ena = '1' then q <= d; end if;
        end if;
    end process;
end behaviour;
```

✓ **VHDL Tesbench:**

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_lfsr_mic IS
    generic (N: integer:= 4);
END tb_lfsr_mic;

ARCHITECTURE behavior OF tb_lfsr_mic IS
    component lfsr_mic
        port ( resetn, clock: in std_logic;
              E: in std_logic;
              P: in std_logic_vector (N-1 downto 0);
              Q: out std_logic_vector (N-1 downto 0));
    end component;

-- Inputs
    signal E : std_logic := '0';
    signal resetn : std_logic := '0';
    signal clock : std_logic := '0';
    signal P: std_logic_vector (N-1 downto 0):= (others => '0');

-- Outputs
    signal Q : std_logic_vector(N-1 downto 0);

-- Clock period definitions
    constant T : time := 20 ns;

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: lfsr_mic PORT MAP (resetn => resetn, clock => clock, E => E, P => P, Q => Q);

    -- Clock process definitions
    clock_process :process
    begin
        clock <= '0'; wait for T/2;
        clock <= '1'; wait for T/2;
    end process;

    -- Stimulus process
    stim_proc: process
    begin
        resetn <= '0'; P <= "0111"; wait for 100 ns;
        resetn <= '1';
        P <= "0111"; E <= '1'; wait for T;
        P <= "1100"; E <= '1'; wait for T;
        P <= "1100"; E <= '0'; wait for T;
        P <= "1100"; E <= '1'; wait for T;
        P <= "1011"; E <= '1'; wait for 4*T;
        P <= "1011"; E <= '0'; wait for T;
        P <= "1011"; E <= '1'; wait for 2*T;
        P <= "1011"; E <= '0'; wait for 2*T;
        P <= "1011"; E <= '1'; wait for T;
        P <= "1101"; E <= '1'; wait for 4*T;
        E <= '0';
        wait;
    end process;

END;
```

