


Solutions - Homework 4

(Due date: March 29th @ 5:30 pm)

Presentation and clarity are very important! Show your procedure!

 PROBLEM 1 (23 PTS)

- Sequence Detector: The machine has to generate $z=1$ when it detects the sequence 0100110. Once the sequence is detected, the circuit looks for a new sequence.




- Draw the State Diagram (any representation), State Table, and Excitation Table. Is this a Mealy or a Moore machine? Why?
- Provide the excitation equations (simplify your circuit using K-maps or the Quine-McCluskey algorithm) (5 pts)
- Sketch the circuit. (3 pts)

- State Diagram, State Table, and Excitation Table:

State Assignment:

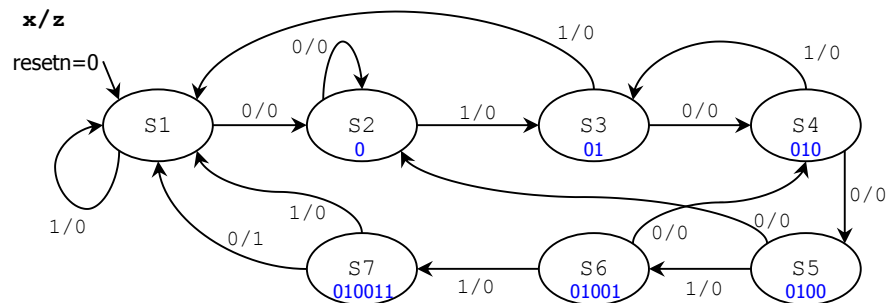S1: Q=000
S2: Q=001
S3: Q=010
S4: Q=011
S5: Q=100
S6: Q=101
S7: Q=110




PRESENT STATE				NEXT STATE			
x	STATE	STATE	z	x	Q ₂ Q ₁ Q ₀ (t)	Q ₂ Q ₁ Q ₀ (t+1)	z
0	S1	S2	0	0	0 0 0 0	0 0 1	0
0	S2	S2	0	0	0 0 0 1	0 0 1	0
0	S3	S4	0	0	0 0 1 0	0 1 1	0
0	S4	S5	0	0	0 0 1 1	1 0 0	0
0	S5	S2	0	0	0 1 0 0	0 0 1	0
0	S6	S4	0	0	0 1 0 1	0 1 1	0
0	S7	S1	1	0	0 1 1 0	0 0 0	1
1	S1	S1	0	0	0 1 1 1	X X X	X
1	S2	S3	0	1	1 0 0 0	0 0 0	0
1	S3	S1	0	1	1 0 0 1	0 1 0	0
1	S4	S3	0	1	1 0 1 0	0 0 0	0
1	S5	S6	0	1	1 0 1 1	0 1 0	0
1	S6	S7	0	1	1 1 0 0	1 0 1	0
1	S7	S1	0	1	1 1 0 1	1 1 0	0
				1	1 1 1 0	0 0 0	0
				1	1 1 1 1	X X X	X

This is a Mealy FSM. The output 'z' depends on the input as well as on the present state.

- Excitation equations, minimization, and circuit implementation:

$$\begin{aligned}
 Q_2(t+1) &\leftarrow xQ_2\bar{Q}_1 + \bar{x}Q_1Q_0 \\
 Q_1(t+1) &\leftarrow Q_2Q_0 + xQ_0 + \bar{x}Q_2Q_1\bar{Q}_0 \\
 Q_0(t+1) &\leftarrow \bar{x}\bar{Q}_1 + Q_2\bar{Q}_1\bar{Q}_0 + \bar{x}Q_2\bar{Q}_0 \\
 z &= \bar{x}Q_2Q_1
 \end{aligned}$$

$\mathbf{z}$ Q_1Q_0	xQ_2 00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	X	X	0
10	0	1	0	0

 

PROBLEM 3 (12 PTS)

- Provide the State Diagram (any representation), the Excitation Table, and the Excitation equations of the following FSM.

w: input, z: output, Q_1Q_0 : state.

$$Q_1(t+1) \leftarrow (Q_1 + Q_0)w$$


$$Q_0(t+1) \leftarrow \overline{Q_1} \oplus w$$

$$z = w\overline{Q_1}Q_0$$

State Assignment:

S1: $Q=00$ S2: $Q=01$


S3: $Q=10$ S4: $Q=11$

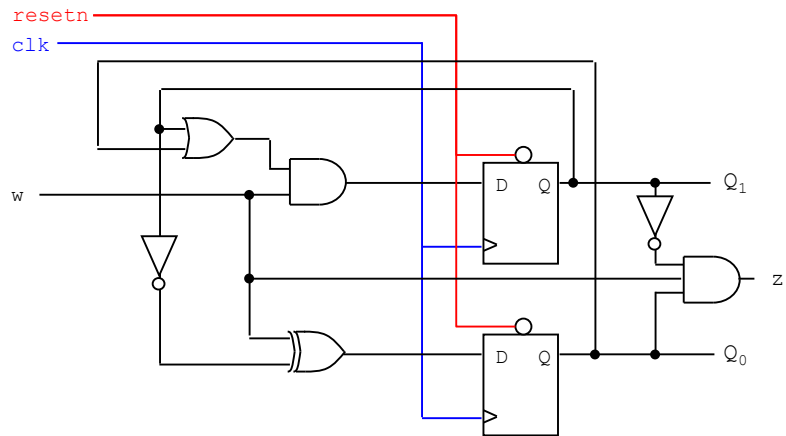

PRESENT STATE			NEXTSTATE		
w	$Q_1Q_0(t)$		$Q_1Q_0(t+1)$	z	
0	0 0	0	0 1	0	
0	0 1	0	0 1	0	
0	1 0	0	0 0	0	
0	1 1	0	0 0	0	
1	0 0	0	0 0	0	
1	0 1	1	1 0	1	
1	1 0	1	1 1	0	
1	1 1	1	1 1	0	



w	PRESENT STATE	NEXT STATE	z
0	S1	S2	0
0	S2	S2	0
0	S3	S1	0
0	S4	S1	0
1	S1	S1	0
1	S2	S3	1
1	S3	S4	0
1	S4	S4	0

 

PROBLEM 4 (17 PTS)


- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. Is it a Mealy or a Moore FSM?
- Complete the Timing Diagram.

```

library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( clk, resetn: in std_logic;
        r, p, q: in std_logic;
        x, w, z: out std_logic);
end circ;

```

 


```

architecture behavioral of circ is
  type state is (S1, S2, S3);
  signal y: state;
begin
  Transitions: process (resetn, clk, r, p, q)
  begin
    if resetn = '0' then y <= S1;
    elsif (clk'event and clk = '1') then
      case y is
        when S1 =>
          if r = '1' then
            y <= S2;
          else
            if p = '1' then y <= S1; else y <= S3; end if;
          end if;
        when S2 =>
          if p = '1' then y <= S1; else y <= S3; end if;
        when S3 =>
          if q = '1' then y <= S3; else y <= S2; end if;
      end case;
    end if;
  end process;

  Outputs: process (y, r, p, q)
  begin
    x <= '0'; w <= '0'; z <= '0';
    case y is
      when S1 => if r = '0' then
                    if p = '1' then
                      w <= '1'; x <= '1';
                    end if;
                  end if;
      when S2 => if q = '0' then x <= '1'; end if;
                  if p = '0' then z <= '1'; end if;
      when S3 => if q = '0' then x <= '1'; end if;
    end case;
  end process;
end behavioral;



```

 This is a Mealy FSM. The outputs 'x,w,z' depend on the input as well as on the present state.



  PROBLEM 5 (18 PTS)

- Complete the timing diagram of the following digital circuit that includes an FSM (in ASM form) and a datapath circuit.



PROBLEM 6 (15 PTS)

- Attach a printout of your Project Status Report (no more than three pages, single-spaced, 2 columns). This report should contain the current status of the project. You **MUST** use the provided template (Final Project - Report Template.docx).