



Tic Tac Toe with VGA Display

By: John Akroush, Nicholas Wheelis, Tao Wang

1	2	3
4	5	6
7	8	9

Introduction


- Tic tac toe is a staple pastime for people to play with friends when they are bored. Instead of using X's and O's as the player marker, red and green rectangles are used. This project covers registers, decoders, multiplexers, addresses, and time with clocks. The project taught us how to display code to a VGA display.

How to Play

- To play Tic Tac Toe on this FPGA device, we start by using SW₀ and SW₁ to select the player. Next, the player will use SW₂ through SW₅ to select the rectangle the player wants to take. The player will then enable the system using SW₆ to store their selection into the registers which will also display their color in the selected rectangle on the VGA display. After a player has won, they should press the resetn button to restart the game.


Main Design

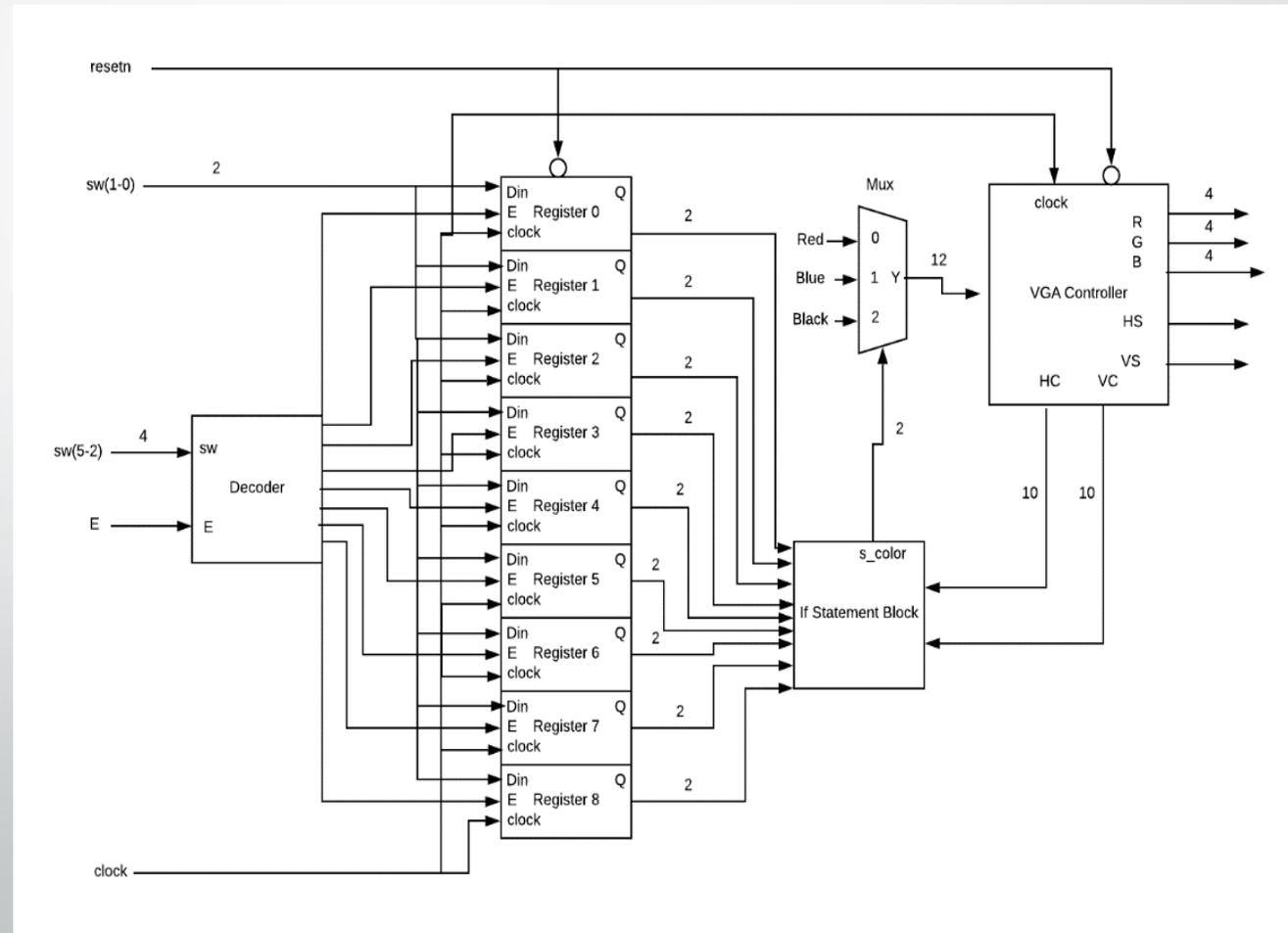- The main parts of this design are a decoder with enable, nine registers, a circuit with a list of if statements, a multiplexer, and a VGA display controller.




Decoder

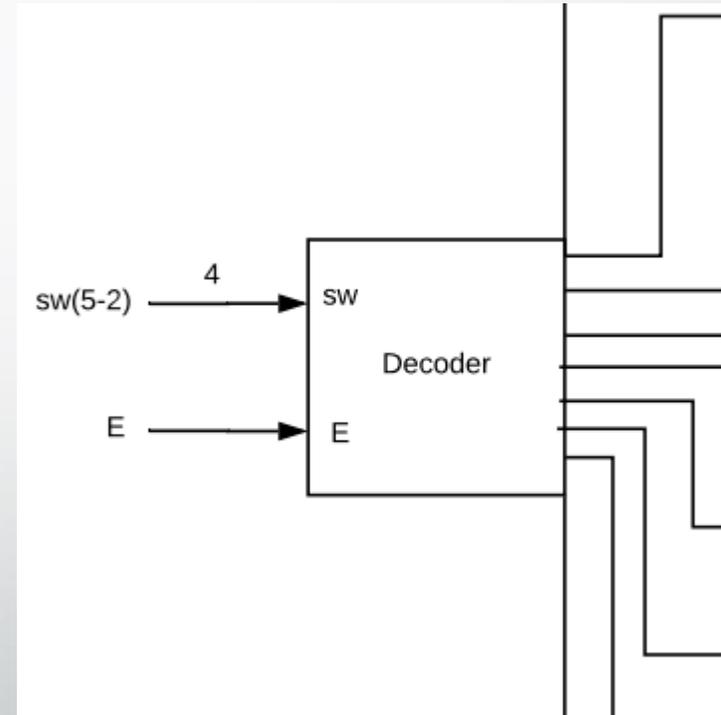- The decoder is used to enable a certain register that the player chooses which corresponds to one rectangle location on the tic tac toe board and is based on their address input. For example: an address of 0110 would enable register 6, which corresponds to the bottom-left rectangle on the board. SW₂-SW₅ are used for the address values, and SW₆ is used for the enable.




Registers

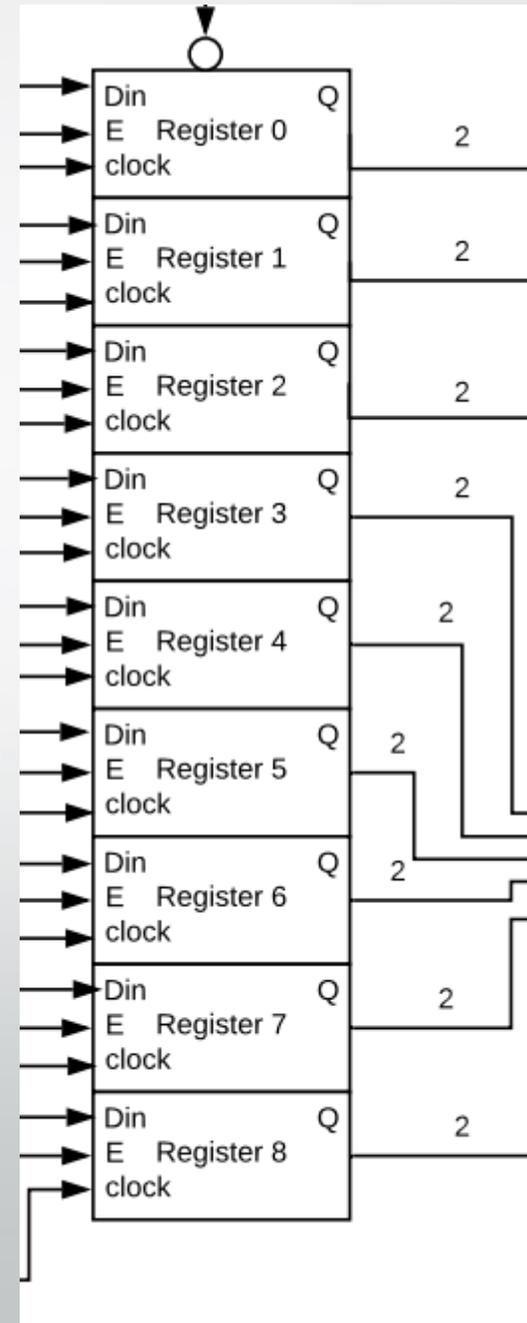- The registers in this design act as the “memory” of the system so when the player ends their turn, their selection is saved. The input of the register is based on SW₀ and SW₁, which is the player number. The register that is used is based on the address put into the decoder.



If Statement Block

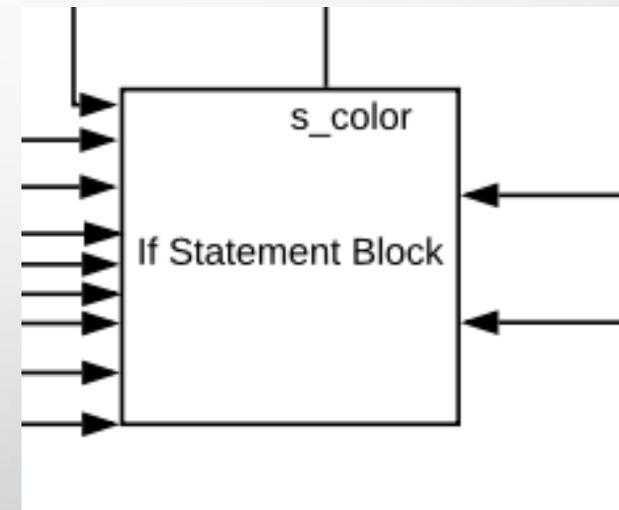- This part of the design is a collection of If statements to decide, based on the H-count and V-count locations, which is from the VGA controller, and all the outputs of the registers to conclude what color goes to which Tic Tac Toe tile.




- If statements for first 5 rectangle box locations on display.

```
70 ⊖ if (HC >= "0000000000") AND (HC <= "0011010100") AND (VC >= "0000000000") AND (VC <= "0010011111") then
71 ⊖   if r0 = "01" then
72     s_color <= "01";
73   elsif r0 = "10" then
74     s_color <= "10";
75   else
76     s_color <= "11";
77 ⊖   end if;
78 ⊖ end if;
79
80 --if "0100000110" <= HC <= "0111011011" AND "0000100001" <= VC <= "0011000000" then
81 ⊖ if (HC >= "0011010101") AND (HC <= "0110101001") AND (VC >= "0000000000") AND (VC <= "0010011111") then
82 ⊖   if r1 = "01" then
83     s_color <= "01";
84   elsif r1 = "10" then
85     s_color <= "10";
86   else
87     s_color <= "11";
88 ⊖   end if;
89 ⊖ end if;
90
91 --if "0111011100" <= HC <= "1010101111" AND "0000100001" <= VC <= "0011000000" then
92 ⊖ if (HC >= "0110101010") AND (HC <= "1001111111") AND (VC >= "0000000000") AND (VC <= "0010011111") then
93 ⊖   if r2 = "01" then
94     s_color <= "01";
95   elsif r2 = "10" then
96     s_color <= "10";
97   else
98     s_color <= "11";
99 ⊖   end if;
100 ⊖ end if;
101
102 --if "0000110000" <= HC <= "0100000101" AND "0011000001" <= VC <= "0101100000" then
103 ⊖ if (HC >= "0000000000") AND (HC <= "0011010100") AND (VC >= "0010100000") AND (VC <= "0100111111") then
104 ⊖   if r3 = "01" then
105     s_color <= "01";
106   elsif r3 = "10" then
107     s_color <= "10";
108   else
109     s_color <= "11";
110 ⊖   end if;
111 ⊖ end if;
112
113 --if "0100000110" <= HC <= "0111011011" AND "0011000001" <= VC <= "0101100000" then
114 ⊖ if (HC >= "0011010101") AND (HC <= "0110101001") AND (VC >= "0010100000") AND (VC <= "0100111111") then
115 ⊖   if r4 = "01" then
116     s_color <= "01";
117   elsif r4 = "10" then
118     s_color <= "10";
119   else
120     s_color <= "11";
121 ⊖   end if;
122 ⊖ end if;
```



Multiplexer

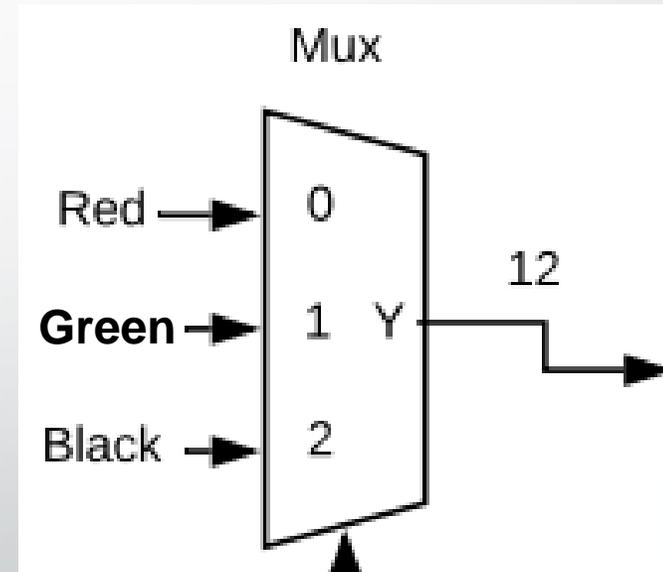- The mux in this design is simple. Its input is the s_color that the If Statement Block outputs. This input selects one of the 3 color inputs of the mux and outputs the 12-bit value for that color.



VGA Controller

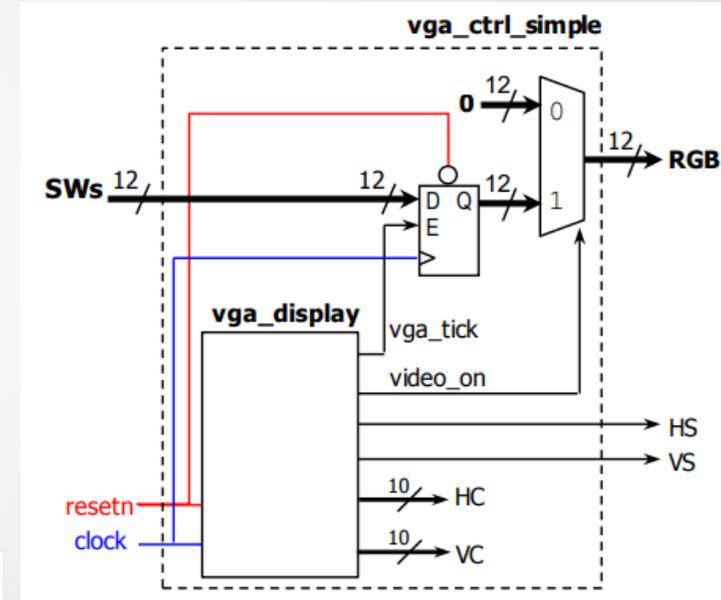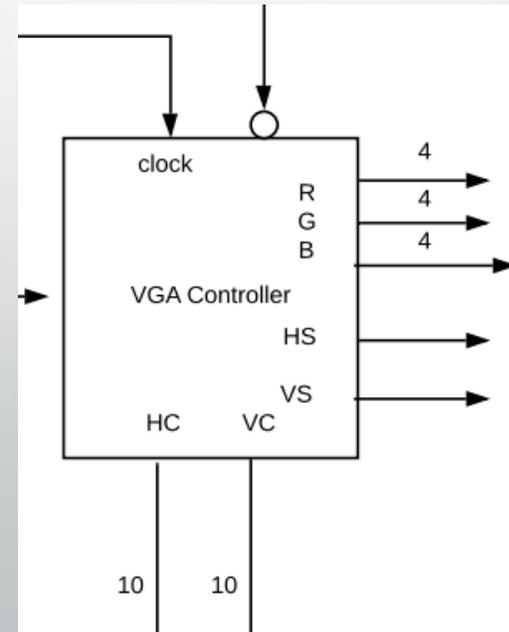- The vga_ctrl_simple component is used to control the VGA display. It uses a 12-bit input to control the color of the pixels.



Demonstration

