


# Homework 3

(Due date: March 14<sup>th</sup> @ 5:30 pm)


Presentation and clarity are very important! Show your procedure!
 
## PROBLEM 1 (12 PTS)

- Complete the timing diagram of the circuit shown below. (5 pts)




 - Complete the timing diagram of the circuits shown below: (7 pts)



 
## PROBLEM 2 (33 PTS)

- Complete the timing diagram of the circuit shown below: (10 pts)



 - Complete the timing diagram of the circuit shown below: (7 pts)



- Complete the timing diagram of the circuit whose VHDL description is shown below: (6 pts)

```


library ieee;
use ieee.std_logic_1164.all;

entity circ is
    port ( prn, a , clk: in std_logic;
          q: out std_logic);
end circ;


architecture t of circ is
    signal qt: std_logic;

begin
    process (prn, clk, x, a)
    begin
        if prn = '0' then
            qt <= '1';
        else
            if (clk'event and clk = '0') then
                if x = '1' then
                    qt <= a xnor (not qt);
                end if;
            end if;
            q <= qt;
        end process;
    end t;

```

 


 - The following circuit is a single-input compressor circuit (SIC), a component in Built-in Self-Test systems. Complete the timing diagram of the following circuit:  $Q = Q_3Q_2Q_1Q_0$  (10 pts)



 
**PROBLEM 3 (18 PTS)**

- Given the following circuit, complete the timing diagram (signals *DO*, *Q* and *DATA*). The LUT 6-to-6 implements the following function:  $OLUT = [ILUT^{0.91}]$ , where *ILUT* is an unsigned number. For example  $ILUT = 35 (100011_2) \rightarrow OLUT = [35^{0.91}] = 26 (011010_2)$



 **PROBLEM 4 (12 PTS)**

- Complete the timing diagram of the following 4-bit parallel access shift register with enable input. Shifting operation:  $s\_1=0$ . Parallel load:  $s\_1=1$ . Note that  $Q = Q_3Q_2Q_1Q_0$ .  $D = D_3D_2D_1D_0$



**PROBLEM 5 (25 PTS)**

- For the following circuit, do:  $R = R_3R_2R_1R_0$ .  $G = G_3G_2G_1G_0$ 
  - Write structural VHDL code. Create two files: i) flip flop, ii) top file (where you will interconnect the flip flops and the logic gates). Provide a printout. (10 pts)
  - Write a VHDL testbench according to the timing diagram shown below. Complete the timing diagram by simulating your circuit (Behavioral Simulation). The clock frequency must be 100 MHz with 50% duty cycle. Provide a printout. (15 pts)

