

Laboratory 2

(Due date : **002/003**: February 4th, **004**: February 5th, **005**: February 6th)

OBJECTIVES

- ✓ Use the Structural Description on VHDL.
- ✓ Test arithmetic circuits on an FPGA.

VHDL CODING

- ✓ Refer to the [Tutorial: VHDL for FPGAs](#) for a list of examples.


FIRST ACTIVITY (100/100)

- **PROBLEM:** BCD Addition of two numbers. The operands (A and B) are 4-bit numbers represented in BCD (where only numbers from 0 to 9 are allowed). The result S is also represented in BCD. There is also a BCD carry out ($cout$). If any of the operands is greater than 9, the result S is invalid.

 
Example: $7 + 8 = 15$. Here, $cout = 1$, and $S = 0101 = 5$.

This circuit can be built out of two 4-bit binary adders and a few logic gates as depicted in the figure \Rightarrow

- ✓ Operation: If $A + B > 9 \rightarrow S = 6 + Z$, $cout = 1$. Here, by adding 6, we "correct" the binary sum to make it look as BCD code. If $A + B \leq 9 \rightarrow S = Z$, $cout = 0$.




 - The figure below depicts the internal architecture of the 4-bit binary adder. The full adder circuit is also shown.



- ✓ **NEXYS A7-50T:** Create a new Vivado Project. Select the **XC7A50T-1CSG324 Artix-7 FPGA** device.
- ✓ Write the VHDL code for the BCD Adder. Use the Structural Description: Create a separate file for the Full Adder, the 4-bit adder, the 'CMP' block, and the top file (BCD Adder).
- ✓ Write the VHDL testbench to test the circuit for the following cases:
 - ♦ $A=0x9$, $B=0x8$, $cin=0 \rightarrow cout=1$, $S=0111$
 - ♦ $A=0x6$, $B=0x7$, $cin=1 \rightarrow cout=1$, $S=0100$
 - ♦ $A=0x5$, $B=0x6$, $cin=1 \rightarrow cout=1$, $S=0010$
 - ♦ $A=0x3$, $B=0x6$, $cin=0 \rightarrow cout=0$, $S=1001$
 - ♦ $A=0x9$, $B=0x1$, $cin=0 \rightarrow cout=1$, $S=0000$

FULL ADDER

 

- ✓ Perform Functional Simulation and Timing Simulation of your design. **Demonstrate this to your TA.**
- ✓ I/O Assignment: Create the XDC file. Nexys A7-50T: Use SW15-SW0 for the inputs, and LED4-LED0 for the outputs.
- ✓ Generate and download the bitstream on the FPGA and test. **Demonstrate this to your TA.**

- Submit (as a .zip file) the five generated files: VHDL code (4 files), VHDL testbench, and XDC file to Moodle (an assignment will be created). DO NOT submit the whole Vivado Project.

TA signature: _____

Date: _____