


Solutions - Final Exam

(April 18th @ 7:00 pm)

Presentation and clarity are very important! Show your procedure!

 
PROBLEM 1 (11 PTS)

- Given the following circuit, complete the timing diagram.
 The LUT 6-to-6 implements the following function: $OLUT = \lceil \sqrt{ILUT} \rceil$, where $ILUT$ is a 6-bit unsigned number.
 For example $ILUT = 34 (100010_2) \rightarrow OLUT = \lceil \sqrt{34} \rceil = 6 (000110_2)$



 
PROBLEM 2 (12 PTS)

- Complete the timing diagram of the following circuit. $G = G_3G_2G_1G_0 = 1001$, $Q = Q_3Q_2Q_1Q_0$



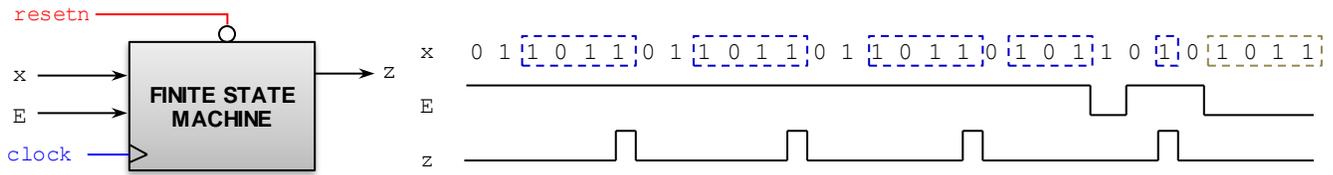PROBLEM 3 (22 PTS)


- Sequence detector: The machine has to generate $z = 1$ when it detects the sequence 1011. Once the sequence is detected, the circuit looks for a new sequence.
- The signal E is an input enable: It validates the input x , i.e., if $E = 1$, x is valid, otherwise x is not valid.



- Draw the State Diagram (any representation), State Table, and the Excitation Table of this circuit with inputs E and x and output z . Is this a Mealy or a Moore machine? Why? (15 pts)
- Provide the excitation equations (simplify your circuit using K-maps or the Quine-McCluskey algorithm) (4 pts)
- Sketch the circuit. (3 pts)

.....

 ▪ *State Diagram, State Table, and Excitation Table:*



State Assignment:
 S1: $Q=00$ S2: $Q=01$
 S3: $Q=10$ S4: $Q=11$

PRESENT STATE		NEXT STATE		z
E	x	STATE	STATE	
0	0	S1	S1	0
0	0	S2	S2	0
0	0	S3	S3	0
0	0	S4	S4	0
0	1	S1	S1	0
0	1	S2	S2	0
0	1	S3	S3	0
0	1	S4	S4	0
1	0	S1	S1	0
1	0	S2	S3	0
1	0	S3	S1	0
1	0	S4	S3	0
1	1	S1	S2	0
1	1	S2	S2	0
1	1	S3	S4	0
1	1	S4	S1	1

PRESENT STATE		NEXT STATE		z
E	x	$Q_1Q_0(t)$	$Q_1Q_0(t+1)$	
0	0	00	00	0
0	0	01	01	0
0	0	10	10	0
0	0	11	11	0
0	1	00	00	0
0	1	01	01	0
0	1	10	11	0
0	1	11	11	0
1	0	00	00	0
1	0	01	10	0
1	0	10	10	0
1	0	11	10	0
1	1	00	01	0
1	1	01	01	0
1	1	10	11	0
1	1	11	00	1

This is a Mealy Machine. The output 'z' depends on the input as well as on the present state.

- Excitation equations, minimization, and circuit implementation:*


$$Q_1(t+1) = \bar{E}Q_1 + E\bar{x}Q_0 + xQ_1\bar{Q}_0$$

$$Q_0(t+1) = \bar{E}Q_0 + Ex\bar{Q}_0 + xQ_1Q_0$$

$$z = ExQ_1Q_0$$


Q_1Q_0	Ex			
	00	01	11	10
00	0	0	0	0
01	0	0	0	1
11	1	1	0	1
10	1	1	1	0

Q_1Q_0	Ex			
	00	01	11	10
00	0	0	1	0
01	1	1	1	0
11	1	1	0	0
10	0	0	1	0

 

 PROBLEM 4 (21 PTS)

- Given the following State Machine Diagram. (9 pts)
 - Is this a Mealy or a Moore machine? Why?
 - Get the excitation equations and the Boolean equation for z. Use S1 (Q=00), S2 (Q=01), S3 (Q=10), S4 (Q=11) to encode the states.



x	PRESENT STATE		z	PRESENT STATE			NEXTSTATE		
	STATE	STATE		x	Q ₁ Q ₀ (t)	Q ₁ Q ₀ (t+1)	z		
0	S1	S3	0	0	0	0	1	0	0
0	S2	S2	0	0	0	1	0	1	0
0	S3	S2	0	0	1	0	0	1	0
0	S4	S1	1	0	1	1	0	0	1
1	S1	S2	0	1	0	0	0	1	0
1	S2	S4	0	1	0	1	1	1	0
1	S3	S4	0	1	1	0	1	1	0
1	S4	S3	0	1	1	1	1	0	0


$$Q_1(t+1) \leftarrow x \oplus (Q_1(t) + Q_0(t))$$

$$Q_0(t+1) \leftarrow (Q_1(t) \oplus Q_0(t)) + xQ_0(t)$$



$$z = \bar{x}Q_1(t)Q_0(t)$$

This is a Mealy Machine. The output 'z' depends on the input as well as on the present state.

 - The following FSM has 4 states, one input w and one output z. (12 pts)
 - The excitation equations are given by:
 - $Q_1(t+1) \leftarrow Q_0(t)$
 - $Q_0(t+1) \leftarrow Q_1(t) \oplus w$
 - The output equation is given by: $z = Q_1(t) \oplus Q_0(t) \oplus w$



w	PRESENT STATE		z	PRESENT STATE			NEXTSTATE		
	Q ₁ Q ₀ (t)	Q ₁ Q ₀ (t+1)		w	STATE	STATE	z		
0	0 0	0 1	0	0	S1	S2	0		
0	0 1	1 1	1	0	S2	S4	1		
0	1 0	0 0	1	0	S3	S1	1		
0	1 1	1 0	0	0	S4	S3	0		
1	0 0	0 0	1	1	S1	S1	1		
1	0 1	1 0	0	1	S2	S3	0		
1	1 0	0 1	0	1	S3	S2	0		
1	1 1	1 1	1	1	S4	S4	1		

  


PROBLEM 5 (16 PTS)

- Draw the State Diagram (in ASM form) of the FSM whose VHDL description in shown below. Is it a Mealy or a Moore FSM?
- Complete the Timing Diagram.

```

library ieee;
use ieee.std_logic_1164.all;

 entity circ is
    port ( clk, resetn: in std_logic;
          r, p, q: in std_logic;
          x, w, z: out std_logic);
end circ;
    
```




```

architecture behavioral of circ is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (resetn, clk, r, p, q)
    begin
        if resetn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if r = '1' then
                        y <= S2;
                    else
                        if p = '1' then y <= S3; else y <= S1; end if;
                    end if;
                when S2 =>
                    if p = '1' then y <= S1; else y <= S3; end if;
                when S3 =>
                    if q = '1' then y <= S3; else y <= S2; end if;
            end case;
        end if;
    end process;

    Outputs: process (y, r, p, q)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => if r = '0' then
                x <= '1';
                if p = '0' then
                    w <= '1';
                end if;
            end if;
            when S2 => if q = '0' then w <= '1'; end if;
                if p = '0' then z <= '1'; end if;
            when S3 => if q = '0' then w <= '1'; end if;
        end case;
    end process;
end behavioral;
    
```

 This is a Mealy Machine. The outputs 'x,w,z' depend on the input as well as on the present state.



PROBLEM 6 (18 PTS)

- “Counting 1’s” Circuit: It counts the number of bits in register A that has the value of ‘1’.

The digital system is depicted below: FSM + Datapath. Example: For $n = 8$: if $A = 00110110$, then $C = 0100$.

 - ✓ m-bit counter: If $E = sclr = 1$, the count is initialized to zero. If $E = 1, sclr = 0$, the count is increased by 1.
 - ✓ Parallel access shift register: If $E = 1: s_l = 1 \rightarrow$ Load, $s_l = 0 \rightarrow$ Shift.
- Complete the timing diagram where $n = 8, m = 4$. A is represented in hexadecimal format, while C is in binary format.

