

Solutions - Homework 1

(Due date: January 17th @ 5:30 pm)
Presentation and clarity are very important!

PROBLEM 1 (27 PTS)

a) Simplify the following functions using ONLY Boolean Algebra Theorems. For each resulting simplified function, sketch the logic circuit using AND, OR, XOR, and NOT gates. (14 pts)


✓ $F = \overline{A(B + \overline{C})} + A$

✓ $F = (Z + X)(\overline{Z} + \overline{Y})(\overline{Y} + X)$


✓ $F(X, Y, Z) = \prod(M_2, M_4, M_6, M_7)$

✓ $F = \overline{(X + Y)Z} + \overline{X\overline{Y}\overline{Z}}$

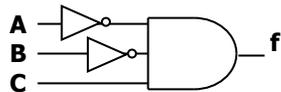
✓ $F = \overline{A(B + \overline{C})} + A = \overline{A(B + \overline{C})} \cdot \overline{A} + (A + B + \overline{C}) \cdot \overline{A} = (\overline{B + \overline{C}}) \cdot \overline{A} = \overline{A} \overline{B} \overline{C}$



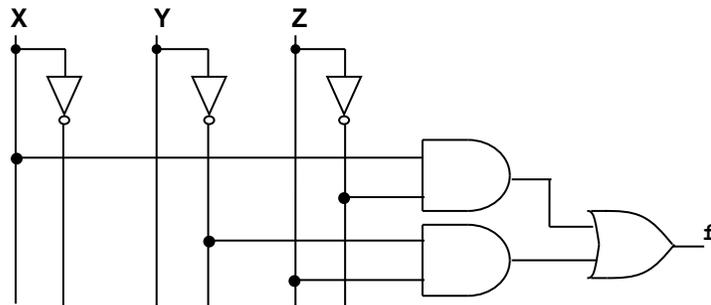
✓ $F = (Z + X)(\overline{Z} + \overline{Y})(X + \overline{Y}) = (Z + X)(\overline{Z} + \overline{Y})$ (Consensus Theorem)
 $(Z + X)(\overline{Z} + \overline{Y}) = Z\overline{Y} + \overline{Z}X + X\overline{Y} = Z\overline{Y} + \overline{Z}X$ (Consensus Theorem)



✓ $F(X, Y, Z) = \prod(M_2, M_4, M_6, M_7) = \sum(m_0, m_1, m_3, m_5) = \overline{X}\overline{Y}\overline{Z} + \overline{X}\overline{Y}Z + \overline{X}Y\overline{Z} + X\overline{Y}\overline{Z} = \overline{X}\overline{Y} + \overline{X}Y\overline{Z} + X\overline{Y}\overline{Z}$
 $F(X, Y, Z) = \overline{X}\overline{Y} + \overline{X}Y\overline{Z} + X\overline{Y}\overline{Z} = \overline{X}(\overline{Y} + Y\overline{Z}) + X\overline{Y}\overline{Z} = \overline{X}(\overline{Y} + Z) + X\overline{Y}\overline{Z} = \overline{X}\overline{Y} + \overline{X}Z + X\overline{Y}\overline{Z}$
 $F(X, Y, Z) = \overline{X}\overline{Y} + \overline{X}Z + X\overline{Y}\overline{Z} = \overline{X}\overline{Y} + Z(\overline{X} + X\overline{Y}) = \overline{X}\overline{Y} + Z(\overline{X} + \overline{Y}) = \overline{X}\overline{Y} + Z\overline{X} + Z\overline{Y}$

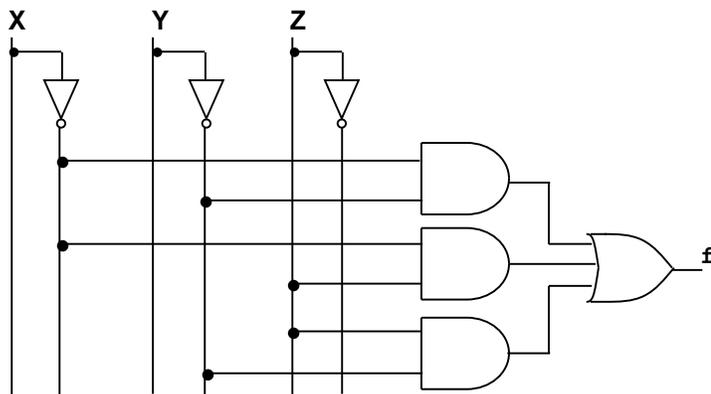

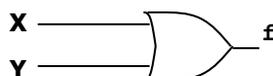✓ $F = \overline{(X + Y)Z} + \overline{X\overline{Y}\overline{Z}} = \overline{(X + Y)Z} \cdot \overline{X\overline{Y}\overline{Z}} = (X + Y + \overline{Z})(X + Y + Z) = (A + \overline{Z})(A + Z), A = X + Y$
 $F = (A + \overline{Z})(A + Z) = A = X + Y$



b) Using ONLY Boolean Algebra Theorems, demonstrate that the XOR operation is associative: (5 pts)

$$(a \oplus b) \oplus c = a \oplus (b \oplus c) = b \oplus (a \oplus c)$$

.....

$(a \oplus b) \oplus c = (a\bar{b} + \bar{a}b) \oplus c = (\overline{a\bar{b} + \bar{a}b})c + (a\bar{b} + \bar{a}b)\bar{c} = (ab + \bar{a}\bar{b})c + (a\bar{b} + \bar{a}b)\bar{c} = abc + \bar{a}\bar{b}c + a\bar{b}\bar{c} + \bar{a}b\bar{c} = \sum m(7,1,4,2).$
 $a \oplus (b \oplus c) = a \oplus (b\bar{c} + \bar{b}c) = a(bc + \bar{b}\bar{c}) + \bar{a}(b\bar{c} + \bar{b}c) = abc + a\bar{b}\bar{c} + \bar{a}b\bar{c} + \bar{a}\bar{b}c = \sum m(7,4,2,1).$
 $b \oplus (a \oplus c) = (a \oplus c) \oplus b = (a\bar{c} + \bar{a}c) \oplus b = (ac + \bar{a}\bar{c})b + (a\bar{c} + \bar{a}c)\bar{b} = acb + \bar{a}\bar{c}b + a\bar{c}\bar{b} + \bar{a}c\bar{b} = \sum m(7,2,4,1).$
 * Note that $x \oplus y = y \oplus x$

c) For the following Truth table with two outputs: (8 pts)

- Provide the Boolean functions using the Canonical Sum of Products (SOP), and Product of Sums (POS).
- Express the Boolean functions using the minterms and maxterms representations.
- Sketch the logic circuits as Canonical Sum of Products and Product of Sums.

x	y	z	f ₁	f ₂
0	0	0	0	0
0	0	1	1	0
0	1	0	1	1
0	1	1	1	1
1	0	0	1	0
1	0	1	0	1
1	1	0	1	1
1	1	1	0	1

Sum of Products

$$f_1 = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + \bar{X}YZ + X\bar{Y}\bar{Z} + XYZ$$


$$f_2 = \bar{X}Y\bar{Z} + \bar{X}YZ + X\bar{Y}Z + XY\bar{Z} + XYZ$$

Product of Sums

$$f_1 = (X + Y + Z)(\bar{X} + Y + \bar{Z})(\bar{X} + \bar{Y} + \bar{Z})$$


$$f_2 = (X + Y + Z)(X + Y + \bar{Z})(\bar{X} + Y + Z)$$

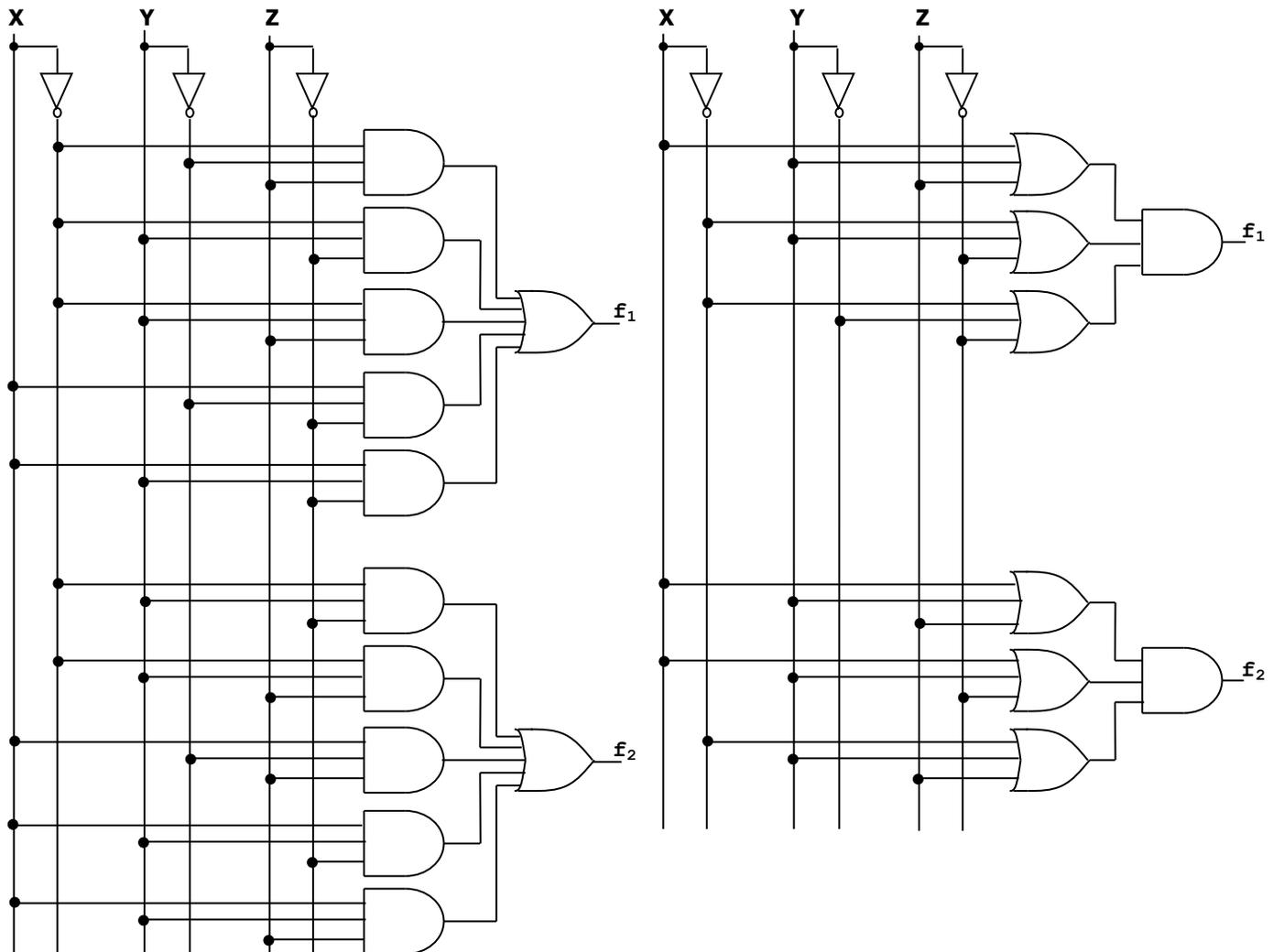Minterms and maxterms: $f_1 = \sum(m_1, m_2, m_3, m_4, m_6) = \prod(M_0, M_5, M_7).$
 $f_2 = \sum(m_2, m_3, m_5, m_6, m_7) = \prod(M_0, M_1, M_4).$



PROBLEM 2 (25 PTS)

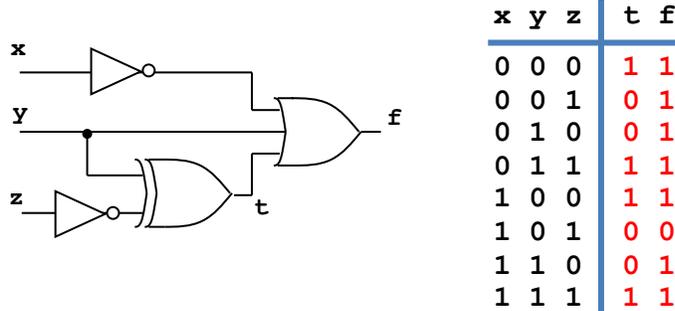a) Construct the truth table describing the output of the following circuit and write the simplified Boolean equation (6 pts).



$f = \bar{x} + y + \bar{z}$


b) Complete the timing diagram of the logic circuit whose VHDL description is shown below: (6 pts)

```

library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end circ;

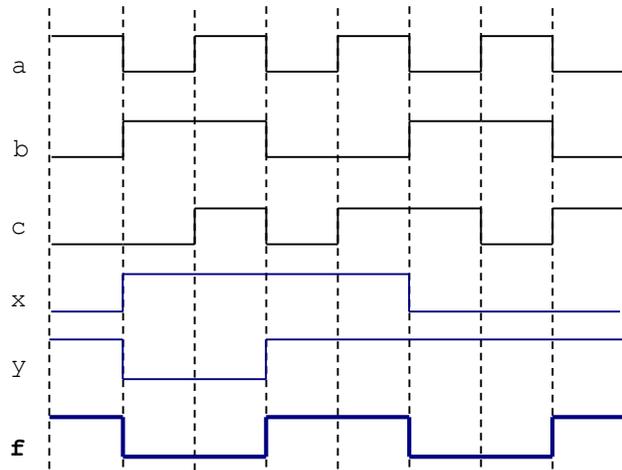architecture struct of circ is
  signal x, y: std_logic;
begin
  x <= a xor (not c);
  y <= x nand b;
  f <= y and (not b);
end struct;
    
```




c) The following is the timing diagram of a logic circuit with 3 inputs. Sketch the logic circuit that generates this waveform. Then, complete the VHDL code. (8 pts)

```



library ieee;
use ieee.std_logic_1164.all;

entity wav is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end wav;


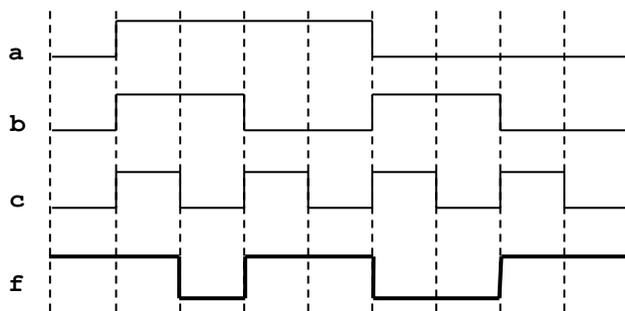
architecture struct of wav is
begin
  f <= not(b) or (a and c);
end struct;
    
```



a	b	c	f
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

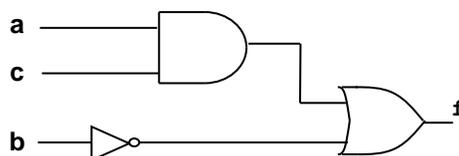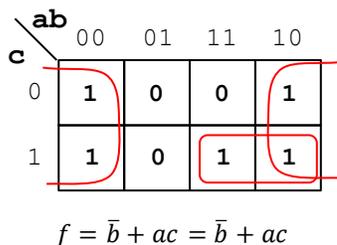


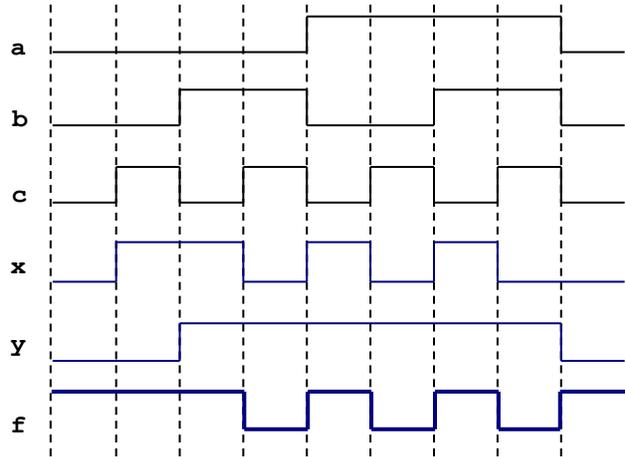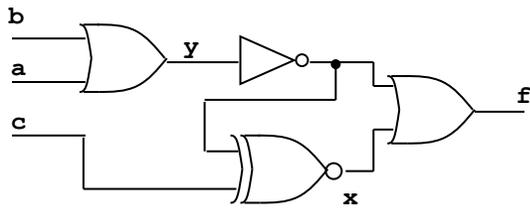d) Complete the timing diagram of the following circuit: (5 pts)




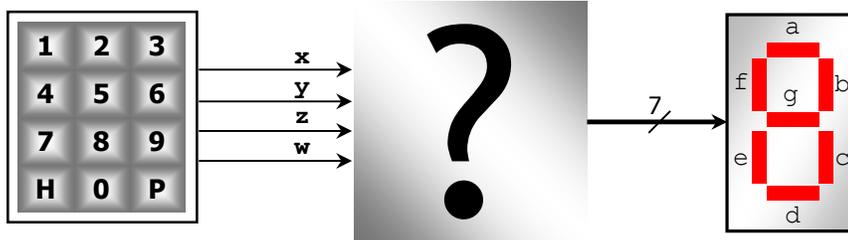PROBLEM 3 (25 PTS)

- A numeric keypad produces a 4-bit code as shown below. We want to design a logic circuit that converts each 4-bit code to a 7-segment code, where each segment is an LED: A LED is ON if it is given a logic '1'. A LED is OFF if it is given a logic '0'.
 - ✓ Complete the truth table for each output (a, b, c, d, e, f, g).
 - ✓ Provide the simplified expression for each output (a, b, c, d, e, f, g). Use Karnaugh maps for c, d, e, f, g and the Quine-McCluskey algorithm for a, b . Note: It is safe to assume that the codes 1100 to 1111 will not be produced by the keypad.




Value	X	Y	Z	W	a	b	c	d	e	f	g
0	0	0	0	0							
1	0	0	0	1							
2	0	0	1	0							
3	0	0	1	1							
4	0	1	0	0							
5	0	1	0	1							
6	0	1	1	0							
7	0	1	1	1							
8	1	0	0	0							
9	1	0	0	1	1	1	1	1	0	1	1
P	1	0	1	0							
H	1	0	1	1							
	1	1	0	0							
	1	1	0	1							
	1	1	1	0							
	1	1	1	1							

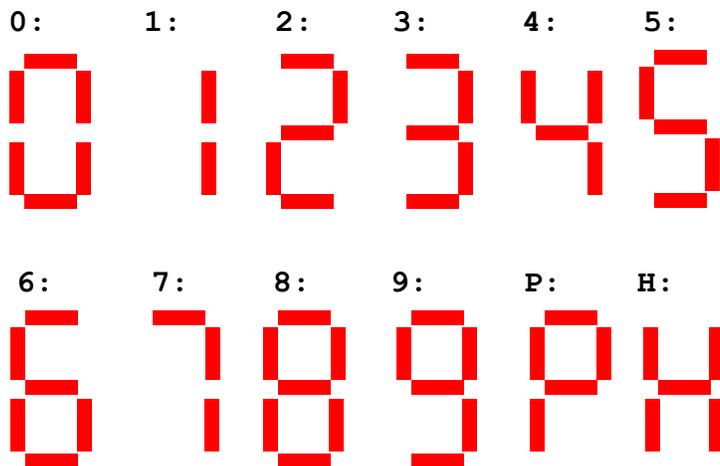

Value	X	Y	Z	W	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1
P	1	0	1	0	1	1	0	0	1	1	1
H	1	0	1	1	0	1	1	0	1	1	1
	1	1	0	0	X	X	X	X	X	X	X
	1	1	0	1	X	X	X	X	X	X	X
	1	1	1	0	X	X	X	X	X	X	X
	1	1	1	1	X	X	X	X	X	X	X

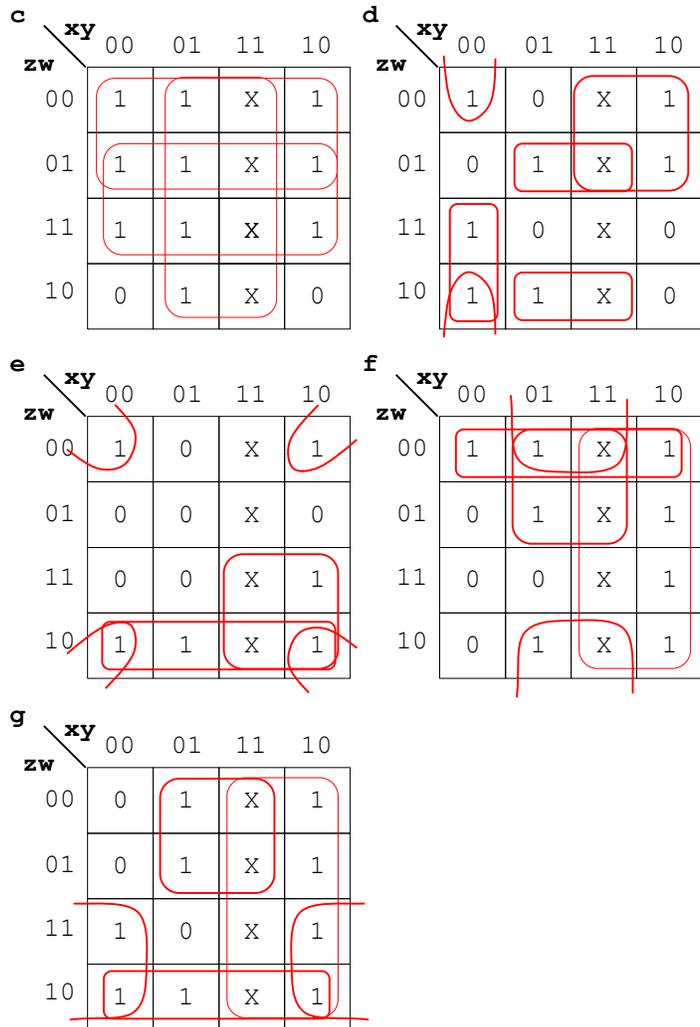$c = y + \bar{z} + w$
 $d = x\bar{z} + \bar{x}\bar{y}w + \bar{x}\bar{y}z + \bar{z}wy + z\bar{w}y$
 $e = \bar{w}\bar{y} + z\bar{w} + xz$
 $f = x + z\bar{w} + y\bar{z} + y\bar{w}$
 $g = x + z\bar{w} + y\bar{z} + \bar{y}z$



- $a = \sum m(0,2,3,5,6,7,8,9,10) + \sum d(12,13,14,15)$.
 Too many minterms. We better optimize: $\bar{a} = \sum m(1,4,11) + \sum d(12,13,14,15)$

Number of ones	4-literal implicants	3-literal implicants	2-literal implicants	1-literal implicants
1	$m_1 = 0001$ $m_4 = 0100$ ✓	$m_{4,12} = -100$		
2	$m_{12} = 1100$ ✓	$m_{12,13} = 110-$ ✓ $m_{12,14} = 11-0$ ✓	$m_{12,13,14,15} = 11--$ $m_{12,14,13,15} = 11--$ ✓	
3	$m_{11} = 1011$ ✓ $m_{13} = 1101$ ✓ $m_{14} = 1110$ ✓	$m_{13,15} = 11-1$ ✓ $m_{14,15} = 111-$ ✓ $m_{11,15} = 1-11$		
4	$m_{15} = 1111$ ✓			

$\bar{a} = \bar{x}\bar{y}\bar{z}w + y\bar{z}\bar{w} + xz\bar{w} + xy$

Prime Implicants		Minterms		
		1	4	11
m_1	$\bar{x}\bar{y}\bar{z}w$	X		
$m_{4,12}$	$y\bar{z}\bar{w}$		X	
$m_{11,15}$	$xz\bar{w}$			X
$m_{12,13,14,15}$	xy			

$\bar{a} = \bar{x}\bar{y}\bar{z}w + y\bar{z}\bar{w} + xz\bar{w} \Rightarrow a = (x + y + z + \bar{w})(\bar{y} + z + w)(\bar{x} + \bar{z} + \bar{w})$

- $b = \sum m(0,1,2,3,4,7,8,9,10,11) + \sum d(12,13,14,15)$.
Too many minterms. We better optimize: $\bar{b} = \sum m(5,6) + \sum d(12,13,14,15)$

Number of ones	4-literal implicants	3-literal implicants	2-literal implicants	1-literal implicants
2	$m_5 = 0101$ ✓ $m_6 = 0110$ ✓ $m_{12} = 1100$ ✓	$m_{5,13} = -101$ $m_{6,14} = -110$ $m_{12,13} = 110-$ ✓ $m_{12,14} = 11-0$ ✓	$m_{12,13,14,15} = 11--$ $m_{12,14,13,15} = 11$ ✓	
3	$m_{13} = 1101$ ✓ $m_{14} = 1110$ ✓	$m_{13,15} = 11-1$ ✓ $m_{14,15} = 111-$ ✓		
4	$m_{15} = 1111$ ✓			


$$\bar{b} = \bar{x}\bar{y}\bar{z}w + yz\bar{w} + xzw + xy$$

Prime Implicants		Minterms	
		5	6
$m_{5,13}$	$y\bar{z}w$	X	
$m_{6,14}$	$yz\bar{w}$		X
$m_{12,13,14,15}$	xy		

$$\bar{b} = yz\bar{w} + yz\bar{w} \Rightarrow b = (\bar{y} + z + \bar{w})(\bar{y} + \bar{z} + w)$$

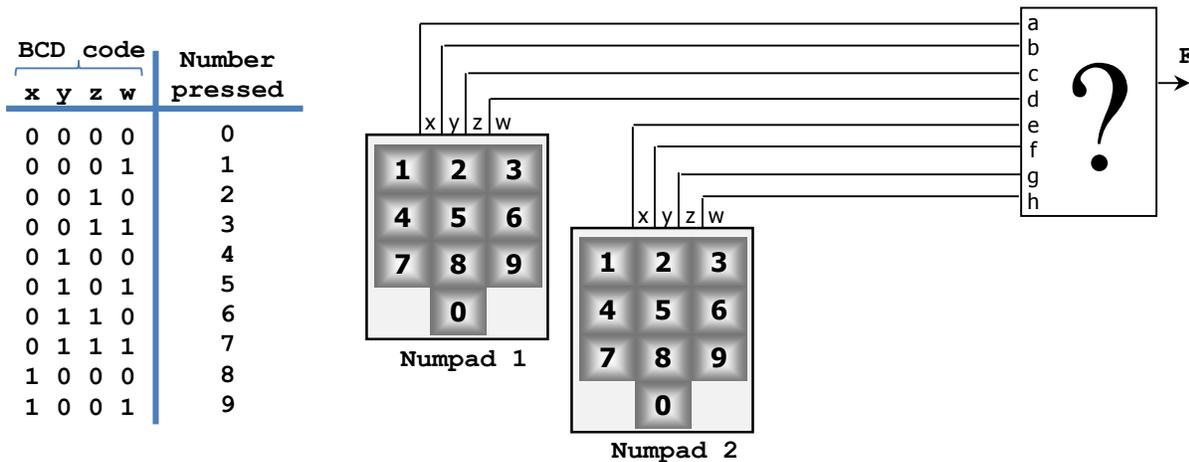PROBLEM 4 (12 PTS)

- Design a logic circuit (simplify your circuit) that opens a lock ($f = 1$) whenever the user presses the correct number on each numpad (numpad 1: **7**, numpad 2: **2**). The numpad encodes each decimal number using BCD encoding (see figure). We expect that the 4-bit groups generated by each numpad be in the range from 0000 to 1001. Note that the values from 1010 to 1111 are assumed not to occur.
Suggestion: Create two circuits: one that verifies the first number (**7**), and another that verifies the second number (**2**). Then perform the AND operation on the two outputs. This avoids creating a truth table with 8 inputs.




x	y	z	w	f ₁	f ₂
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	0
0	1	0	0	0	0
0	1	0	1	0	0
0	1	1	0	0	0
0	1	1	1	1	0
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	X	X
1	0	1	1	X	X
1	1	0	0	X	X
1	1	0	1	X	X
1	1	1	0	X	X
1	1	1	1	X	X

$f_1 = yzw$

zw \ xy	00	01	11	10
00	0	0	X	0
01	0	0	X	0
11	0	1	X	X
10	0	0	X	X

$f_2 = \bar{y}z\bar{w}$



zw \ xy	00	01	11	10
00	0	0	X	0
01	0	0	X	0
11	0	0	X	X
10	1	0	X	X

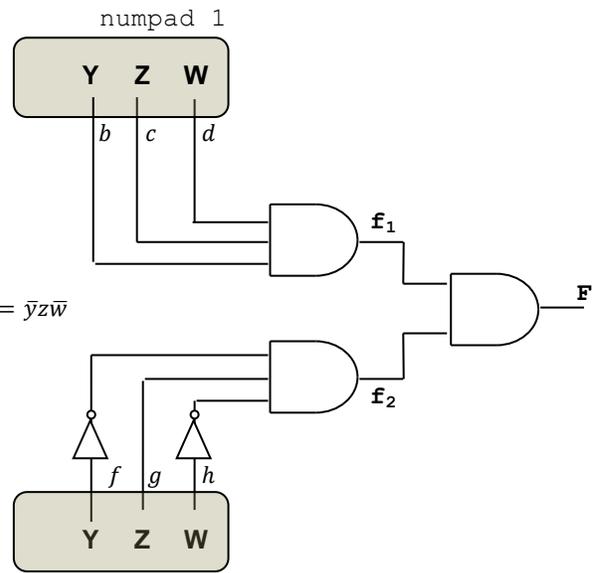

$$F = bcd\bar{f}g\bar{h} = (bcd)(\bar{f}g\bar{h})$$

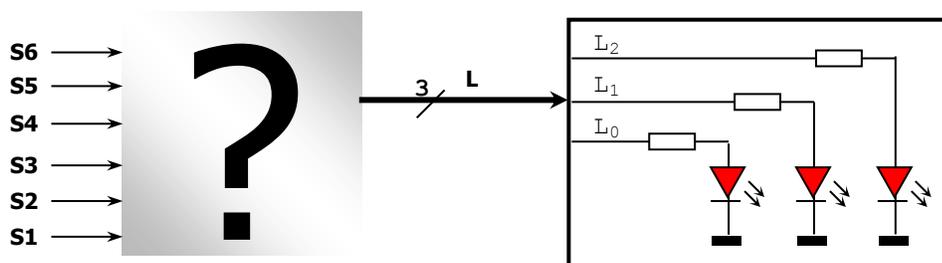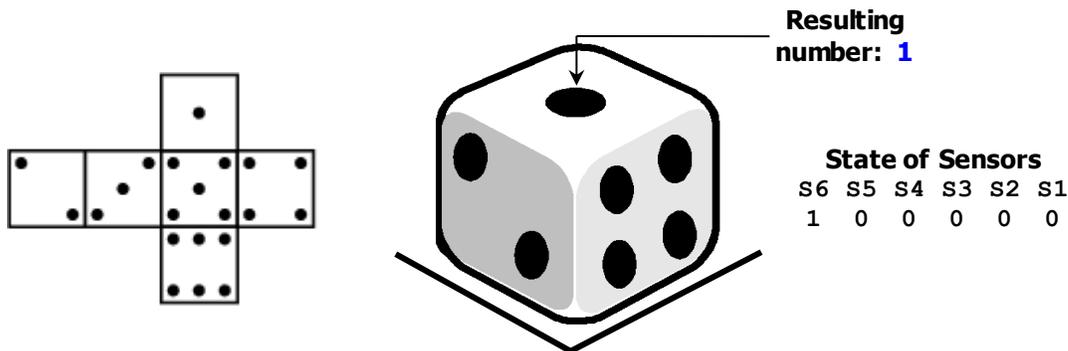PROBLEM 5 (11 PTS)

- The following die has a sensor on each side. Whenever a side rests on a surface, the sensor on that side generates a logic '1' (transmitted wirelessly to a controller); otherwise, it generates a '0'. The sensors outputs are named S1, S2, S3, S4, S5, S6.
- We want to design a circuit that reads the state of the 6 sensors and outputs a 3-bit value L representing the decimal value (unsigned integer) of the opposite side (upper surface). The output L is connected to 3 LEDs: A LED ON is represented by a logic '1', while the LED OFF is represented by '0'. For example, in the figure below:
 - The resting side has six dots. This means that the state of the sensors is S6=1, S5=0, S4=0, S3=0, S2=0, S1=0.
 - The opposite side (upper surface) has one dot representing the decimal number '1'. Thus, the output L must be 001.
- Under normal operation, we expect only one sensor activated at a time. However, due to a variety of problems, we might have the following cases:
 - Two or more sensors produce a '1' at the same time: Here, the state of the LEDs must be 000.
 - No sensor produces a '1': In this case, the state of the LEDs must be 000.
- Using the state of the sensors as inputs, provide the Boolean expression for each LED: L₂, L₁, L₀. First, build the truth table where the inputs are S6-S1 and the outputs are L2-L0.



L ₂	L ₁	L ₀	Number
0	0	0	-
0	0	1	1
0	1	0	2
0	1	1	3
1	0	0	4
1	0	1	5
1	1	0	6
1	1	1	-

S1	S2	S3	S4	S5	S6	L ₂	L ₁	L ₀	Number
0	0	0	0	0	0	0	0	0	-
0	0	0	0	0	1	0	0	1	1
0	0	0	0	1	0	0	1	0	2
0	0	0	1	0	0	0	1	1	3
0	0	1	0	0	0	1	0	0	4
0	1	0	0	0	0	1	0	1	5
1	0	0	0	0	0	1	1	0	6
					...	0	0	0	-

$$L_2 = \overline{S1} \overline{S2} \overline{S3} \overline{S4} \overline{S5} \overline{S6} + \overline{S1} \overline{S2} \overline{S3} \overline{S4} \overline{S5} \overline{S6} + S1 \overline{S2} \overline{S3} \overline{S4} \overline{S5} \overline{S6}$$

$$L_1 = \overline{S1} \overline{S2} \overline{S3} \overline{S4} \overline{S5} \overline{S6} + \overline{S1} \overline{S2} \overline{S3} \overline{S4} \overline{S5} \overline{S6} + S1 \overline{S2} \overline{S3} \overline{S4} \overline{S5} \overline{S6}$$

$$L_0 = \overline{S1} \overline{S2} \overline{S3} \overline{S4} \overline{S5} \overline{S6} + \overline{S1} \overline{S2} \overline{S3} \overline{S4} \overline{S5} \overline{S6} + \overline{S1} \overline{S2} \overline{S3} \overline{S4} \overline{S5} \overline{S6}$$