
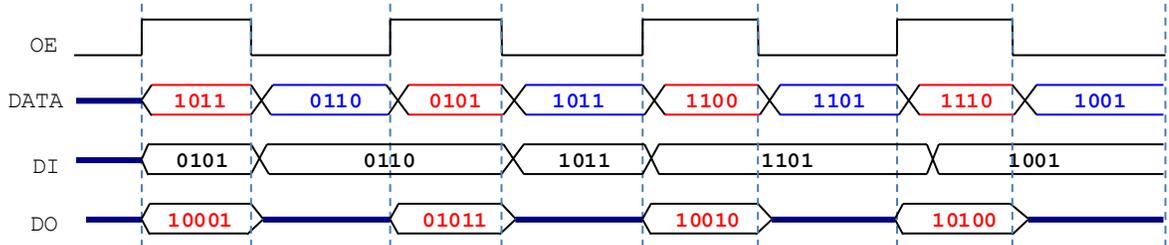


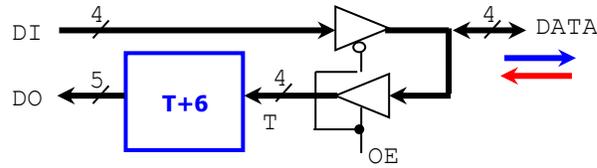PROBLEM 3 (8 PTS)

- Complete the timing diagram (signals *DO* and *DATA*) of the following circuit. The circuit in the blue box computes the summation $T+6$, with the result having 5 bits. *T* is an unsigned 4-bit number.




PROBLEM 4 (12 PTS)

- A microprocessor has a memory space of 512 KB. Each memory address occupies one byte. $1\text{KB} = 2^{10}$ bytes, $1\text{MB} = 2^{20}$ bytes, $1\text{GB} = 2^{30}$ bytes. We want to connect four 128 KB memory chips to this microprocessor.
 - What is the address bus size (number of bits of the address) of the microprocessor? (1 pt).
Size of memory space: $512\text{ KB} = 2^{19}$ bytes. Thus, we require 19 bits to address the memory space.
 - For a memory chip of 128 KB, how many bits do we require to address 128 KB of memory? (1 pt).
128 KB memory device: $128\text{ KB} = 2^{17}$ bytes. Thus, we require 17 bits to address the memory device.
 - Complete the address ranges (lowest to highest, in hexadecimal) for each of the memory chips in the figure. (4 pts).

Address	8 bits
000 0000 0000 0000 0000: 0x00000	1 128KB
000 0000 0000 0000 0001: 0x00001	
...	
001 1111 1111 1111 1111: 0x1FFFF	2 128KB
010 0000 0000 0000 0000: 0x20000	
010 0000 0000 0000 0001: 0x20001	
...	
011 1111 1111 1111 1111: 0x3FFFF	3 128KB
100 0000 0000 0000 0000: 0x40000	
100 0000 0000 0000 0001: 0x40001	
...	
101 1111 1111 1111 1111: 0x5FFFF	4 128KB
110 0000 0000 0000 0000: 0x60000	
110 0000 0000 0000 0001: 0x60001	
...	
111 1111 1111 1111 1111: 0x7FFFF	

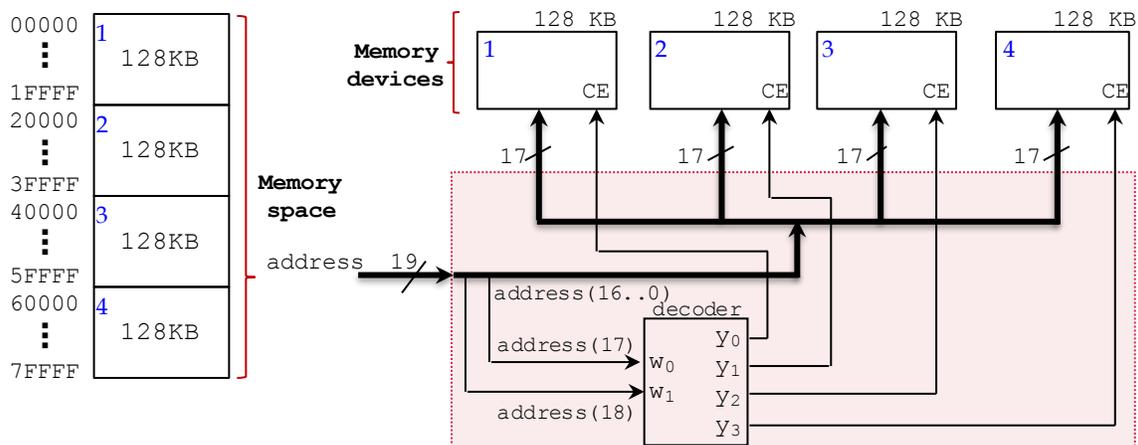- Sketch the circuit that: i) addresses the memory chips, and ii) enables only one memory chip (via CE: chip enable) when the address falls in the corresponding range. Example: if address= $0x2FFFF$, \rightarrow only memory chip 2 is enabled (CE=1). If address= $0x6ABC0$, \rightarrow only memory chip 4 is enabled.



PROBLEM 5 (17 PTS)

a) Perform the following additions and subtractions of the following unsigned integers. Use the fewest number of bits n to represent both operators. Indicate every carry (or borrow) from c_0 to c_n (or b_0 to b_n). For the addition, determine whether there is an overflow. For the subtraction, determine whether we need to keep borrowing from a higher byte. (6 pts)

✓ $49 + 18$

$$\begin{array}{r}
 \overset{c_6}{1} \quad \overset{c_5}{1} \quad \overset{c_4}{0} \quad \overset{c_3}{0} \quad \overset{c_2}{0} \quad \overset{c_1}{0} \quad \overset{c_0}{0} \\
 49 = 0x31 = \quad 1 \ 1 \ 0 \ 0 \ 0 \ 1 \ + \\
 18 = 0x12 = \quad 0 \ 1 \ 0 \ 0 \ 1 \ 0 \\
 \hline
 \text{Overflow!} \rightarrow 1 \ 0 \ 0 \ 0 \ 0 \ 1 \ 1
 \end{array}$$

✓ $38 - 42$

Borrow out! \rightarrow

$$\begin{array}{r}
 \overset{b_5}{1} \quad \overset{b_4}{1} \quad \overset{b_3}{0} \quad \overset{b_2}{0} \quad \overset{b_1}{0} \quad \overset{b_0}{0} \\
 38 = 0x26 = \quad 1 \ 0 \ 0 \ 1 \ 1 \ 0 \ - \\
 42 = 0x2A = \quad 1 \ 0 \ 1 \ 0 \ 1 \ 0 \\
 \hline
 1 \ 1 \ 1 \ 1 \ 0 \ 0
 \end{array}$$

b) Perform the following operations, where numbers are represented in 2's complement. Indicate every carry from c_0 to c_n . For each case, use the fewest number of bits to represent the summands and the result so that overflow is avoided. (8 pts)

✓ $-37 + 50$

$n = 7$ bits

$$\begin{array}{r}
 \overset{c_6}{1} \quad \overset{c_5}{1} \quad \overset{c_4}{0} \quad \overset{c_3}{0} \quad \overset{c_2}{0} \quad \overset{c_1}{1} \quad \overset{c_0}{0} \\
 -37 = 1 \ 0 \ 1 \ 1 \ 0 \ 1 \ 1 \ + \\
 50 = 0 \ 1 \ 1 \ 0 \ 0 \ 1 \ 0 \\
 \hline
 13 = 0 \ 0 \ 0 \ 1 \ 1 \ 0 \ 1 \\
 -37 + 50 = 13 \in [-2^6, 2^6-1] \rightarrow \text{no overflow}
 \end{array}$$

$c_7 \oplus c_6 = 0$
No Overflow

✓ $-26 - 40$

$n = 7$ bits

$$\begin{array}{r}
 \overset{c_6}{1} \quad \overset{c_5}{0} \quad \overset{c_4}{0} \quad \overset{c_3}{0} \quad \overset{c_2}{0} \quad \overset{c_1}{1} \quad \overset{c_0}{0} \\
 -40 = 1 \ 0 \ 1 \ 1 \ 0 \ 0 \ 0 \ + \\
 -26 = 1 \ 1 \ 0 \ 0 \ 1 \ 1 \ 0 \\
 \hline
 0 \ 1 \ 1 \ 1 \ 1 \ 1 \ 0 \\
 -40 - 26 = -66 \notin [-2^6, 2^6-1] \rightarrow \text{overflow!}
 \end{array}$$

$c_7 \oplus c_6 = 1$
Overflow!

To avoid overflow: $n = 8$ bits (sign-extension)

$$\begin{array}{r}
 \overset{c_7}{1} \quad \overset{c_6}{1} \quad \overset{c_5}{0} \quad \overset{c_4}{0} \quad \overset{c_3}{0} \quad \overset{c_2}{0} \quad \overset{c_1}{1} \quad \overset{c_0}{0} \\
 -40 = 1 \ 1 \ 0 \ 1 \ 1 \ 0 \ 0 \ 0 \ + \\
 -26 = 1 \ 1 \ 1 \ 0 \ 0 \ 1 \ 1 \ 0 \\
 \hline
 1 \ 0 \ 1 \ 1 \ 1 \ 1 \ 1 \ 0 \\
 -40 - 26 = -66 \in [-2^7, 2^7-1] \rightarrow \text{no overflow}
 \end{array}$$

$c_8 \oplus c_7 = 0$
No Overflow

c) Perform binary multiplication of the following numbers that are represented in 2's complement arithmetic. (3 pts)

✓ -6×9

$$\begin{array}{r}
 1 \ 0 \ 1 \ 0 \times \\
 0 \ 1 \ 0 \ 0 \ 1 \\
 \hline
 0 \ 0 \ 0 \ 0 \\
 1 \ 0 \ 0 \ 1 \\
 1 \ 0 \ 0 \ 1 \\
 0 \ 0 \ 0 \ 0 \\
 \hline
 0 \ 1 \ 1 \ 0 \ 1 \ 1 \ 0 \\
 \hline
 1 \ 0 \ 0 \ 1 \ 0 \ 1 \ 0
 \end{array}$$

PROBLEM 6 (10 PTS)


Given two 4-bit signed numbers A, B , sketch the circuit that computes $|A - 2B|$. For example: $A = 1010, B = 0110 \rightarrow |A - 2B| = |-6 - 2 \times 6| = 18$. You can only use full adders and logic gates. Your circuit must avoid overflow: design your circuit so that the result and intermediate operations have the proper number of bits.

$A = a_3a_2a_1a_0, B = b_3b_2b_1b_0$: signed numbers

$A, B \in [-8,7] \rightarrow 2B \in [-16,14]$ requires 5 bits in 2C. $2B = b_3b_2b_1b_00$

✓ $X = A - 2B \in [-22,23]$ requires 6 bits in 2C. Thus, the operation $A - 2B$ requires 6 bits (we sign-extend A and $2B$).
 $A - 2B = a_3a_3a_3a_2a_1a_0 - b_3b_3b_2b_1b_00$

- ✓ $|X| = |A - 2B| \in [0,23]$ requires 6 bits in 2C. Thus, the second operation $0 \pm X$ only requires 6 bits.
 - If $x_5 = 1 \rightarrow X < 0 \rightarrow$ we do $0 - X$.
 - If $x_5 = 0 \rightarrow X \geq 0 \rightarrow$ we do $0 + X$.

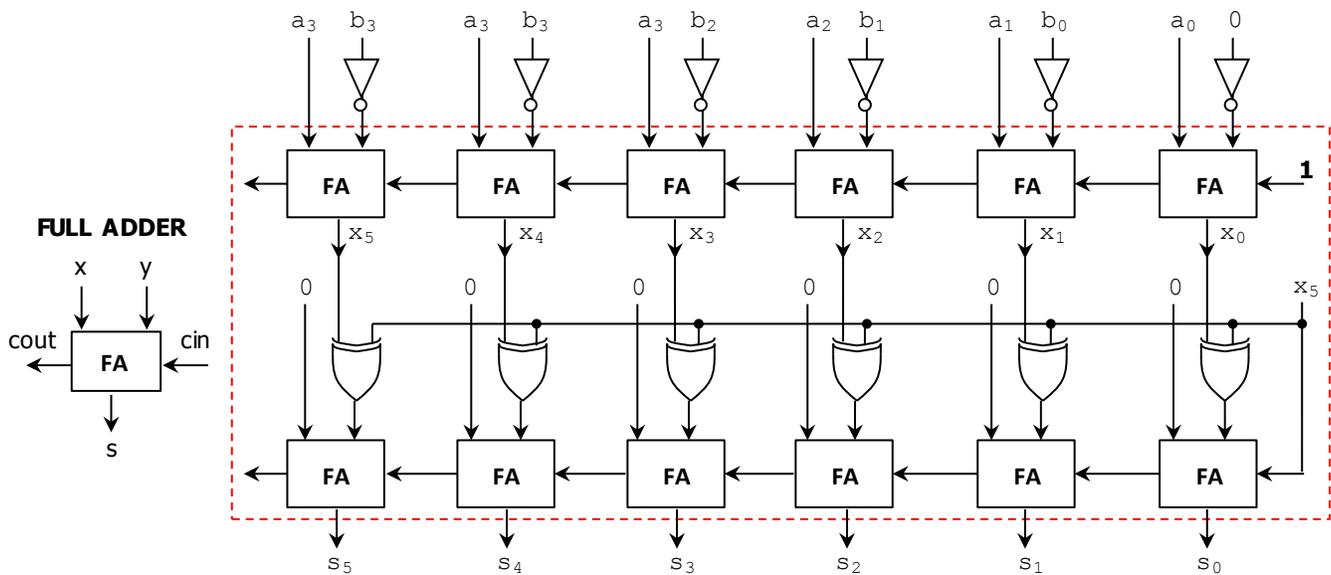

PROBLEM 7 (18 PTS)

- Sketch the circuit that implements the following Boolean function: $f(a, b, c, d) = (\overline{a \oplus b})(\overline{c \oplus d})$
 ✓ Using ONLY 2-to-1 MUXs (AND, OR, NOT, XOR gates are not allowed). (12 pts)

$$f(a, b, c, d) = (\overline{a \oplus b})(\overline{c \oplus d})$$


$$f = \overline{a}f(0, b, c, d) + af(1, b, c, d) = \overline{a}(\overline{b(c \oplus d)}) + a(b(c \oplus d)) = \overline{a}g(b, c, d) + ah(b, c, d)$$

$$g(b, c, d) = \overline{b(c \oplus d)} + b(0)$$


$$h(b, c, d) = \overline{b}(0) + b(c \oplus d)$$

$$t(c, d) = (\overline{c \oplus d}) = \overline{c}(\overline{d}) + c(d)$$
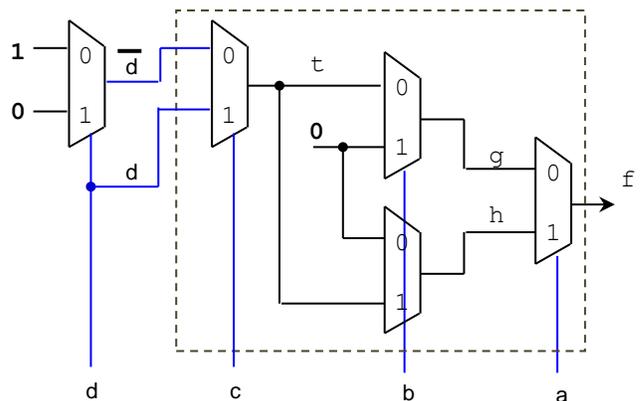
$$\text{Also: } \overline{d} = \overline{d}(1) + d(0)$$



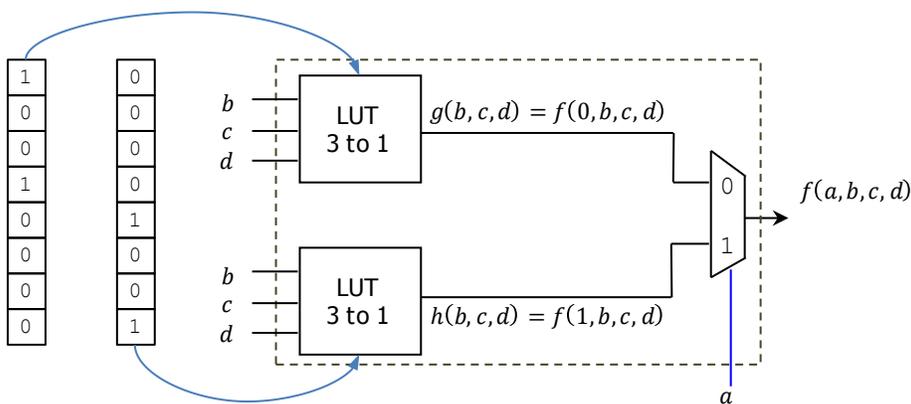- ✓ Using two 3-to-1 LUTs and a 2-to-1 MUX. Specify the contents of each of the 3-to-1 LUTs. (6 pts)



a	b	c	d	f
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1