

Student Honor Pledge:

All work submitted is completed by me directly without the use of any unauthorized resources or assistance

Final Exam



Initials: _____

(April 21st @ 7:00 pm)

Presentation and clarity are very important! Show your procedure!

 
 
PROBLEM 1 (12 PTS)

- Complete the timing diagram of the following circuit. $G = G_3G_2G_1G_0 = 0110$, $Q = Q_3Q_2Q_1Q_0$



 
 
PROBLEM 2 (10 PTS)

- Given the following circuit, complete the timing diagram. The LUT 6-to-6 implements the following function: $OLUT = \lceil \sqrt{ILUT} \rceil$, where $ILUT$ is a 6-bit unsigned number. For example $ILUT = 41 (101001_2) \rightarrow OLUT = \lceil \sqrt{41} \rceil = 7 (000111_2)$




  PROBLEM 3 (21 PTS)

- Two-pulse Detector: The timing diagram shows the behavior of the circuit. The FSM generates $z = 1$ when it detects two pulses. Note how in this design, the output z is 1 as soon as the second $1 \rightarrow 0$ transition is detected. Once the two pulses are detected, the FSM looks for a new pair of pulses. Assumption: For the circuit to detect a '1' or a '0' on x , this value needs to happen when a rising edge occurs. Draw the State Diagram (any representation) of the given FSM (10 pts).




 - The following FSM has 4 states, one input w and one output z . (11 pts)
 - ✓ The excitation equations are given by:
 - $Q_1(t+1) \leftarrow Q_0(t)$
 - $Q_0(t+1) \leftarrow Q_1(t) \oplus \bar{w}$
 - ✓ The output equation is given by: $z = Q_1(t) \oplus Q_0(t) \oplus w$
 - ✓ Provide the State Diagram (any representation) and the Excitation Table.
 - ✓ Sketch the Finite State Machine circuit.



 PROBLEM 4 (11 PTS)

- Sequence detector: This FSM has to generate $z = 1$ when it detects the sequence 01011 or 11100. Once the sequence is detected, the circuit looks for a new sequence. Note that once we start detecting a sequence, we prioritize the sequence that we have over the other (e.g.: last sequence inside a dotted red rectangle is not considered).



- ✓ Draw the State Diagram (any representation) and provide the State Table of this circuit with input x and output z . Is this a Mealy or a Moore machine? Why?

PROBLEM 5 (28 PTS)


- Draw the State Diagram (in ASM form) of the FSM whose VHDL description in shown below. (5 pts)
- Complete the Timing Diagram. (7 pts)
- Provide the State Table and the Excitation Table. Is it a Mealy or a Moore FSM? (6 pts).
- Provide the excitation equations and the Boolean output equations (simplify your circuit: K-maps or Quine-McCluskey).
- Sketch the circuit. (3 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity myfsm is
    port ( clk, resetn: in std_logic;
          r, p: in std_logic;
          x, w, z: out std_logic);
end myfsm;
```

```
architecture behavioral of myfsm is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (resetn, clk, r, p)
    begin
        if resetn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if r = '1' then
                        y <= S2;
                    else
                        if p = '1' then y <= S3; else y <= S1; end if;
                    end if;
                when S2 =>
                    if p = '1' then y <= S1; else y <= S3; end if;
                when S3 =>
                    if p = '1' then y <= S3; else y <= S2; end if;
            end case;
        end if;
    end process;

    Outputs: process (y, r, p)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => if r = '0' then
                if p = '0' then
                    z <= '1';
                end if;
            end if;
            when S2 => if r = '0' then x <= '1'; end if;
                if p = '0' then w <= '1'; end if;
            when S3 => if p = '0' then x <= '1'; end if;
        end case;
    end process;
end behavioral;
```

 

PROBLEM 6 (18 PTS)

- "Counting 0's" Circuit: It counts the number of bits in register *A* that has the value of '0'. The digital system is depicted below: FSM + Datapath. Example: For $n = 8$: if $A = 00110010$, then $C = 0101$.
 - ✓ *m*-bit counter: If $E = sclr = 1$, the count is initialized to zero. If $E = 1, sclr = 0$, the count is incremented by 1.
 - ✓ Parallel access shift register: If $E = 1, s_l = 1 \rightarrow$ Load. If $E = 1, s_l = 0 \rightarrow$ Shift.
- Complete the timing diagram where $n = 8, m = 4$. *A* is represented in hexadecimal format, while *C* is in binary format.

