

4-Way Traffic Intersection Control

Christopher Thweatt, Joseph Asteeфан, John
Drabik, Madison Cornett





Introduction



Photo By Christopher Evans/MediaNews Group/Boston Herald


- Proof of Concept: To reduce the footprint and complexity of hardware necessary to prototype and install flexible traffic control systems.
- Traffic control simulation built in VHDL code:
 - Finite State Machine
 - Counter
 - Decoder
 - Serializer
 - Segment and LED Display






Methodology

 - Artix-A7 FPGA, bread board, and colored LEDs
- Integer counter
- State machine:
 - Each state represents a different light sequence for each of the signals, and changes dependent on the accumulated count value.
 - Six bit output. Example: 100 (green) for the north/south signals and 001 (red) for the east/west signals.



Top Level Design

 

Counter

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity counter is
5      port ( clock, resetn: in std_logic;
6            Q: out integer range -15000000000 to 15000000000);
7  end counter;
8
9  architecture bhv of counter is
10     signal Qt: integer range -15000000000 to 15000000000;
11
12     begin
13
14     process (resetn,clock)
15     begin
16         if resetn = '0' then
17             Qt <= -15000000000;
18         elsif (clock'event and clock='1') then
19             if Qt = 15000000000 then
20                 Qt <= -15000000000;
21             else
22                 Qt <= Qt + 1;
23             end if;
24         end if;
25     end process;
26     Q <= Qt;
27 end bhv;
```

- Initially used 0 to 30 counter
- Integer instead of BCD

State Machine

```

11 architecture Behavioral of fsm is
12     type state_type is (s0, s1, s2, s3, s4, s5);
13     signal state: state_type;
14     begin
15         transitions: process (clk, rstn)
16         begin
17             if rstn = '0' then state <= s0;
18             elsif (clk'event and clk = '1') then
19                 case state is
20                     when s0 =>
21                         if Q = -500000000 then state <= s1;
22                         else state <= s0;
23                         end if;
24                     when s1 =>
25                         if Q = -200000000 then state <= s2;
26                         else state <= s1;
27                         end if;
28                     when s2 =>
29                         if Q = 0 then state <= s3;
30                         else state <= s2;
31                         end if;
32                     when s3 =>
33                         if Q = 1000000000 then state <= s4;
34                         else state <= s3;
35                         end if;
36                     when s4 =>
37                         if Q = 1300000000 then state <= s5;
38                         else state <= s4;
39                         end if;
40                     when s5 =>
41                         if Q = 1500000000 then state <= s0;
42                         else state <= s5;
43                         end if;
44                     end case;
45                 end if;
46             end process;
47


```

```

48     --100 is green, 010 is yellow, 001 is red
49     outputs: process(state)
50     begin
51         case state is
52             when s0 => northeast <= "100001";
53                         southwest <= "100001";
54             when s1 => northeast <= "010001";
55                         southwest <= "010001";
56             when s2 => northeast <= "001001";
57                         southwest <= "001001";
58             when s3 => northeast <= "001100";
59                         southwest <= "001100";
60             when s4 => northeast <= "001010";
61                         southwest <= "001010";
62             when s5 => northeast <= "001001";
63                         southwest <= "001001";
64         end case;
65     end process;
66 end Behavioral;

```

North/South			East/West			State
G	Y	R	G	Y	R	
1	0	0	0	0	1	S0
0	1	0	0	0	1	S1
0	0	1	0	0	1	S2
0	0	1	1	0	0	S3
0	0	1	0	1	0	S4
0	0	1	0	0	1	S5


 


Serializer and Decoder

```

9 architecture Behavioral of dec is
10
11 begin
12 process (Q)
13 begin
14 if Q < -1400000001 then A <= "0000"; B <= "0000";
15 elsif Q < -1300000001 then A <= "0001"; B <= "0000";
16 elsif Q < -1200000001 then A <= "0010"; B <= "0000";
17 elsif Q < -1100000001 then A <= "0011"; B <= "0000";
18 elsif Q < -1000000001 then A <= "0100"; B <= "0000";
19 elsif Q < -900000001 then A <= "0101"; B <= "0000";
20 elsif Q < -800000001 then A <= "0110"; B <= "0000";
21 elsif Q < -700000001 then A <= "0111"; B <= "0000";
22 elsif Q < -600000001 then A <= "1000"; B <= "0000";
23 elsif Q < -500000001 then A <= "1001"; B <= "0000";
24 elsif Q < -400000001 then A <= "0000"; B <= "0001";
25 elsif Q < -300000001 then A <= "0001"; B <= "0001";
26 elsif Q < -200000001 then A <= "0010"; B <= "0001";
27 elsif Q < -100000001 then A <= "0011"; B <= "0001";
28 elsif Q < -000000001 then A <= "0100"; B <= "0001";
29 elsif Q < 0999999999 then A <= "0101"; B <= "0001";
30 elsif Q < 1999999999 then A <= "0110"; B <= "0001";
31 elsif Q < 2999999999 then A <= "0111"; B <= "0001";
32 elsif Q < 3999999999 then A <= "1000"; B <= "0001";
33 elsif Q < 4999999999 then A <= "1001"; B <= "0001";
34 elsif Q < 5999999999 then A <= "0000"; B <= "0010";
35 elsif Q < 6999999999 then A <= "0001"; B <= "0010";
36 elsif Q < 7999999999 then A <= "0010"; B <= "0010";
37 elsif Q < 8999999999 then A <= "0011"; B <= "0010";
38 elsif Q < 9999999999 then A <= "0100"; B <= "0010";
39 elsif Q < 10999999999 then A <= "0101"; B <= "0010";
40 elsif Q < 11999999999 then A <= "0110"; B <= "0010";
41 elsif Q < 12999999999 then A <= "0111"; B <= "0010";
42 elsif Q < 13999999999 then A <= "1000"; B <= "0010";
43 elsif Q < 14999999999 then A <= "1001"; B <= "0010";
44 elsif Q < 15000000001 then A <= "0000"; B <= "0011";
45 end if;
46 end process;
47 end Behavioral;


```

  

XDC file / Experimental Setup

- Clock signal
- 7 segment display
 - First 7 ports
 - AN 0-7
- Buttons
 - CPU reset
- Pmod headers JA and JB
 - JA first 6 ports
 - JB first 6 ports

 
- Breadboard
- Wires
- Resistors
- External LEDs





Demo
 
<https://drive.google.com/file/d/1FN8xiAmwgKfuOerfLMHYy7eFkHJUG4fz/view?usp=sharing>





Conclusion

- Knowledge of VHDL programming and the use of a finite state machine
- Decoders, counters, and serializers
 - Being able to apply prior knowledge and modify existing code to adapt to the situation.
- Learned how to use the different ports to connect to a breadboard
- Used previous knowledge of LEDs and the function of a breadboard to implement the function.
- Strengthened our abilities to solve problems even in the most unideal situations.