

Laboratory 3

(Due date : **002/003**: February 17th, **004**: February 18th, **006**: February 19th)

OBJECTIVES



- ✓ Use the Structural Description on VHDL.
- ✓ Test arithmetic circuits on an FPGA.

VHDL CODING

- ✓ Refer to the [Tutorial: VHDL for FPGAs](#) for a list of examples.

FIRST ACTIVITY (100/100)

  - **PROBLEM:** The figure depicts a 2's complement array multiplier for two 4-bit signed numbers. It is based on the basic unsigned multiplier with some adjustments.



- ✓ **NEXYS A7-50T:** Create a new Vivado Project. Select the **XC7A50T-1CSG324 Artix-7 FPGA** device.
 - ✓ Write the VHDL code for this signed array multiplier. Use the Structural Description: Create a separate file for the Full Adder, the Processing Unit (PU), the flipped Processing Unit (PU_n) and the top file (Array Multiplier). Synthesize the code.
 - ✓ Write the VHDL testbench to test the circuit for all possible cases (256 cases). Use 'for loop'.
 - ✓ Perform Behavioral Simulation and Timing Simulation of your design. Make sure to represent data as signed (2C) integers (use Radix → Signed Decimal). **Demonstrate this to your TA.**
 - ✓ I/O Assignment: Create the XDC file. Nexys-4: Use SW_0 to SW_7 for the inputs, and LED_7 to LED_0 for the output.
 - ✓ Generate and download the bitstream on the FPGA and test. **Demonstrate this to your TA.**
- Submit (as a .zip file) the five generated files: VHDL code (4 files), VHDL testbench, and XDC file to Moodle (an assignment will be created). DO NOT submit the whole Vivado Project.

TA signature: _____

Date: _____