

# Laboratory 6

(Due date: **002/003**: April 6<sup>th</sup>, **004**: April 7<sup>th</sup>, **005**: April 8<sup>th</sup>)

## OBJECTIVES


- ✓ Describe Finite State Machines (FSMs) in VHDL.
- ✓ Implement a Digital System: Control Unit and Datapath Unit.

## VHDL CODING

- ✓ Refer to the [Tutorial: VHDL for FPGAs](#) for parametric code for: register, shift register, counter, adder.
 
## ITERATIVE DIVIDER IMPLEMENTATION (100/100)

- Given two unsigned numbers  $A$  and  $B$ , we want to design a circuit that produces the quotient  $Q$  and a remainder  $R$ .  $A = B \times Q + R$ . The algorithm that implements the traditional long-hand division is as follows:





### ALGORITHM

```

R = 0
for i = n-1 downto 0
  left shift R (input = ai)
  if R ≥ B
    qi = 1, R ← R-B
  else
    qi = 0
  end
end
end
    
```

- An iterative architecture is depicted in the figure for  $DA$  with 6 bits and  $DB$  with 4 bits. The register  $R$  stores the remainder. A division operation is started when  $E = 1$  (where  $DA$  and  $DB$  values are captured). Then, at every clock cycle, we either: i) shift in the next bit of  $A$ , or ii) shift in the next bit of  $A$  and subtract  $B$ . The signal  $done$  is asserted to indicate that the operation has been completed and the result appears in  $Q$  and  $R$ .

  

- Modulo-6 counter: It includes: i) a synchronous input *sclr* that clears the count when  $E = sclr = 1$ , and ii) an output *zC* that is asserted when the count reaches 5. The counter increases its value when  $E = 1$  and  $sclr = 0$ .
- Parallel Access Left-shift register: Note that one of the shift registers includes a synchronous input *sclr* that clears the register outputs when  $E = sclr = 1$ . Refer to 'Notes – Unit 6' for a description of the circuit and its operation.
- Each sequential component has *resetsn* and *clock* inputs.
- The circuit is an example of a Digital System: It includes a Control Circuit (FSM) and a Datapath Circuit. The Datapath Circuit is made from combinational and sequential components. The circuit is also called a Special-Purpose Processor. In this case, the special purpose is the unsigned division.
- ✓ **NEXYS A7-50T:** Create a new Vivado Project. Select the **XC7A50T-1CSG324 Artix-7 FPGA** device.
- ✓ Write the VHDL code for the given circuit. Suggestion: create a separate file for modulo-6 counter, shift Register, shift register with *sclr* input, register, adder, hex to 7-segments decoder, FSM, and top file. Synthesize your circuit.
- ✓ Write the VHDL testbench (generate a 100 MHz input clock for your simulations) to test the following cases:
  - DA = 111011 (59), DB = 0101 (5)
  - DA = 011100 (28), DB = 1010 (10)
  - DA = 100111 (39), DB = 1000 (8)
  - DA = 010011 (19), DB = 0011 (3)
  - DA = 110011 (51), DB = 1110 (14)
  - DA = 111100 (60), DB = 1101 (13)
- ✓ Perform Behavioral Simulation and Timing Simulation of your design. **Demonstrate this to your TA.**
  - Behavioral Simulation: Add the internal signal *R* to the waveform view. Then, re-run the simulation.
  - For the following set of inputs, complete the expected values (when *done*=1) of the internal signal *R* as well as the outputs *Q* and *CA-CG*. Then, run the simulation and compare the values in the simulation waveform (when *done*=1) with the ones you computed. This will facilitate the debugging of this circuit.

DA	DB	R	Q	CA-CG
111011	0101			
011100	1010			
100111	1000			
010011	0011			
110011	1110			
111100	1101			

- ✓ I/O Assignment: Create the XDC file. Nexys A7-50T: Use SW0 to SW10 for the inputs (*DA*, *DB*, and *E*), CLK100MHZ for the input *clock*, BTN\_RES (CPU Reset) push-button for *resetsn*, LED15 for *done*, LED5 to LED0 for *Q*, *CA-CG* (7-segment display signals), and AN7-AN0 (anode enable for each 7-segment display; enable only one 7-segment display).  
 \* Note: If you are using the **Basys3 Trainer Board**, use SW11 for *resetsn*, and AN3-AN0 (there are only 4 7-seg displays).
- ✓ Generate and download the bitstream on the FPGA and test. **Demonstrate this to your TA.**
- Submit (as a .zip file) all the generated files: VHDL code files, VHDL testbench, and XDC file to Moodle (an assignment will be created). DO NOT submit the whole Vivado Project.

TA signature: \_\_\_\_\_

Date: \_\_\_\_\_