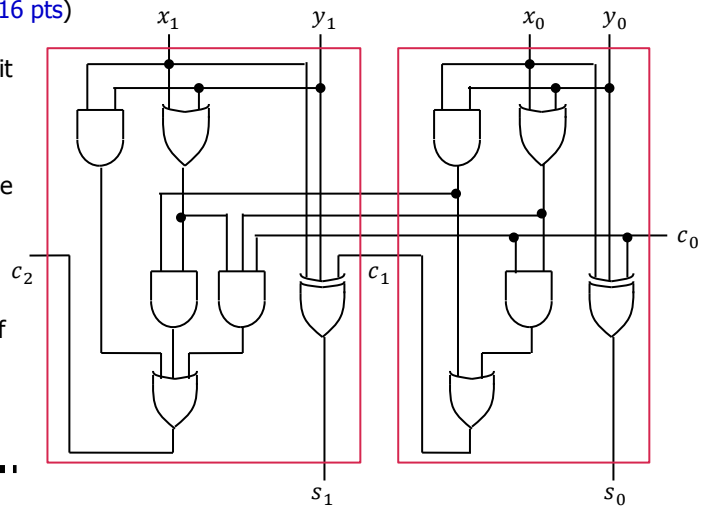




b) Given the following circuit with inputs  $x_0, x_1, y_0, y_1, c_0$ : (16 pts)

- Provide the Boolean expression (based on the circuit inputs) for  $s_0, s_1, c_1, c_2$ . (7 pts)
- For  $s_0$  and  $c_1$ : (9 pts)
  - Express the Boolean functions using both the minterms and maxterms representations. (4 pts)
  - Provide the Boolean functions using the Canonical Sum of Products (SOP), and Product of Sums (POS). (3 pts)
  - Sketch the logic circuits as Canonical Sum of Products and Product of Sums. (3 pts)



$$\begin{aligned}
 s_0 &= x_0 \oplus y_0 \oplus c_0 \\
 c_1 &= x_0 y_0 + (x_0 + y_0) c_0 = x_0 y_0 + x_0 c_0 + y_0 c_0 \\
 s_1 &= x_0 \oplus y_0 \oplus c_1 = x_0 \oplus y_0 \oplus (x_0 y_0 + x_0 c_0 + y_0 c_0) \\
 c_2 &= x_1 y_1 + (x_1 + y_1) x_0 y_0 + (x_1 + y_1) (x_0 + y_0) c_0
 \end{aligned}$$

**Minterms and maxterms:**

$$\begin{aligned}
 \Rightarrow c_1(x_0, y_0, c_0) &= \sum(m_3, m_5, m_6, m_7) = \prod(M_0, M_1, M_2, M_4) \\
 \Rightarrow s_0(x_0, y_0, c_0) &= \sum(m_1, m_2, m_4, m_7) = \prod(M_0, M_3, M_5, M_6)
 \end{aligned}$$



**Sum of Products:**

$$\begin{aligned}
 c_1 &= \overline{x_0} y_0 c_0 + x_0 \overline{y_0} c_0 + x_0 y_0 \overline{c_0} + x_0 y_0 c_0 \\
 s_0 &= \overline{x_0} \overline{y_0} c_0 + \overline{x_0} y_0 \overline{c_0} + x_0 \overline{y_0} \overline{c_0} + x_0 y_0 c_0
 \end{aligned}$$

**Product of Sums:**


$$\begin{aligned}
 c_1 &= (x_0 + y_0 + c_0)(x_0 + y_0 + \overline{c_0})(x_0 + \overline{y_0} + c_0)(\overline{x_0} + y_0 + c_0) \\
 s_0 &= (x_0 + y_0 + c_0)(x_0 + \overline{y_0} + \overline{c_0})(\overline{x_0} + y_0 + \overline{c_0})(\overline{x_0} + \overline{y_0} + c_0)
 \end{aligned}$$

| $x_0$ | $y_0$ | $c_0$ | $c_1$ | $s_0$ |
|-------|-------|-------|-------|-------|
| 0     | 0     | 0     | 0     | 0     |
| 0     | 0     | 1     | 0     | 1     |
| 0     | 1     | 0     | 0     | 1     |
| 0     | 1     | 1     | 1     | 0     |
| 1     | 0     | 0     | 0     | 1     |
| 1     | 0     | 1     | 1     | 0     |
| 1     | 1     | 0     | 1     | 0     |
| 1     | 1     | 1     | 1     | 1     |

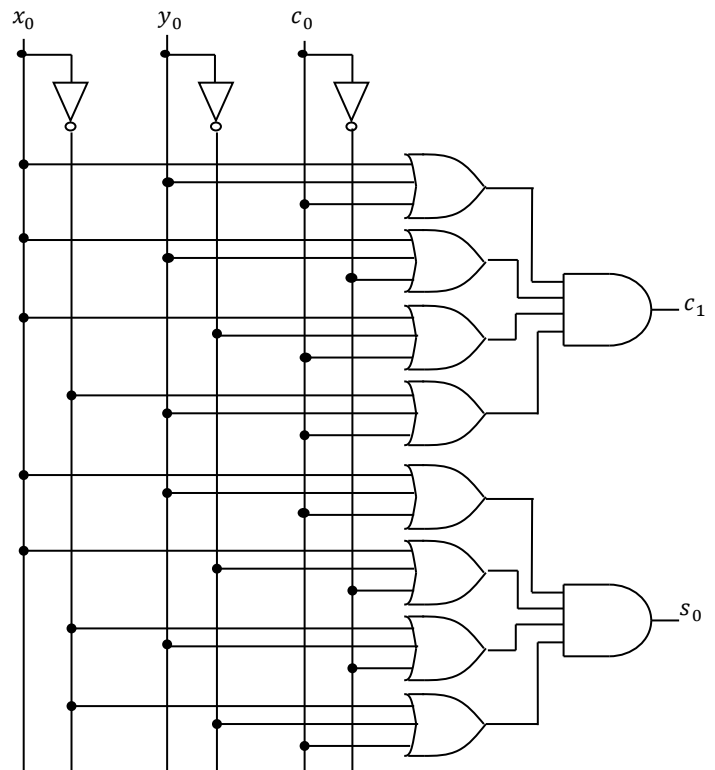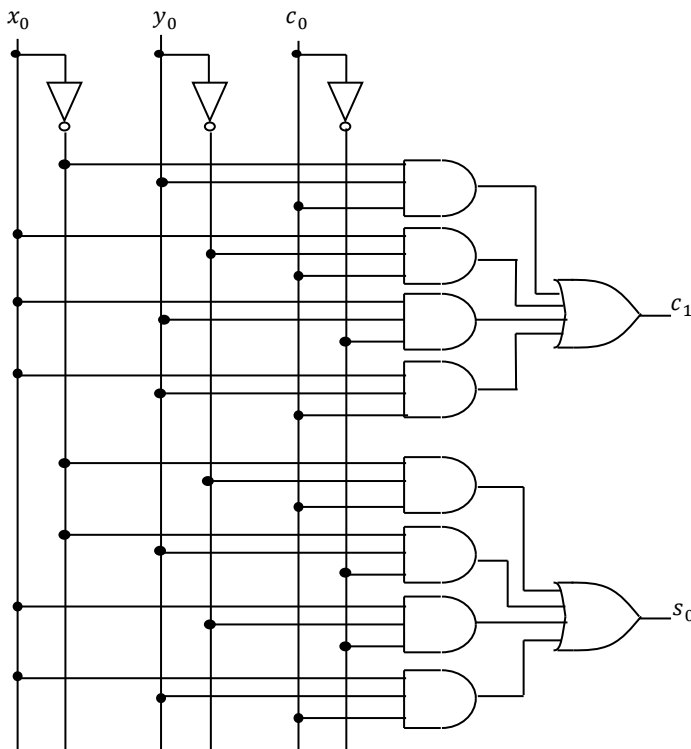

## PROBLEM 2 (24 PTS)

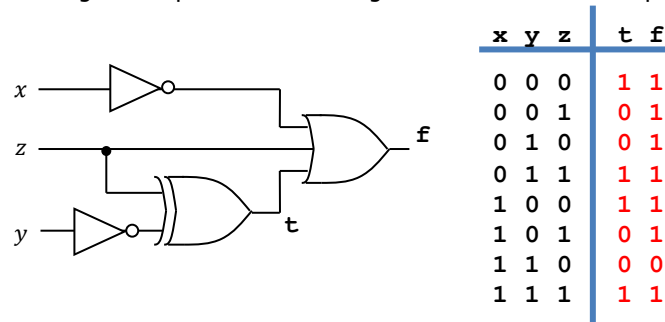- a) Complete the truth table describing the output of the following circuit and write the simplified Boolean equation (6 pts).




$$f = \bar{x} + \bar{y} + z$$

- b) Complete the timing diagram of the logic circuit whose VHDL description is shown below: (5 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end circ;

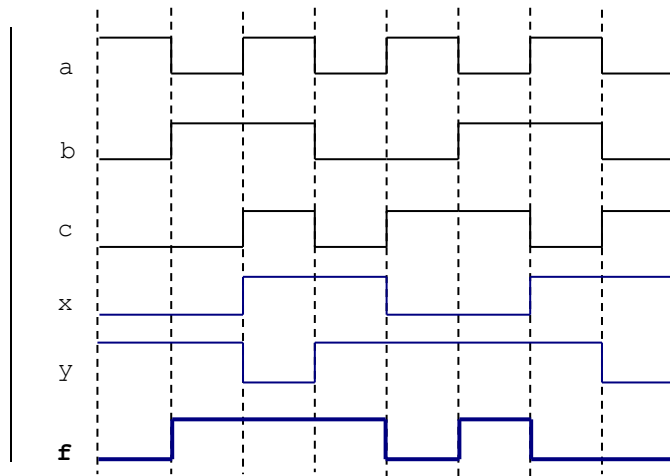architecture struct of circ is
  signal x, y: std_logic;
begin
  f <= y xnor (not a);
  x <= a xor (not b);
  y <= x nand c;
end struct;
```




- c) The following is the timing diagram of a logic circuit with 3 inputs. Sketch the logic circuit that generates this waveform. Then, complete the VHDL code. (8 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity wave is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end wave;

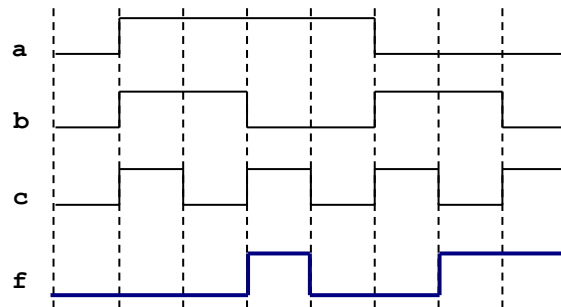
architecture struct of wave is
  signal x: std_logic;
begin
  x <= not(a) and b and not(c);
  f <= (not(b) and c) or x;
end struct;
```





| a | b | c | f |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |

| ab |   | 00 | 01 | 11 | 10 |
|----|---|----|----|----|----|
| c  | 0 | 0  | 1  | 0  | 0  |
|    | 1 | 1  | 0  | 0  | 1  |

$f = \bar{b}c + \bar{a}b\bar{c}$

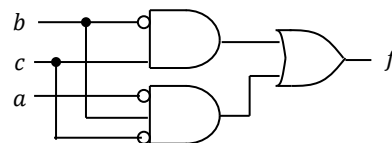

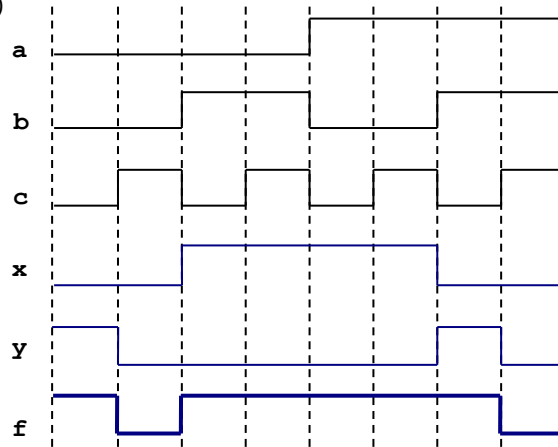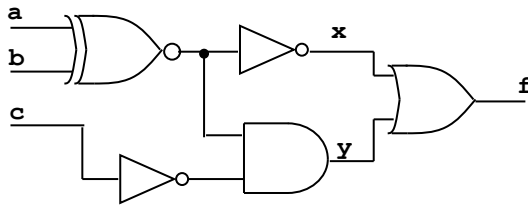d) Complete the timing diagram of the following circuit: (5 pts)



### PROBLEM 3 (10 PTS)


- A majority gate has an output value of 1 if there are more 1's than 0's on its inputs. The output is 0 otherwise.
- Design (provide the simplified Boolean equation and sketch the logic circuit) a 4-input majority gate with inputs  $a, b, c, d$ , and output  $f$ .

The function break ties in favor of zeros when the number of inputs is even. Example:  $abcd=1100 \rightarrow f=0$ .

| x | y | z | w | f |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

| zw \ xy |    | xy        |           |           |           |           |           |
|---------|----|-----------|-----------|-----------|-----------|-----------|-----------|
|         |    | 00        | 01        | 11        | 10        |           |           |
| zw      | 00 | 0         | 0         | 0         | 0         | $\bar{z}$ | $\bar{w}$ |
|         | 01 | 0         | 0         | 1         | 0         | $\bar{z}$ | $w$       |
|         | 11 | 0         | 1         | 1         | 1         | $z$       | $w$       |
|         | 10 | 0         | 0         | 1         | 0         | $z$       | $\bar{w}$ |
|         |    | $\bar{x}$ | $\bar{y}$ | $\bar{x}$ | $y$       | $x$       | $\bar{y}$ |
|         |    | $\bar{x}$ |           | $y$       |           | $x$       |           |
|         |    | $\bar{y}$ | $y$       |           | $\bar{y}$ |           |           |

$$f = yzw + xzw + xyw + xyz$$

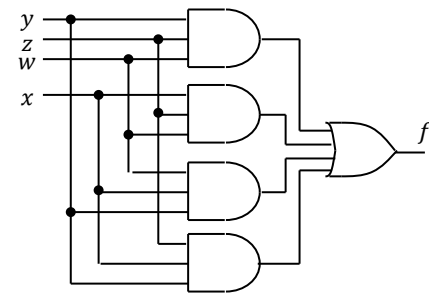



### PROBLEM 4 (11 PTS)

- Design a logic circuit (simplify your circuit) that opens a lock ( $f = 1$ ) whenever the user presses the correct number on each numpad (numpad 1: **9**, numpad 2: **4**). The numpad encodes each decimal number using BCD encoding (see figure). We expect that the 4-bit groups generated by each numpad be in the range from 0000 to 1001. Note that the values from 1010 to 1111 are assumed not to occur.

Suggestion: Create two circuits: one that verifies the first number (**9**), and another that verifies the second number (**4**). Then perform the AND operation on the two outputs. This avoids creating a truth table with 8 inputs.

| BCD code |   |   |   | Number pressed |
|----------|---|---|---|----------------|
| x        | y | z | w |                |
| 0        | 0 | 0 | 0 | 0              |
| 0        | 0 | 0 | 1 | 1              |
| 0        | 0 | 1 | 0 | 2              |
| 0        | 0 | 1 | 1 | 3              |
| 0        | 1 | 0 | 0 | 4              |
| 0        | 1 | 0 | 1 | 5              |
| 0        | 1 | 1 | 0 | 6              |
| 0        | 1 | 1 | 1 | 7              |
| 1        | 0 | 0 | 0 | 8              |
| 1        | 0 | 0 | 1 | 9              |

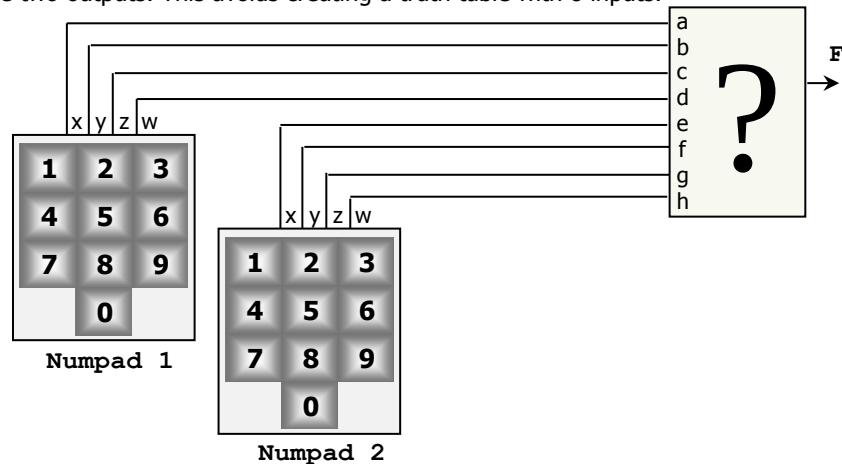


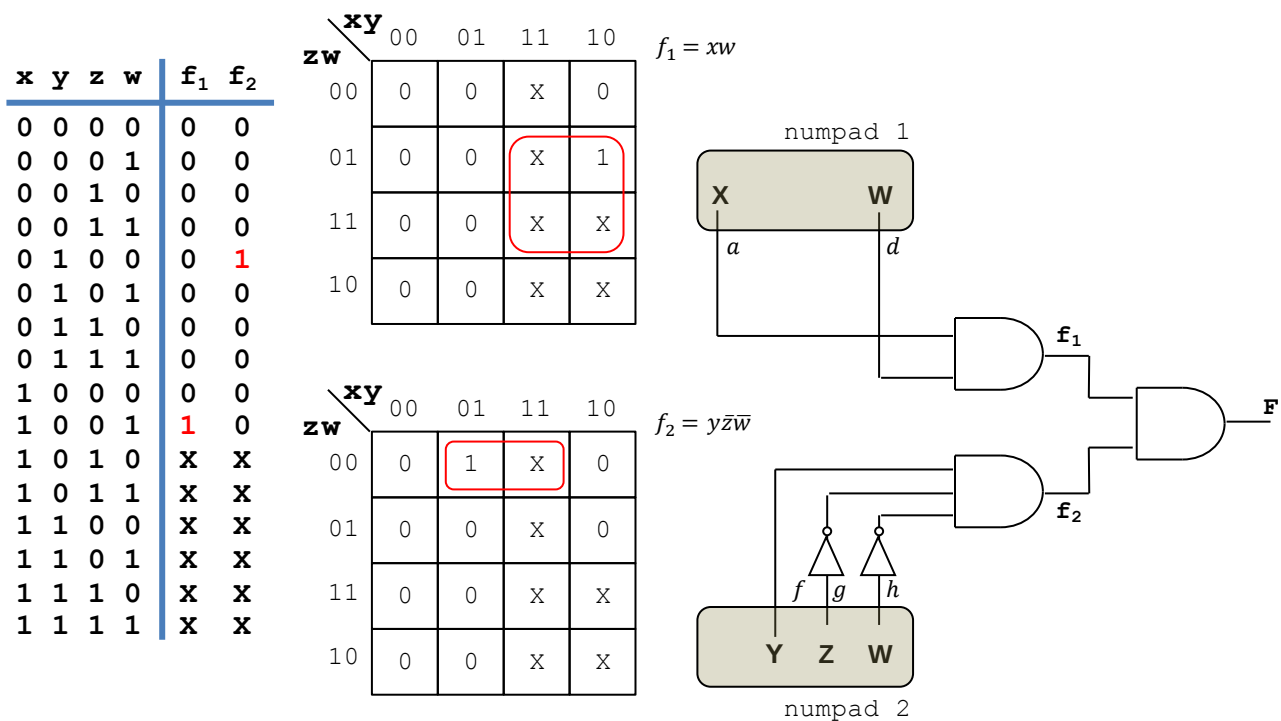


$$F = ad\bar{f}g\bar{h}$$
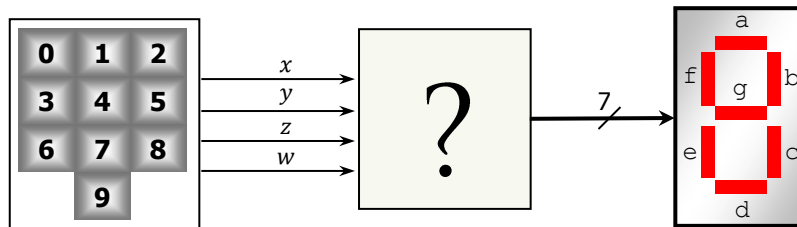
### PROBLEM 5 (25 PTS)

- A numeric keypad produces a 4-bit code as shown below. We want to design a logic circuit that converts each 4-bit code to a 7-segment code, where each segment is an LED: A LED is ON if it is given a logic '1'. A LED is OFF if it is given a logic '0'.
- Complete the truth table for each output ( $a, b, c, d, e, f, g$ ).
- Provide the simplified expression for each output ( $a, b, c, d, e, f, g$ ). Use Karnaugh maps for  $a, b, c, d, e$  and the Quine-McCluskey algorithm for  $f, g$ . Note it is safe to assume that the codes 1010 to 1111 will not be produced by the keypad.



| Value | x | y | z | w | a | b | c | d | e | f | g |
|-------|---|---|---|---|---|---|---|---|---|---|---|
| 0     | 0 | 0 | 0 | 0 |   |   |   |   |   |   |   |
| 1     | 0 | 0 | 0 | 1 |   |   |   |   |   |   |   |
| 2     | 0 | 0 | 1 | 0 |   |   |   |   |   |   |   |
| 3     | 0 | 0 | 1 | 1 |   |   |   |   |   |   |   |
| 4     | 0 | 1 | 0 | 0 |   |   |   |   |   |   |   |
| 5     | 0 | 1 | 0 | 1 |   |   |   |   |   |   |   |
| 6     | 0 | 1 | 1 | 0 |   |   |   |   |   |   |   |
| 7     | 0 | 1 | 1 | 1 |   |   |   |   |   |   |   |
| 8     | 1 | 0 | 0 | 0 |   |   |   |   |   |   |   |
| 9     | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |
|       | 1 | 0 | 1 | 0 |   |   |   |   |   |   |   |
|       | 1 | 0 | 1 | 1 |   |   |   |   |   |   |   |
|       | 1 | 1 | 0 | 0 |   |   |   |   |   |   |   |
|       | 1 | 1 | 0 | 1 |   |   |   |   |   |   |   |
|       | 1 | 1 | 1 | 0 |   |   |   |   |   |   |   |
|       | 1 | 1 | 1 | 1 |   |   |   |   |   |   |   |

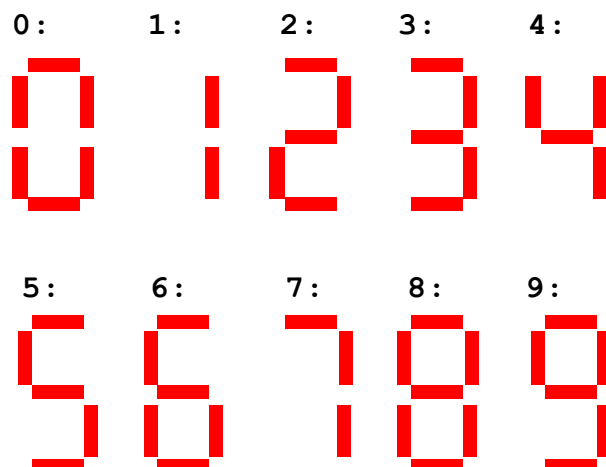

| Value | x | y | z | w | a | b | c | d | e | f | g |
|-------|---|---|---|---|---|---|---|---|---|---|---|
| 0     | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1     | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 2     | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 3     | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |
| 4     | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 5     | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 6     | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 7     | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| 8     | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 9     | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |
|       | 1 | 0 | 1 | 0 | X | X | X | X | X | X | X |
|       | 1 | 0 | 1 | 1 | X | X | X | X | X | X | X |
|       | 1 | 1 | 0 | 0 | X | X | X | X | X | X | X |
|       | 1 | 1 | 0 | 1 | X | X | X | X | X | X | X |
|       | 1 | 1 | 1 | 0 | X | X | X | X | X | X | X |
|       | 1 | 1 | 1 | 1 | X | X | X | X | X | X | X |


$$a = \bar{y}\bar{w} + wy + x + z$$

$$b = \bar{y} + \bar{z}\bar{w} + zw$$

$$c = y + \bar{z} + w$$

$$d = x + z\bar{w} + \bar{y}z + \bar{w}\bar{y} + \bar{z}wy$$

$$e = \bar{w}\bar{y} + z\bar{w}$$

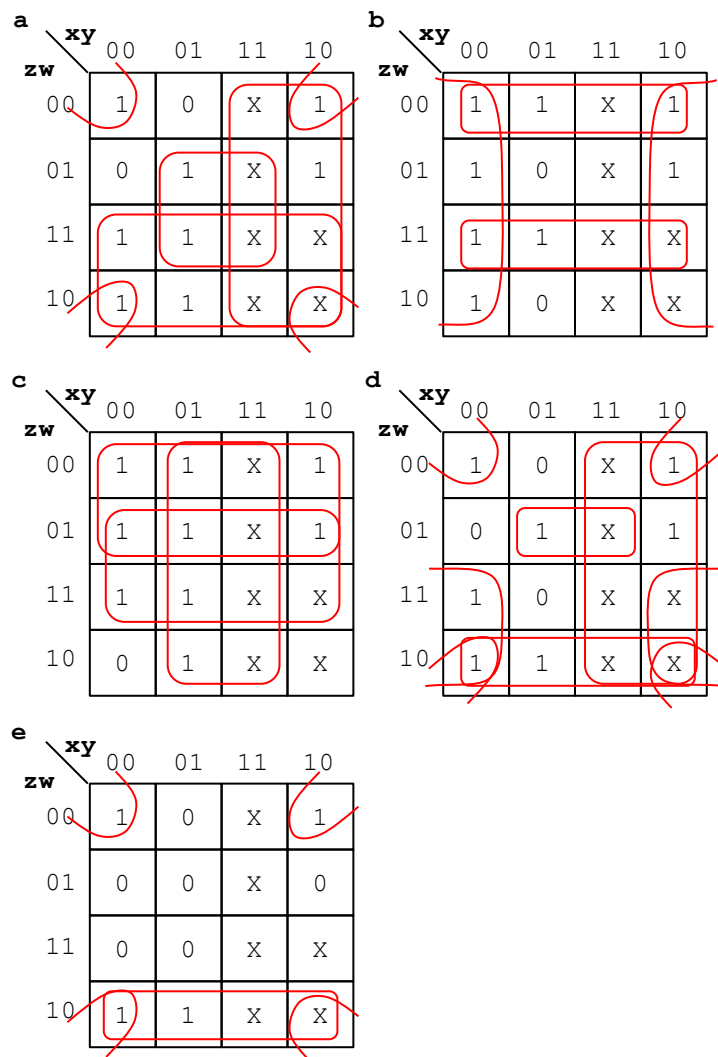

$$f = \sum m(0,4,5,6,8,9) + \sum d(10,11,12,13,14,15).$$

| Number of ones | 4-literal implicants                                                                                                                      | 3-literal implicants                                                                                                                                                                                                                                             | 2-literal implicants                                                                                                                                                                                                                                                                                                                                                                                       | 1-literal implicants                                                                           |
|----------------|-------------------------------------------------------------------------------------------------------------------------------------------|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|------------------------------------------------------------------------------------------------|
| 0              | $m_0 = 0000 \checkmark$                                                                                                                   | $m_{0,4} = 0-00 \checkmark$<br>$m_{0,8} = -000 \checkmark$                                                                                                                                                                                                       | $m_{0,4,8,12} = --00$<br><del><math>m_{0,8,4,12} = --00</math></del>                                                                                                                                                                                                                                                                                                                                       |                                                                                                |
| 1              | $m_4 = 0100 \checkmark$<br>$m_8 = 1000 \checkmark$                                                                                        | $m_{4,5} = 010- \checkmark$<br>$m_{4,6} = 01-0 \checkmark$<br>$m_{4,12} = -100 \checkmark$<br>$m_{8,9} = 100- \checkmark$<br>$m_{8,10} = 10-0 \checkmark$<br>$m_{8,12} = 1-00 \checkmark$                                                                        | $m_{4,5,12,13} = -10-$<br><del><math>m_{4,12,5,13} = -10-</math></del><br>$m_{4,6,12,14} = -1-0$<br><del><math>m_{4,12,6,14} = -1-0</math></del><br>$m_{8,9,10,11} = 10--$<br><del><math>m_{8,10,9,11} = 10--</math></del><br>$m_{8,9,12,13} = 1-0-$ $\checkmark$<br><del><math>m_{8,12,9,13} = 1-0-</math></del><br>$m_{8,10,12,14} = 1--0$ $\checkmark$<br><del><math>m_{8,12,10,14} = 1--0</math></del> | $m_{8,10,12,14,9,13,11,15} = 1---$<br><del><math>m_{8,9,12,13,10,14,11,15} = 1---</math></del> |
| 2              | $m_5 = 0101 \checkmark$<br>$m_6 = 0110 \checkmark$<br>$m_9 = 1001 \checkmark$<br>$m_{10} = 1010 \checkmark$<br>$m_{12} = 1100 \checkmark$ | $m_{5,13} = -101 \checkmark$<br>$m_{6,14} = -110 \checkmark$<br>$m_{9,11} = 10-1 \checkmark$<br>$m_{9,13} = 1-01 \checkmark$<br>$m_{10,11} = 101- \checkmark$<br>$m_{10,14} = 1-10 \checkmark$<br>$m_{12,13} = 110- \checkmark$<br>$m_{12,14} = 11-0 \checkmark$ | $m_{9,13,11,15} = 1--1 \checkmark$<br>$m_{10,14,11,15} = 1-1- \checkmark$                                                                                                                                                                                                                                                                                                                                  |                                                                                                |
| 3              | $m_{11} = 1011 \checkmark$<br>$m_{13} = 1101 \checkmark$<br>$m_{14} = 1110 \checkmark$                                                    | $m_{11,15} = 1-11 \checkmark$                                                                                                                                                                                                                                    |                                                                                                                                                                                                                                                                                                                                                                                                            |                                                                                                |
| 4              | $m_{15} = 1111 \checkmark$                                                                                                                |                                                                                                                                                                                                                                                                  |                                                                                                                                                                                                                                                                                                                                                                                                            |                                                                                                |

$$f = \bar{z}\bar{w} + y\bar{z} + y\bar{w} + x\bar{y} + x$$

| Prime Implicants            |                  | Minterms |   |          |          |   |          |
|-----------------------------|------------------|----------|---|----------|----------|---|----------|
|                             |                  | 0        | 4 | 5        | 6        | 8 | 9        |
| $m_{0,4,8,12}$              | $\bar{z}\bar{w}$ | <b>X</b> | X |          |          | X |          |
| $m_{4,5,12,13}$             | $y\bar{z}$       |          | X | <b>X</b> |          |   |          |
| $m_{4,6,12,14}$             | $y\bar{w}$       |          | X |          | <b>X</b> |   |          |
| $m_{8,9,10,11}$             | $x\bar{y}$       |          |   |          |          | X | <b>X</b> |
| $m_{8,10,12,14,9,13,11,15}$ | $x$              |          |   |          |          | X | <b>X</b> |

$$f = \bar{z}\bar{w} + y\bar{z} + y\bar{w} + x$$

- $g = \sum m(2,3,4,5,6,8,9) + \sum d(10,11,12,13,14,15)$ .  
Too many minterms. We better optimize:  $\bar{g} = \sum m(0,1,7) + \sum d(10,11,12,13,14,15)$

| Number of ones | 4-literal implicants                                                          | 3-literal implicants                                                                         | 2-literal implicants                                                                                                                                         | 1-literal implicants |
|----------------|-------------------------------------------------------------------------------|----------------------------------------------------------------------------------------------|--------------------------------------------------------------------------------------------------------------------------------------------------------------|----------------------|
| 0              | $m_0 = 0000$ ✓                                                                | $m_{0,1} = 000-$                                                                             |                                                                                                                                                              |                      |
| 1              | $m_1 = 0001$                                                                  |                                                                                              |                                                                                                                                                              |                      |
| 2              | $m_{10} = 1010$ ✓<br>$m_{12} = 1100$ ✓                                        | $m_{10,11} = 101-$ ✓<br>$m_{10,14} = 1-10$ ✓<br>$m_{12,13} = 110-$ ✓<br>$m_{12,14} = 11-0$ ✓ | $m_{10,14,11,15} = 1-1-$<br><del><math>m_{10,11,14,15} = 1-1-</math></del> ✓<br>$m_{12,14,13,15} = 11--$<br><del><math>m_{12,13,14,15} = 11--</math></del> ✓ |                      |
| 3              | $m_7 = 0111$ ✓<br>$m_{11} = 1011$ ✓<br>$m_{13} = 1101$ ✓<br>$m_{14} = 1110$ ✓ | $m_{7,15} = -111$<br>$m_{11,15} = 1-11$ ✓<br>$m_{13,15} = 11-1$ ✓<br>$m_{14,15} = 111-$ ✓    |                                                                                                                                                              |                      |
| 4              | $m_{15} = 1111$ ✓                                                             |                                                                                              |                                                                                                                                                              |                      |

$$\bar{g} = \bar{x}\bar{y}\bar{z}w + \bar{x}\bar{y}z + yzw + xz + xy$$

| Prime Implicants  |                          | Minterms |   |          |
|-------------------|--------------------------|----------|---|----------|
|                   |                          | 0        | 1 | 7        |
| $m_1$             | $\bar{x}\bar{y}\bar{z}w$ |          | X |          |
| $m_{0,1}$         | $\bar{x}\bar{y}z$        | <b>X</b> | X |          |
| $m_{7,15}$        | $yzw$                    |          |   | <b>X</b> |
| $m_{10,14,11,15}$ | $xz$                     |          |   |          |
| $m_{12,14,13,15}$ | $xy$                     |          |   |          |

$$\bar{g} = \bar{x}\bar{y}z + yzw \quad \Rightarrow \quad g = (x + y + z)(\bar{y} + \bar{z} + \bar{w})$$