


Solutions Homework 3

(Due date: March 19th @ 5:30 pm)


Presentation and clarity are very important! Show your procedure!

 PROBLEM 1 (12 PTS)

- Complete the timing diagram of the circuit shown below. (7 pts)




 - Complete the timing diagram of the circuit shown below: (5 pts)




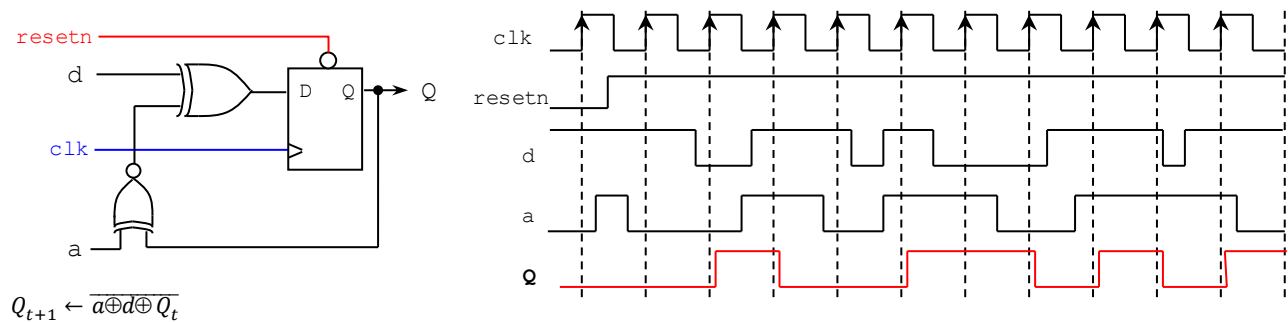PROBLEM 2 (17 PTS)

- Complete the timing diagram of the circuit shown below: (7 pts)




 - Complete the timing diagram of the circuit shown below: (10 pts)




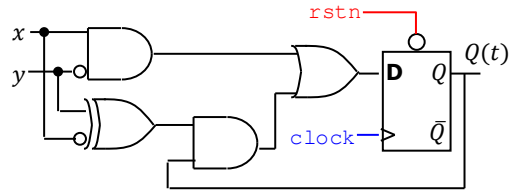PROBLEM 3 (16 PTS)

- With a D flip flop and logic gates, sketch the circuit whose excitation equation is given by:
✓ $Q(t+1) \leftarrow x\bar{y} + Q(t)(x \oplus y)$ (4 pts)



 - Given the following circuit, get the excitation equations for each flip flop output $Q = Q_3 Q_2 Q_1 Q_0$ (6 pts)



- Complete the timing diagram of the circuit whose VHDL description is shown below. Also, get the excitation equation for q .

```
library ieee;
use ieee.std_logic_1164.all;


entity circ is
  port (clrn, clk, a: in std_logic;
        q: out std_logic);
end circ;
```

```
architecture t of circ is
```

```
  signal qt: std_logic;
```

```
begin
  process (clrn, clk, x, a)
  begin
    if clrn = '0' then
      qt <= '0';
```

 
```
    elsif (clk'event and clk = '1') then
      if x = '0' then
        qt <= not(a) xor not(qt);
      end if;
    end if;
  end process;
  q <= qt;
end t;
```



$$q(t+1) \leftarrow \bar{x}.a \oplus q(t) + xq(t)$$

 PROBLEM 4 (18 PTS)


- Given the following circuit, complete the timing diagram (signals DO , Q and $DATA$).
The LUT 6-to-6 implements the following function: $OLUT = \lceil ILUT^{0.5} \rceil$, where $ILUT$ is an unsigned number.
For example: $ILUT = 35$ (10011_2) $\rightarrow OLUT = \lceil 35^{0.5} \rceil = 6$ (000110_2)



$$\begin{aligned} \lceil 20^{0.5} \rceil &= 5 \\ \lceil 48^{0.5} \rceil &= 7 \\ \lceil 26^{0.5} \rceil &= 6 \\ \lceil 17^{0.5} \rceil &= 5 \end{aligned}$$

 
PROBLEM 5 (12 PTS)

- Complete the timing diagram of the following 4-bit parallel access shift register with enable input. Shifting operation: $s_1=0$. Parallel load: $s_1=1$. Note that $Q = Q_3Q_2Q_1Q_0$. $D = D_3D_2D_1D_0$



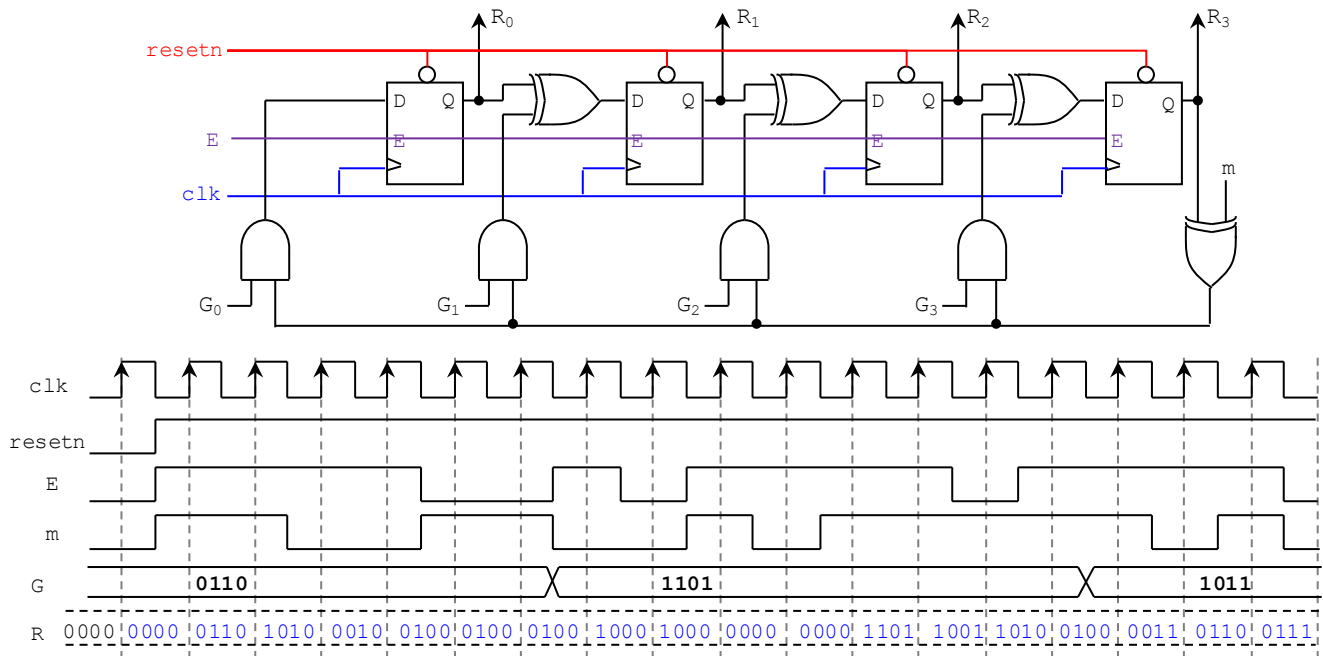PROBLEM 6 (25 PTS)

- For the following circuit, we have $R = R_3 R_2 R_1 R_0$. $G = G_3 G_2 G_1 G_0$
 - ✓ Write **structural** VHDL code. Create two files: i) flip flop, ii) top file (where you will interconnect the flip flops and the logic gates). Provide a printout. (10 pts)
 - ✓ Write a VHDL testbench according to the timing diagram shown below. Complete the timing diagram by simulating your circuit (Behavioral Simulation). The clock frequency must be 100 MHz with 50% duty cycle. Provide a printout. (15 pts)



✓ **VHDL Code: Top File**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity lfsr_crc2 is
    generic (N: INTEGER:= 4);
    port ( m_in, E: in std_logic;
          resetn, clock: in std_logic;
          G: in std_logic_vector (N-1 downto 0);
          R: out std_logic_vector (N-1 downto 0));
end lfsr_crc2;

architecture structural of lfsr_crc2 is

    component dffe
        port ( d : in  STD_LOGIC;
              clrn: in std_logic:= '1';
              prn: in std_logic:= '1';
              clk : in  STD_LOGIC;
              ena: in std_logic;
              q : out  STD_LOGIC);
    end component;

    signal B, D, Q: std_logic_vector (N-1 downto 0);

begin

    D(0) <= B(0);

    g0: for i in 1 to N-1 generate
        D(i) <= B(i) xor Q(i-1);
    end generate;

    g1: for i in 0 to N-1 generate
        di: dffe port map (d => D(i), clrn => resetn, prn => '1', clk => clock, ena => E, q => Q(i));
        R(i) <= Q(i);
        B(i) <= G(i) and (Q(N-1) xor m_in);
    end generate;

end structural;
```

✓ **VHDL Code: D-Type flip flop**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity dffe is
    port ( d : in  STD_LOGIC;
          clrn, prn, clk, ena: in std_logic;
          q : out  STD_LOGIC);
end dffe;

architecture behaviour of dffe is

begin
    process (clk, ena, prn, clrn)
    begin
        if clrn = '0' then q <= '0';
        elsif prn = '0' then q <= '1';
        elsif (clk'event and clk='1') then
            if ena = '1' then q <= d; end if;
        end if;
    end process;
end behaviour;
```

✓ **VHDL Tesbench:**

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_lfsr_crc2 IS
    generic (N: integer:= 4);
END tb_lfsr_crc2;

ARCHITECTURE behavior OF tb_lfsr_crc2 IS
    component lfsr_crc2
        port( m_in, E : IN  std_logic;
              resetn : IN  std_logic;
              clock : IN  std_logic;
              G: in std_logic_vector (N-1 downto 0);
              R : OUT  std_logic_vector(N-1 downto 0));
    end component;

    --Inputs
    signal m_in, E : std_logic := '0';
    signal resetn, clock : std_logic := '0';
    signal G: std_logic_vector (N-1 downto 0);

    --Outputs
    signal R : std_logic_vector(N-1 downto 0);

    constant T : time := 10 ns;    -- clock period definition

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: lfsr_crc2 PORT MAP (m_in => m_in, E => E, resetn => resetn, clock => clock, G => G, R => R);

    -- Clock process definitions
    clock_process: process
    begin
        clock <= '0'; wait for T/2;
        clock <= '1'; wait for T/2;
    end process;

    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
        resetn <= '0'; m_in <= '0'; G <= "1001";
        wait for 100 ns;
        resetn <= '1';

        -- insert stimulus here
        G <= "0110"; E <= '1'; m_in <= '1'; wait for 2*T;
        G <= "0110"; E <= '1'; m_in <= '0'; wait for 2*T;
        G <= "0110"; E <= '0'; m_in <= '1'; wait for 2*T;
        G <= "1101"; E <= '1'; m_in <= '0'; wait for T;
        G <= "1101"; E <= '0'; m_in <= '0'; wait for T;
        G <= "1101"; E <= '1'; m_in <= '1'; wait for T;
        G <= "1101"; E <= '1'; m_in <= '0'; wait for T;
        G <= "1101"; E <= '1'; m_in <= '1'; wait for 2*T;
        G <= "1101"; E <= '0'; m_in <= '1'; wait for T;
        G <= "1101"; E <= '1'; m_in <= '1'; wait for T;
        G <= "1011"; E <= '1'; m_in <= '1'; wait for T;
        G <= "1011"; E <= '1'; m_in <= '0'; wait for T;
        G <= "1011"; E <= '1'; m_in <= '1'; wait for T;
        G <= "1011"; E <= '0'; m_in <= '0'; wait for T;

        wait;
    end process;

END;
```