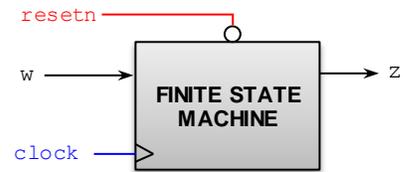


Solutions - Quiz 4

(April 7th @ 5:30 pm)

PROBLEM 1 (35 PTS)


- The following FSM has 4 states, one input w and one output z . (12 pts)
 - The excitation equations are given by:
 - $Q_1(t+1) \leftarrow Q_0(t)$
 - $Q_0(t+1) \leftarrow \overline{Q_1(t)} \oplus w$
 - The output equation is given by: $z = Q_1(t) \oplus Q_0(t) \oplus w$
- Provide the Excitation Table and the State Diagram (any representation).



PRESENT STATE			NEXTSTATE		
w	Q ₁ Q ₀ (t)		Q ₁ Q ₀ (t+1)		z
0	0	0	0	1	0
0	0	1	1	1	1
0	1	0	0	0	1
0	1	1	1	0	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	1	0
1	1	1	1	1	1



PRESENT STATE		NEXT STATE	
w	STATE	STATE	z
0	S0	S1	0
0	S1	S3	1
0	S2	S0	1
0	S3	S2	0
1	S0	S0	1
1	S1	S2	0
1	S2	S1	0
1	S3	S3	1

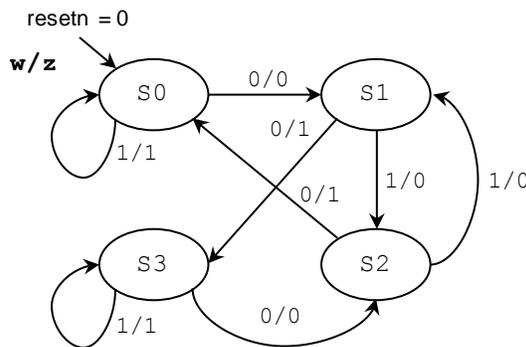State Assignment:
 S0: Q=00 S1: Q=01
 S3: Q=10 S2: Q=11



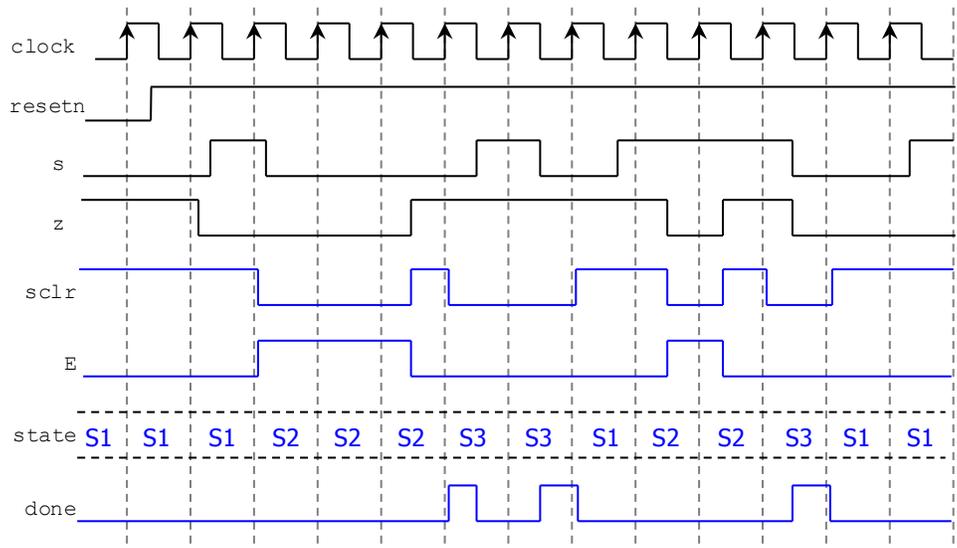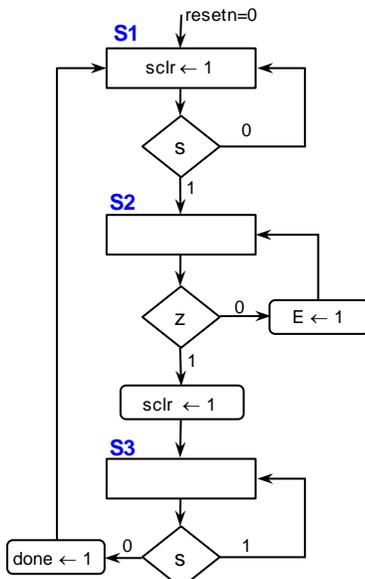PROBLEM 2 (35 PTS)

- Complete the timing diagram of the following FSM (represented in ASM form):



PROBLEM 3 (30 PTS)

- Sequence detector: Draw the state diagram (any representation) of an FSM with input x and output z . The detector asserts $z = 1$ when the sequence 0110 is detected. Right after the sequence is detected, the circuit looks for a new sequence.

