

**Student Honor Pledge:**

All work submitted is completed by me directly without the use of any unauthorized resources or assistance

# Final Exam


Initials: \_\_\_\_\_

(April 27<sup>th</sup> @ 7:00 pm)

Presentation and clarity are very important! Show your procedure!


## PROBLEM 1 (11 PTS)

- Given the following circuit, complete the timing diagram. The LUT 6-to-6 implements the following function:  $OLUT = |ILUT|$  (absolute value), where  $ILUT$  is a 6-bit signed (2C) number, and  $OLUT$  is a 6-bit unsigned number. For example  $ILUT = -29 = 10011_2 \rightarrow OLUT = |-29| = 29 (011101_2)$

 

 
## PROBLEM 2 (12 PTS)

- Complete the timing diagram of the following circuit.  $G = G_3G_2G_1G_0 = 0110$ ,  $Q = Q_3Q_2Q_1Q_0$



 **PROBLEM 3 (24 PTS)**


- Sequence detector: The machine generates  $z = 1$  when it detects the sequence 0100. Once the sequence is detected, the circuit looks for a new sequence.
- The signal E is an input enable: It validates the input  $x$ , i.e., if  $E=1$ ,  $x$  is valid, otherwise  $x$  is not valid.



- Draw the State Diagram (any representation) of this circuit with inputs E and x and output z. (7 pts)
- Complete the State Table and the Excitation Table (8 pts.)
- Provide the excitation equations and the Boolean output equation (simplify your circuit: K-maps or Quine-McCluskey).
- Sketch the circuit. (3 pts)
- Which type is this FSM? (Mealy) (Moore) Why? \_\_\_\_\_

**PROBLEM 4 (22 PTS)**

 - a) Given the following State Machine Diagram: (11 pts)
- ✓ Provide the State Table and the Excitation Table (4 pts.)
  - ✓ Get the excitation equations and the Boolean equation for z. (3 pts.)  
Use S0 (Q=00), S1 (Q=01), S2 (Q=10), S3 (Q=11) to encode the states.
  - ✓ Sketch the Finite State Machine circuit. (3 pts.)
  - ✓ Which type is this FSM? (Mealy) (Moore)




- b) A synchronous circuit (with *resetn* and *clock*), is described by these excitation equations (E is a synchronous input): (11 pts.)

$$Q_1(t+1) \leftarrow Q_1(t) \cdot Q_0(t) + \bar{E} \cdot Q_1(t) + Q_1(t) \cdot Q_0(t)$$

$$Q_0(t+1) \leftarrow E \cdot Q_0(t) + \bar{E} \cdot \overline{Q_0(t)}$$

 - ✓ With flip flops and logic gates, sketch the circuit.
- ✓ Complete the timing diagram.  $Q = Q_1Q_0$  (Tip: get the excitation table) (6 pts)



**PROBLEM 5 (13 PTS)**

- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. (7 pts.)

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
    port ( clk, resetn: in std_logic;
          r, p, q: in std_logic;
          x, w, z: out std_logic);
end circ;
```

```
architecture behavioral of circ is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (resetn, clk, r, p, q)
    begin
        if resetn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if r = '0' then
                        y <= S2;
                    else
                        if p = '1' then y <= S3; else y <= S1; end if;
                    end if;

                when S2 =>
                    if q = '1' then y <= S1; else y <= S3; end if;


                when S3 =>
                    if p = '1' then y <= S3; else y <= S2; end if;
            end case;
        end if;
    end process;

    Outputs: process (y, r, p, q)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => w <= '1';
                if r = '1' then x <= '1'; end if;

            when S2 => if p = '1' then x <= '1'; end if;
                if q = '0' then z <= '1'; end if;

            when S3 => if p = '0' then x <= '1'; end if;
        end case;
    end process;
end behavioral;
```

 - The figure shows an FSM model representing the circuit described in VHDL. The state (signal 'y' in the VHDL code) is represented by the bits  $Q_1$  and  $Q_0$ .



- ✓ If we use S1 (Q=00), S2 (Q=01), S3 (Q=10) to encode the states, what is the Boolean equation for w? (2 pts.)  
w =

- ✓ Circle the correct answer: (4 pts.)

- The 'Outputs' process outputs depend on clock and resetn? TRUE      FALSE
  - The relationship between [r,p,q, present state] and [next state] is described by: Transitions      Outputs  
Process              Process
  - The relationship between [r,p,q, present state] and [outputs x,w,z] is described by: Transitions      Outputs  
Process              Process
  - Is this a Mealy or a Moore FSM? Moore              Mealy

PROBLEM 6 (18 PTS)

- Complete the timing diagram of the following digital circuit that includes an FSM (in ASM form) and a Datapath circuit.
- The behavior (on the clock tick) of the generic register is as follows:

4-bit register: If E=0, the output is kept

```

if E = 1 then
  if sclr = 1 then
    Q ← 0
  else
    Q ← D
  end if;
end if;
    
```

