

Homework 1

(Due date: January 21st @ 11:59 pm)
Presentation and clarity are very important!

PROBLEM 1 (25 PTS)

a) Simplify the following functions using ONLY Boolean Algebra Theorems. For each resulting simplified function, sketch the logic circuit using AND, OR, XOR, and NOT gates. (15 pts).

✓ $F(x, y, z) = \prod(M_1, M_2, M_4, M_6)$ ✓ $F = \overline{B(\bar{C} + \bar{A})} + \overline{AB}$ ✓ $F = \overline{(x \oplus \bar{y})z} + xy\bar{z}$

b) For the following Truth table with two outputs: (10 pts)


- Provide the Boolean functions using the Canonical Sum of Products (SOP), and Product of Sums (POS). (4 pts)
- Express the Boolean functions using the minterms and maxterms representations.
- Sketch the logic circuits as Canonical Sum of Products and Product of Sums. (4 pts)

x	y	z	f ₁	f ₂
0	0	0	0	1
0	0	1	0	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	1	1
1	1	1	1	0

PROBLEM 2 (13 PTS)

 a) The following circuit (trapezoid) has the following logic function: $f = \bar{s}a + sb$.

- Complete the truth table of the circuit and sketch the logic circuit. (3 pts)




b) We can use several instances of the previous circuit (trapezoid) to implement different functions. (10 pts)

- For the given inputs, provide the resulting function g (minimize the function).

in1	in2	in3	in4	in5	in6	in7
x_1	0	x_3	1	0	x_1	x_2

- The following selection of inputs generate the function: $g = x_1x_2 + x_2x_3$. Demonstrate that this is the case.


in1	in2	in3	in4	in5	in6	in7
0	x_3	x_2	0	1	x_2	x_1

 

 PROBLEM 3 (11 PTS)


- Security combinations: A lock opens ($z = 0$) when the 4 switches (x_1, x_2, x_3, x_4) are set in any of the 3 configurations shown in the figure, otherwise the lock is closed ($z = 1$). A switch generates a '1' in the ON position, and a '0' in the OFF position.

- Provide the simplified Boolean equation for the output z and sketch the logic circuit.



PROBLEM 4 (26 PTS)

 a) Complete the truth table describing the output of the following circuit and write the simplified Boolean equation (6 pts).



b) Complete the timing diagram of the logic circuit whose VHDL description is shown below: (6 pts)


```

library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end circ;

architecture st of circ is
  signal x, y: std_logic;
begin
  x <= b xor (not a);
  f <= y nand (not b);
  y <= x nor c;
end st;

```

 

c) The following is the timing diagram of a logic circuit with 3 inputs. Sketch the logic circuit that generates this waveform. Then, complete the VHDL code. (8 pts)


```

library ieee;
use ieee.std_logic_1164.all;


entity wav is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end wav;

architecture st of wav is
-- ???
begin
-- ???
end st;

```

 


 d) Complete the timing diagram of the following circuit: (6 pts)



 PROBLEM 5 (25 PTS)

- A numeric keypad produces a 4-bit code as shown below. We want to design a logic circuit that converts each 4-bit code to a 7-segment code, where each segment is an LED: A LED is ON if it is given a logic '1'. A LED is OFF if it is given a logic '0'.
- ✓ Complete the truth table for each output (a, b, c, d, e, f, g). (4 pts)
- ✓ Provide the simplified expression for each output (a, b, c, d, e, f, g). Use Karnaugh maps for c, d, e, f, g and the Quine-McCluskey algorithm for a, b . Note that it is safe to assume that the codes 1100 to 1111 will not be produced by the keypad.



Value	x	y	z	w	a	b	c	d	e	f	g
0	0	0	0	0							
1	0	0	0	1							
2	0	0	1	0							
3	0	0	1	1							
4	0	1	0	0							
5	0	1	0	1							
6	0	1	1	0							
7	0	1	1	1							
8	1	0	0	0							
9	1	0	0	1	1	1	1	1	0	1	1
P	1	0	1	0							
H	1	0	1	1							
	1	1	0	0							
	1	1	0	1							
	1	1	1	0							
	1	1	1	1							

