


# Homework 4

(Due date: April 1<sup>st</sup> @ 11:59 pm)

Presentation and clarity are very important! Show your procedure!

 
## PROBLEM 1 (13 PTS)

- Complete the timing diagram of the following circuit.  $G = G_3G_2G_1G_0 = 1101$ ,  $Q = Q_3Q_2Q_1Q_0$



 
## PROBLEM 2 (20 PTS)

- Given the following State Machine Diagram: (10 pts)
  - Provide the State Table and the Excitation Table. (3 pts)
  - Get the excitation equations and the Boolean equation for z. (3 pts)  
Use S0 (Q=00), S1 (Q=01), S2 (Q=10), S3 (Q=11) to encode the states.
  - Sketch the Finite State Machine circuit. (3 pts)
  - Is it a Mealy or Moore Machine?




 - Provide the State Diagram (any representation), the Excitation Table, and the Excitation equations of the following Finite State Machine: (10 pts)



 **PROBLEM 3 (21 PTS)**

- Sequence detector: The machine generates  $z = 1$  when it detects the sequence 1010011. Once the sequence is detected, the circuit looks for a new sequence.



- Draw the State Diagram (any representation), State Table, and the Excitation Table of this circuit with input  $x$  and output  $z$ . (14 pts)
- Provide the excitation equations and the Boolean equation for  $z$  (simplify your circuit: K-maps or Quine-McCluskey).
- Sketch the circuit. Is this a Mealy or a Moore machine? Why? (3 pts)

**PROBLEM 4 (14 PTS)**

- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. Is it a Mealy or a Moore FSM?
- Complete the Timing Diagram.

```
library ieee;
use ieee.std_logic_1164.all;


entity circ is
    port ( clk, resetn: in std_logic;
          a, b: in std_logic;
          x,w,z: out std_logic);
end circ;
```

```
architecture behavioral of circ is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (resetn, clk, a, b)
    begin
        if resetn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if a = '1' then
                        if b = '1' then y <= S3; else y <= S1; end if;
                    else
                        y <= S2;
                    end if;

                when S2 =>
                    if b = '1' then y <= S3; else y <= S2; end if;



                when S3 =>
                    if a = b then y <= S3; else y <= S1; end if;
            end case;
        end if;
    end process;

     Outputs: process (y, a, b)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => if a = '1' then x <= '1'; end if;
            when S2 => w <= '1';
            when S3 => if a = b then z <= '1'; end if;
        end case;
    end process;
end behavioral;
```



  **PROBLEM 5 (17 PTS)**

- Complete the following timing diagram (A and P are specified as hexadecimals) of the following Iterative unsigned multiplier. The circuit includes an FSM (in ASM form) and a datapath circuit.
- Refer to the Lecture Notes for more details of the behavior of the generic components:
  - Register (for P): *sclr*: synchronous clear. Here, if  $E = sclr = 1$ , the register contents are initialized to 0.
  - Parallel access shift registers (for A and B): If  $E = 1$ :  $s_l = 1 \rightarrow$  Load,  $s_l = 0 \rightarrow$  Shift



**PROBLEM 6 (15 PTS)**

- Attach a printout of your Project Status Report (no more than 3 pages, single-spaced, 2 columns). This report should contain the current status of the project, including more details about the design and its components. You **MUST** use the provided template (Final Project - Report Template.docx).