

Student Honor Pledge:


All work submitted is completed by me directly without the use of any unauthorized resources or assistance
Initials: _____

Quiz 1

(January 26th @ 5:30 pm)

 PROBLEM 1 (30 PTS)

- Complete the timing diagram of the digital circuit shown below. You must consider the propagation delays. Assume the propagation delay of every gate is 5 ns. The initial values of all signals are plotted in the figure.




PROBLEM 2 (30 PTS)

- Complete the timing diagram of the logic circuit whose VHDL description is shown below:

```
library ieee;
use ieee.std_logic_1164.all;

entity test is
  port ( a, b, c: in std_logic;
         f: out std_logic);
end test;

 architecture struct of test is
  signal x: std_logic;
begin
  f <= x xor b;
  x <= not(a) and c;
end struct;
```



PROBLEM 3 (40 PTS)

- The following is the timing diagram of a logic circuit with three inputs. Simplify the Boolean expression of the circuit and sketch the minimized circuit.

