

Student Honor Pledge:



All work submitted is completed by me directly without the use of any unauthorized resources or assistance
Initials: _____

Quiz 3

(March 23rd @ 5:30 pm)

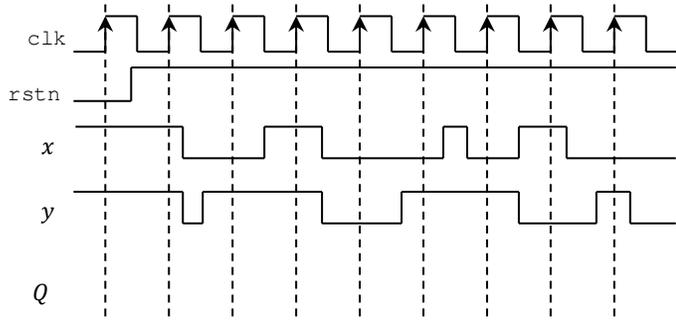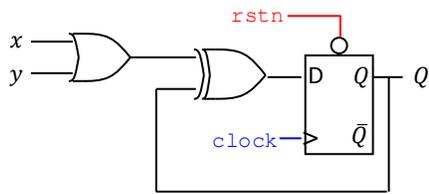PROBLEM 1 (30 PTS)



- Given the following circuit, complete the timing diagram and get the excitation equation for Q .



$Q(t + 1) \leftarrow$

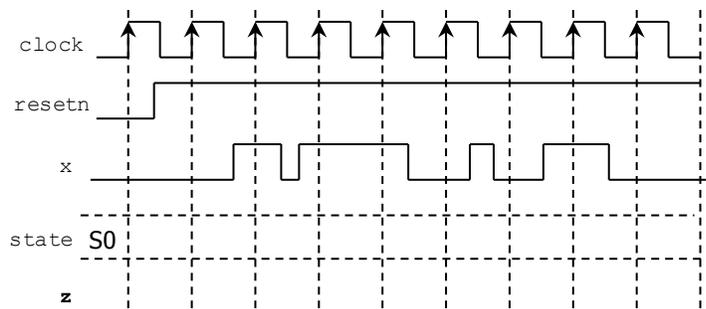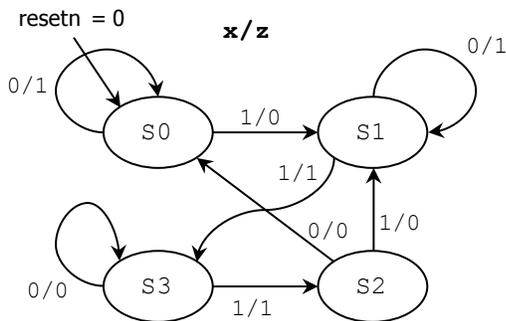PROBLEM 2 (35 PTS)

- Complete the timing diagram of the following state machine (30 pts):



- For the given FSM diagram, circle or mark the correct FSM type: (Mealy) (Moore)

PROBLEM 3 (35 PTS)

- Complete the timing diagram of the following circuit. $Q = Q_3Q_2Q_1Q_0$

