

Solutions - Homework 1

(Due date: January 21st @ 11:59 pm)


Presentation and clarity are very important!

PROBLEM 1 (25 PTS)

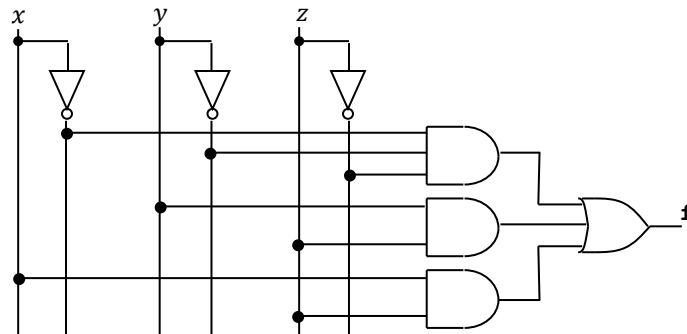
- a) Simplify the following functions using ONLY Boolean Algebra Theorems. For each resulting simplified function, sketch the logic circuit using AND, OR, XOR, and NOT gates. (15 pts).

✓ $F(x, y, z) = \prod(M_1, M_2, M_4, M_6)$ ✓ $F = \overline{B(\bar{C} + \bar{A})} + \overline{AB}$ ✓ $F = \overline{(x \oplus \bar{y})z + xy\bar{z}}$


✓ $F(X, Y, Z) = \prod(M_1, M_2, M_4, M_6) = \sum(m_0, m_3, m_5, m_7) = \bar{X}\bar{Y}\bar{Z} + \bar{X}YZ + X\bar{Y}\bar{Z} + XYZ = \bar{X}\bar{Y}\bar{Z} + Z(\bar{X}Y + X\bar{Y} + XY) = \bar{X}\bar{Y}\bar{Z} + Z(\bar{X}Y + X) = \bar{X}\bar{Y}\bar{Z} + Z(\bar{X} + X)(Y + X) = \bar{X}\bar{Y}\bar{Z} + ZY + ZX$



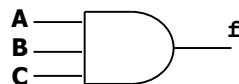✓ $F = \overline{B(\bar{C} + \bar{A})} + \overline{AB} = \overline{B\bar{C}} + \overline{B\bar{A}} + \overline{AB} = \overline{B\bar{C}} + \bar{A} + \bar{B} = \overline{B\bar{C}} + \bar{A} + (\bar{B} + B)(\bar{B} + \bar{C}) = \bar{A} + \bar{B} + \bar{C} = ABC$



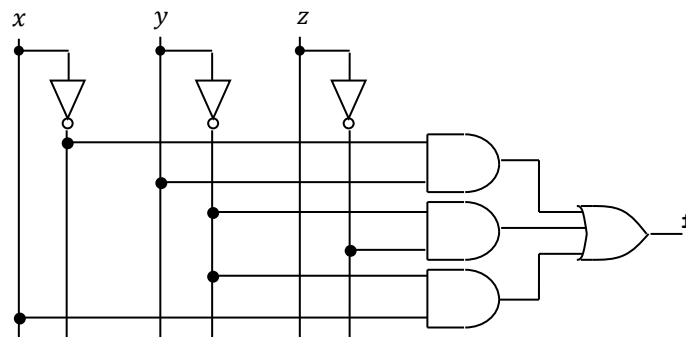✓ $F = \overline{(X \oplus \bar{Y})Z + XY\bar{Z}} = \overline{(XY + \bar{X}\bar{Y})Z + XY\bar{Z}} = \overline{XYZ + \bar{X}\bar{Y}Z + XY\bar{Z}} = \overline{XY + \bar{X}\bar{Y}Z} = \overline{XY} \cdot \overline{\bar{X}\bar{Y}Z} = (\bar{X} + \bar{Y})(X + Y + Z) = \bar{X}Y + \bar{X}Z + \bar{Y}X + \bar{Y}Z = \bar{X}Y + \bar{X}Z + \bar{Y}X + \bar{Y}Z = Y\bar{X} + \bar{Y}Z + \bar{Y}X$



- b) For the following Truth table with two outputs: (10 pts)

- Provide the Boolean functions using the Canonical Sum of Products (SOP), and Product of Sums (POS). (4 pts)
- Express the Boolean functions using the minterms and maxterms representations.
- Sketch the logic circuits as Canonical Sum of Products and Product of Sums. (4 pts)

x	y	z	f ₁	f ₂
0	0	0	0	1
0	0	1	0	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	1	1
1	1	1	1	0

Sum of Products

$$f_1 = \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XY\bar{Z} + XYZ$$

$$f_2 = \bar{X}\bar{Y}\bar{Z} + \bar{X}\bar{Y}Z + \bar{X}YZ + \bar{X}YZ + XYZ$$

Product of Sums


$$f_1 = (X + Y + Z)(X + Y + \bar{Z})(X + \bar{Y} + \bar{Z})(\bar{X} + Y + \bar{Z})$$

$$f_2 = (\bar{X} + Y + Z)(\bar{X} + Y + \bar{Z})(\bar{X} + \bar{Y} + \bar{Z})$$

Minterms and maxterms:


$$f_1 = \sum(m_2, m_4, m_6, m_7) = \prod(M_0, M_1, M_3, M_5).$$
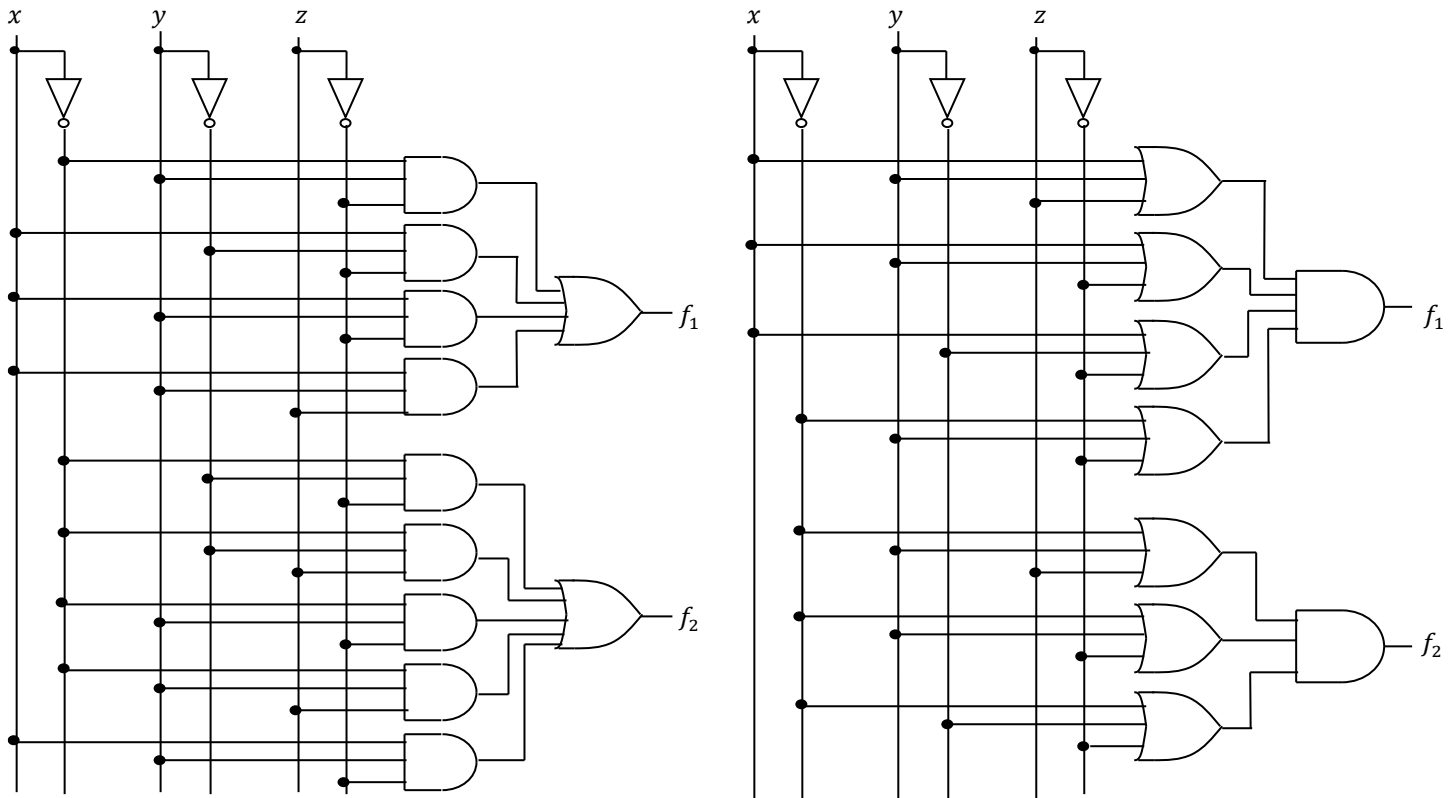
$$f_2 = \sum(m_0, m_1, m_2, m_3, m_6) = \prod(M_4, M_5, M_7).$$



PROBLEM 2 (13 PTS)

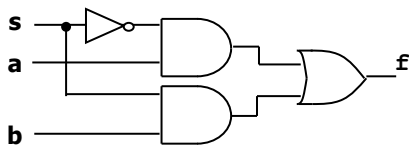- a) The following circuit (trapezoid) has the following logic function: $f = \bar{s}a + sb$.
 ▪ Complete the truth table of the circuit and sketch the logic circuit. (3 pts)




s	a	b	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

- b) We can use several instances of the previous circuit (trapezoid) to implement different functions. (10 pts)

- For the given inputs, provide the resulting function g (minimize the function).


in1	in2	in3	in4	in5	in6	in7
x_1	0	x_3	1	0	x_1	x_2

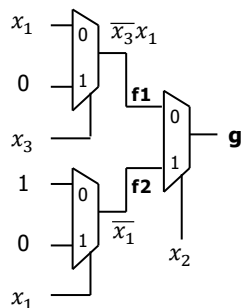

$$f_1 = \bar{x}_3(x_1) + x_3(0) = \bar{x}_3(x_1)$$


$$f_2 = \bar{x}_1(1) + x_1(0) = \bar{x}_1$$
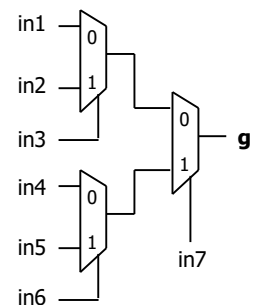
$$g = \bar{x}_2(\bar{x}_3x_1) + x_2(\bar{x}_1) = \bar{x}_1x_2 + \bar{x}_2x_1\bar{x}_3$$



- The following selection of inputs generate the function: $g = x_1x_2 + x_2x_3$. Demonstrate that this is the case.

in1	in2	in3	in4	in5	in6	in7
0	x_3	x_2	0	1	x_2	x_1

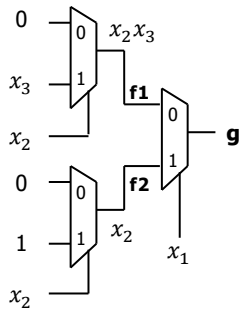

$$f_1 = \overline{x_2}(0) + x_2(x_3) = x_2x_3$$

$$f_2 = \overline{x_2}(0) + x_2(1) = x_2$$


$$g = \overline{x_1}(x_2x_3) + x_1(x_2) = x_2(x_1 + \overline{x_1}x_3) = x_2(x_1 + \overline{x_1})(x_1 + x_3)$$

$$g = x_2(x_1 + x_3) = x_1x_2 + x_2x_3$$

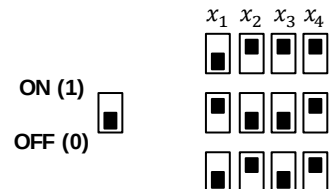PROBLEM 3 (11 PTS)


- Security combinations: A lock opens ($z = 0$) when the 4 switches (x_1, x_2, x_3, x_4) are set in any of the 3 configurations shown in the figure, otherwise the lock is closed ($z = 1$). A switch generates a '1' in the ON position, and a '0' in the OFF position.

✓ Provide the simplified Boolean equation for the output z and sketch the logic circuit.



x_1	x_2	x_3	x_4	z
0	1	1	1	0
1	0	0	1	0
0	1	0	1	0
All remaining cases				1

x_1x_2	00	01	11	10
0	1	0	1	0
1	1	0	1	1

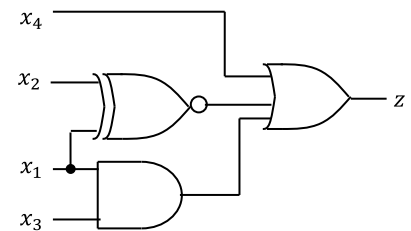

$$\bar{z} = \overline{x_1}x_2x_3x_4 + x_1\overline{x_2}\overline{x_3}x_4 + \overline{x_1}x_2\overline{x_3}x_4 = x_4(\overline{x_1}x_2x_3 + x_1\overline{x_2}\overline{x_3} + \overline{x_1}x_2\overline{x_3})$$


$$\bar{z} = x_4 \cdot f(x_1, x_2, x_3)$$

$$* f(x_1, x_2, x_3) = \sum m(3, 4, 2) \rightarrow \bar{f}(x_1, x_2, x_3) = \sum m(0, 1, 5, 6, 7)$$

$$z = \overline{x_4 \cdot f(x_1, x_2, x_3)} = \overline{x_4} + \bar{f}(x_1, x_2, x_3) = x_4 + x_1x_2 + \overline{x_1} \cdot \overline{x_2} + x_1 \cdot x_3$$

PROBLEM 4 (26 PTS)

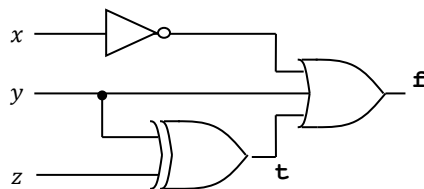- a) Complete the truth table describing the output of the following circuit and write the simplified Boolean equation (6 pts).



x	y	z	t	f
0	0	0	0	1
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	0	1


$$f = \bar{x} + y + (y \oplus z) = \bar{x} + y + z$$

- b) Complete the timing diagram of the logic circuit whose VHDL description is shown below: (6 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
    port ( a, b, c: in std_logic;
          f: out std_logic);
end circ;

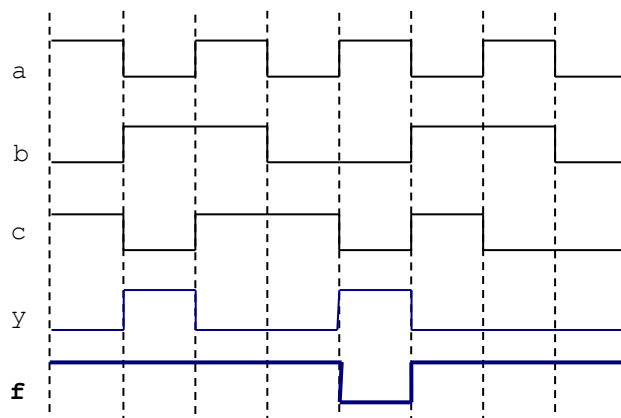architecture st of circ is
    signal x, y: std_logic;
begin
    x <= b xor (not a);
    f <= y nand (not b);
    y <= x nor c;
```




end st;

- c) The following is the timing diagram of a logic circuit with 3 inputs. Sketch the logic circuit that generates this waveform. Then, complete the VHDL code. (8 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity wav is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end wav;

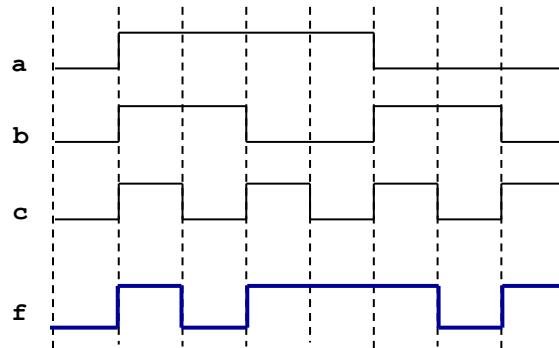
architecture st of wav is
  signal x: std_logic;
begin
  x <= a and not (b);
  f <= c or x;
end st;
```




a	b	c	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

ab		00	01	11	10
c	0	0	0	0	1
	1	1	1	1	1


$f = c + ab$

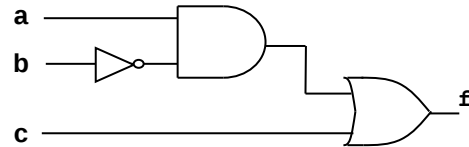

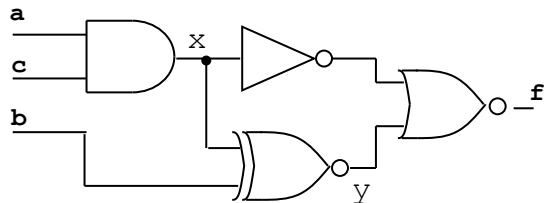- d) Complete the timing diagram of the following circuit: (6 pts)




$$f = a\bar{b}c$$

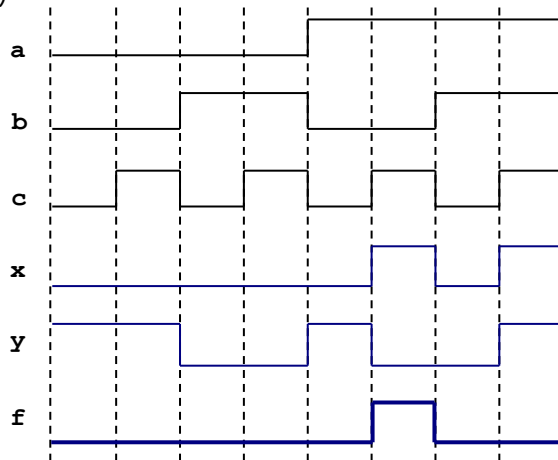


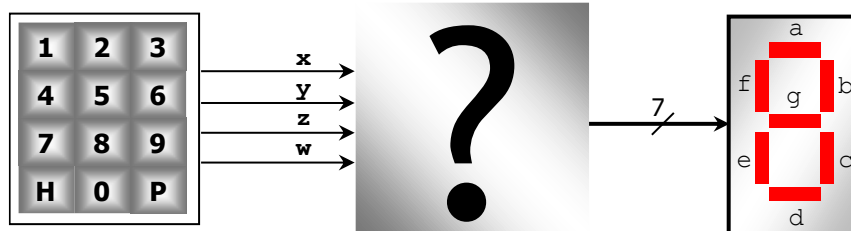PROBLEM 5 (25 PTS)

- A numeric keypad produces a 4-bit code as shown below. We want to design a logic circuit that converts each 4-bit code to a 7-segment code, where each segment is an LED: A LED is ON if it is given a logic '1'. A LED is OFF if it is given a logic '0'.
- Complete the truth table for each output (a, b, c, d, e, f, g). (4 pts)
- Provide the simplified expression for each output (a, b, c, d, e, f, g). Use Karnaugh maps for c, d, e, f, g and the Quine-McCluskey algorithm for a, b . Note that it is safe to assume that the codes 1100 to 1111 will not be produced by the keypad.




Value	X	Y	Z	W	a	b	c	d	e	f	g
0	0	0	0	0							
1	0	0	0	1							
2	0	0	1	0							
3	0	0	1	1							
4	0	1	0	0							
5	0	1	0	1							
6	0	1	1	0							
7	0	1	1	1							
8	1	0	0	0							
9	1	0	0	1	1	1	1	1	0	1	1
P	1	0	1	0							
H	1	0	1	1							
	1	1	0	0							
	1	1	0	1							
	1	1	1	0							
	1	1	1	1							

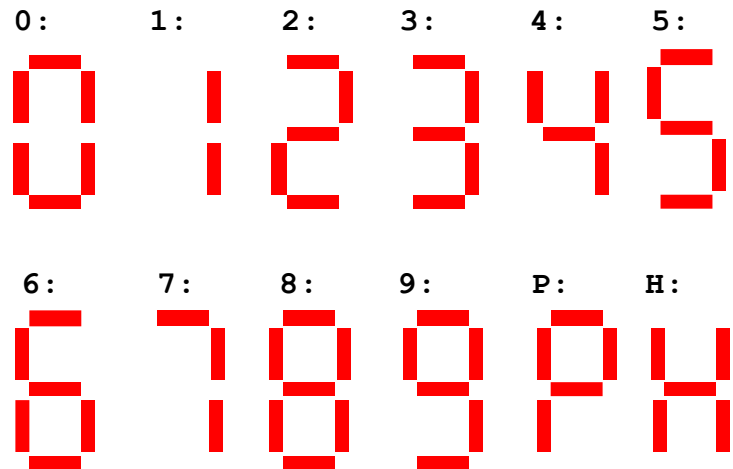

Value	X	Y	Z	W	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1
P	1	0	1	0	1	1	0	0	1	1	1
H	1	0	1	1	0	1	1	0	1	1	1
	1	1	0	0	X	X	X	X	X	X	X
	1	1	0	1	X	X	X	X	X	X	X
	1	1	1	0	X	X	X	X	X	X	X
	1	1	1	1	X	X	X	X	X	X	X
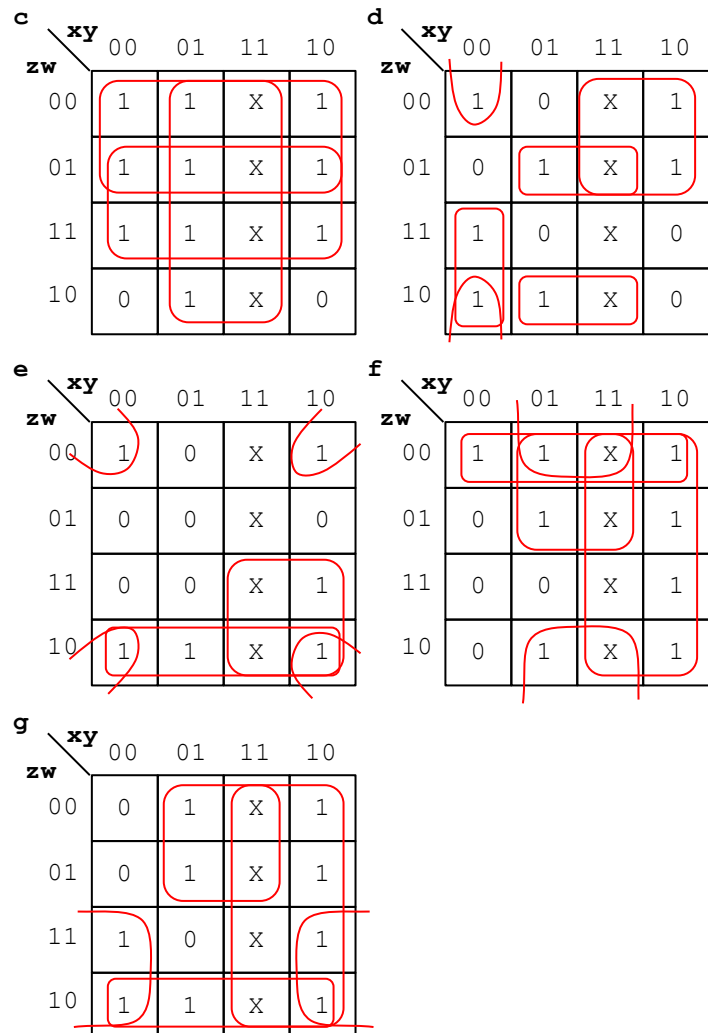
$$\begin{aligned}
 c &= y + \bar{z} + w \\
 d &= x\bar{z} + \bar{x}\bar{y}\bar{w} + \bar{x}\bar{y}z + \bar{z}wy + z\bar{w}y \\
 e &= \bar{w}\bar{y} + z\bar{w} + xz \\
 f &= x + \bar{z}\bar{w} + y\bar{z} + y\bar{w} \\
 g &= x + z\bar{w} + y\bar{z} + \bar{y}z
 \end{aligned}$$



- $a = \sum m(0,2,3,5,6,7,8,9,10) + \sum d(12,13,14,15)$.
Too many minterms. We better optimize: $\bar{a} = \sum m(1,4,11) + \sum d(12,13,14,15)$

Number of ones	4-literal implicants	3-literal implicants	2-literal implicants	1-literal implicants
1	$m_1 = 0001$ $m_4 = 0100$ ✓	$m_{4,12} = -100$		
2	$m_{12} = 1100$ ✓	$m_{12,13} = 110-$ ✓ $m_{12,14} = 11-0$ ✓	$m_{12,13,14,15} = 11--$ $m_{12,14,13,15} = 11--$ ✓	
3	$m_{11} = 1011$ ✓ $m_{13} = 1101$ ✓ $m_{14} = 1110$ ✓	$m_{13,15} = 11-1$ ✓ $m_{14,15} = 111-$ ✓ $m_{11,15} = 1-11$		
4	$m_{15} = 1111$ ✓			

$$\bar{a} = \bar{x}\bar{y}\bar{z}w + y\bar{z}\bar{w} + xzw + xy$$

Prime Implicants		Minterms		
		1	4	11
m_1	$\bar{x}\bar{y}\bar{z}w$	X		
$m_{4,12}$	$y\bar{z}\bar{w}$		X	
$m_{11,15}$	xzw			X
$m_{12,13,14,15}$	xy			

$$\bar{a} = \bar{x}\bar{y}\bar{z}w + y\bar{z}\bar{w} + xzw \Rightarrow a = (x + y + z + \bar{w})(\bar{y} + z + w)(\bar{x} + \bar{z} + \bar{w})$$

- $b = \sum m(0,1,2,3,4,7,8,9,10,11) + \sum d(12,13,14,15)$.
Too many minterms. We better optimize: $\bar{b} = \sum m(5,6) + \sum d(12,13,14,15)$

Number of ones	4-literal implicants	3-literal implicants	2-literal implicants	1-literal implicants
2	$m_5 = 0101$ ✓ $m_6 = 0110$ ✓ $m_{12} = 1100$ ✓	$m_{5,13} = -101$ $m_{6,14} = -110$ $m_{12,13} = 110-$ ✓ $m_{12,14} = 11-0$ ✓	$m_{12,13,14,15} = 11--$ $m_{12,14,13,15} = 11--$ ✓	
3	$m_{13} = 1101$ ✓ $m_{14} = 1110$ ✓	$m_{13,15} = 11-1$ ✓ $m_{14,15} = 111-$ ✓		
4	$m_{15} = 1111$ ✓			

$$\bar{b} = \bar{x}\bar{y}\bar{z}w + y\bar{z}\bar{w} + xzw + xy$$

Prime Implicants		Minterms	
		5	6
$m_{5,13}$	$y\bar{z}w$	X	
$m_{6,14}$	$yz\bar{w}$		X
$m_{12,13,14,15}$	xy		

$$\bar{b} = y\bar{z}w + yz\bar{w} \Rightarrow b = (\bar{y} + z + \bar{w})(\bar{y} + \bar{z} + w)$$