


Solutions - Homework 4

(Due date: April 1st @ 11:59 pm)

Presentation and clarity are very important! Show your procedure!

 PROBLEM 1 (13 PTS)

- Complete the timing diagram of the following circuit. $G = G_3G_2G_1G_0 = 1101$, $Q = Q_3Q_2Q_1Q_0$




PROBLEM 2 (20 PTS)

- Given the following State Machine Diagram: (10 pts)
 - Provide the State Table and the Excitation Table. (3 pts)
 - Get the excitation equations and the Boolean equation for z . (3 pts)
 - Use S_0 ($Q=00$), S_1 ($Q=01$), S_2 ($Q=10$), S_3 ($Q=11$) to encode the states.
 - Sketch the Finite State Machine circuit. (3 pts)

PRESENT STATE		NEXT STATE		
w	$Q_1Q_0(t)$	$Q_1Q_0(t+1)$	z	
0	0 0	1 0	0	
0	0 1	0 0	0	
0	1 0	0 0	0	
0	1 1	0 0	1	
1	0 0	0 1	0	
1	0 1	1 1	0	
1	1 0	1 1	0	
1	1 1	1 0	0	



	PRESENT STATE	NEXT STATE	
w	STATE	STATE	z
0	S0	S2	0
0	S1	S0	0
0	S2	S0	0
0	S3	S0	1
1	S0	S1	0
1	S1	S3	0
1	S2	S3	0
1	S3	S2	0

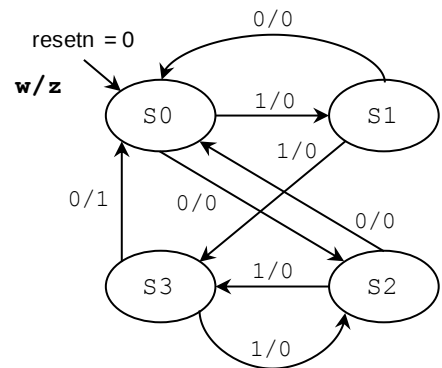

$$Q_1(t+1) \leftarrow (Q_1 + Q_0) \oplus w$$

$$Q_0(t+1) \leftarrow \overline{Q_1} \overline{Q_0} w$$

$$z = \overline{w} Q_1 Q_0$$


State Assignment:

$S_0: Q=00$ $S_1: Q=01$

$S_2: Q=10$ $S_3: Q=11$

- Is it a Mealy or Moore Machine?

This is a Mealy FSM

 

- Provide the State Diagram (any representation), the Excitation Table, and the Excitation equations of the following Finite State Machine: (10 pts)

$$Q_1(t+1) \leftarrow (Q_1 + Q_0)w$$

$$Q_0(t+1) \leftarrow (Q_1 Q_0) \oplus w$$

$$z = Q_1 + Q_0$$


State Assignment:

S0: Q = 00

S1: Q = 01

S2: Q = 10


S3: Q = 11

 

PRESENT STATE			NEXTSTATE		
w	Q ₁ Q ₀ (t)		Q ₁ Q ₀ (t+1)	z	
0	0 0	0	0 0	0	
0	0 1	1	0 1	1	
0	1 0	1	0 0	1	
0	1 1	1	0 0	1	
1	0 0	0	0 1	0	
1	0 1	1	1 0	1	
1	1 0	1	1 1	1	
1	1 1	1	1 1	1	




PRESENT STATE		NEXT STATE		
w	STATE	STATE	z	
0	S0	S0	0	
0	S1	S1	1	
0	S2	S0	1	
0	S3	S0	1	
1	S0	S1	0	
1	S1	S2	1	
1	S2	S3	1	
1	S3	S3	1	

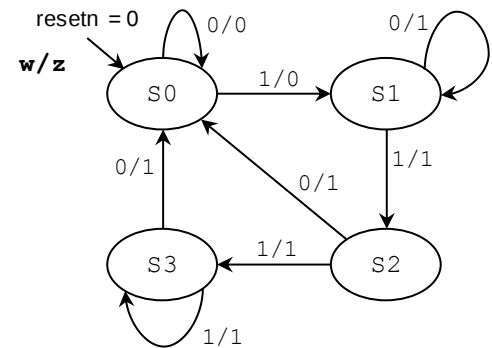

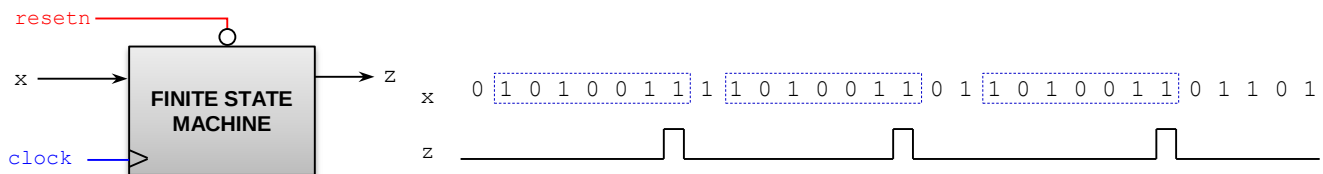PROBLEM 3 (21 PTS)

- Sequence detector: The machine generates $z = 1$ when it detects the sequence 1010011. Once the sequence is detected, the circuit looks for a new sequence.



- Draw the State Diagram (any representation), State Table, and the Excitation Table of this circuit with input x and output z . (14 pts)
- Provide the excitation equations and the Boolean equation for z (simplify your circuit: K-maps or Quine-McCluskey).
- Sketch the circuit. Is this a Mealy or a Moore machine? Why? (3 pts)

- State Diagram, State Table, and Excitation Table:


State Assignment:

S0: Q=000 S1: Q=001

S2: Q=010 S3: Q=011

S4: Q=100 S5: Q=101

S6: Q=110

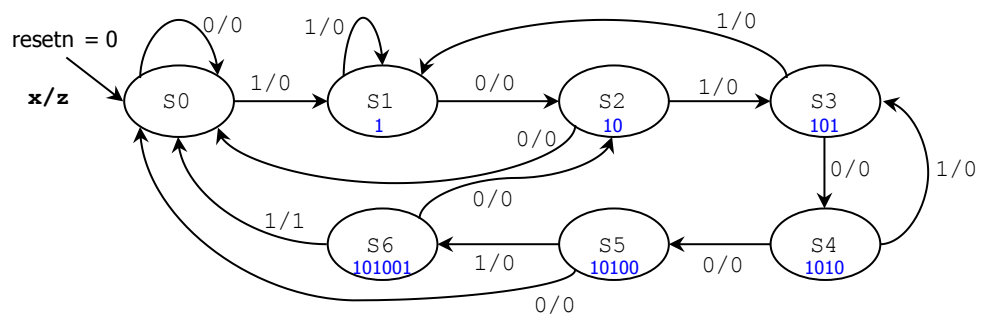

This a Mealy Machine. The output 'z' depends on the input as well as on the present state.

				PRESENT STATE		NEXT STATE	
x	STATE	STATE	z	x	Q ₂ Q ₁ Q ₀ (t)	Q ₂ Q ₁ Q ₀ (t+1)	z
0	S0	S0	0	0	0 0 0	0 0 0	0
0	S1	S2	0	0	0 0 1	0 1 0	0
0	S2	S0	0	0	0 1 0	0 0 0	0
0	S3	S4	0	0	0 1 1	1 0 0	0
0	S4	S5	0	0	1 0 0	1 0 1	0
0	S5	S0	0	0	1 0 1	0 0 0	0
0	S6	S2	0	0	1 1 0	0 1 0	0
1	S0	S1	0	1	0 1 1	X X X	X
1	S1	S1	0	1	1 0 0	0 0 1	0
1	S2	S3	0	1	1 0 0	0 0 1	0
1	S3	S1	0	1	1 0 1	0 1 1	0
1	S4	S3	0	1	1 0 1	0 0 1	0
1	S5	S6	0	1	1 1 0	0 1 1	0
1	S6	S0	1	1	1 1 0	1 1 0	0
					1 1 1	0 0 0	1
					1 1 1	X X X	X

- Excitation equations, minimization, and circuit implementation:

$$Q_2(t+1) = \bar{x}Q_2\bar{Q}_1\bar{Q}_0 + xQ_2Q_0 + \bar{x}Q_1Q_0$$


$$Q_1(t+1) = \bar{x}Q_2\bar{Q}_1Q_0 + xQ_2Q_1\bar{Q}_0 + xQ_2Q_1 + \bar{x}Q_2Q_1 = \bar{x}Q_2\bar{Q}_1Q_0 + xQ_2Q_1\bar{Q}_0 + Q_2(x \oplus Q_1)$$

$$Q_0(t+1) = Q_2\bar{Q}_1\bar{Q}_0 + xQ_2$$

$$z = xQ_2Q_1$$

$Q_2(t+1)$		$Q_1(t+1)$	
xQ_2		xQ_2	
Q ₁ Q ₀	00 01 11 10	Q ₁ Q ₀	00 01 11 10
00	0 1 0 0	00	0 0 1 0
01	0 0 1 0	01	1 0 1 0
11	1 X X 0	11	0 X X 0
10	0 0 0 0	10	0 1 0 1

$Q_0(t+1)$		z	
xQ_2		xQ_2	
Q ₁ Q ₀	00 01 11 10	Q ₁ Q ₀	00 01 11 10
00	0 1 1 1	00	0 0 0 0
01	0 0 0 1	01	0 0 0 0
11	0 X X 1	11	0 X X 0
10	0 0 0 1	10	0 0 1 0

 


PROBLEM 4 (14 PTS)

- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. Is it a Mealy or a Moore FSM?
- Complete the Timing Diagram.

```
library ieee;
use ieee.std_logic_1164.all;
```

 
```
entity circ is
    port ( clk, resetn: in std_logic;
          a, b: in std_logic;
          x,w,z: out std_logic);
end circ;
```



```
architecture behavioral of circ is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (resetn, clk, a, b)
    begin
        if resetn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if a = '1' then
                        if b = '1' then y <= S3; else y <= S1; end if;
                    else
                        y <= S2;
                    end if;
                when S2 =>
                    if b = '1' then y <= S3; else y <= S2; end if;
                when S3 =>
                    if a = b then y <= S1; else y <= S2; end if;
            end case;
        end if;
    end process;



    Outputs: process (y, a, b)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => if a = '1' then x <= '1'; end if;
            when S2 => w <= '1';
            when S3 => if a = b then z <= '1'; end if;
        end case;
    end process;
end behavioral;
```

 This a Mealy Machine. The outputs depend on the input as well as on the present state.



  PROBLEM 5 (17 PTS)

- Complete the following timing diagram (A and P are specified as hexadecimals) of the following Iterative unsigned multiplier. The circuit includes an FSM (in ASM form) and a datapath circuit.
- Refer to the Lecture Notes for more details of the behavior of the generic components:
 - Register (for P): *sclr*: synchronous clear. Here, if $E = sclr = 1$, the register contents are initialized to 0.
 - Parallel access shift registers (for A and B): If $E = 1$: $s_l = 1 \rightarrow \text{Load}$, $s_l = 0 \rightarrow \text{Shift}$



PROBLEM 6 (15 PTS)

- Attach a printout of your Project Status Report (no more than 3 pages, single-spaced, 2 columns). This report should contain the current status of the project, including more details about the design and its components. You **MUST** use the provided template (Final Project - Report Template.docx).