

Digital Stopwatch

ECE-2700 FINAL PROJECT

Everardo Mejia, Sara Jamu, Hansen Shamoon, Tom Tooma

Design Objective


Using the Nexys A7 FPGA Development Board, design and develop a functional digital stopwatch.

- ❖ The stopwatch will display different units of time such as:
 - i. Minutes
 - ii. Seconds
 - iii. Deciseconds (tenths of a second)
 - iv. Centiseconds (hundredths of a second)

- ❖ Stopwatch will have multiple functions such as:
 - i. Start
 - ii. Lap
 - iii. Pause
 - iv. Reset



Logic Board Controls

 


- ❖ Center Button BTNC is used to set lap times.
- ❖ Switches 14 to 11 are used to toggle between lap times 1-4.
- ❖ CPU Reset button is used to reset the stopwatch.
- ❖ Switch 15 is used as a start/stop toggle switch for the stopwatch.
- ❖ All 7-segment displays will be used and will turn on automatically with the stopwatch.

Digilent Nexys A7-100T

Wiring Diagram


❖ Design has:

 - i. BCD counters and FSM counters
- ii. Finite State Machines
- iii. Multiplexors
- iv. Seven-Segment Displays
- v. Encoders
- vi. Decoders




Counters

 - ❖ Stopwatch has 6 counters for time unit tick rate and a counter for incrementing tick rate to the hundredth of a second, or centisecond.
- ❖ Top counter enables centi second counter for every 10^6 ns which then enables the centi second counter and so forth.





7-Segment Displays

 


- ❖ In the above diagram, all 7-segment displays but the first two are used to display the time. They are combined to work together.
- ❖ By using a 2-to-1 Mux, the stopwatch can toggle between showing lap times or watch time.
- ❖ Used a 6-to-1 Mux for the 7-segment displays connected to a 7-segment decoder.

Project Extra Feature

  


Lap Memory

 - ❖ Created 4 registers for 4 different lap times using a lap encoder with 2 bits to differentiate states of lap.
- ❖ Each lap belongs to a switch when toggled to show different lap times.
- ❖ Registers are connected to BCD Counters and outputs are 24 bit with shared connection which feed to the 2-to-1 Mux.
- ❖ FSM redirects data from the first register to the next register.



Finite State Machine

 - ❖ There are 6 different states for the FSM. Each state is connected to a 7-segment display.
- S0: Centisecond Display
S1: Decisecond Display
S2: Second Display
S3: Tens Second Display
S4: Minute Display
S5: Tens Minute Display
- ❖ Finite State Machine has a counter to tick between different states.
- ❖ Max Time Display: 59:59.99





Thank You!

Demonstration Video

https://drive.google.com/file/d/12X9szibKPFOjxEwfYIRO_UEvrL2FZXeN/view?usp=sharing

References

<http://www.secs.oakland.edu/~llamocca/VHDLforFPGAs.html>

<https://kcmedicine.org/healthminute/stopwatch/#>