

4-Way Traffic Light Controller

Rafil Yousif, Yuan Wei, Joe Kocenda

ECE 2700 Final Project - Daniel Llamocca


What Does it Do?

- 4-way traffic light controller simulating a real-life 4-way intersection
- Switches between two modes (regular and light traffic)
 - **Regular Traffic Mode:**
 - 15 second duration for the following states
 - N/S = **Green** & E/W = **Red**
 - N/S = **Red** & E/W = **Green**
 - 3 second duration for the following states
 - N/S = **Yellow** & E/W = **Red**
 - N/S = **Red** & E/W = **Yellow**
 - 1 second duration for the following state
 - N/S = **Red** & E/W = **Red**
 - **Light Traffic Mode:**
 - 1 second flashing yellow and red
 - N/S = **Yellow** & E/W = **Red**




Components

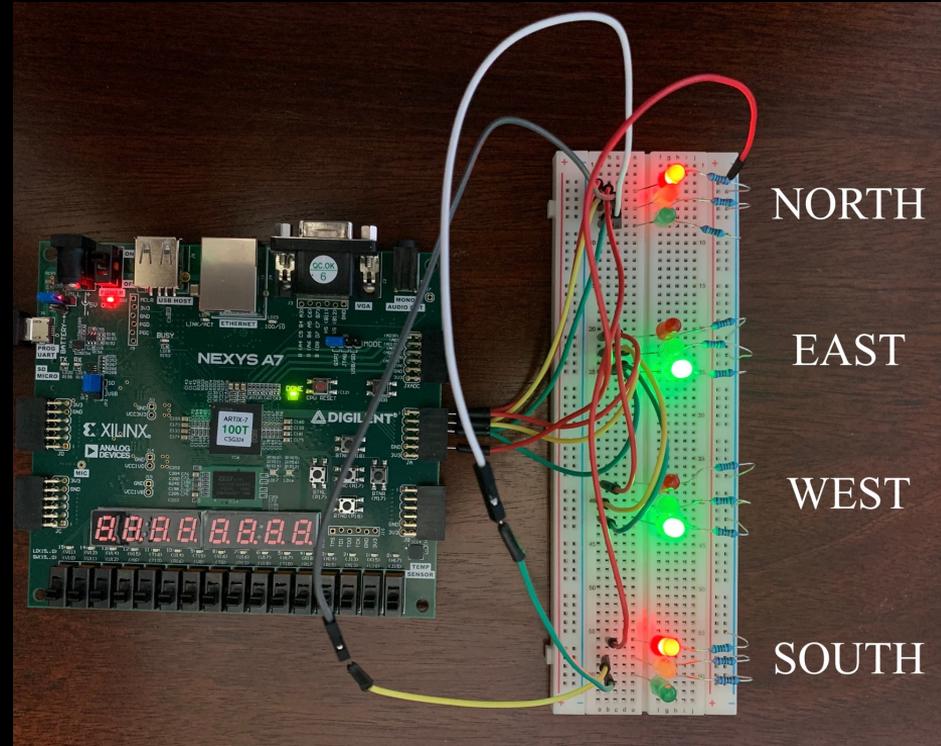- Nexys A7-100T with Vivado Software
- 4 Counters (15 sec, 3 sec, 1 sec 2x)
- 2 Finite State Machines
- 1 2-to-1 MUX
- Breadboard
- 12 Light Emitting Diodes (LED)
- 12 220 Ohm Resistors



Schematic/Block Diagram

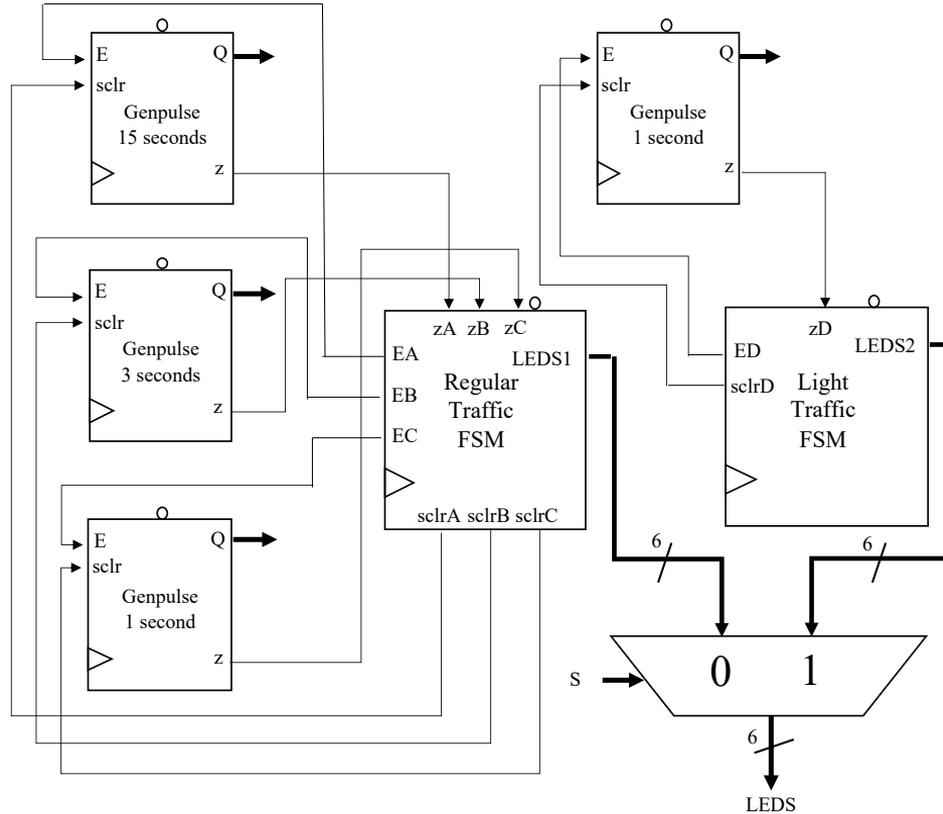


Circuit Functionality

- 4 total counters determine the amount of time elapsed.
 - 15 seconds, 3 seconds, 1 second x2
- The FSM's control the shifting of lights/states based on the outputs of the counters.
- Multiplexer is used to switch between the regular and light traffic modes (2 FSM's)

Regular Traffic ASM


- **State 0:** North/South = **Red**, East/West = **Green**
 - Utilizes 15 second counter $\rightarrow zA$
- **State 1:** North/South = **Red**, East/West = **Yellow**
 - Utilizes 3 second counter $\rightarrow zB$
- **State 2:** North/South = **Red**, East/West = **Red**
 - Utilizes 1 second counter $\rightarrow zC$
- **State 3:** North/South = **Green**, East/West = **Red**
 - Utilizes 15 second counter $\rightarrow zA$
- **State 4:** North/South = **Yellow**, East/West = **Red**
 - Utilizes 3 second counter $\rightarrow zB$
- **State 5:** North/South = **Red**, East/West = **Red**
 - Utilizes 1 second counter $\rightarrow zC$

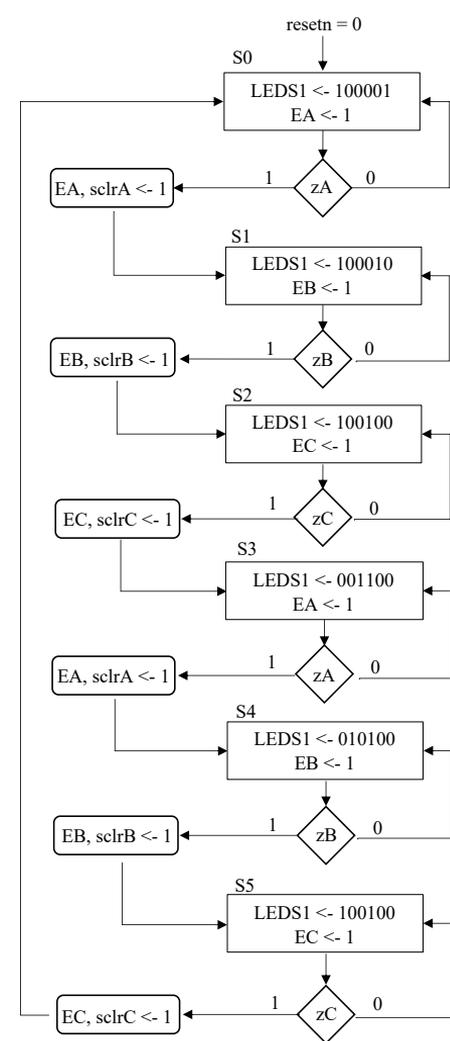

Light Traffic ASM


- Flashing Yellow/Red Mode

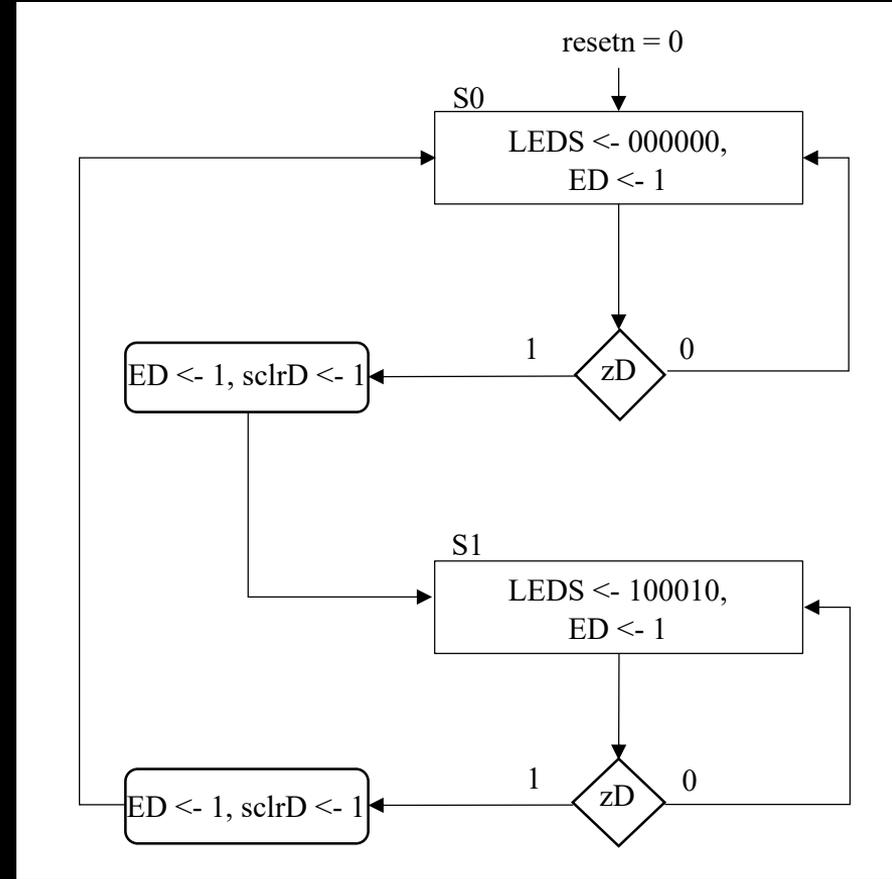- **State 0:** North/South = OFF, East/West = OFF
- **State 1:** North/South = **Yellow**, East/West = **Red**
 - Both utilize 1 second counter → zD



PMOD LED Implementation

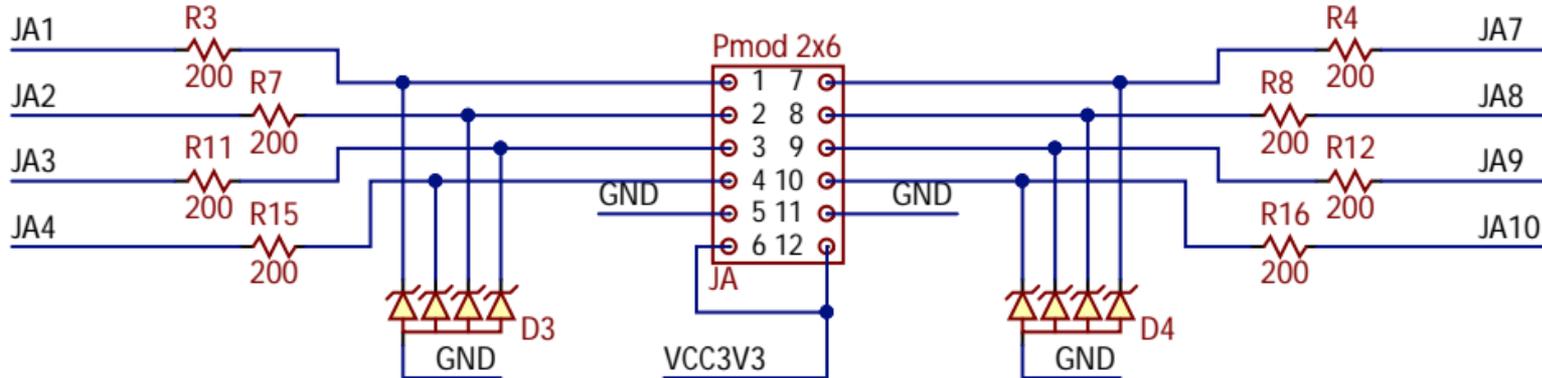- Allows for the connection between peripheral modules and the FPGA board.
- The PMOD port JA on the Nexys board was used to send signals to the LEDs on the breadboard.
 - Pins 1, 2, 3, 7, 8, and 9 were used for the 6-bit output, with pin 5 as GND.



Issues and Improvements

Issues

- Went through multiple different designs.
- Originally used only 1 FSM, but was too difficult to configure the flashing yellow mode, thus led to using 2 FSM's.
- Attempted to use the same 1 second counter for both FSM's, but coding had numerous issues.
- Implementing the circuit on a peripheral/outside source (breadboard) offered challenges as we never utilized the PMOD ports previously.
- During simulation, the regular traffic FSM wasn't transitioning between states at first and debugging the code took longer than expected.

Improvements

- Could have implemented a crosswalk system using more counters, or possibly the 7-segment display.
- Could have implemented left and right turns using more FSM's and counters.

Demonstration Video

<https://youtu.be/NsF06DjWaTg>