

Midterm Exam

(February 15th @ 5:30 pm)

Presentation and clarity are very important! Show your procedure!

PROBLEM 1 (22 PTS)

a) Complete the following table. The decimal numbers are unsigned: (3 pts.)

Decimal	BCD	Binary	Reflective Gray Code
			101011
	000100101000		

b) Complete the following table. The decimal numbers are signed. Use the fewest number of bits in each case: (15 pts.)

Decimal	REPRESENTATION		
	Sign-and-magnitude	1's complement	2's complement
	110001		
			10000
-32			1111
			0101001
		1011010	


c) Convert the following decimal numbers to their 2's complement representations. (4 pts)

✓ -17.25

✓ 16.75

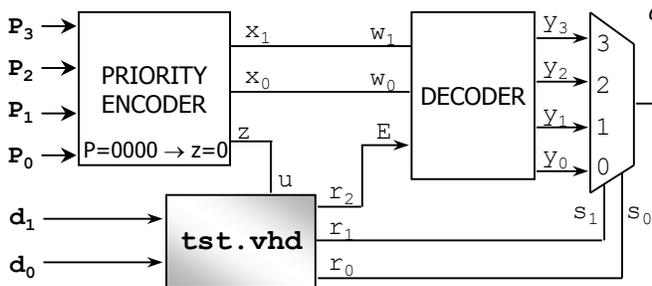PROBLEM 2 (14 PTS)

Complete the timing diagram of the following circuit. The VHDL code (tst.vhd) corresponds to the shaded circuit.




$$d = d_1d_0, w = w_1w_0, r = r_2r_1r_0, y = y_3y_2y_1y_0$$

```

library ieee;
use ieee.std_logic_1164.all;
entity tst is
    port (d: in std_logic_vector(1 downto 0);
          r: out std_logic_vector(2 downto 0);
          u: in std_logic);
end tst;
    
```

```

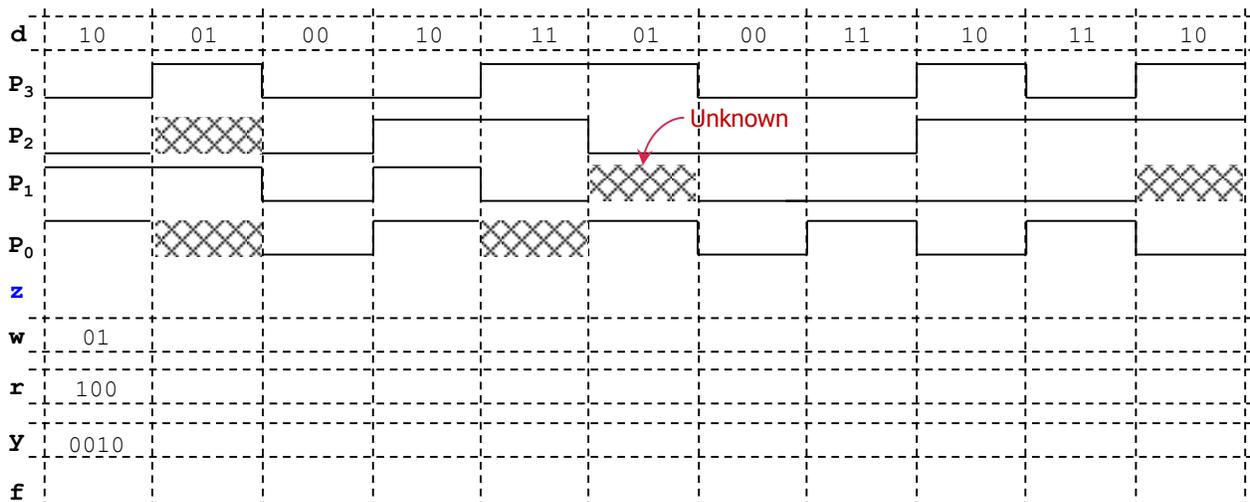architecture bhv of tst is
begin
    process (d, u)
    begin
        r <= '1'&d;
        if u = '1' then
            r <= d&'0';
        end if;
    end process;
end bhv;
    
```





PROBLEM 3 (11 PTS)

- Complete the timing diagram (signals *DO* and *DATA*) of the following circuit. The circuit in the blue box computes the signed operation $T-7$, with the result having 5 bits. T is a 4-bit signed (2C) number.

✓ Example: if $T=1010$:

$DO = 1010 - 0111 = 11010 + 11001$


$DO = 10011$

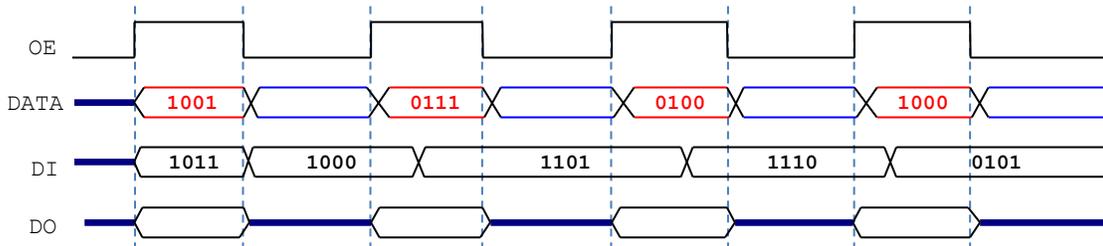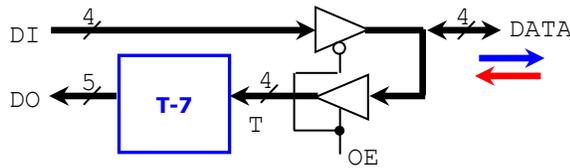

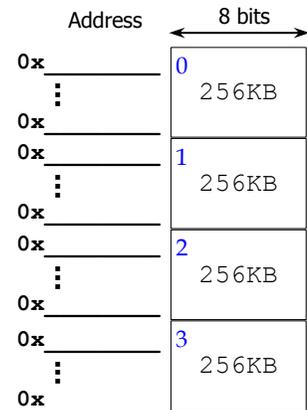PROBLEM 4 (10 PTS)

- A microprocessor has a memory space of 1 MB. Each memory address occupies one byte. $1KB = 2^{10}$ bytes, $1MB = 2^{20}$ bytes, $1GB = 2^{30}$ bytes.


- What is the address bus size (number of bits of the address) of the microprocessor?
- What is the range (lowest to highest, in hexadecimal) of the memory space for this microprocessor? (1 pt.)
- The figure to the right shows four memory chips that are placed in the given positions:
 - Complete the address ranges (lowest to highest, in hexadecimal) for each of the memory chips. (8 pts)



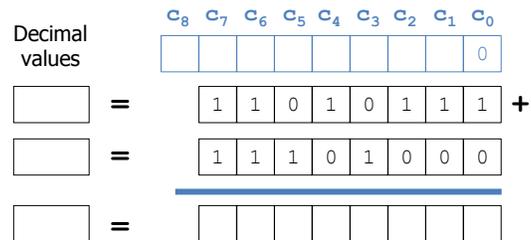PROBLEM 5 (15 PTS)

- Perform the following additions and subtractions of the following unsigned integers. Use the fewest number of bits n to represent both operators. Indicate every carry (or borrow) from c_0 to c_n (or b_0 to b_n). For the addition, determine whether there is an overflow. For the subtraction, determine whether we need to keep borrowing from a higher bit. (6 pts)
 - ✓ $37 + 41$
 - ✓ $37 - 41$

- The figure shows two 8-bit operands represented in 2's complement. Perform the 8-bit addition operation, i.e., complete all the carries and the summation bits. Also, indicate the corresponding decimal numbers for the 8-bit operands and the 8-bit result.



Does this 8-bit operation incur in overflow? Yes No
Value of the overflow bit: _____
Value of carry out bit: _____

- Perform binary multiplication of the following numbers that are represented in 2's complement arithmetic. (3 pts)
 - ✓ -7×9

PROBLEM 6 (10 PTS)

- Sketch the circuit that computes $|A - B|$, where A, B are 4-bit unsigned numbers. For example, $A = 0101, B = 1101 \rightarrow |A - B| = |5 - 13| = 8$. You can only use full adders (or multi-bit adders) and logic gates. Your circuit must avoid overflow: design your circuit so that the result and intermediate operations have the proper number of bits.

PROBLEM 7 (18 PTS)

- Sketch the circuit that implements the following Boolean function: $f(a, b, c, d) = (\bar{a} \oplus b)(c \oplus d)$
 - Using ONLY 2-to-1 MUXs (AND, OR, NOT, XOR gates are not allowed). (12 pts)
 - Using two 3-to-1 LUTs and a 2-to-1 MUX. Specify the contents of each of the 3-to-1 LUTs. (6 pts)