




Don't forget your bits (Combinational Lock)


Zachary Hill | Zachary Jump | Aidan Gallagher | Stephen Hayes

Objective & Function

- ◆ This digital combinational lock has the ability to:
 - ◆ Store a user's combination consisting of 3 initial 4 bit inputs including 0-9 and A-F with a button
 - ◆ Allows the user to attempt the stored combination using the switches
 - ◆ Provide input feedback and validation outputs when guessing combination (Seven Segment Display & LED)
 - ◆ Green light = correct combination
 - ◆ Red light = incorrect combination

 


Block Diagram & Components

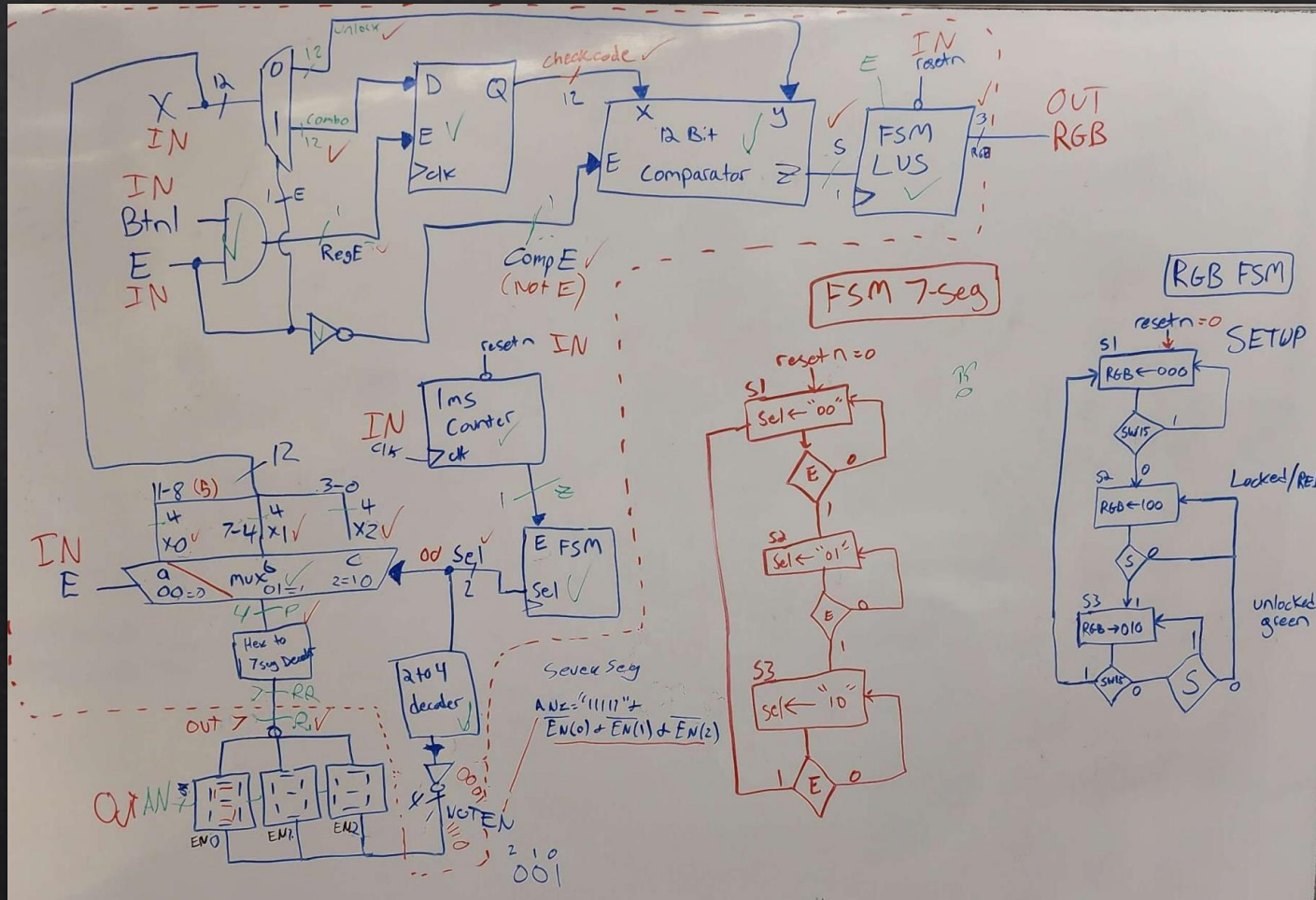

- ◇ Multiplexor & Demultiplexer
- ◇ Register
- ◇ Comparator
- ◇ Counter
- ◇ Decoder
- ◇ FSM(s)
 - ◇ Seven Segment FSM
 - ◇ RGB LED FSM


Demultiplexor (Demux) & Register

 
- ❖ The Demux passes the 12-bit code to the register or comparator based on the state of the enable switch
- ❖ The Register has 2 inputs: "D" & "E"
1 output: "Q" that goes to the comparator
 - ❖ D is the signal "combo" outputted from the Demux when E = '1'
 - ❖ E is Btn1 and the enable switch



Comparator

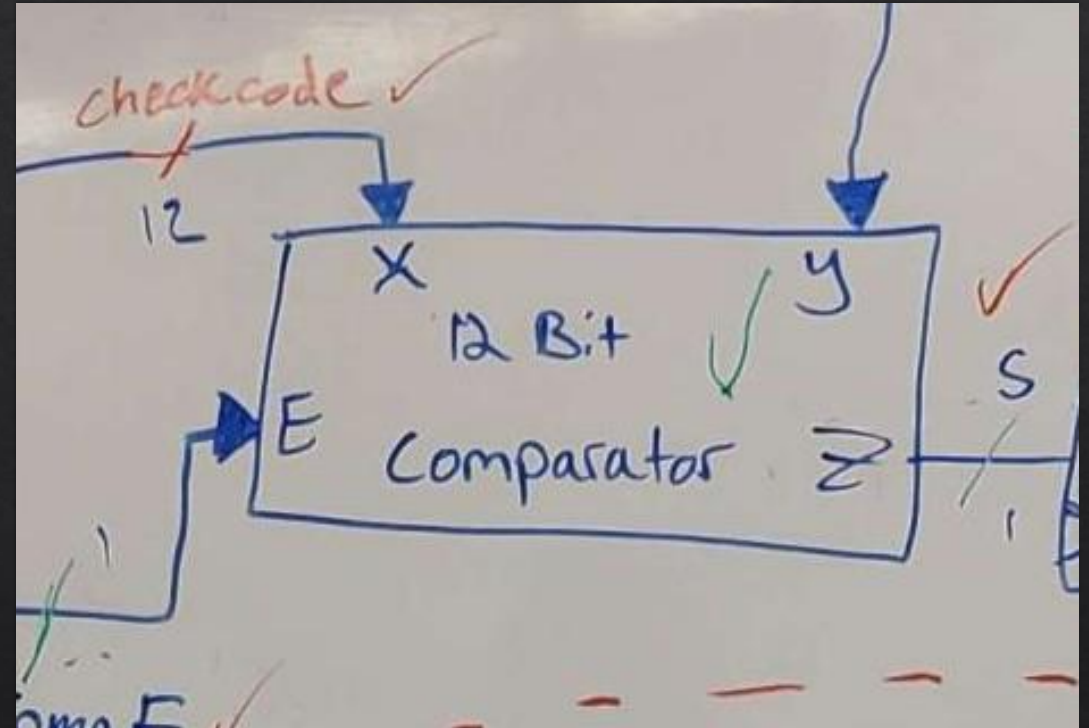
- ❖ Three inputs: "x", "y", and "E"
- ❖ One output: "z"
- ❖ While "E" is '1', the component will compare "x" and "y", outputting '1' when they are equal
- ❖ While "E" is '0' the component will output "z" as '0'




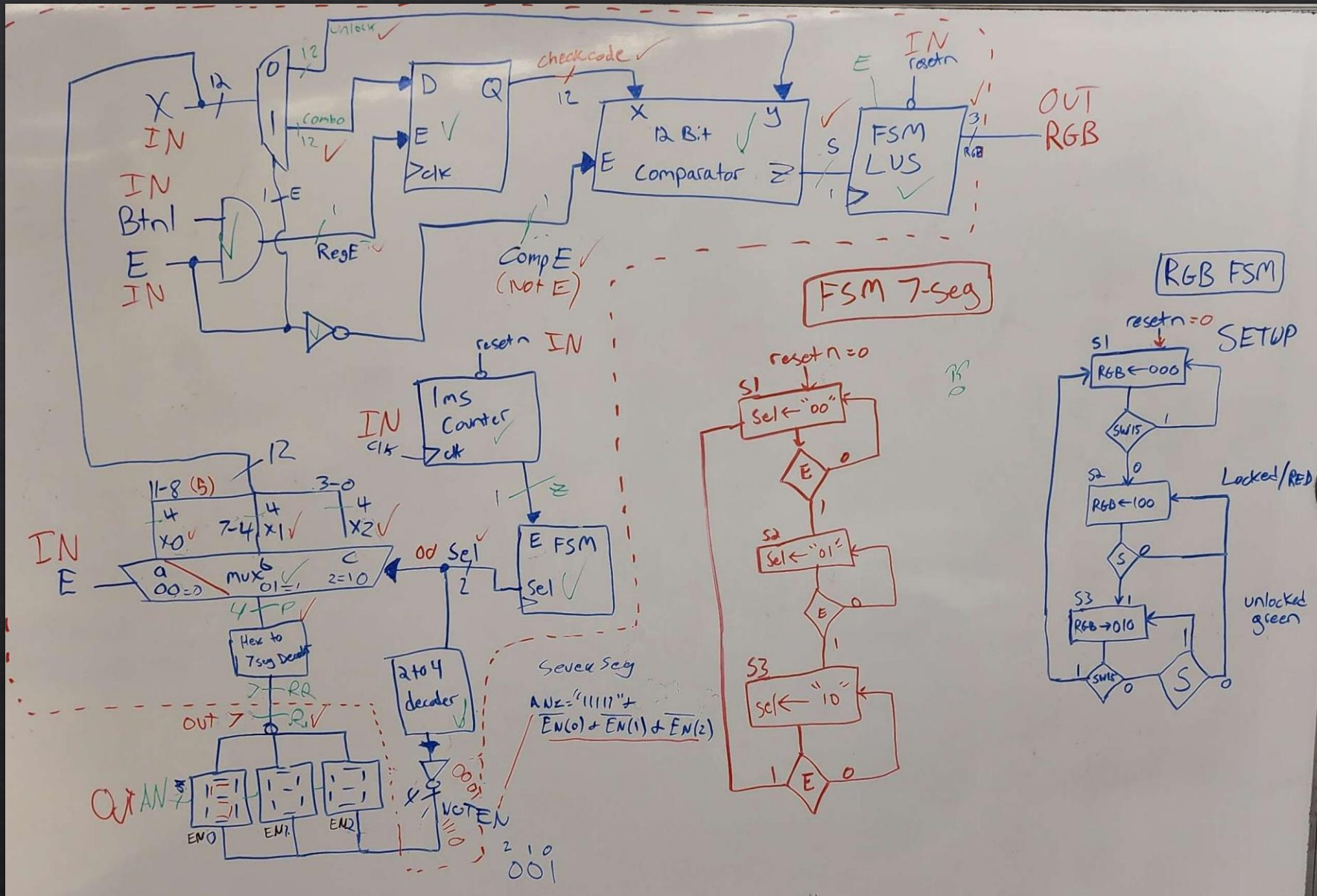

2 to 4 Decoder

 
- ❖ 2 to 4 decoder
1 input: "sel"
1 output: "y"
- ❖ The 2 to 4 decoder takes the value of sel and decodes it to activate the respected Seven Segment displays.
- ❖ The decoder will assign a 1 to the bit indicated by the decimal representation of the 2-bit input so 00 would decode to 0001 , 01 would decode to 0010 and so on



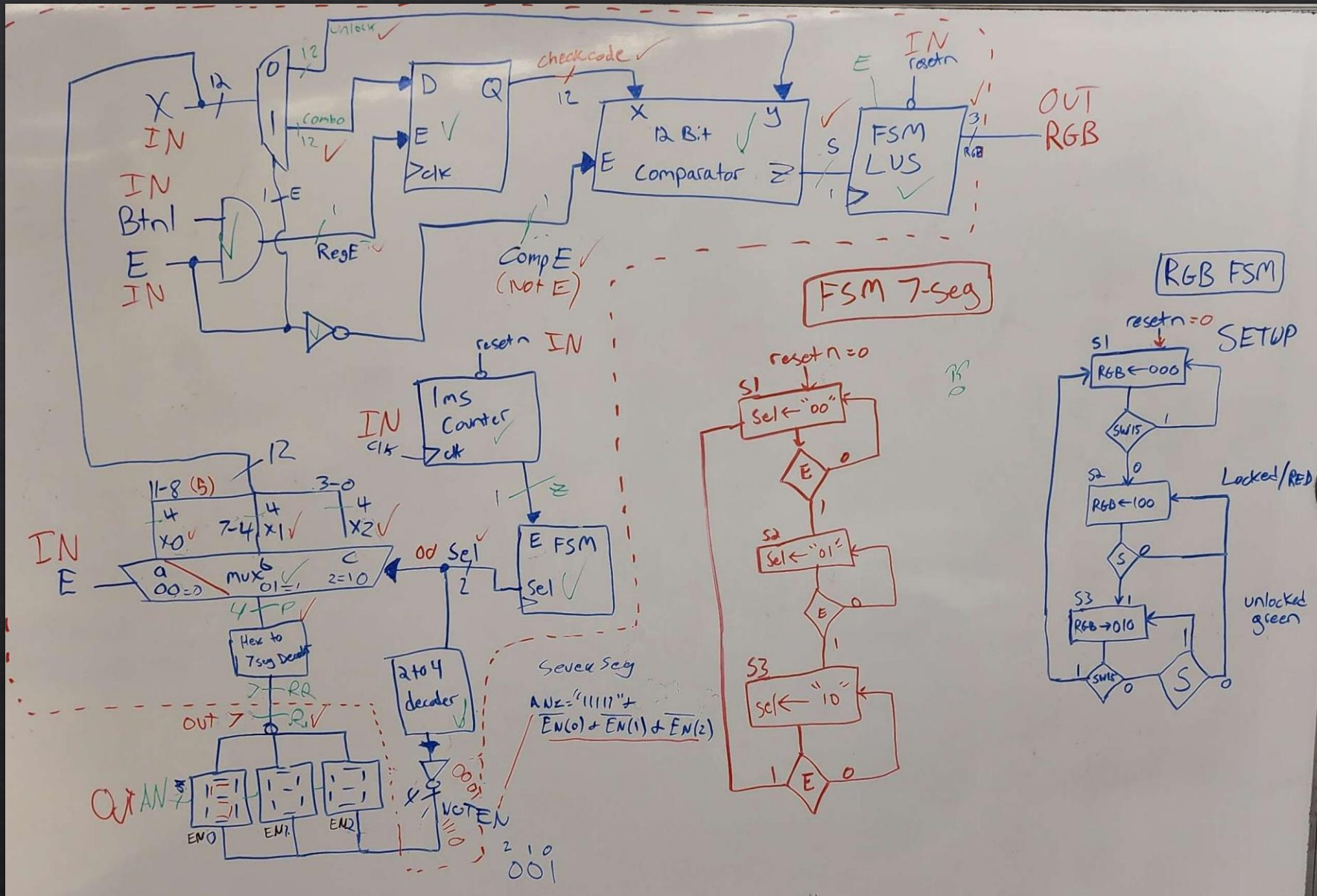


Counter

 - ❖ Two inputs: "clk" and "resetn"
- ❖ One output: "z"
- ❖ At the height of every clock tick, a signal tracks how many times the circuit has ran.
- ❖ In this case, an output of '1' is given when enough cycles of $T=10\text{ns}$ have ran to equate to 1 ms.




Multiplexor (Mux)

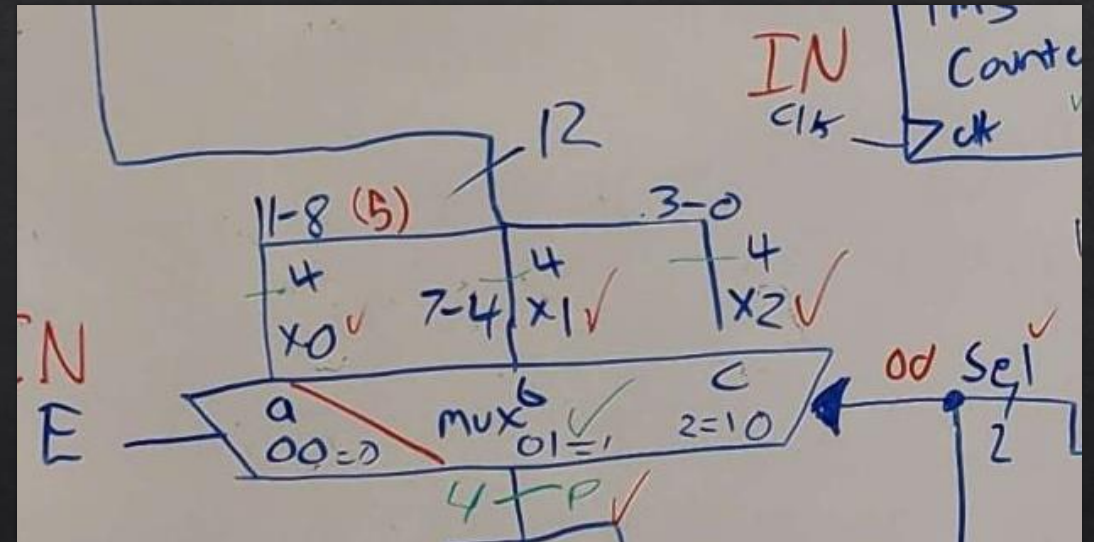
- ❖ 5 inputs: A, B, C, E, and Sel.
- ❖ A, B, and C are each 4 bits that are dependent on the input X from the 12 switches on the FPGA.
- ❖ E (Enable) and Sel (Select)
- ❖ There is one 4-bit output P



Hex to 7 Segment Decoder

 
- ◆ The Hex 7Seg Decoder has one input P and one output RR
- ◆ It takes the value given to it by the Mux and converts it to a 7-bit output that can will display on the seven segment displays



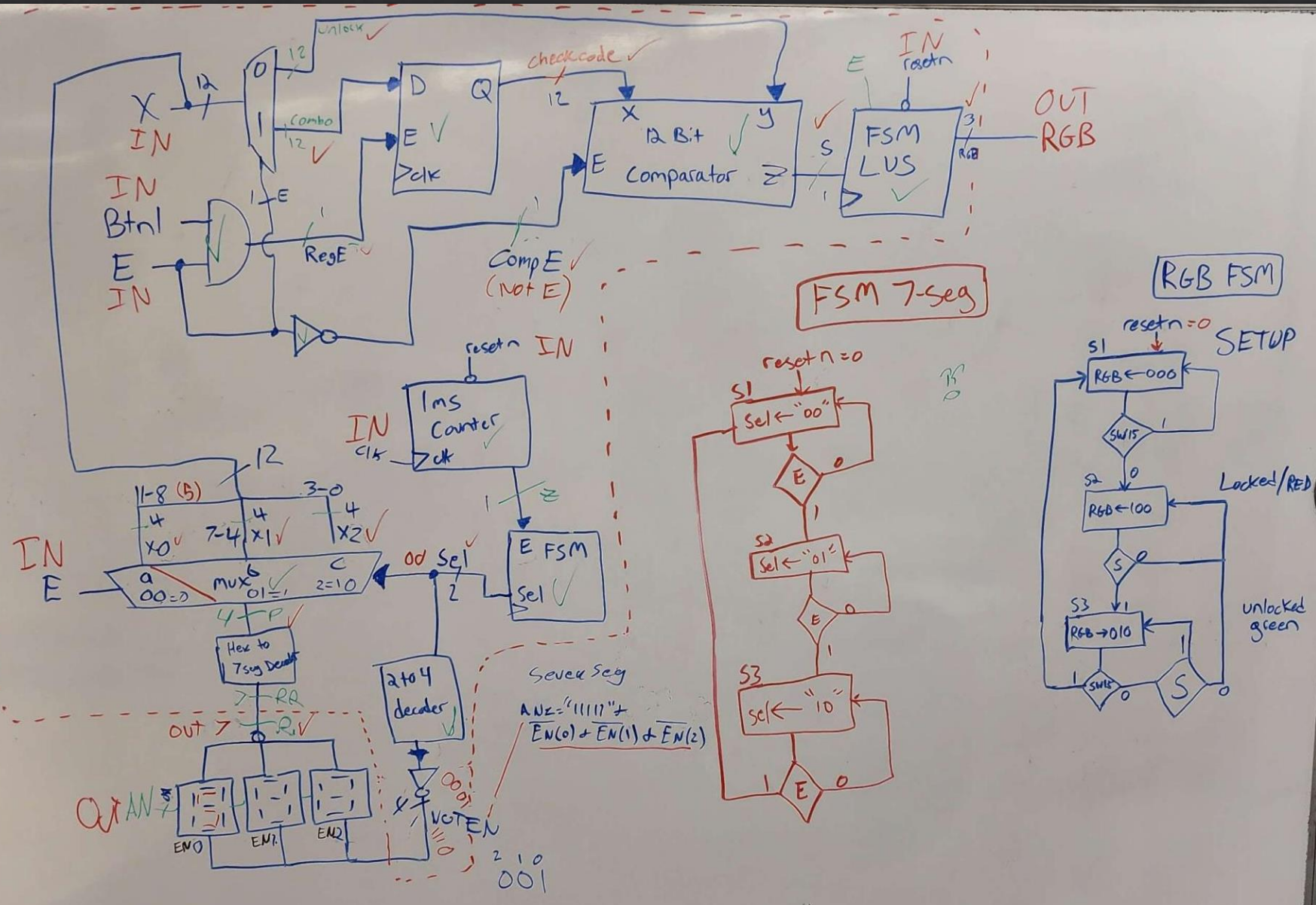

Seven Segment FSM

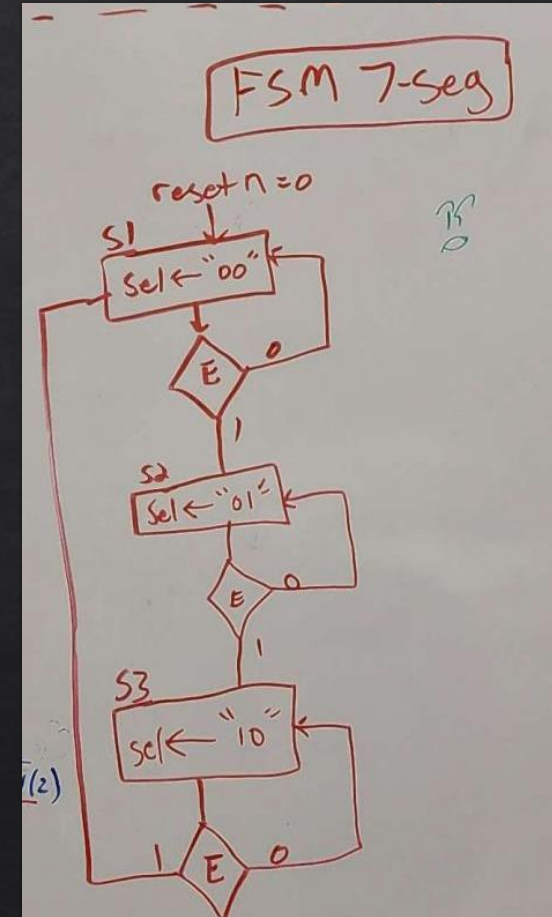- ◆ 3 State FSM
 - ◆ "Sel" 2-bit value tells the 3to1Mux which seven segment display to use
 - ◆ Enable value transitions between each states
- ◆ Transitions : "y" (controlled by resetn, clock, E)
- ◆ Outputs : "sel" (controlled by y, E)
- ◆ This FSM controls the MUX and the Decoder at the same time. This allows the 7 segment display to show different values on each of the displays



RGB LED FSM

◇ 3 State FSM

◇ Setup

◇ Locked

◇ Unlocked

◇ RGB Color definitions

R	G	B
0	0	0
1	0	0
0	1	0


◇ Off

◇ Red (Incorrect combination)


◇ Green (Correct combination)

◇ Transitions : y (controlled by resetn, clock, s, SW15)

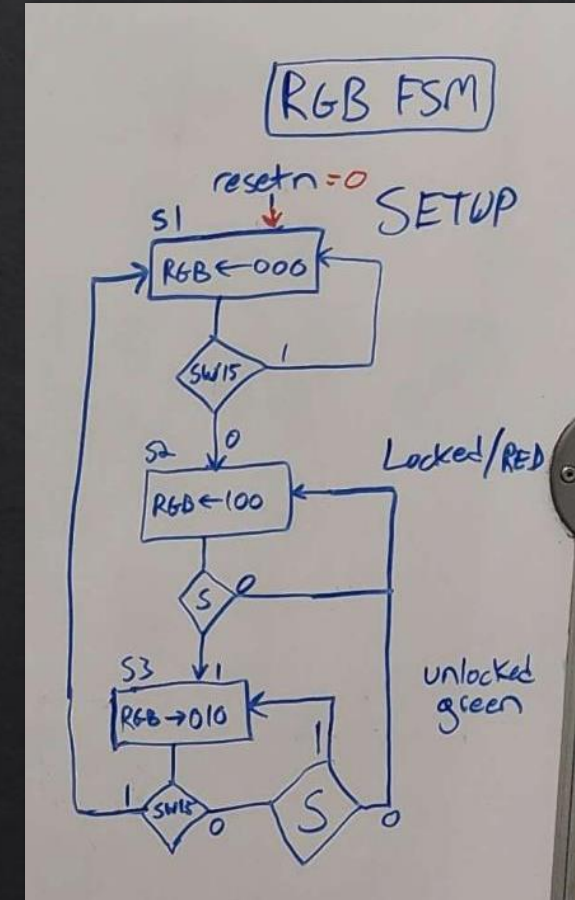◇ Outputs : RGB (controlled by y, s, SW15)




Constraints

 

Simulation

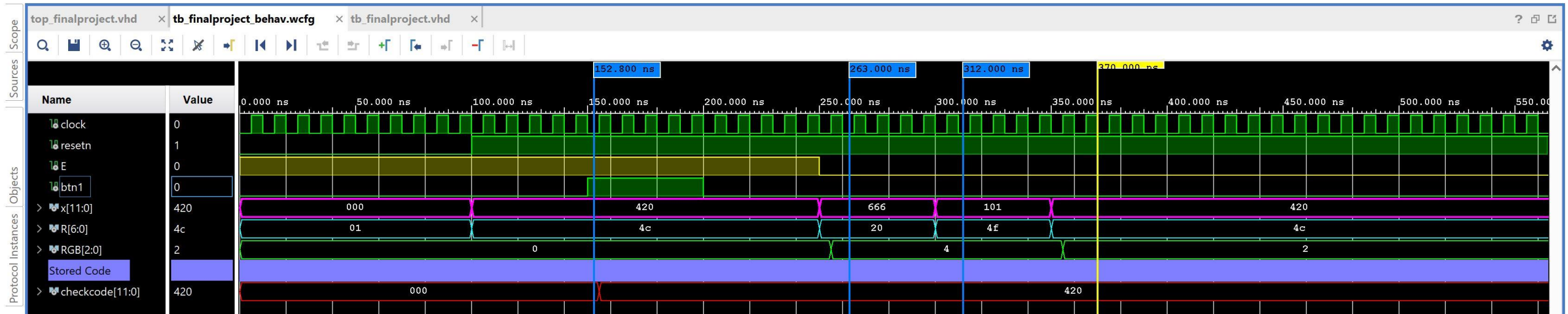SIMULATION - Behavioral Simulation - Functional - sim_1 - tb_finalproject



- ◇ User sets combination to 420
- ◇ Attempted combinations 666 and 101
 - ◇ RGB LED is still red (4)
- ◇ User attempts combination of 420
 - ◇ RGB LED becomes green (2)

Video Demonstration





Thank You!
Questions?