

# Homework 1

(Due date: January 19<sup>th</sup> @ 11:59 pm)

Presentation and clarity are very important! Show your procedure!

## PROBLEM 1 (28 PTS)

a) Simplify the following functions using ONLY Boolean Algebra Theorems. For each resulting simplified function, sketch the logic circuit using AND, OR, XOR, and NOT gates. (15 pts)

✓  $F(a, b, c) = \prod(M_0, M_1, M_4, M_6)$       ✓  $F = \overline{x(y \oplus z)} + \bar{y}$       ✓  $F = (A + \bar{B} + D)(\bar{A}B + \bar{D})$

b) Determine whether or not the following expression is valid, i.e., whether the left- and right-hand sides represent the same function. Suggestion: complete the truth tables for both sides: (5 pts)

$$x_1x_3 + \bar{x}_2\bar{x}_3 + \bar{x}_1x_2 = x_2x_3 + \bar{x}_1\bar{x}_3 + x_1\bar{x}_2$$


c) For the following Truth table with two outputs: (8 pts)

- Provide the Boolean functions using the Canonical Sum of Products (SOP), and Product of Sums (POS). (4 pts)
- Express the Boolean functions using the minterms and maxterms representations.
- Sketch the logic circuits as Canonical Sum of Products and Product of Sums. (3 pts)

x	y	z	f <sub>1</sub>	f <sub>2</sub>
0	0	0	1	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	0

## PROBLEM 2 (18 PTS)

 a) Security combinations: A lock only opens ( $z = 0$ ) when the 5 switches ( $x_1, x_2, x_3, x_4, x_5$ ) are set in any of the 3 configurations shown in the figure, otherwise the lock is closed ( $z = 1$ ). A switch generates a '1' in the ON position, and a '0' in the OFF position.



- Provide the simplified Boolean equation for the output  $z$  and sketch the logic circuit.


b) A doctoral student is defending his Dissertation. A 4-member committee determines whether to accept or reject the work. A simple majority vote is required. In case of a tie, the outcome is determined by the vote of the chair of the committee.

- Design the circuit (provide the simplified Boolean equation and sketch the logic circuit) that generates  $f = 1$  if the committee accepts the work, and  $f = 0$  if the work is rejected. We assign  $x, y, z, w$  to the vote of each committee member ( $w$  is the vote of the chair of the committee), where '1' means accept, and '0' reject. (8 pts)

## PROBLEM 3 (11 PTS)

 a) The following circuit has the following logic function:  $f = \bar{s}a + sb$ .

- Complete the truth table of the circuit, and sketch the logic circuit (3 pts)




b) We can use several instances of the previous circuit to implement different functions. (8 pts)

- For example, the following selection of inputs produce the function:  $g = \bar{x}_1x_2 + x_2x_3$ . Demonstrate that this is the case.

in1	in2	in3	in4	in5	in6	in7
0	1	$x_2$	0	$x_3$	$x_2$	$x_1$


- Given the following inputs, provide the resulting function  $g$  (minimize the function).

in1	in2	in3	in4	in5	in6	in7
$x_3$	0	$x_1$	1	0	$x_1$	$x_2$

 

**PROBLEM 4 (25 PTS)**

 a) Complete the truth table describing the output of the following circuit and write the simplified Boolean equation (6 pts).



f =


b) Complete the timing diagram of the logic circuit whose VHDL description is shown below: (6 pts)

```

library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end circ;

 architecture struct of circ is
  signal x, y: std_logic;
begin
  x <= not(a) xor not(c);
  f <= y and (not b);
  y <= x nor b;
end struct;
    
```




c) The following is the timing diagram of a logic circuit with 3 inputs. Sketch the logic circuit that generates this waveform. Then, complete the VHDL code (using VHDL signals is optional). (8 pts)

```



library ieee;
use ieee.std_logic_1164.all;

entity wave is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end wave;

 architecture struct of wave is
-- ???
begin
-- ???
end struct;
    
```




  d) Complete the timing diagram of the following circuit: (5 pts)



 PROBLEM 5 (18 PTS)

- A numeric keypad produces a 4-bit code  $xyzw$  representing an unsigned number from 0 to 9. We want to design a logic circuit that converts each 4-bit code to Morse code (where alphanumeric characters are encoded into sequences of dots and dashes). The figure depicts the Morse code representations for numbers from 0 to 9. The circuit generates 5 bits, where a '0' represents a dot, and '1' represents a dash.



- Complete the truth table for each output ( $q_4, q_3, q_2, q_1, q_0$ ). (3 pts)
- Provide the simplified expression for each output ( $q_4, q_3, q_2, q_1, q_0$ ). Use Karnaugh maps for  $q_4, q_3, q_2$ , and the Quine-McCluskey algorithm for  $q_1, q_0$ . Note it is safe to assume that the codes 1010 to 1111 will not be produced by the keypad. (15 pts)

Value	x	y	z	w	$q_4$	$q_3$	$q_2$	$q_1$	$q_0$
0	0	0	0	0					
1	0	0	0	1					
2	0	0	1	0					
3	0	0	1	1					
4	0	1	0	0					
5	0	1	0	1					
6	0	1	1	0					
7	0	1	1	1					
8	1	0	0	0					
9	1	0	0	1					
	1	0	1	0					
	1	0	1	1					
	1	1	0	0					
	1	1	0	1					
	1	1	1	0					
	1	1	1	1					