

Midterm Exam

(February 14th @ 5:30 pm)

Presentation and clarity are very important! Show your procedure!

PROBLEM 1 (22 PTS)

a) Complete the following table. The decimal numbers are unsigned: (3 pts.)

Decimal	BCD	Binary	Reflective Gray Code
			101011
	000100101000		

b) Complete the following table. The decimal numbers are signed. Use the fewest number of bits in each case: (15 pts.)

Decimal	REPRESENTATION		
	Sign-and-magnitude	1's complement	2's complement
	110001		
			10000
-32			1111
			0101001
		1111	

c) Convert the following decimal numbers to their 2's complement representations. (4 pts)


✓ -17.25

✓ 16.75

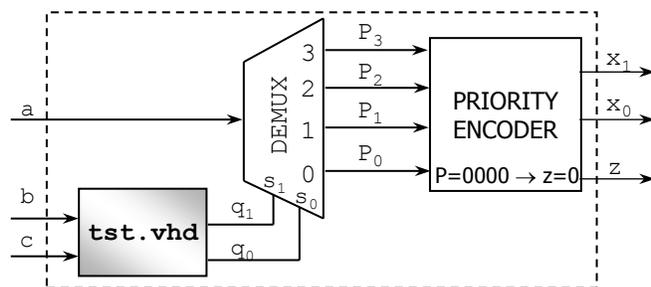PROBLEM 2 (15 PTS)

Complete the timing diagram of the following circuit. The VHDL code (tst.vhd) corresponds to the shaded circuit.

$$q = q_1q_0, P = p_3p_2p_1p_0, x = x_1x_0$$



```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity tst is
  port (b, c : in std_logic;
        q : out std_logic_vector(1 downto 0));
end tst;
```


architecture bhv of tst is

```
  signal t : std_logic;
```

```
begin
```

```
  t <= b xnor c;
  process (b,c,t)
  begin
    q <= b & c;
    if t = '0' then
      q <= c & b;
    end if;
  end process;
```



```
end bhv;
```

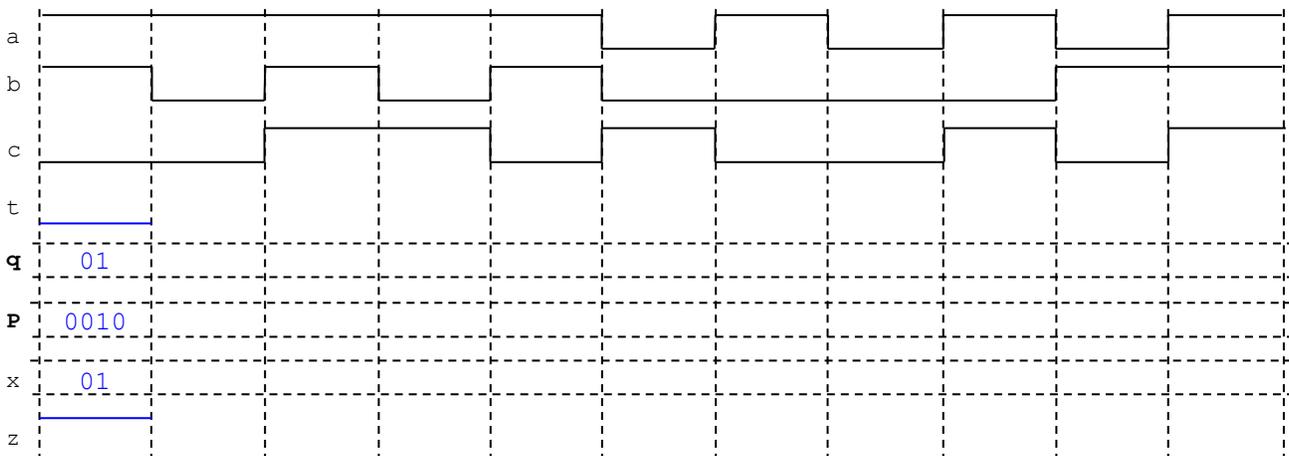

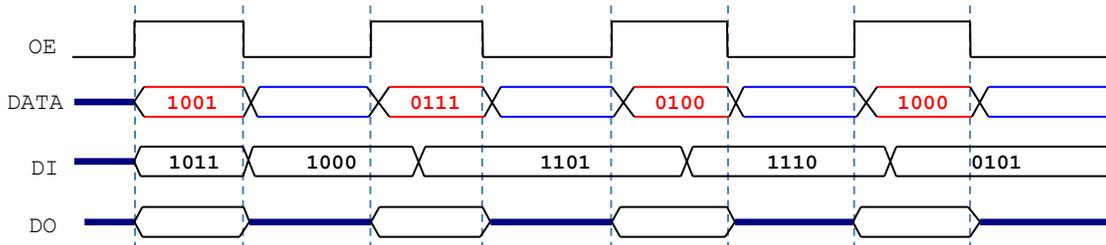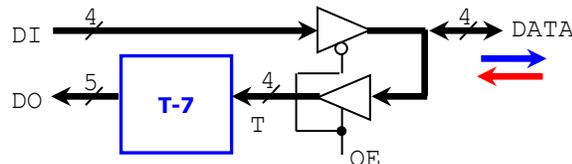PROBLEM 3 (12 PTS)


- Complete the timing diagram (signals *DO* and *DATA*) of the following circuit. The circuit in the blue box computes the signed operation $T-7$, with the result having 5 bits. T is a 4-bit signed (2C) number.

✓ Example: if $T=1010$:
 $DO = 1010-0111 = 11010 + 11001$
 $DO = 10011$



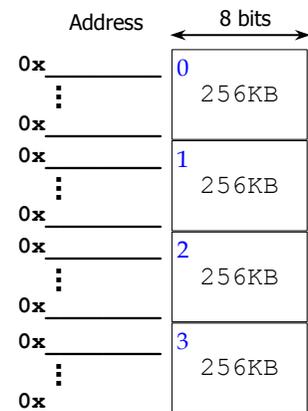PROBLEM 4 (10 PTS)


- A microprocessor has a memory space of 1 MB. Each memory address occupies one byte. $1KB = 2^{10}$ bytes, $1MB = 2^{20}$ bytes, $1GB = 2^{30}$ bytes.
 - What is the address bus size (number of bits of the address) of the microprocessor?
 - What is the range (lowest to highest, in hexadecimal) of the memory space for this microprocessor? (1 pt.)
 - The figure to the right shows four memory chips that are placed in the given positions:
 - Complete the address ranges (lowest to highest, in hexadecimal) for each of the memory chips. (8 pts)



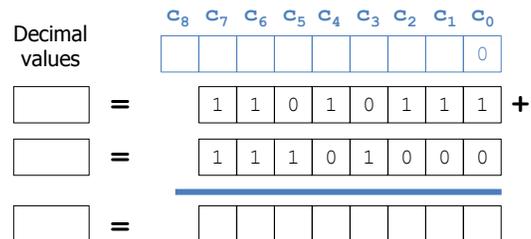PROBLEM 5 (15 PTS)

- Perform the following additions and subtractions of the following unsigned integers. Use the fewest number of bits n to represent both operators. Indicate every carry (or borrow) from c_0 to c_n (or b_0 to b_n). For the addition, determine whether there is an overflow. For the subtraction, determine whether we need to keep borrowing from a higher bit. (6 pts)
 - ✓ $37 + 41$
 - ✓ $37 - 41$

- The figure shows two 8-bit operands represented in 2's complement. Perform the 8-bit addition operation, i.e., complete all the carries and the summation bits. Also, indicate the corresponding decimal numbers for the 8-bit operands and the 8-bit result.



Does this 8-bit operation incur in overflow? Yes No
 Value of the overflow bit: _____
 Value of carry out bit: _____

- Perform binary multiplication of the following numbers that are represented in 2's complement arithmetic. (3 pts)
 ✓ 1001×01001

PROBLEM 6 (10 PTS)

- Sketch the circuit that computes $|A - B|$, where A, B are 4-bit signed numbers. For example, $A = 0101, B = 1101 \rightarrow |A - B| = |5 - (-3)| = 8$. You can only use full adders (or multi-bit adders) and logic gates. Your circuit must avoid overflow: design your circuit so that the result and intermediate operations have the proper number of bits.

PROBLEM 7 (16 PTS)

- In a 4-to-2 priority encoder (like the one in Problem 2), it can be demonstrated that the output $x_0 = \overline{p_3} \overline{p_2} p_1 + p_3$.
 - Provide the simplified expression for x_0 and sketch this circuit using logic gates. (3 pts)
 - Implement x_0 using ONLY an 8-to-1 MUX. (3 pts)
 - Implement x_0 using ONLY 2-to-1 MUXs (AND, OR, NOT, XOR gates are not allowed) (10 pts)