


Solutions - Final Exam

(April 18th @ 7:00 pm)

Presentation and clarity are very important! Show your procedure!

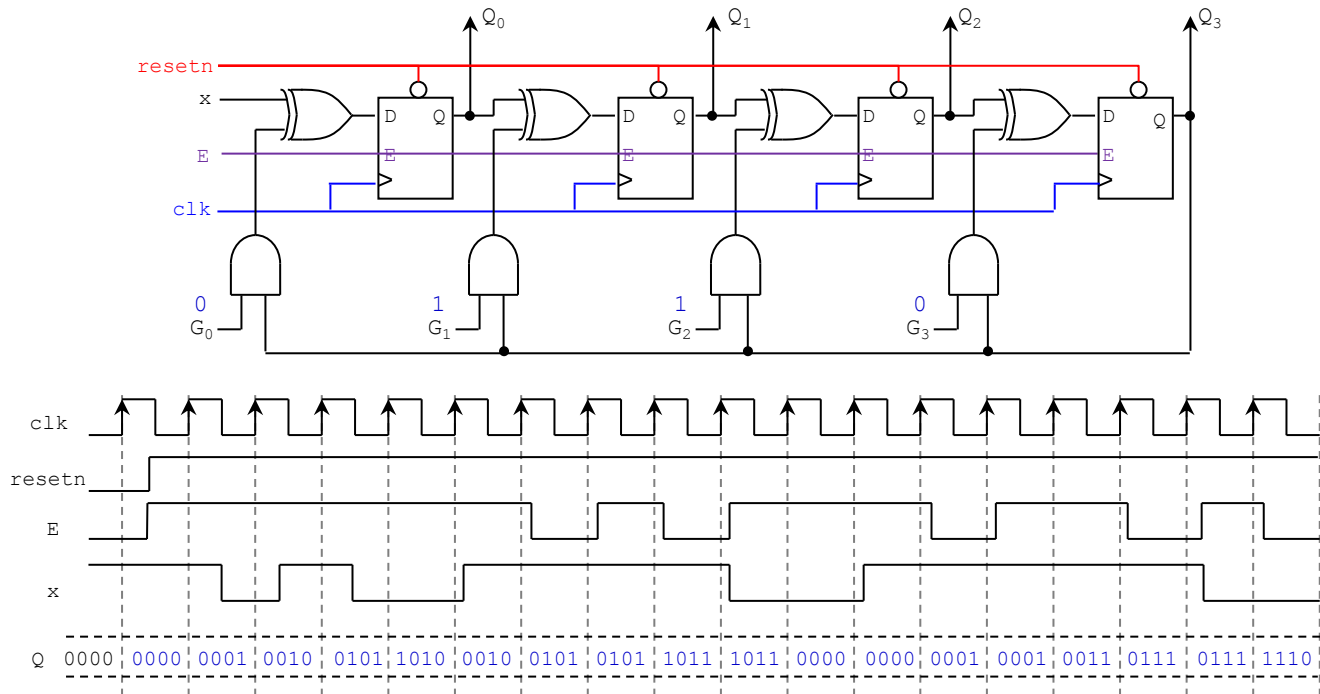
PROBLEM 1 (12 PTS)

- Complete the timing diagram of the following circuit. $G = G_3G_2G_1G_0 = 0110$, $Q = Q_3Q_2Q_1Q_0$




PROBLEM 2 (11 PTS)

- Given the following circuit, complete the timing diagram.
The LUT 6-to-6 implements the following function: $OLUT = |ILUT|$ (absolute value), where $ILUT$ is a 6-bit signed (2C) number, and $OLUT$ is a 6-bit unsigned number.
For example $ILUT = -29 = 10011_2 \rightarrow OLUT = |-29| = 29 (011101_2)$

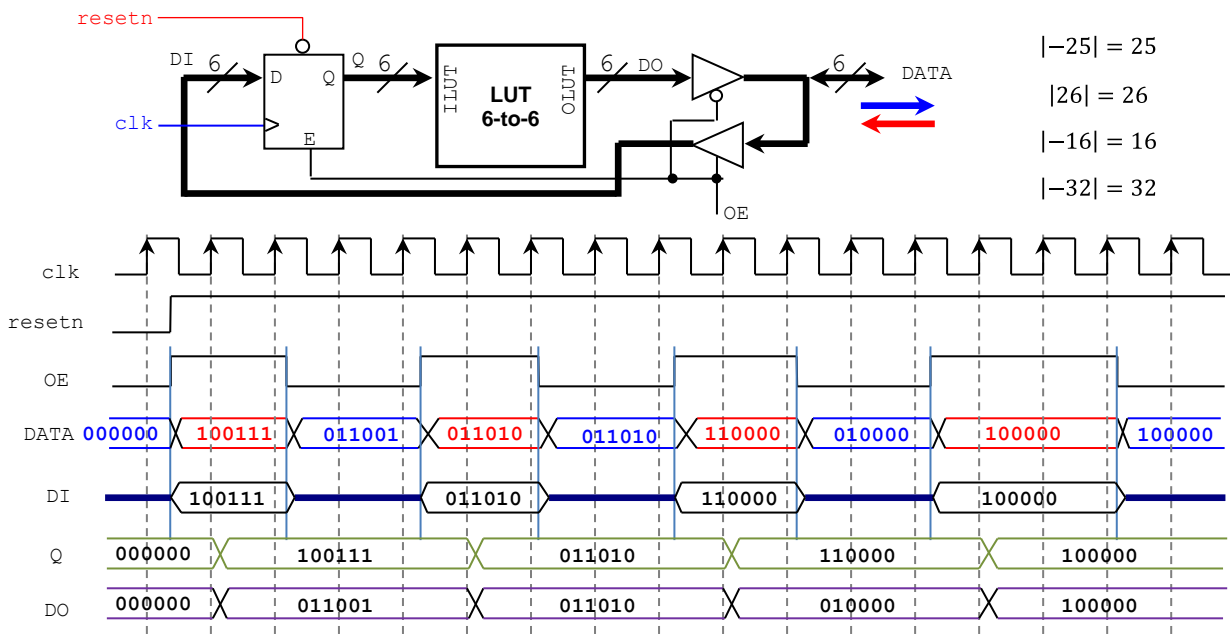

 
PROBLEM 3 (24 PTS)

- Sequence detector: The machine generates $z = 1$ when it detects the sequence 0100. Once the sequence is detected, the circuit looks for a new sequence.
- The signal E is an input enable: It validates the input x , i.e., if $E=1$, x is valid, otherwise x is not valid.



- Draw the State Diagram (any representation) of this circuit with inputs E and x and output z . (7 pts)
- Complete the State Table and the Excitation Table (8 pts.)
- Provide the excitation equations and the Boolean output equation (simplify your circuit: K-maps or Quine-McCluskey).
- Sketch the circuit. (3 pts)
- Which type is this FSM? ~~(Mealy)~~ (Moore) Why? _____

 - State Diagram, State Table, and Excitation Table:



		PRESENT STATE		NEXT STATE		PRESENT STATE		NEXT STATE			
		E	x	STATE	STATE	z	E	x	$Q_1Q_0(t)$	$Q_1Q_0(t+1)$	z
0	0	0	0	S0	S0	0	0	0	0	0	0
0	0	0	0	S1	S1	0	0	0	1	0	0
0	0	0	0	S2	S2	0	0	1	0	1	0
0	0	0	0	S3	S3	0	0	1	1	1	0
0	1	0	0	S0	S0	0	0	1	0	0	0
0	1	0	1	S1	S1	0	0	1	0	1	0
0	1	0	1	S2	S2	0	0	1	1	0	0
0	1	0	1	S3	S3	0	0	1	1	1	0
1	0	0	0	S0	S1	0	1	0	0	0	0
1	0	0	1	S1	S1	0	1	0	0	1	0
1	0	0	1	S2	S3	0	1	0	1	0	0
1	0	0	1	S3	S0	1	1	0	1	1	0
1	1	0	0	S0	S0	0	1	1	0	0	0
1	1	0	1	S1	S2	0	1	1	0	1	0
1	1	0	1	S2	S0	0	1	1	1	0	0
1	1	0	1	S3	S2	0	1	1	1	1	0

This is a Mealy Machine. The output z depends on the input as well as on the present state.


- Excitation equations, minimization, and circuit implementation:

$$Q_1(t+1) \leftarrow \bar{E}Q_1 + ExQ_0 + \bar{x}Q_1\bar{Q}_0$$

$$Q_0(t+1) \leftarrow \bar{E}Q_0 + E\bar{x}Q_1 + E\bar{x}Q_0$$

$$z = E\bar{x}Q_1Q_0$$


$Q_1(t+1)$		$Q_0(t+1)$	
Ex		Ex	
Q_1Q_0		Q_1Q_0	
00	0 0	00	0 0
01	0 0	01	1 1
11	1 1	11	1 1
10	1 1	10	0 1

 

PROBLEM 4 (22 PTS)

 a) Given the following State Machine Diagram: (11 pts)

- ✓ Provide the State Table and the Excitation Table (4 pts.)
- ✓ Get the excitation equations and the Boolean equation for z. (3 pts.)
Use S0 (Q=00), S1 (Q=01), S2 (Q=10), S3 (Q=11) to encode the states.
- ✓ Sketch the Finite State Machine circuit. (3 pts.)
- ✓ Which type is this FSM? ~~(Mealy)~~ (Moore)



PRESENT STATE				NEXT STATE			
x	STATE	NEXT STATE	z	x	Q ₁ Q ₀ (t)	Q ₁ Q ₀ (t+1)	z
0	S0	S2	0	0	0 0	1 0	0
0	S1	S0	0	0	0 1	0 0	0
0	S2	S1	1	0	1 0	0 1	1
0	S3	S0	1	0	1 1	0 0	1
1	S0	S1	0	1	0 0	0 1	0
1	S1	S3	0	1	0 1	1 1	0
1	S2	S3	0	1	1 0	1 1	0
1	S3	S2	1	1	1 1	1 0	1

$$Q_1(t+1) \leftarrow \overline{(Q_1 + Q_0)} \oplus x$$


$$Q_0(t+1) \leftarrow xQ_1 + Q_1Q_0$$

$$z = \bar{x}Q_1 + Q_1Q_0$$

State Assignment:

S0: Q=00 S1: Q=01

S2: Q=10 S3: Q=11

 

b) A synchronous circuit (with *resetn* and *clock*), is described by these excitation equations (E is a synchronous input): (11 pts.)


$$Q_1(t+1) \leftarrow Q_1(t) \cdot Q_0(t) + \bar{E} \cdot Q_1(t) + \overline{Q_1(t)} \cdot Q_0(t)$$

$$Q_0(t+1) \leftarrow E \cdot Q_0(t) + \bar{E} \cdot \overline{Q_0(t)}$$


- ✓ With flip flops and logic gates, sketch the circuit.

$$Q_1(t+1) \leftarrow Q_1(t) \oplus Q_0(t) + \bar{E} \cdot Q_1(t)$$
 
$$Q_0(t+1) \leftarrow \overline{E \oplus Q_0(t)}$$



 - ✓ Complete the timing diagram. $Q = Q_1Q_0$ (Tip: get the excitation table) (6 pts)




PROBLEM 5 (13 PTS)

- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. (7 pts.)

```
library ieee;
use ieee.std_logic_1164.all;

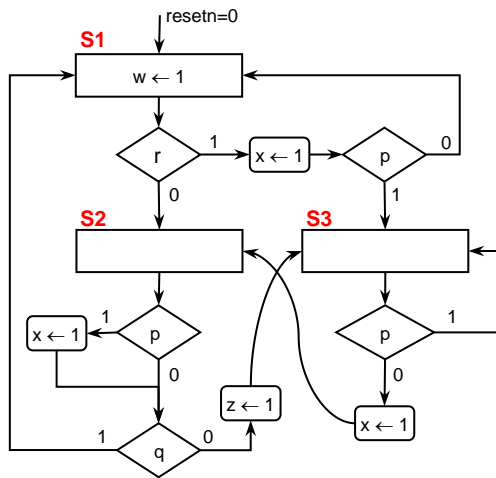
entity circ is
  port ( clk, resetn: in std_logic;
        r, p, q: in std_logic;
        x, w, z: out std_logic);
end circ;
```



```
architecture behavioral of circ is
  type state is (S1, S2, S3);
  signal y: state;
begin
  Transitions: process (resetn, clk, r, p, q)
  begin
    if resetn = '0' then y <= S1;
    elsif (clk'event and clk = '1') then
      case y is
        when S1 =>
          if r = '0' then
            y <= S2;
          else
            if p = '1' then y <= S3; else y <= S1; end if;
          end if;
        when S2 =>
          if q = '1' then y <= S1; else y <= S3; end if;
        when S3 =>
          if p = '1' then y <= S3; else y <= S2; end if;
      end case;
    end if;
  end process;

  Outputs: process (y, r, p, q)
  begin
    x <= '0'; w <= '0'; z <= '0';
    case y is
      when S1 => w <= '1';
        if r = '1' then x <= '1'; end if;
      when S2 => if p = '1' then x <= '1'; end if;
        if q = '0' then z <= '1'; end if;
      when S3 => if p = '0' then x <= '1'; end if;
    end case;
  end process;
end behavioral;
```

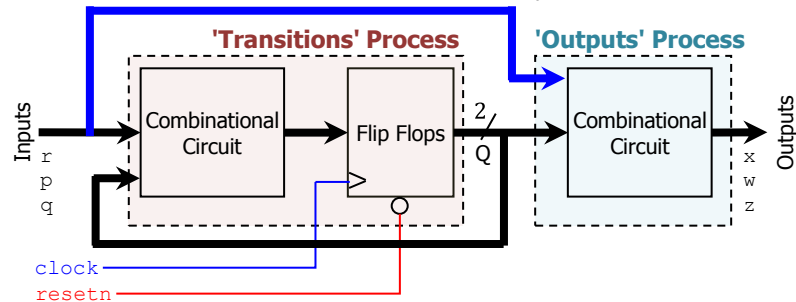- The figure shows an FSM model representing the circuit described in VHDL. The state (signal 'y' in the VHDL code) is represented by the bits Q_1 and Q_0 .



- ✓ If we use S1 ($Q=00$), S2 ($Q=01$), S3 ($Q=10$) to encode the states, what is the Boolean equation for w ? (2 pts.)

$$w = \overline{Q_1(t)} \cdot \overline{Q_0(t)}$$

- ✓ Circle the correct answer: (4 pts.)

- The 'Outputs' process outputs depend on clock and resetn?

TRUE ~~FALSE~~

- The relationship between $[r, p, q, \text{present state}]$ and $[\text{next state}]$ is described by:

~~Transitions Process~~ Outputs Process

- The relationship between $[r, p, q, \text{present state}]$ and $[\text{outputs } x, w, z]$ is described by:

Transitions Process ~~Outputs Process~~

- Is this a Mealy or a Moore FSM?

Moore ~~Mealy~~

PROBLEM 6 (18 PTS)

- Complete the timing diagram of the following digital circuit that includes an FSM (in ASM form) and a Datapath circuit.
- The behavior (on the clock tick) of the generic register is as follows:

4-bit register: If E=0, the output is kept

```

if E = 1 then
  if sclr = 1 then
    Q ← 0
  else
    Q ← D
  end if;
end if;
end if;
    
```

