


Solutions - Homework 3

(Due date: March 16th @ 5:30 pm)


Presentation and clarity are very important! Show your procedure!

PROBLEM 1 (11 PTS)

 a) Complete the timing diagram of the circuits shown below. (6 pts)




 b) Complete the timing diagram of the circuit shown below: (5 pts)




 PROBLEM 2 (17 PTS)

▪ Complete the timing diagram of the circuit shown below. Get the excitation equation for Q. (7 pts)



 ▪ Complete the timing diagram of the circuit shown below. Get the excitation equation for Q. (10 pts)



PROBLEM 3 (10 PTS)

a) Complete the timing diagram of the circuit whose VHDL description is shown below. Also, get the excitation equation for q .

```

library ieee;
use ieee.std_logic_1164.all;

entity circ is
port (clrn, clk, a, x: in std_logic;
      q: out std_logic);
end circ;

architecture a of circ is


    signal qt: std_logic;

begin
    process (clrn, clk, x, a)
    begin
        if clrn = '0' then
            qt <= '0';
        
```

```

        elsif (clk'event and clk = '1') then
            if x = '1' then
                qt <= a xor not (qt);
            end if;
        end if;
    end process;
    q <= qt;
end a;



```

 

$$q(t+1) \leftarrow \bar{x}q(t) + x(a \oplus q(t))$$

 
 
b) Complete the timing diagram and sketch the circuit (use a flip flop and logic gates) whose excitation equation is (4 pts):

$$Q(t+1) \leftarrow (x \oplus y) \oplus Q(t)$$



  
PROBLEM 4 (10 PTS)

Complete the timing diagram of the following 4-bit parallel access shift register with enable input. When $E=1$: If $s_1=0$ (shifting operation). If $s_1=1$ (parallel load) Note that $Q = Q_3Q_2Q_1Q_0$. $D = D_3D_2D_1D_0$



 
PROBLEM 5 (12 PTS)

- Given the following circuit, complete the timing diagram (signals *DO*, *DI*, *Q*, and *DATA*). The LUT 6-to-6 implements the following function: $OLUT = \lceil \sqrt{ILUT} \rceil$, where *ILUT* is an unsigned number.
Example: $ILUT = 47 (011111_2) \rightarrow OLUT = \lceil \sqrt{47} \rceil = 7 (000111_2)$



 PROBLEM 6 (22 PTS)

- For the following circuit, complete the timing diagram and get the excitation equations of the flip flop outputs. $R = R_3R_2R_1R_0$.
 $R_3(t+1) \leftarrow \bar{E}R_3(t) + E \cdot ((G_3(t)(R_3(t) \oplus m)) \oplus R_2(t))$
 $R_2(t+1) \leftarrow \bar{E}R_2(t) + E \cdot ((G_2(t)(R_3(t) \oplus m)) \oplus R_1(t))$
 $R_1(t+1) \leftarrow \bar{E}R_1(t) + E \cdot ((G_1(t)(R_3(t) \oplus m)) \oplus R_0(t))$
 $R_0(t+1) \leftarrow \bar{E}R_0(t) + E \cdot (G_0(t)(R_3(t) \oplus m))$
- Write the VHDL for the given circuit and simulate your circuit.
 - Write structural VHDL code. Create two files: i) flip flop, ii) top file (where you will interconnect the flip flops and the logic gates). (10 pts)
 - Write a VHDL testbench according to the timing diagram shown below (100 MHz clock with 50% duty cycle). Run the simulation (Behavioral Simulation). Verify the results: compare them with the manually completed timing diagram (8 pts)
- Upload (as a .zip file) the following files to Moodle (an assignment will be created):
 - VHDL code files and testbench.
 - A screenshot of your Vivado simulation results for (it should all the values for R).



✓ **VHDL Code: Top File**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity lfsr_crc2 is
    generic (N: INTEGER:= 4);
    port ( m_in, E: in std_logic;
          resetn, clock: in std_logic;
          G: in std_logic_vector (N-1 downto 0);
          R: out std_logic_vector (N-1 downto 0));
end lfsr_crc2;

architecture structural of lfsr_crc2 is

    component dffe
        port ( d : in  STD_LOGIC;
              clrn: in std_logic:= '1';
              prn: in std_logic:= '1';
              clk : in  STD_LOGIC;
              ena: in std_logic;
              q : out STD_LOGIC);
    end component;

    signal B, D, Q: std_logic_vector (N-1 downto 0);

begin

D(0) <= B(0);

g0: for i in 1 to N-1 generate
    D(i) <= B(i) xor Q(i-1);
end generate;

g1: for i in 0 to N-1 generate
    di: dffe port map (d => D(i), clrn => resetn, prn => '1', clk => clock, ena => E, q => Q(i));
    R(i) <= Q(i);
    B(i) <= G(i) and (Q(N-1) xor m_in);
end generate;

end structural;
```

✓ **VHDL Code: D-Type flip flop**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity dffe is
    port ( d : in  STD_LOGIC;
          clrn, prn, clk, ena: in std_logic;
          q : out  STD_LOGIC);
end dffe;

architecture behaviour of dffe is

begin
    process (clk, ena, prn, clrn)
    begin
        if clrn = '0' then q <= '0';
        elsif prn = '0' then q <= '1';
        elsif (clk'event and clk='1') then
            if ena = '1' then q <= d; end if;
        end if;
    end process;
end behaviour;
```

✓ VHDL Tesbench:

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_lfsr_crc2 IS
    generic (N: integer:= 4);
END tb_lfsr_crc2;

ARCHITECTURE behavior OF tb_lfsr_crc2 IS
    component lfsr_crc2
        port( m_in, E, resetn, clock : IN std_logic;
              G: in std_logic_vector (N-1 downto 0);
              R : OUT std_logic_vector(N-1 downto 0));
    end component;

    -- Inputs
    signal m_in, E : std_logic := '0';
    signal resetn, clock : std_logic := '0';
    signal G: std_logic_vector (N-1 downto 0);

    -- Outputs
    signal R : std_logic_vector(N-1 downto 0);


    constant T : time := 10 ns;    -- clock period definition

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: lfsr_crc2 PORT MAP (m_in => m_in, E => E, resetn => resetn, clock => clock, G => G, R => R);

    clock_process: process    -- Clock process definitions
    begin
        clock <= '0'; wait for T/2;
        clock <= '1'; wait for T/2;
    end process;



    stim_proc: process    -- Stimulus process
    begin
        resetn <= '0'; m_in <= '0'; G <= "0110"; wait for 100 ns;
        resetn <= '1';
        G <= "0110"; E <= '1'; m_in <= '1'; wait for 2*T;
        G <= "0110"; E <= '1'; m_in <= '0'; wait for 2*T;
        G <= "0110"; E <= '0'; m_in <= '1'; wait for 2*T;
        G <= "1101"; E <= '1'; m_in <= '0'; wait for T;
        G <= "1101"; E <= '0'; m_in <= '0'; wait for T;
        G <= "1101"; E <= '1'; m_in <= '1'; wait for T;
        G <= "1101"; E <= '1'; m_in <= '0'; wait for T;
        G <= "1101"; E <= '1'; m_in <= '1'; wait for 2*T;
        G <= "1101"; E <= '0'; m_in <= '1'; wait for T;
        G <= "1101"; E <= '1'; m_in <= '1'; wait for T;
        G <= "1011"; E <= '1'; m_in <= '1'; wait for T;
        G <= "1011"; E <= '1'; m_in <= '0'; wait for T;
        G <= "1011"; E <= '1'; m_in <= '1'; wait for 2*T;
        G <= "1011"; E <= '0'; m_in <= '0'; wait for T;
        wait;
    end process;
END;
```

END;

 

  PROBLEM 7 (8 PTS)

- Complete the timing diagram (output DO) of the following Random Memory Access (RAM) Emulator.
- RAM Emulator: It has 8 addresses, where each address holds a 4-bit data. The memory positions are implemented by 4-bit registers. The *resetn* and *clock* signals are shared by all the registers. Data is written or read onto/from one of the registers (selected by the signal address).
- Operations:
 - ✓ Writing onto memory (*wr_rd*=‘1’): The 4-bit input data (DI) is written into one of the 8 registers. The address signal selects which register is to be written.
 - For example: if address = “101”, then the value of DI is written into register 5.
 - Note that because the BusMUX 8-to-1 includes an enable input, if *wr_rd*=1, then the BusMUX outputs are 0’s.
 - ✓ Reading from memory (*wr_rd*=‘0’): The address signal selects the register from which data is read. This data appears on the BusMUX output.
 - For example: If address = “010”, then data from register 2 appears on BusMUX output.



PROBLEM 8 (10 PTS)

- Attach your Project Status Report (no more than 1 page, single-spaced, 2 columns, only one submission per group). This report should contain the initial status of your project. For formatting, use the provided template (Final Project - Report Template.docx). The sections included in the template are the ones required in your Final Report. At this stage, you are only required to:
 - ✓ Include a (draft) project description and title.
 - ✓ Include a draft Block Diagram of your hardware architecture.
- As a guideline, the figure shows a simple Block Diagram. There are input and output signals, as well as internal components along with their interconnection.
 - ✓ At this stage, only a rough draft is required. There is no need to go into details: it is enough to show the tentative top-level components that would constitute your system as well as the tentative inputs and outputs.
- Only student is needed to attach the report (make sure to indicate all the team members).

