 


Solutions - Quiz 4

(April 4th @ 5:30 pm)

PROBLEM 1 (35 PTS)

- The following FSM has 4 states, one input x and one output z .
 - The excitation equations are given by:
 - $Q_1(t+1) \leftarrow Q_0(t)$
 - $Q_0(t+1) \leftarrow \bar{x} \oplus Q_1(t)$
 - The output equation is given by: $z = \bar{x} \oplus Q_1(t) \oplus Q_0(t)$
- Provide the Excitation Table and the State Diagram (any representation).
- Which type is this FSM? Circle or mark the correct one: ~~(Mealy)~~ (Moore)




State Assignment: S0: Q=00, S1: Q=01, S2: Q=10, S3: Q=11

PRESENT STATE			NEXTSTATE		
x	Q ₁ Q ₀ (t)		Q ₁ Q ₀ (t+1)	z	
0	0	0	0	1	1
0	0	1	1	1	0
0	1	0	0	0	0
0	1	1	1	0	1
1	0	0	0	0	0
1	0	1	1	0	1
1	1	0	0	1	1
1	1	1	1	1	0



x	PRESENT STATE	NEXT STATE	z
0	S0	S1	1
0	S1	S3	0
0	S2	S0	0
0	S3	S2	1
1	S0	S0	0
1	S1	S2	1
1	S2	S1	1
1	S3	S3	0

 

PROBLEM 2 (35 PTS)

- Draw the state diagram (in ASM form) of the FSM whose VHDL description is listed below:

```


library ieee;
use ieee.std_logic_1164.all;

entity myfsm is
    port ( clk, rstn: in std_logic;
          a, b: in std_logic;
          x,w,z: out std_logic);
end myfsm;
    
```

```

architecture behavioral of myfsm is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (rstn, clk, a, b)
    begin
        if rstn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if b = '1' then y <= S2;
                    else if a = '1' then y <= S3; else y <= S1; end if;
                end if;
                when S2 =>
                    if a = '1' then y <= S1; else y <= S2; end if;
                when S3 =>
                    if b = '1' then y <= S3; else y <= S1; end if;
            end case;
        end if;
    end process;

     Outputs: process (y,a,b)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => if b = '0' then x <= '1'; end if;
            when S2 => z <= '1';
            when S3 => if a = '0' then w <= '1'; end if;
        end case;
    end process;
end behavioral;
    
```



- Circle or mark the correct FSM type: ~~(Mealy)~~ (Moore)

PROBLEM 3 (30 PTS)

- Sequence detector: Draw the state diagram (any representation) of an FSM with input x and output z . The detector asserts $z = 1$ when the sequence 11010 is detected. Right after the sequence is detected, the circuit looks for a new sequence.

