
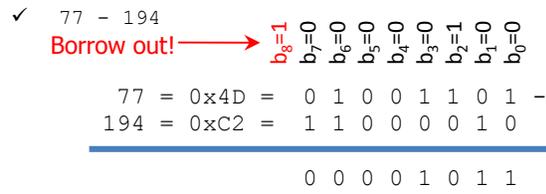


PROBLEM 3 (30 PTS)

a) Perform the following additions and subtractions of the following unsigned integers. Use the fewest number of bits n to represent both operators. Indicate every carry (or borrow) from c_0 to c_n (or b_0 to b_n). For the addition, determine whether there is an overflow. For the subtraction, determine whether we need to keep borrowing from a higher byte. (8 pts)

Example ($n=8$):

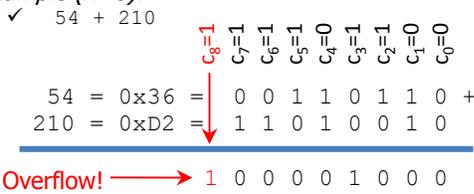

- ✓ $271 + 137$
- ✓ $111 + 75$

- ✓ $43 - 97$
- ✓ $128 - 43$

b) We need to perform the following operations, where numbers are represented in 2's complement: (16 pts)

- ✓ $-97 + 256$
- ✓ $413 + 617$
- ✓ $99 - 62$
- ✓ $-127 - 37$

- For each case:
 - ✓ Determine the minimum number of bits required to represent both summands. You might need to sign-extend one of the summands, since for proper summation, both summands must have the same number of bits.
 - ✓ Perform the binary addition in 2's complement arithmetic. The result must have the same number of bits as the summands.
 - ✓ Determine whether there is overflow by:
 - i. Using c_n, c_{n-1} (carries).
 - ii. Performing the operation in the decimal system and checking whether the result is within the allowed range for n bits, where n is the minimum number of bits for the summands.
 - ✓ If we want to avoid overflow, what is the minimum number of bits required to represent both the summands and the result?

c) Get the multiplication results of the following numbers that are represented in 2's complement arithmetic with 4 bits. (6 pts)

- ✓ $0100 \times 0101, 1000 \times 0110, 1001 \times 1001.$

PROBLEM 4 (15 PTS)

- In these problems, you can use full adders and logic gates. Make sure your circuit works for all cases. If there is overflow, design your circuit so that the final answer is always the correct one with the correct number of bits.
 - a) Given two 4-bit numbers provided in gray code, sketch the circuit that computes the summation of the unsigned decimal numbers these gray codes represent.
 - b) Given two 4-bit signed (2's complement) numbers A, B, sketch the circuit that computes $(A - B) \times 4$.

PROBLEM 5 (20 PTS)

- a) Implement the following functions using i) decoders (and OR gates) and ii) multiplexers: (5 pts)
 - ✓ $F = \bar{Y} + \bar{Z} + XY$
 - ✓ $F = \bar{X} \oplus Y \oplus \bar{Z}$
- b) Using only a 4-to-1 MUX, implement the following functions. (5 pts)
 - ✓ $F(X, Y, Z) = \sum(m_0, m_2, m_4, m_6)$
 - ✓ $F(X, Y, Z) = \prod(M_2, M_4, M_5, M_6)$
- c) Complete the timing diagram of the circuit shown below: (10 pts)

