 


Notes - Unit 7


INTRODUCTION TO DIGITAL SYSTEM DESIGN

DIGITAL SYSTEM MODEL

- FSM + Datapath Circuit:



EXAMPLE: CAR LOT COUNTER

 

If A = 1 → No light received (car obstructing LED A)
If B = 1 → No light received (car obstructing LED B)


If car enters the lot, the following sequence (A|B) must be followed:
00 → 10 → 11 → 01 → 00

If car leaves the lot, the following sequence (A|B) must be followed:
00 → 01 → 11 → 10 → 00


A car might stay in a state for many cycles since the car speed is very large compared to that of the clock frequency.

DIGITAL SYSTEM (FSM + Datapath circuit)

 
- Usually, when 'resetrn' (asynchronous clear) and 'clock' are not drawn, they are implied.



▪ Finite State Machine (FSM):

 


▪ Algorithmic State Machine (ASM) chart:

 

 EXAMPLE: ACCUMULATOR


DIGITAL SYSTEM (FSM + Datapath circuit)

- sclr: Synchronous clear. If $E = '1'$ and $sclr = '1'$, then the output bits of the registers are set to zero.




Finite State Machine (FSM):

$E | \text{restart} / Ei | sclr$

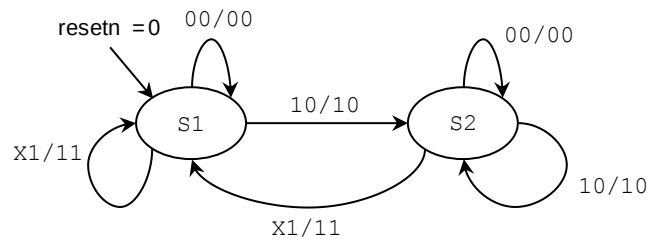


Algorithmic State Machine (ASM):

 

 
EXAMPLE: 7-SEGMENT SERIALIZER

DIGITAL SYSTEM (FSM + Datapath circuit)

- Most FPGA Development board have a number of 7-segment displays (e.g., 4, 8). However, only one can be used at a time.
- If we want to display four digits (inputs A, B, C, D), we can design a serializer that will only show one digit at a time on the 7-segment displays.
- Since only one 7-segment display can be used at a time, we need to serialize the four BCD outputs. In order for each digit to appear bright and continuously illuminated, each digit is illuminated for 1 ms every 4 ms (i.e. a digit is un-illuminated for 3 ms and illuminated for 1 ms). This is taken care of by feeding the output 'z' of the counter to 0.001 s to the enable input of the FSM. This way, state transitions only occur each 0.001 s.
- In the figure, the enable signals for the four 7-segment displays are active low (this is usually the case).



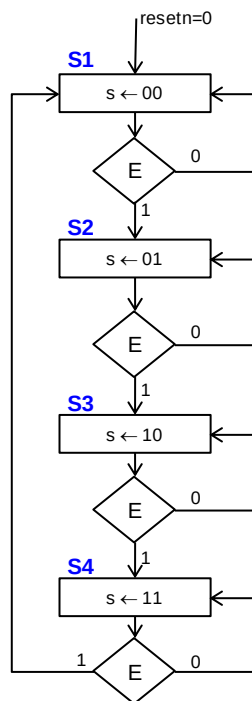- Algorithmic State Machine (ASM) chart:** This is a Moore-type FSM.



EXAMPLE: BIT-COUNTING CIRCUIT


SEQUENTIAL ALGORITHM

```


C ← 0
while A ≠ 0
  if a0 = 1 then
    C ← C + 1
  end if
  right shift A
end while
    
```

DIGITAL SYSTEM (FSM + Datapath circuit)

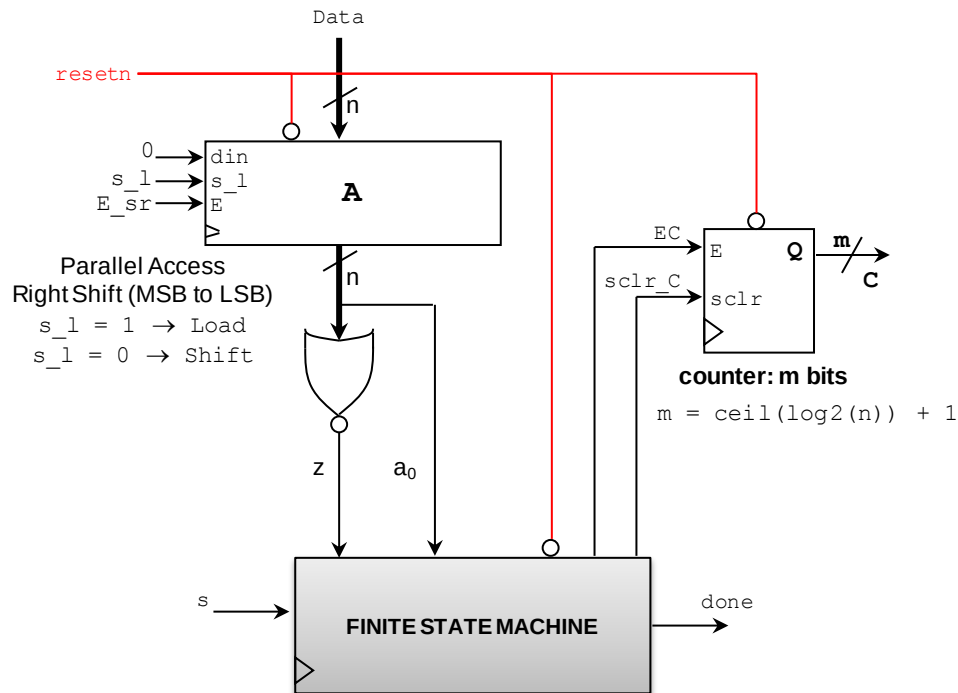
- sclr: Synchronous clear. In this case, if sclr = '1', the count is initialized to zero (here, we do not need EC to be 1).



Algorithmic State Machine (ASM) chart:

 


▪ **Algorithmic State Machine (ASM):**

 

 
EXAMPLE: ARBITER CIRCUIT

DIGITAL SYSTEM (FSM + Datapath circuit)

- Three devices can request access to a certain resource at any time (example: access to a bus made of tri-state buffers, only one tri-state buffer can be enabled at a time). The FSM can only grant access to one device at a time. There should be a priority level among devices.
- If the FSM grants access to one device, one must wait until the request signal to that device is deasserted (i.e. set to zero) before granting access to a different device.




Algorithmic State Machine (ASM) chart:

 


 EXAMPLE: DISPLAYING PATTERNS ON 7-SEGMENT DISPLAYS


- Different patterns are shown based on the selector 'sel' signal. Two 7-segment displays are used.
- 'stop' input: If it is asserted (stop = 1), the lights' pattern freezes.
- The input 'x' selects the rate of change (every 1.5, 1.0, 0.5, or 0.25 seconds).




DIGITAL SYSTEM (FSM + Datapath circuit)

 

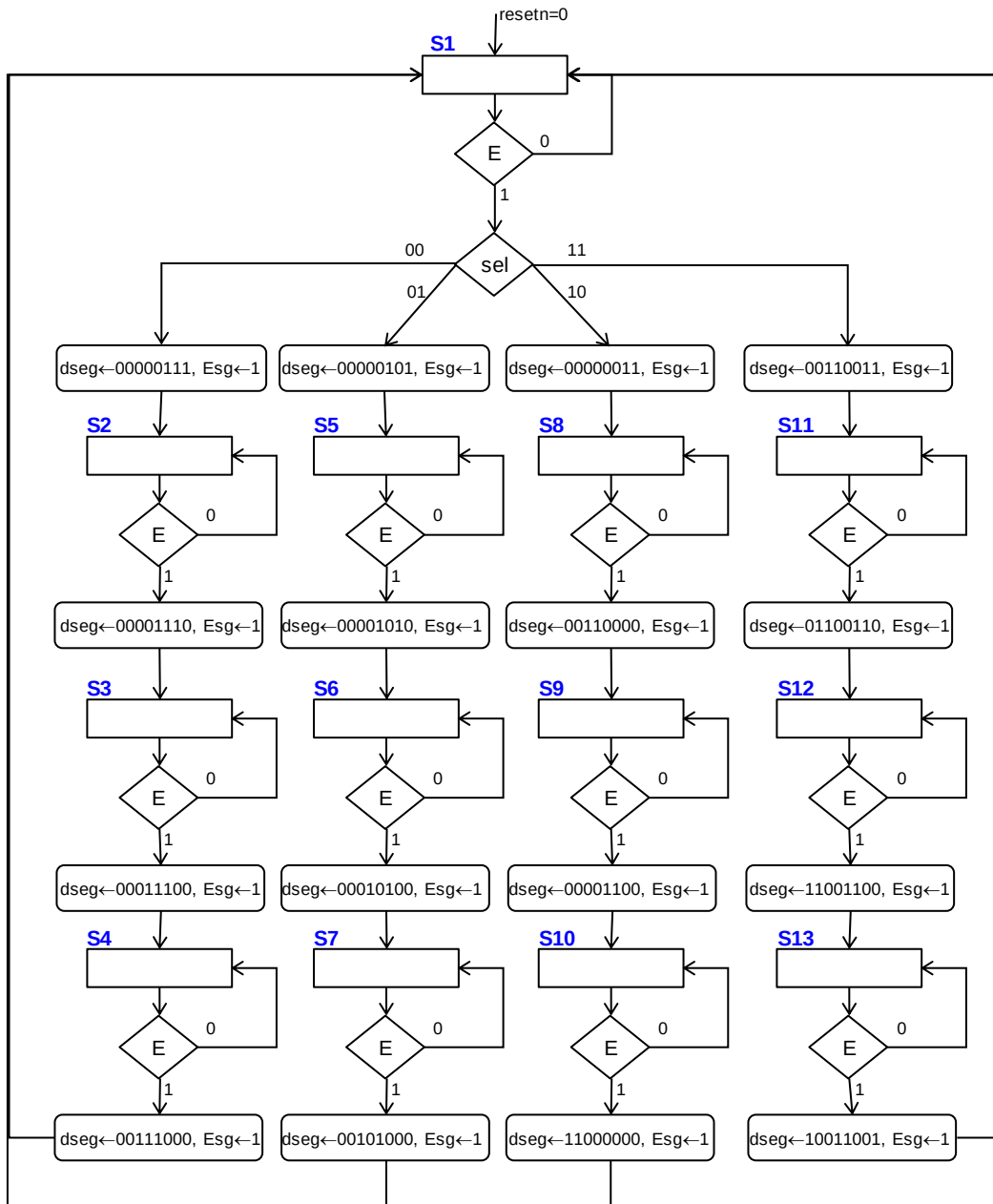▪ **Algorithmic State Machine (ASM) chart:**



 ▪ **Algorithmic State Machine (ASM) chart:** This is the FSM that controls the output MUX



EXAMPLE: SERIAL MULTIPLIER


SEQUENTIAL ALGORITHM

```

P ← 0, Load A,B
while B ≠ 0
  if b0 = 1 then
    P ← P + A
  end if
  left shift A
  right shift B
end while
    
```

DIGITAL SYSTEM (FSM + Datapath circuit)

 - Note that this algorithm can also be run on a simple processor. Here, we use dedicated circuitry.
sclr: Synchronous clear. In this case, if sclr = '1' and E = '1', the register contents are initialized to 0.



Algorithmic State Machine (ASM) chart:

