

Solutions - Quiz 2

(February 10th @ 5:30 pm)

PROBLEM 1 (30 PTS)

- Complete the following table. Use the fewest number of bits in each case:

Decimal	REPRESENTATION		
	Sign-and-magnitude	1's complement	2's complement
-30	111110	100001	100010
-16	110000	101111	10000
-17	110001	101110	101111
-9	11001	10110	10111

- Convert the following decimal number to its 2's complement representation: -30.375

$$30.375 = 011110.011_2 \rightarrow -30.375 = 100001.101_2$$

PROBLEM 2 (30 PTS)


- Implement the following function using ONLY 2-to-1 MUXs:

$$f(x, y, z) = xy + yz + xz$$

$$f(x, y, z) = \bar{x}f(0, y, z) + xf(1, y, z) = \bar{x}(yz) + x(y + yz + z) = \bar{x}g(y, z) + xh(y, z)$$

$$g(y, z) = \bar{y}g(0, z) + yg(1, z) = \bar{y}(0) + y(z)$$
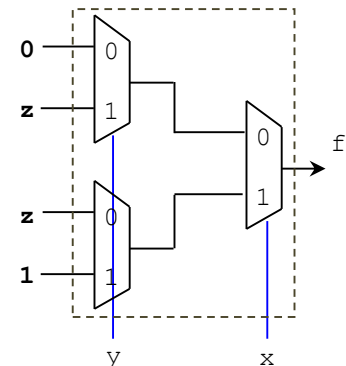
$$h(y, z) = \bar{y}h(0, z) + yh(1, z) = \bar{y}(z) + y(1)$$



PROBLEM 3 (40 PTS)

- Complete the timing diagram of the circuit shown below:

