


Solutions - Homework 3

(Due date: March 22nd @ 7:30 pm)


Presentation and clarity are very important! Show your procedure!

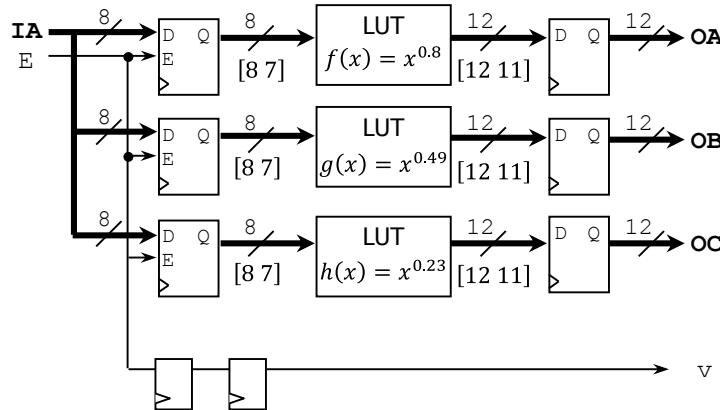PROBLEM 1 (75 PTS)

- Implement the following circuit using the LUT approach.
 - ✓ Input format: [8 7] (unsigned)
 - ✓ Output format: [12 11] (unsigned)



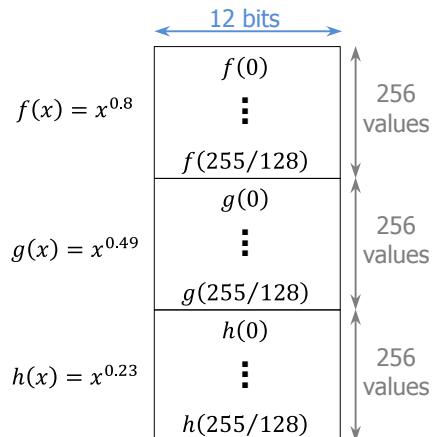- Pre-compute the LUT values and store them as binary numbers in a text file. Your VHDL code should read the text file.
- The text file should be divided as follows: the first 256 entries for the first function, the second 256 entries for the second function, and the third 256 entries for the third function:




SIMULATION

- Create a testbench to test your circuit. The testbench must generate all the possible input cases (from 00000000 to 11111111) and write the output results in a text file. For simplicity's sake, it is suggested that you write three 12-bit words per line (256 lines), where each 12-bit word represents the output of a different function.
- To verify the correct operation of your circuit, compare the text file you are generating on the Simulation with the input text file you created for Synthesis.
- Upload the following files to Moodle (an assignment will be created):
 - ✓ VHDL code
 - ✓ VHDL testbench
 - ✓ Input and output text files.

See attached .zip file: SolutionsHW3_p1.zip.

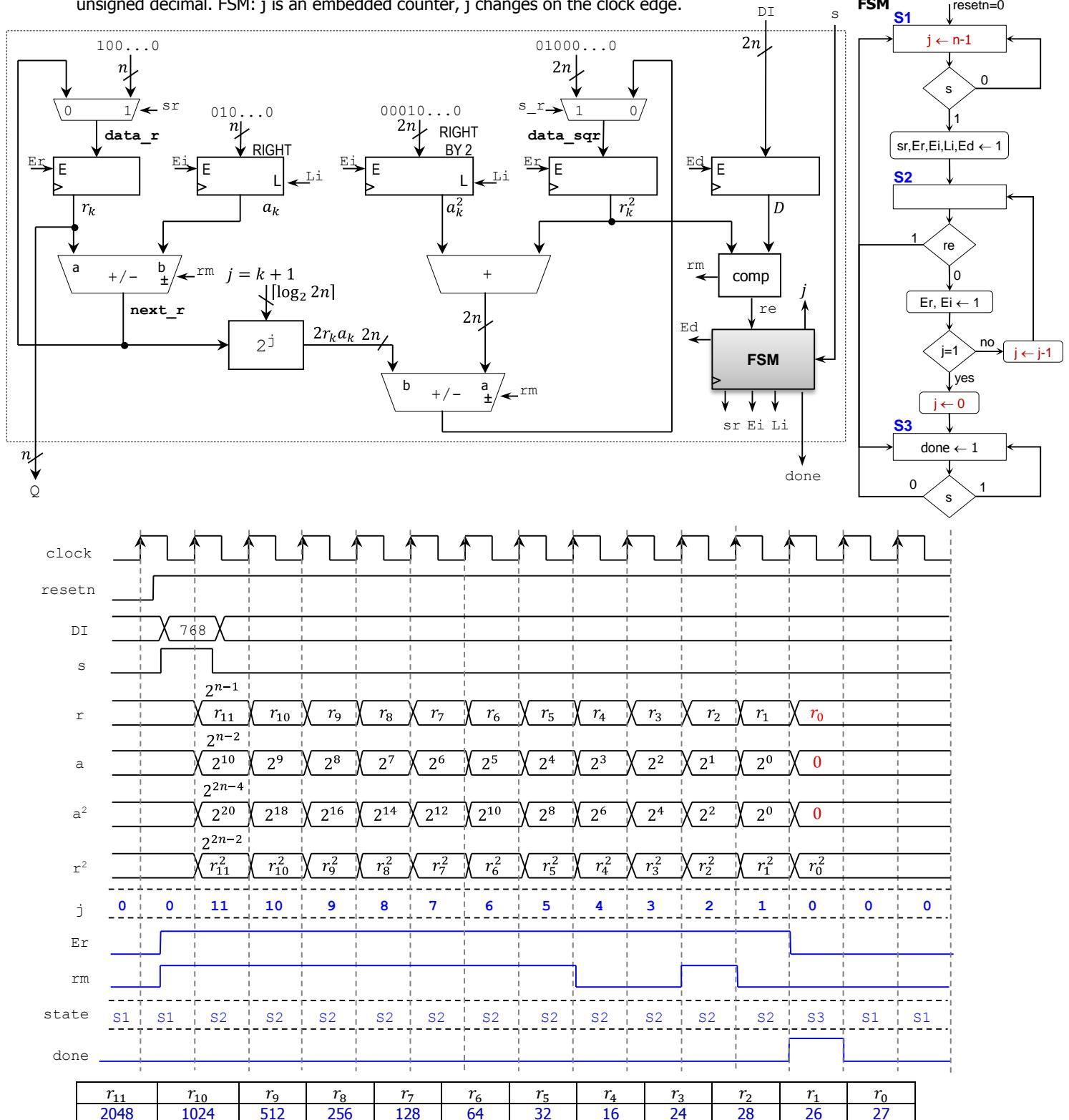PROBLEM 2 (15 PTS)

- Complete the timing diagram of the following circuit, which computes integer square root using a binary search approach. $n = 12$. Note that $rm = 1$ if $r_k^2 > D$, else 0, $re = 1$ if $r_k^2 = D$, else 0. Shift registers: serial input is '0'. The value of D is an unsigned decimal. FSM: j is an embedded counter, j changes on the clock edge.



PROBLEM 3 (10 PTS)

- Attach a printout of your Initial Project Report (no more than a page). This report should contain the project title, a brief project description, and the current status of the project. Use the provided template (Final Project - Report Template.docx).