

**- ECE 3710 -  
SIGNED FIXED POINT  
CALCULATOR**

**Joshua Boczar**

**Alexander Ivanovic**

**Andrew Korte**

**Benley Mathew**


# INTRODUCTION

- This calculator will take in a 12-bit, sign and magnitude binary number [12 4], convert it to signed fixed point for the arithmetic operations and provide the user with a signed decimal output.
- Topics in this project include...
  - Calculating signed fixed-point binary
  - Being able to create, simulate, and port map multiple components into VHDL
  - Being able to troubleshoot and see multiple components in timing diagrams for errors.

# MAIN COMPONENTS


- **Input Interface**
- **Adder/Subtractor**
- **Multiplier**
- **Divider**
- **Bin-to-BCD Converter**
- **2's Complement Converter**
- **Operation Select FSM**
- **Seven Segment Display Controller**

# TOP FILE BLOCK DIAGRAM

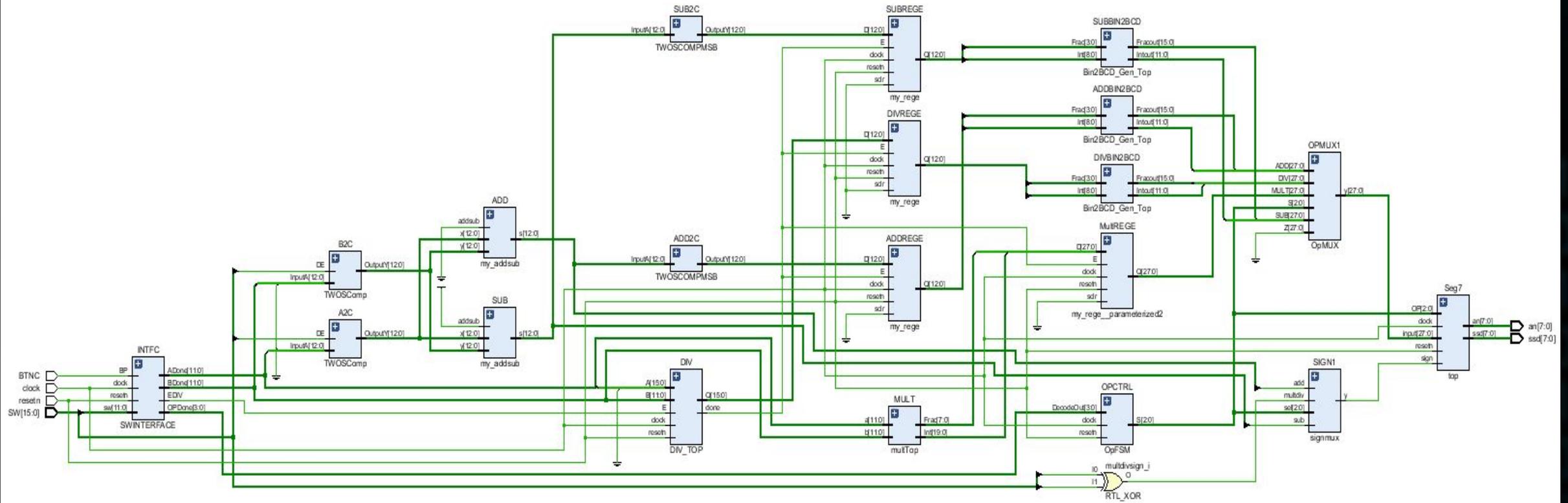
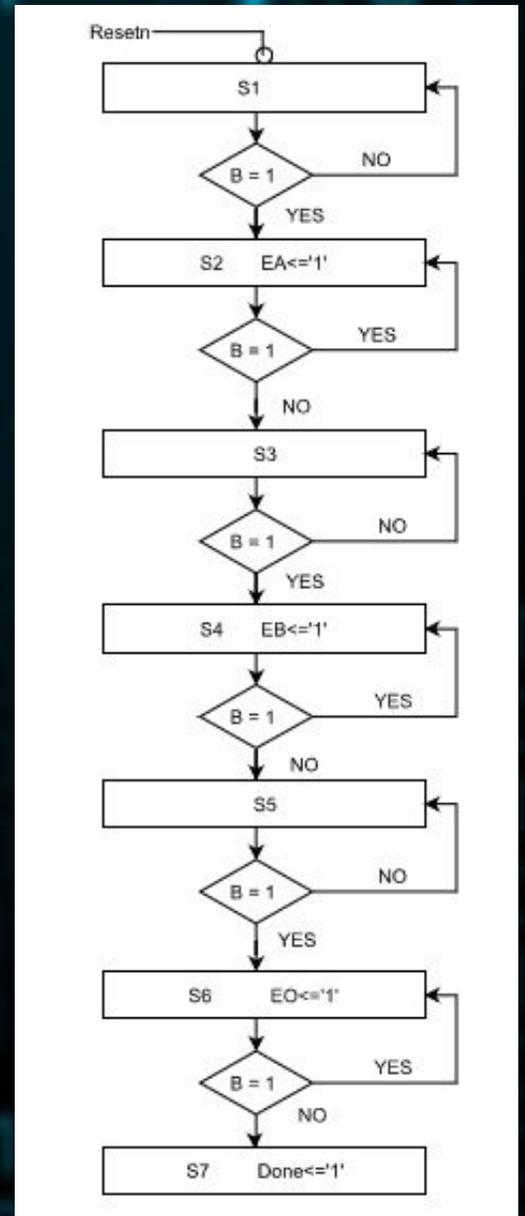
# INPUT INTERFACE

- Switches 14 and 15 used for sign
- Switches 11 through 0 used for inputs A and B
- Switches 3 through 0 used for operation
- Center button used for loading data
- Inputs A, B, and operation all have their own register enabled by the state machine.



# OPERATIONS


- **Addition / Subtraction : 13 bits, 9 integer and 4 fractional**
- **Multiplication: 12 bit input, 8 integer and 4 fractional. Special Bin-to-BCD**
- **Division: The iterative divider method was used, and an extra 4 bits were added to the LSB of the numerator for extra precision.**

# BIN TO BCD

- The method used for the converters is called double-dabble.
- For the fractional numbers you multiply the binary number by 10 and grab the top 4 bits.
- These numbers will all be in BCD form.
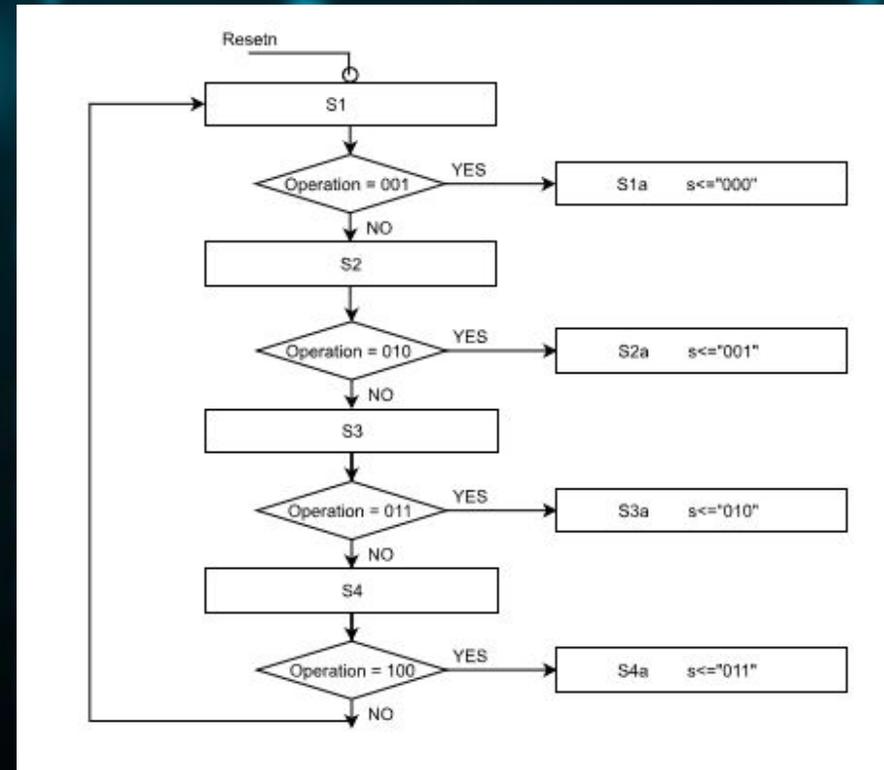
# OPERATION SELECT FSM

- Responsible for controlling the select line to the MUX that feeds data to the seven segment display. The input to the FSM is the output to the operation register.




# SEVEN SEGMENT DISPLAY CONTROLLER

- Separate decoder hooked up to output of Bin-to-BCD component split into groups of 4
- Outputs of decoders hooked up to a display control
  - Controls when group of segments turns on
- Decimal point is controlled by concatenating a bit to the MSB of the normal 6 down to 0 signal
  - Makes the signal 7 down to 0, or 8 bits
  - Because decimal point changes places based on operation, an if statement is used to turn on the 5th displays decimal point or the 3rd display's
- Modified decoder was made for the sign display
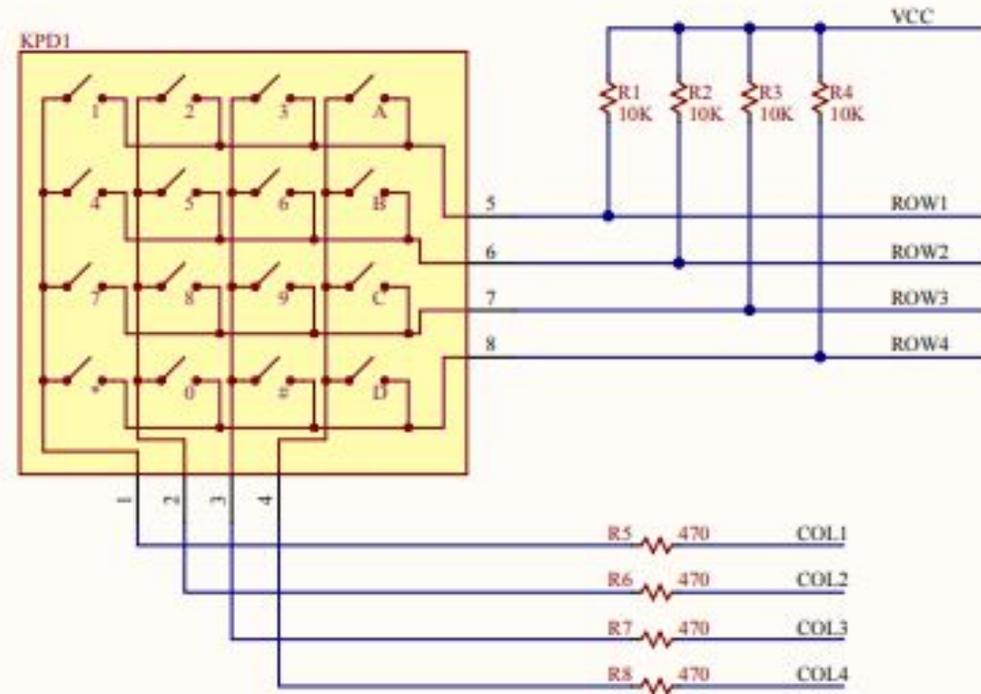
# ADDITIONAL IDEAS

- Keypad Interface
- Have the inputs appear as they are entered





**THANKYOU!**

**Any Questions?**

# DEMO

1.  $30.0625 + 50.375 = 80.4375$
2.  $-1.4375 - 10.6875 = -12.125$
3.  $-127.5 * -100.5625 = 12821.7188$
4.  $-28.9375 / 15.875 = -1.8228$