
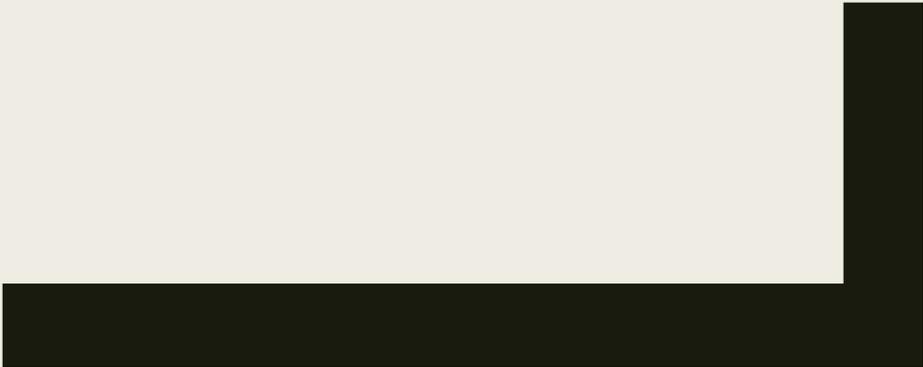



CONNECT FOUR

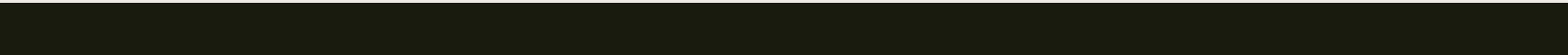

By: Fabrisio Ballo, David Herweyer, and Ryan Thomas



Goals

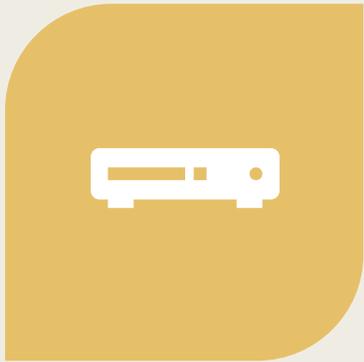

CREATE A WORKING CONNECT
FOUR GAME BOARD USING VGA



DISPLAY WINNER & TOTAL
NUMBER OF WINS



IMPLEMENT GAME WITH
CONTROLLER


How To Play!


Turn Based Game


Choose where you want to Drop your Game Piece

First Person to get at Least Four in a Row Wins!

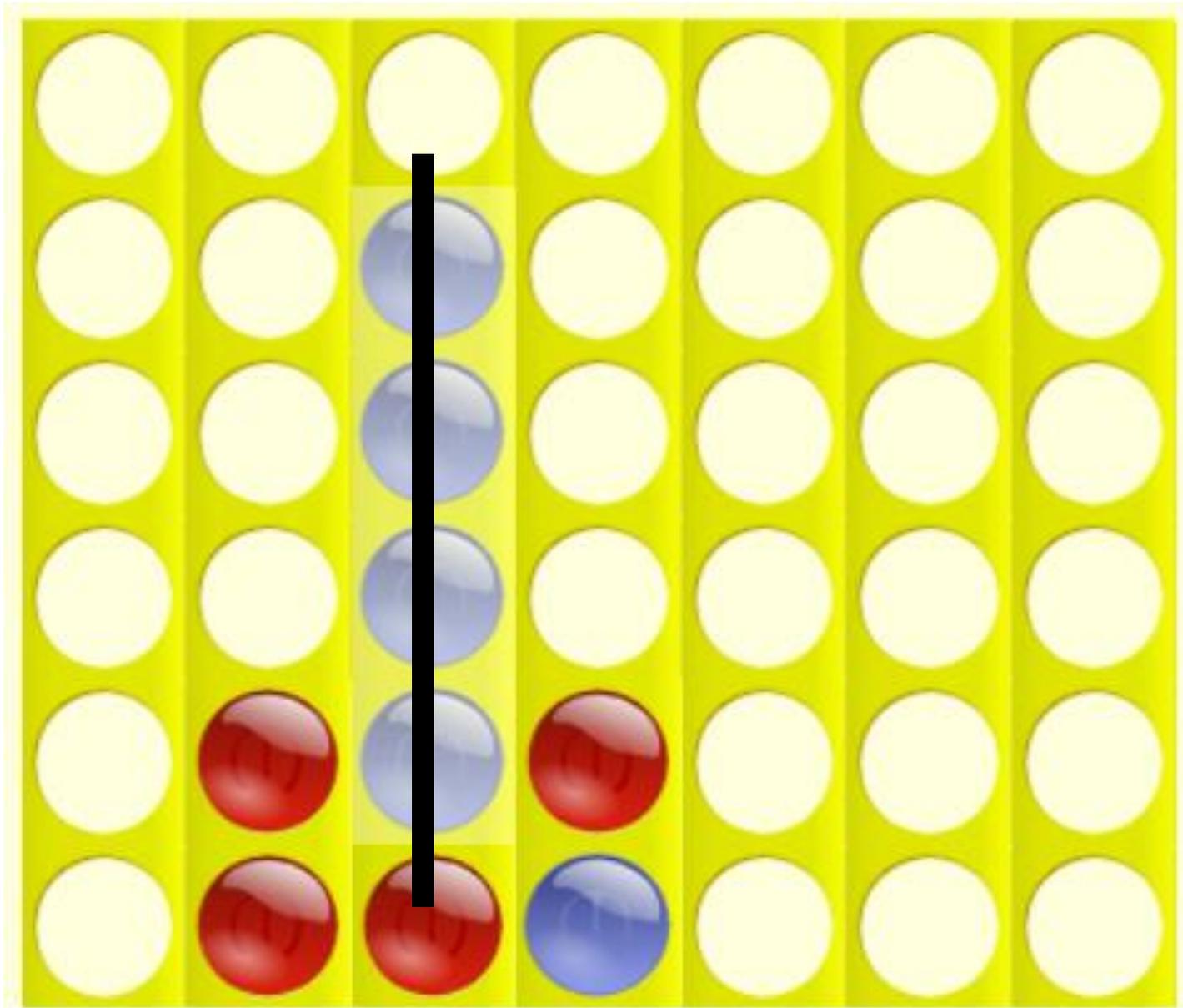
If the Board Fills up Before Anyone Wins, this Results in a Tie



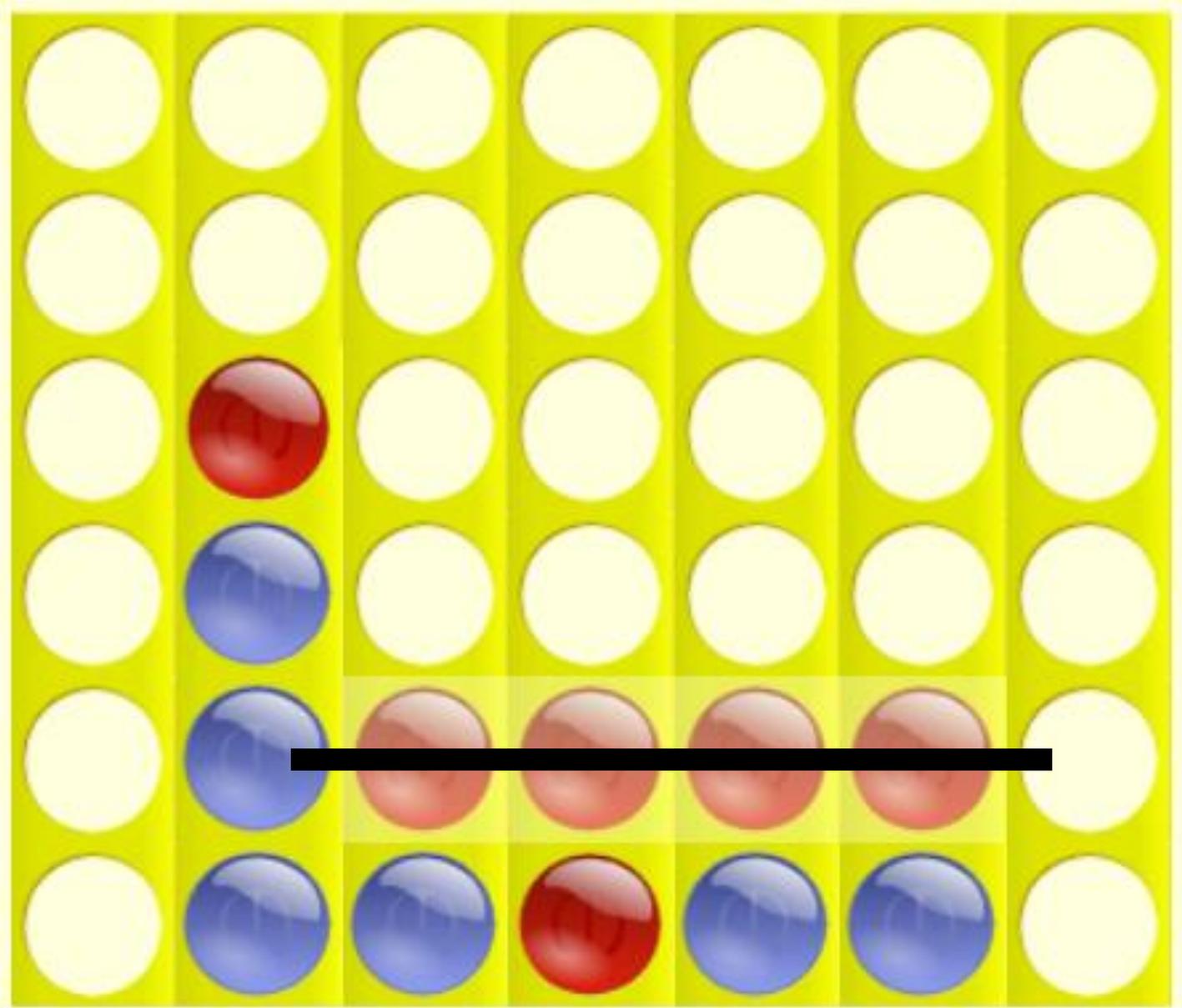


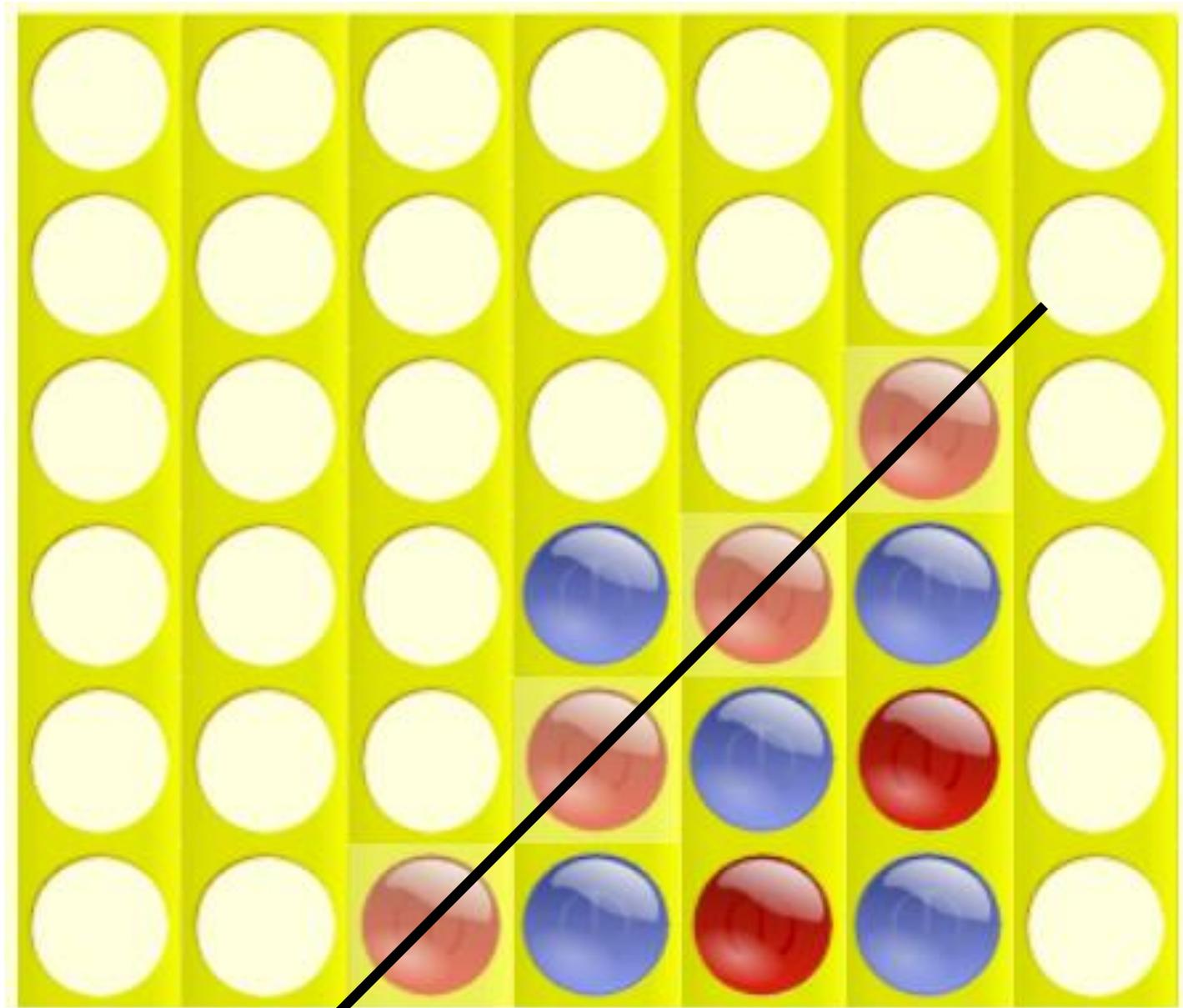


BLOCK DIAGRAM

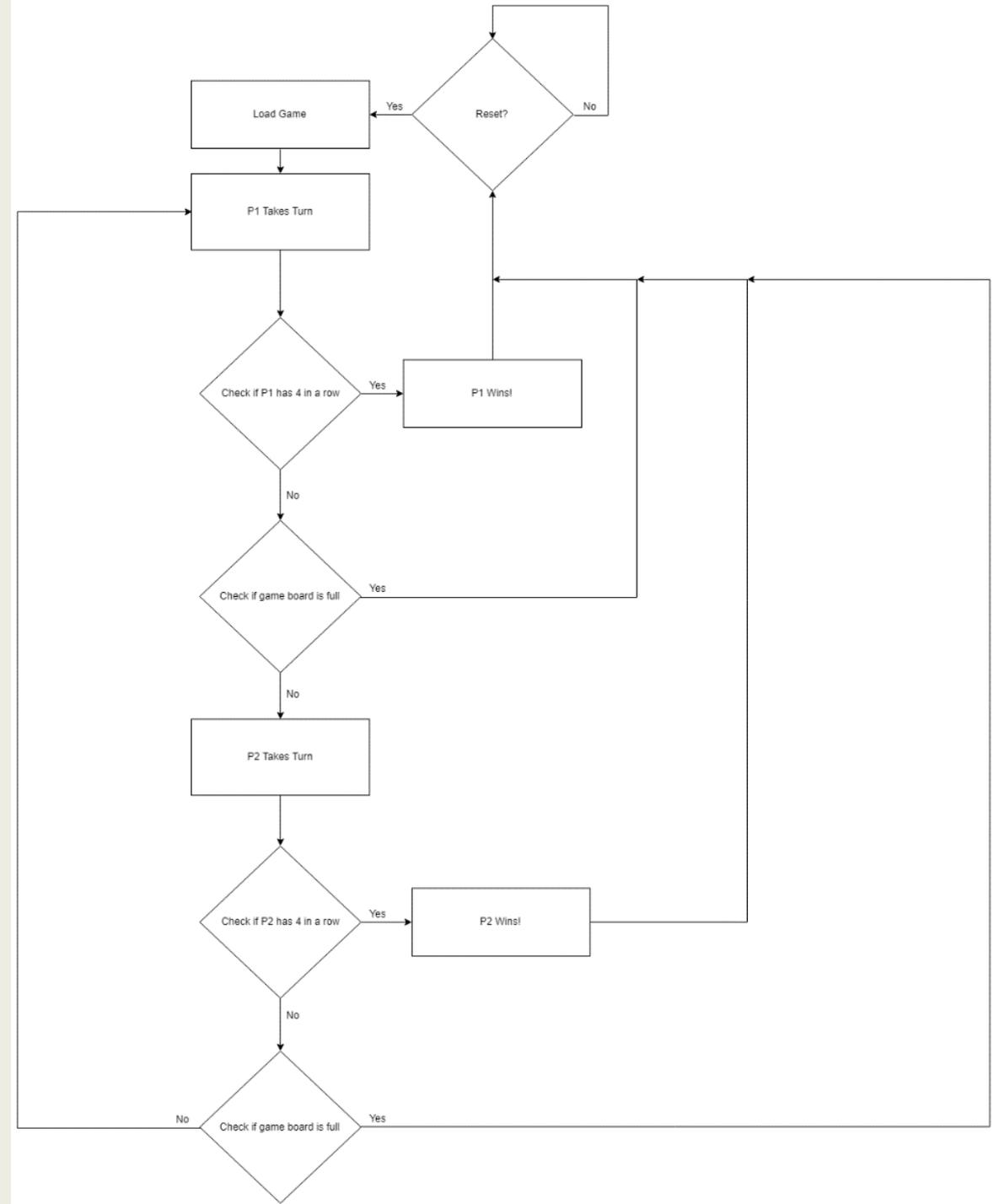



FSM

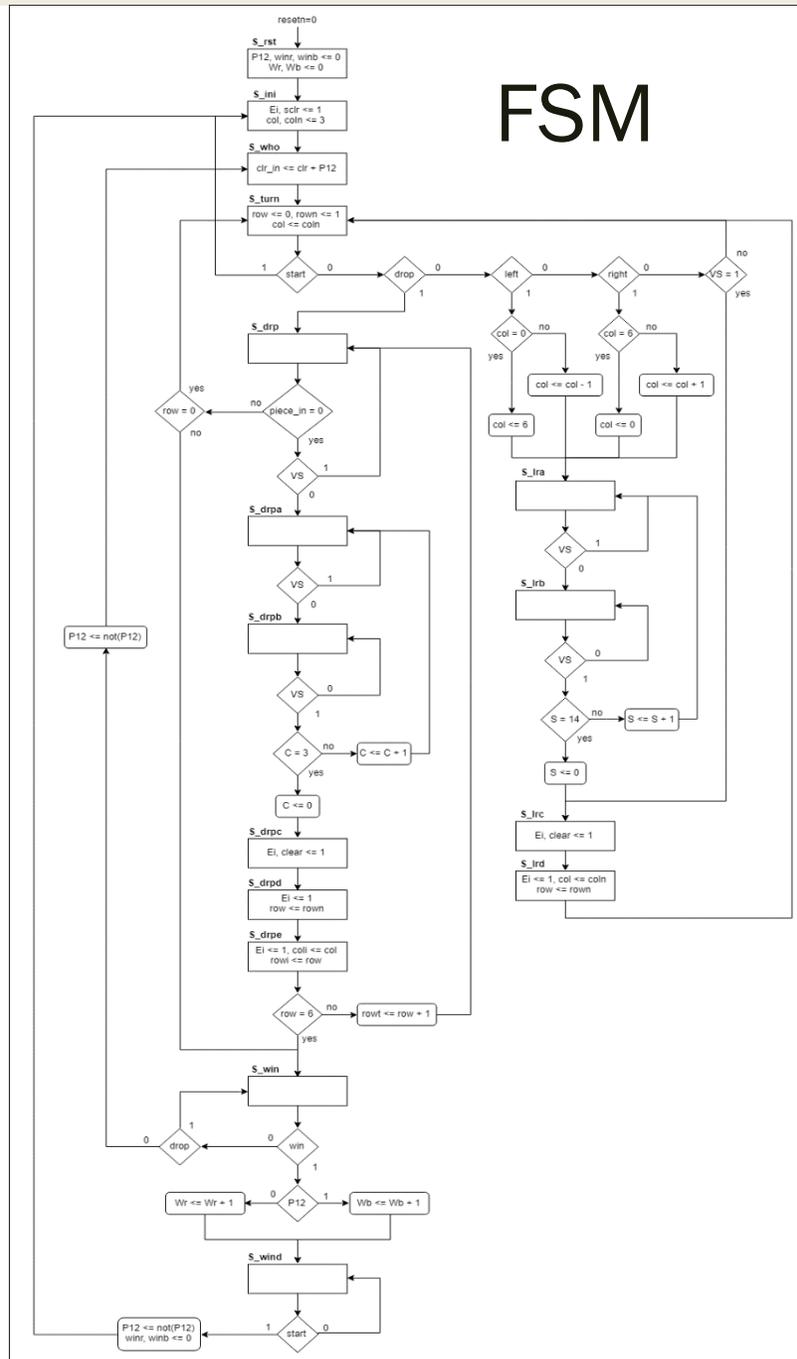


Connect4 Game

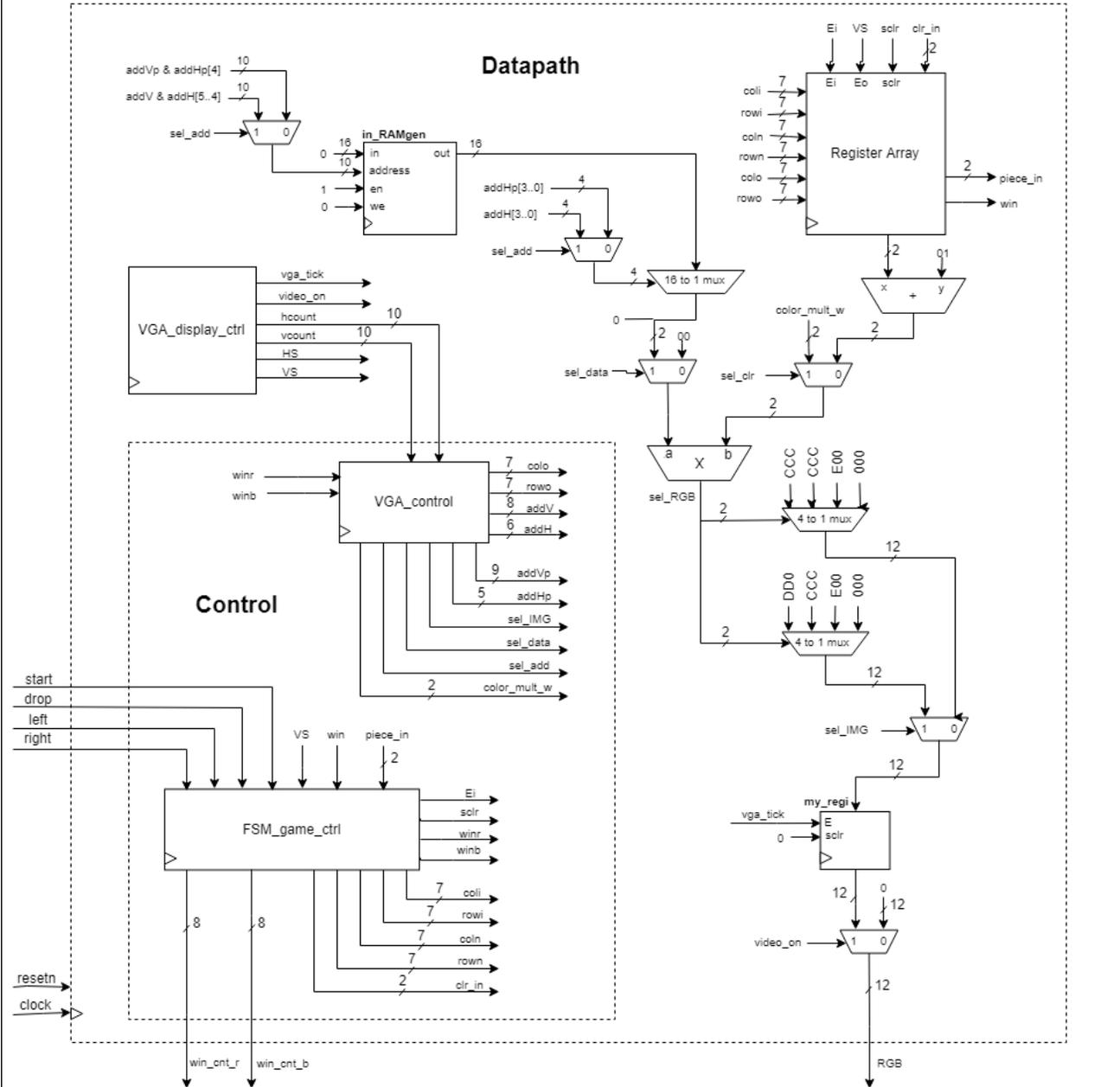


NES Controller

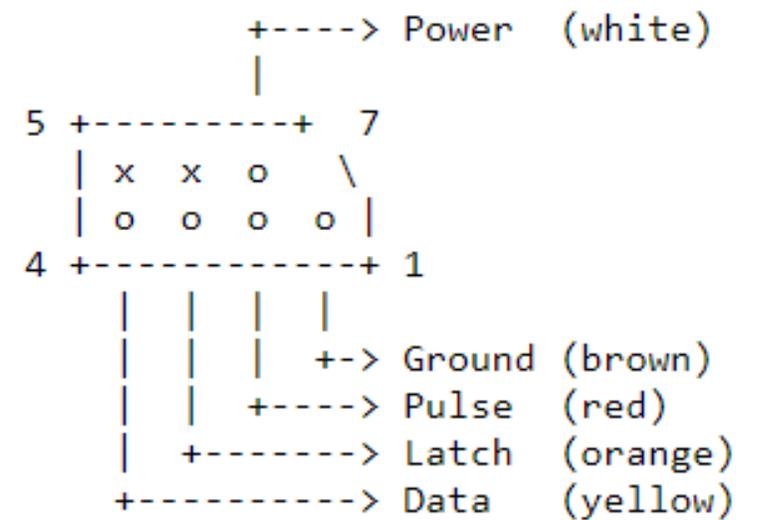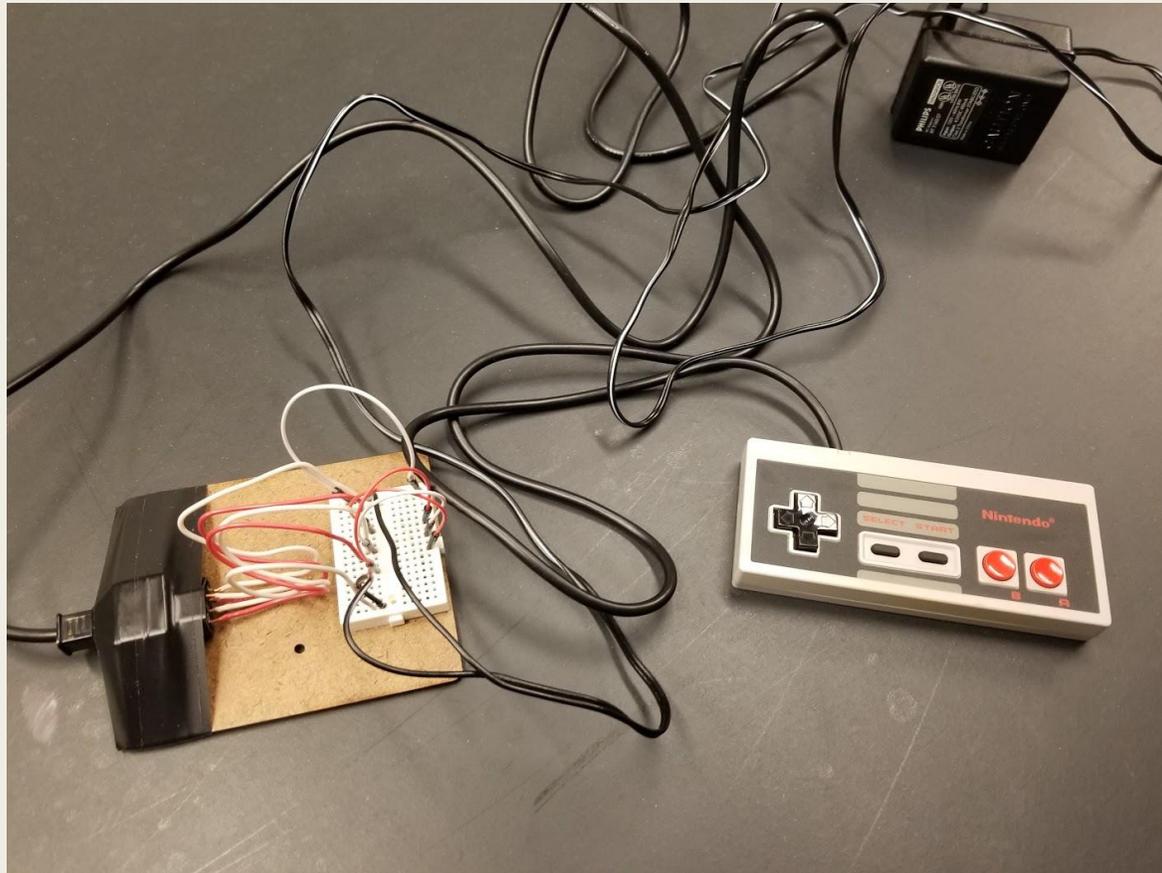

NES Controller - Timing Diagram

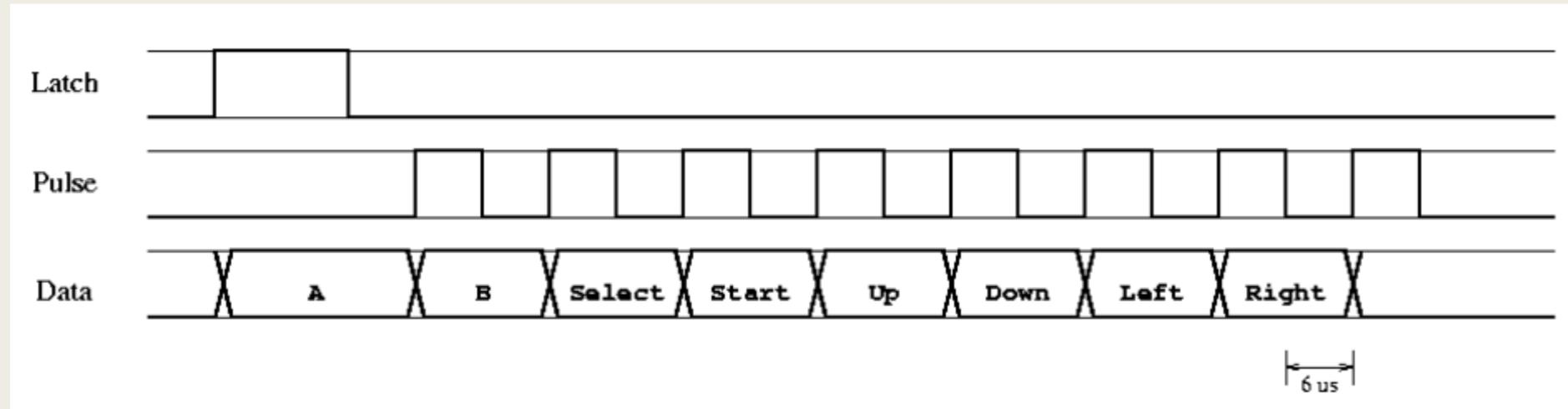

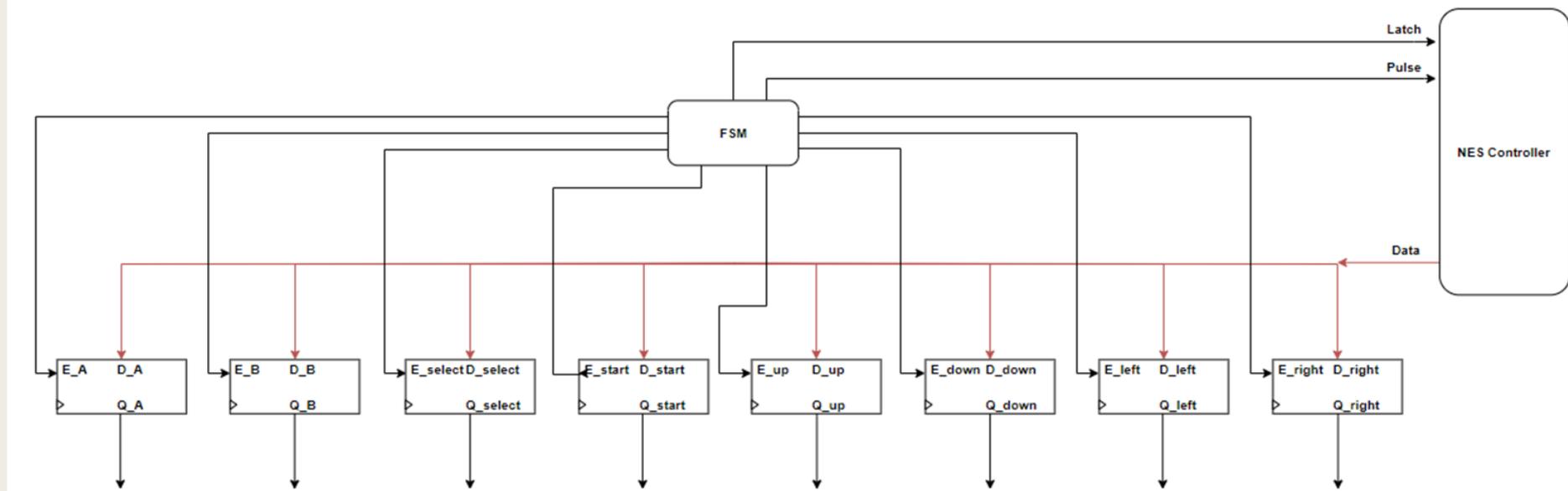- Latch freezes state of the buttons on the controller
- Data is shifted out of the controller 1 bit at a time with 8 pulses



NES CONTROLLER - DATAPATH

Registers to hold button press inputs

NES Controller


- Control

- State Machine with embedded “my_genpulse_sclr” Counters

- 60hz Counter
 - *COUNT = 1666666*

- 12us Counter
 - *COUNT = 1200*

- 6us Counter
 - *COUNT = 600*

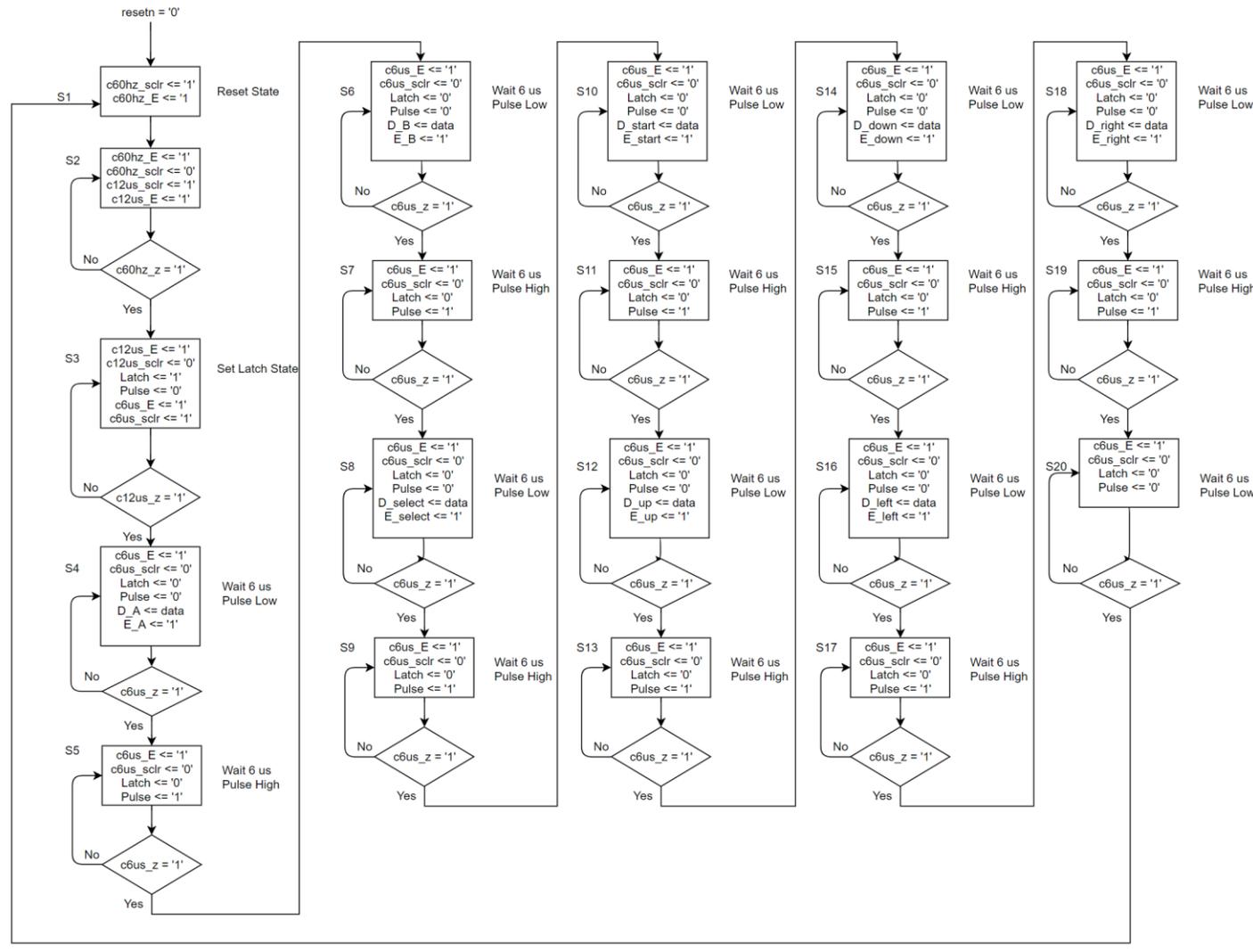

Future Improvements



INCLUDING SOUND EFFECTS



ADD MORE GAMES



IMPLEMENT A SECOND
CONTROLLER



THE END



QUESTIONS?

Please Ask Us!