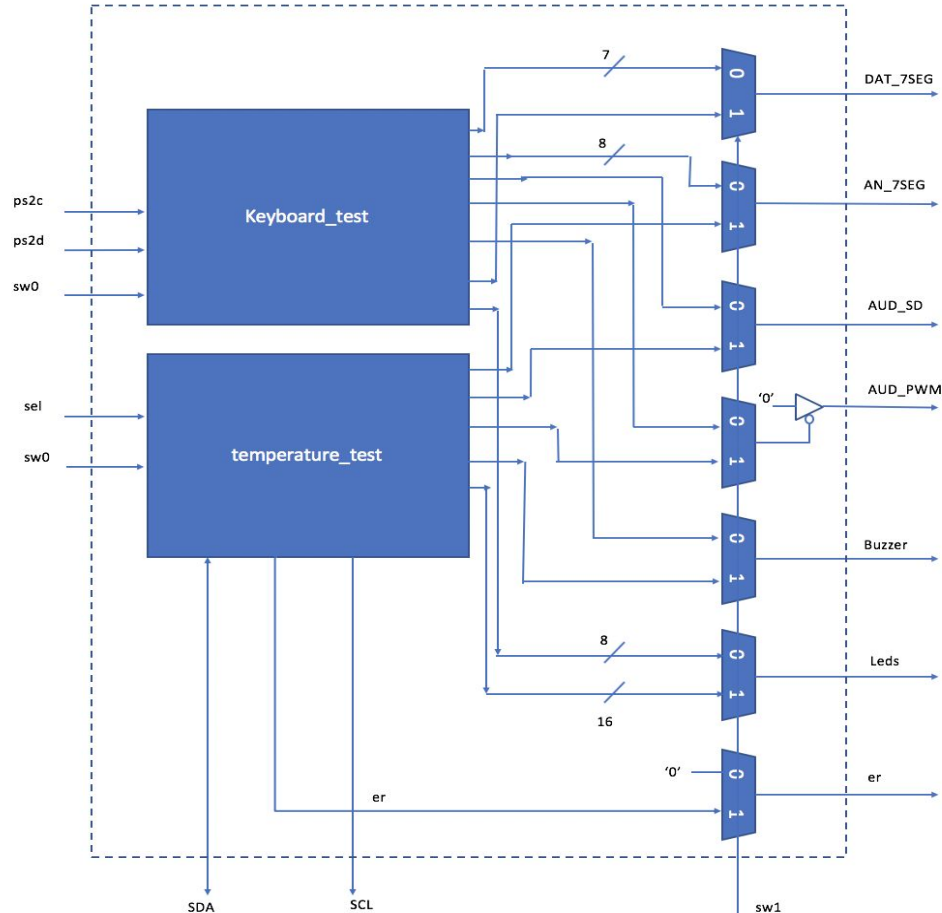


Tones from Keyboard and Temperature Sensor

Arsha Ali, Zhenye Li, Stefanie Kozera

Overview




- **Outputs**

- Mono Audio Output
- Buzzer
- Seven Segment Display
- LEDs

- **Inputs**



- Keyboard or Temp. Sensor
- Mono Audio or Buzzer
- Temperature or Status and ID
- PS/2 signals for keyboard
- I2C signals for temp. sensor

Keyboard

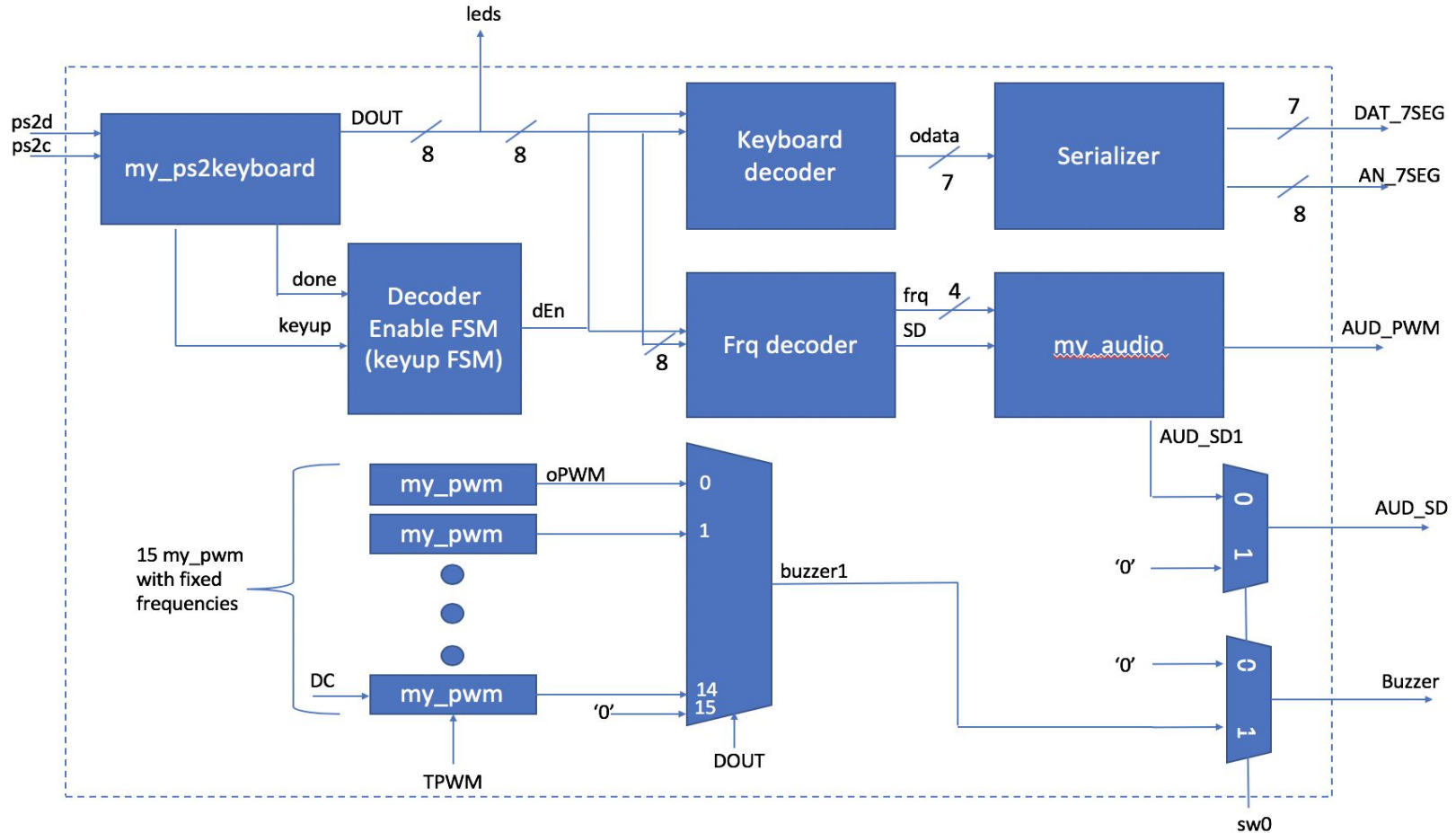


Keyboard

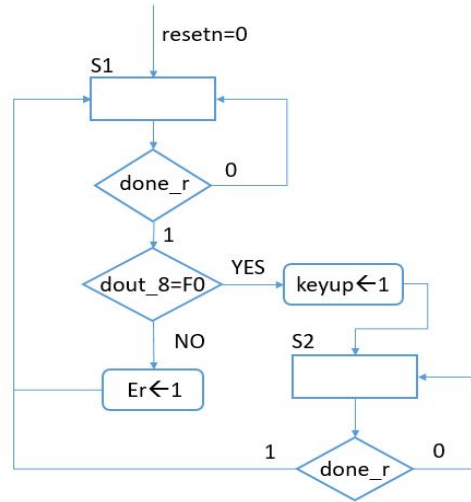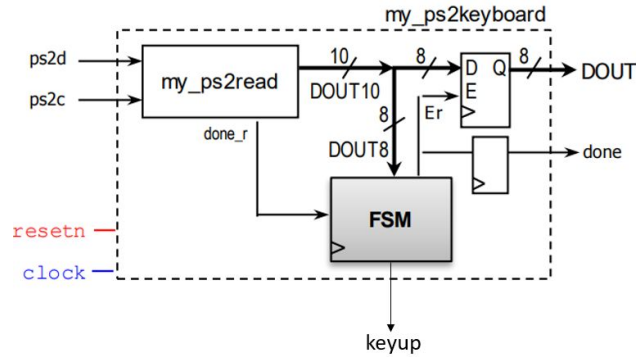- PS/2 Protocol:
 - Scan code sent every 100ms
 - Key up scan code
 - Repeated scan code
- PIC24FJ128 chip
- Enable other blocks only while a key is being pressed




FSM to detect key up scan code

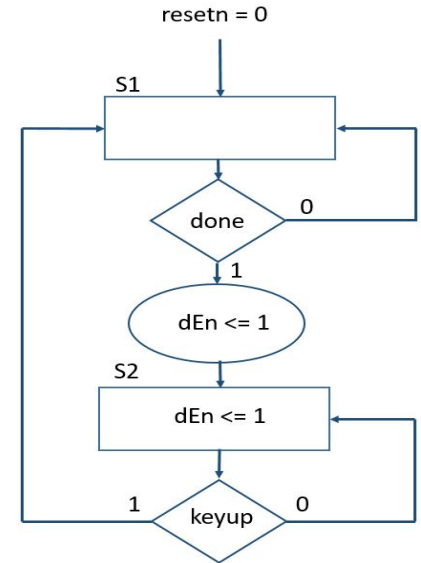



Keyup FSM

Keyboard

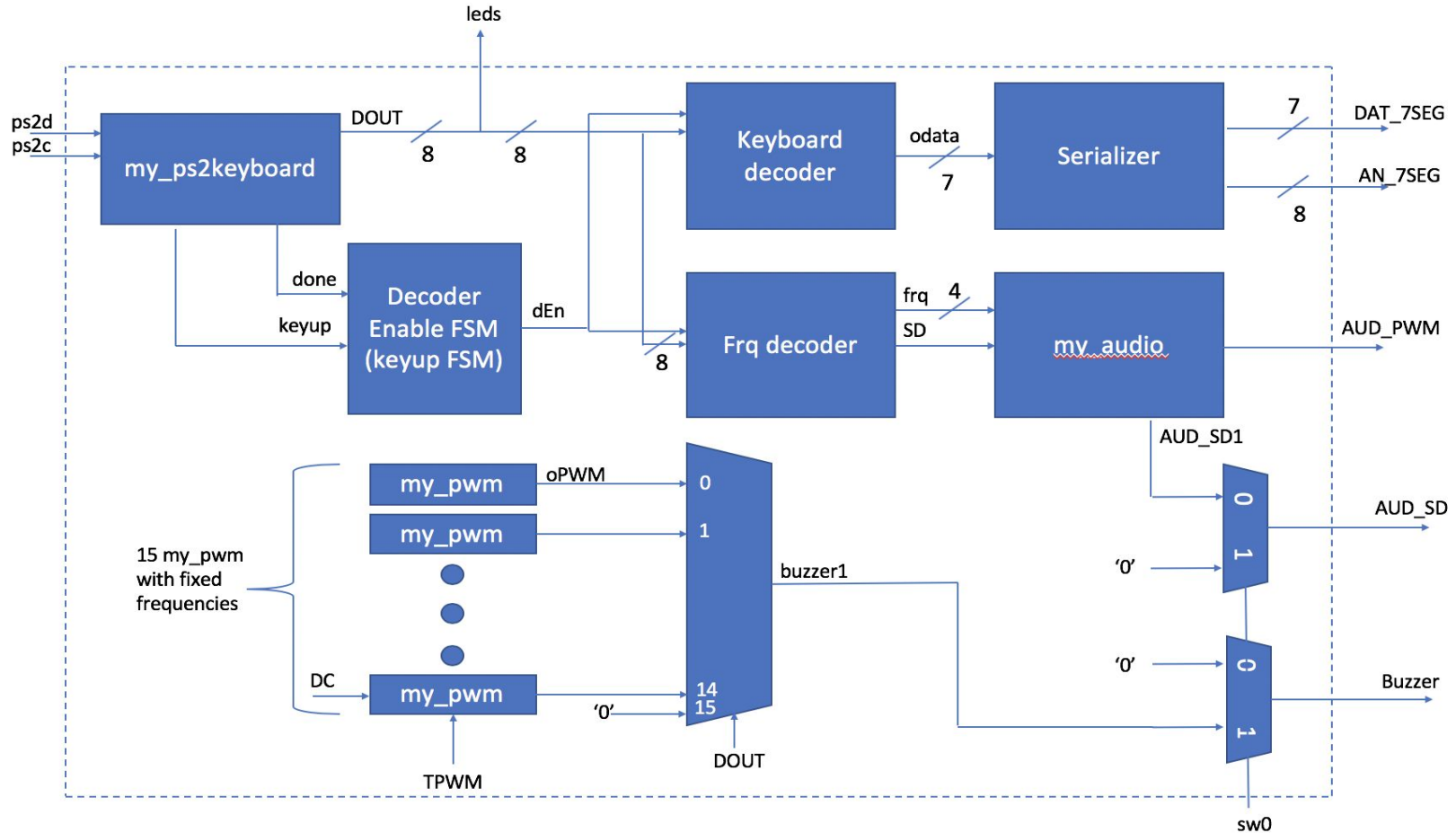


Temperature Sensor

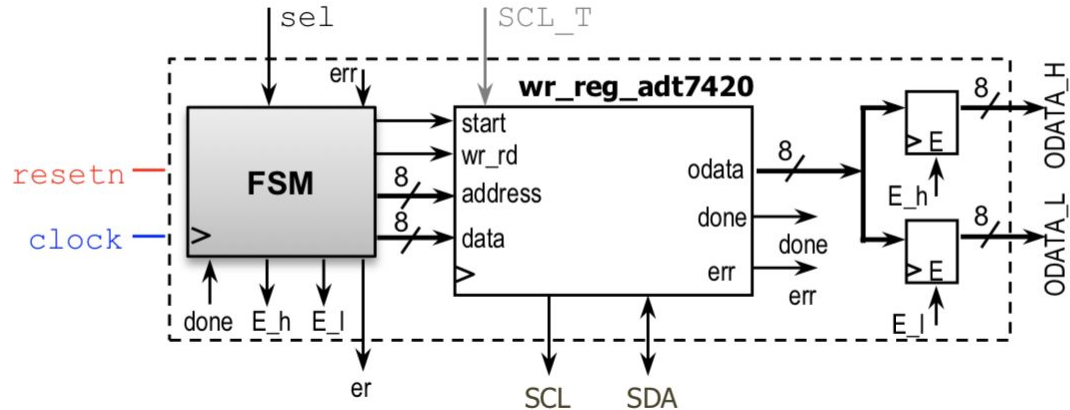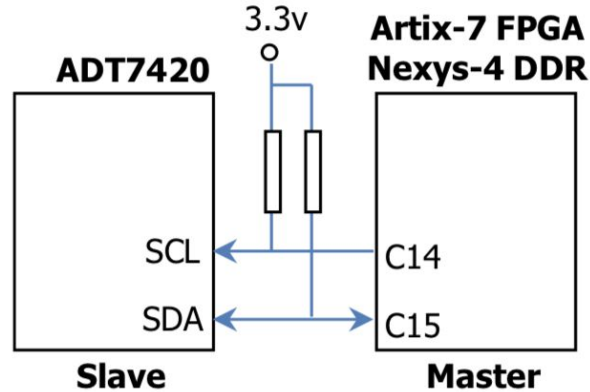
- ADT7420 chip
- 16-bit mode:
 - 0.0078°C resolution
- I²C Interface



Temperature Sensor


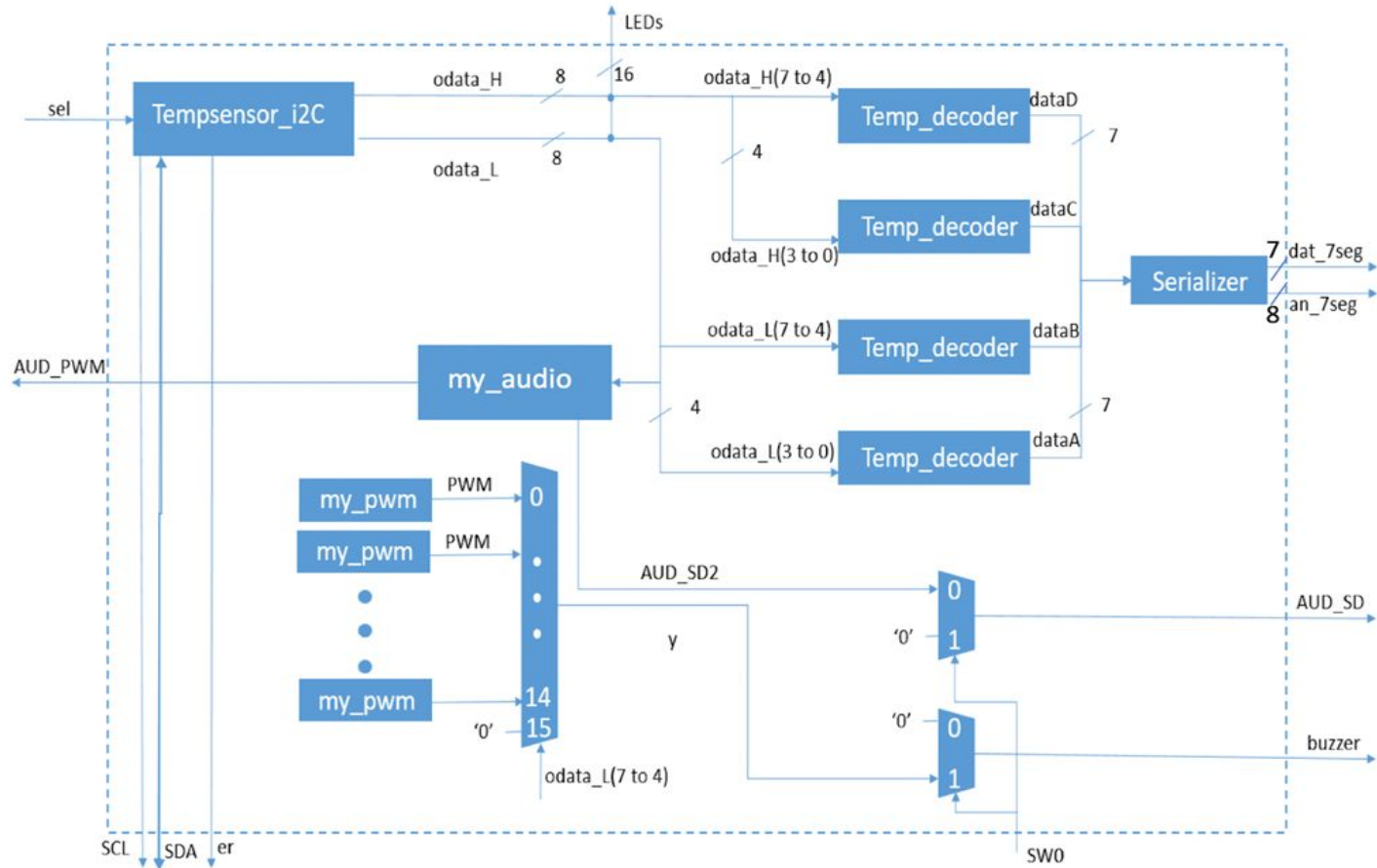


Mono Audio Output

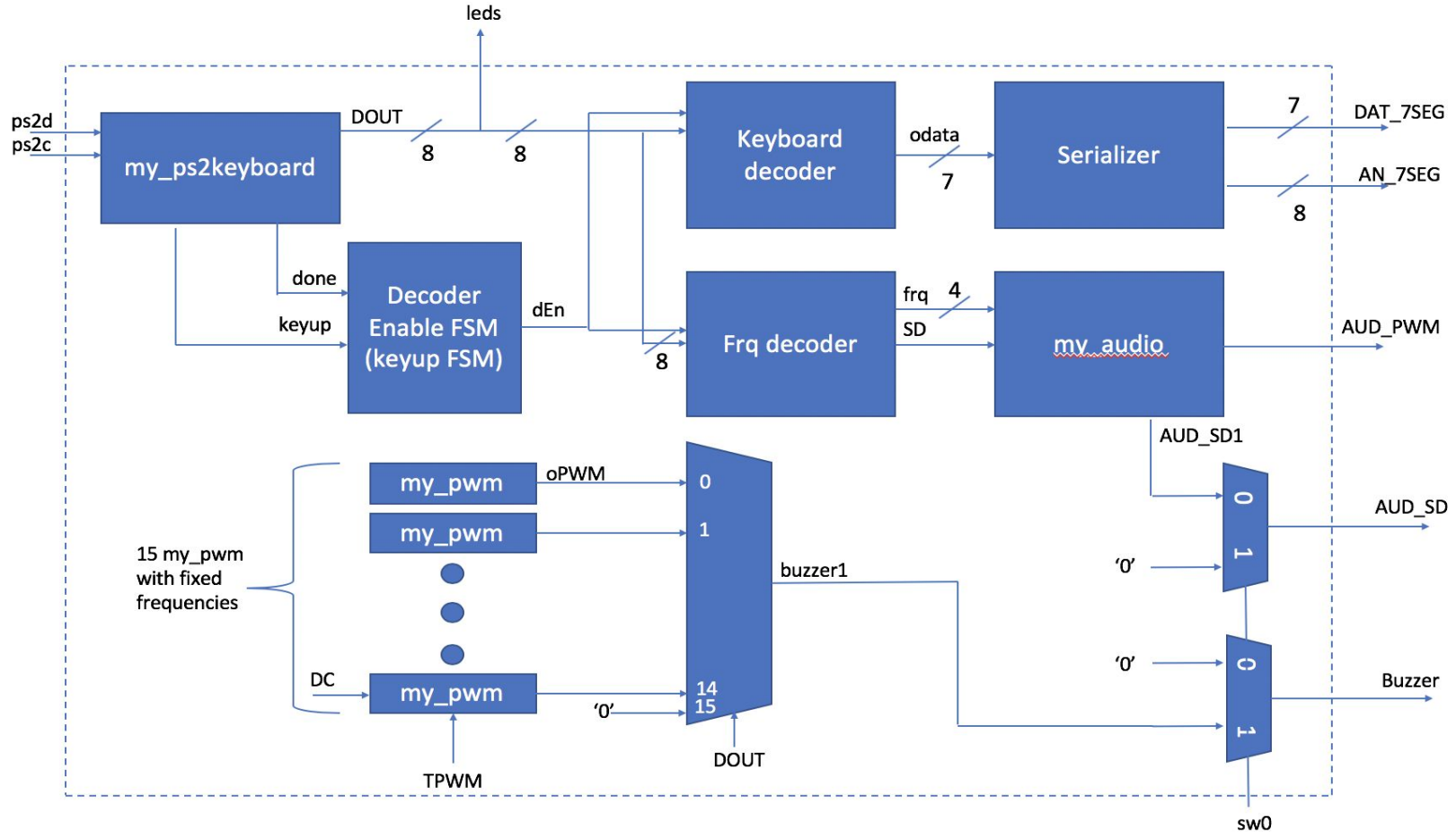


Mono Audio Output - my_audio

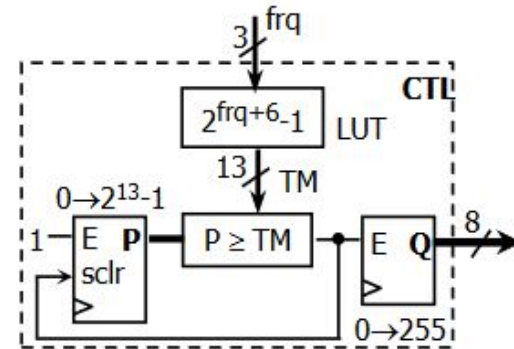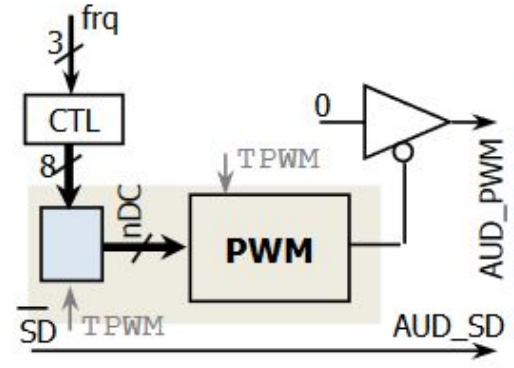- Generates a PWM signal from a 4-bit number
 - Modified from existing code, originally only support for 3-bit number
- The PWM signal with varying duty cycle turned into a sinusoid by a low pass filter on the nexys board




Buzzer

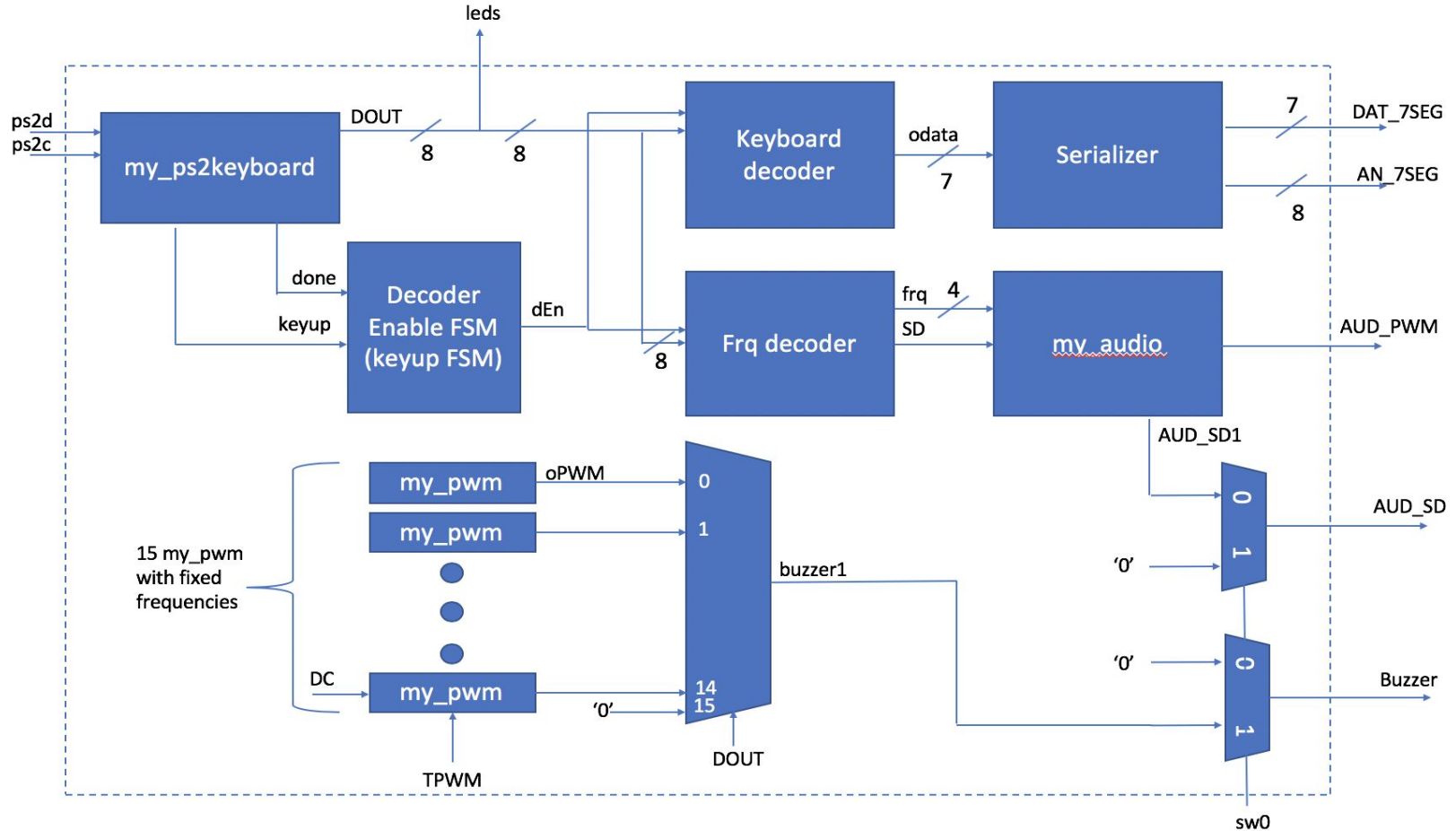


Buzzer - mypwm

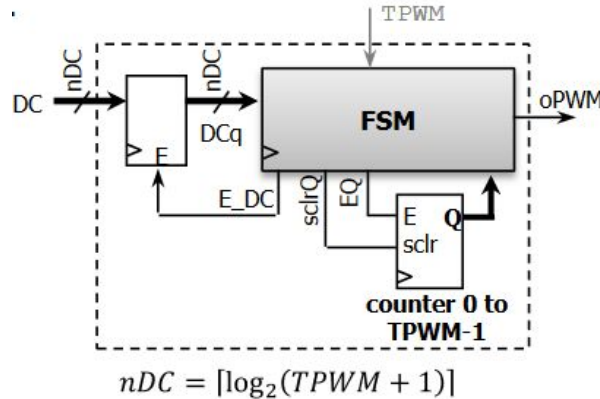- Generates a PWM signal at a fixed frequency
- Sent through a multiplexor and then output onto a buzzer




If $DC = 0 \rightarrow oPWM = 0$



If $DC = TPWM \rightarrow oPWM = 1$

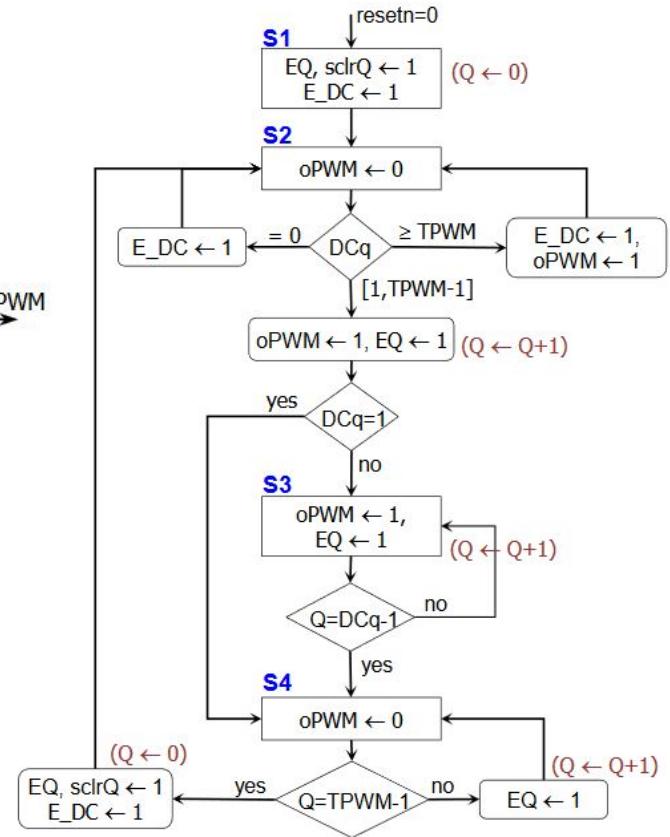

Buzzer and Audio - Temperature Sensor

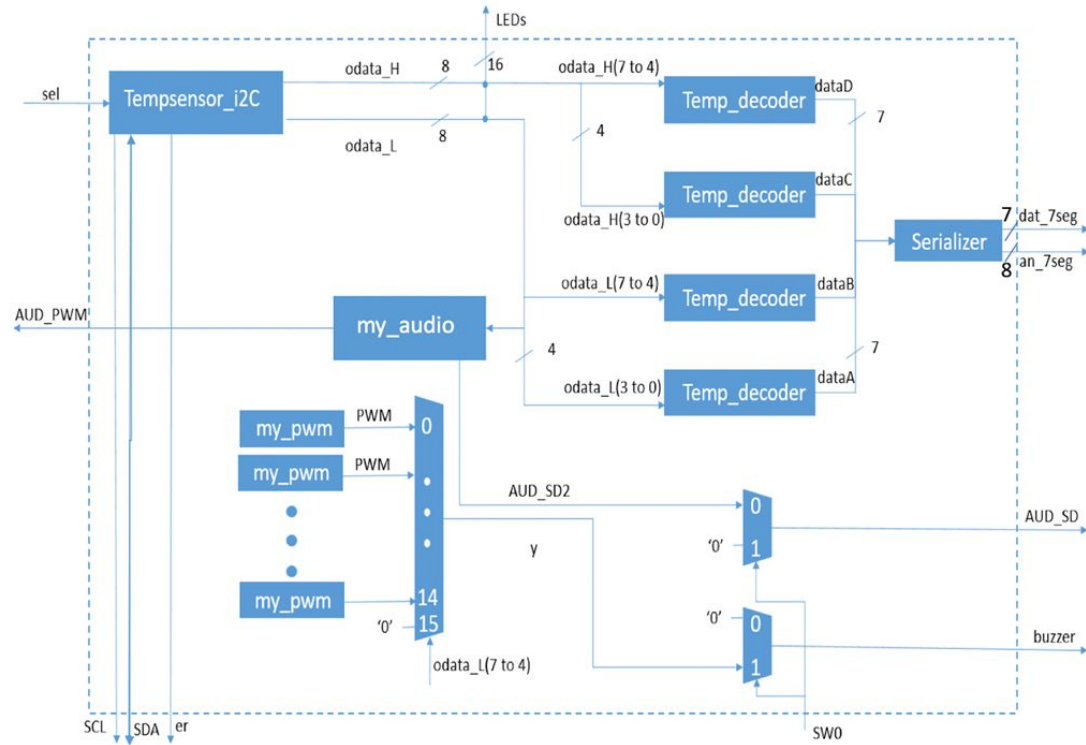

Demo

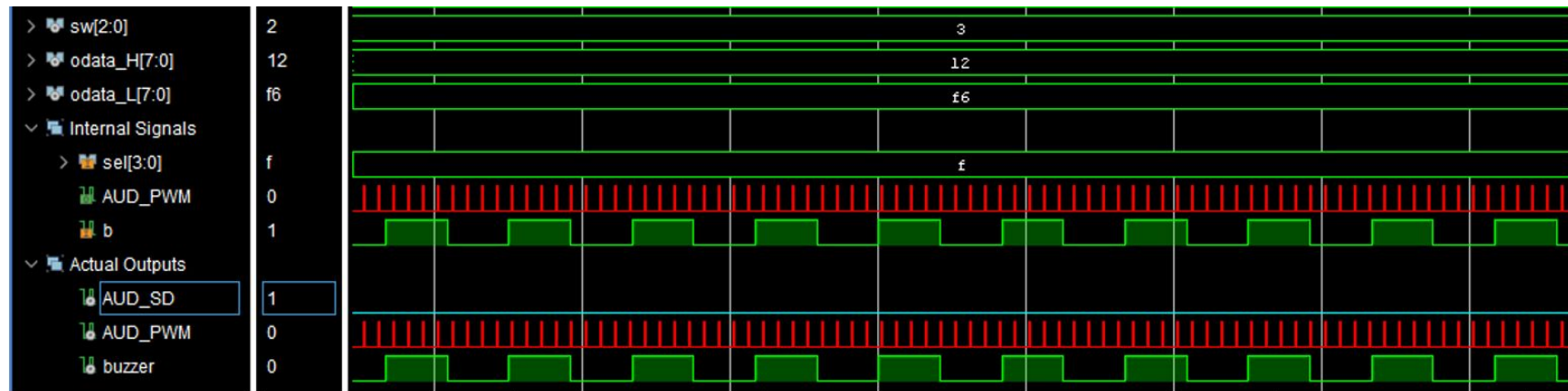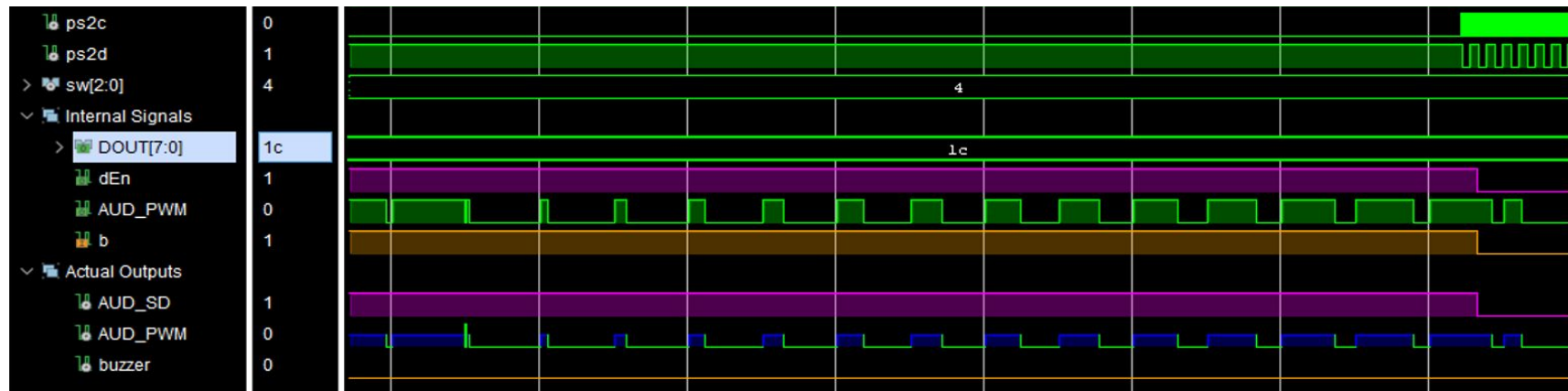

Conclusions

- Keyboard
- Temperature Sensor
- Mono Audio Output
- Buzzer
- Seven Segment Display
- LEDs
- Communication Protocols
- PWM
- PDM

References

- D. Llamocca, “Unit 3-External Peripherals: Interfacing,” Mar. 2019, pp. 2-3, 7-14.,
https://moodle.oakland.edu/pluginfile.php/5005747/mod_resource/content/7/Notes%20-%20Unit%203.pdf
- D. Llamocca, “PS/2 Keyboard Controller (XDC included),”
<http://www.secs.oakland.edu/~llamocca/VHDLforFPGAs.html>
- D. Llamocca, “ADT4720 Temp. Sensor (I2C)-Basic Control (XDC included),”
<http://www.secs.oakland.edu/~llamocca/VHDLforFPGAs.html>
- D. Llamocca, “PWM: Tone control. Mono audio output with Low-Pass Filter (XDC included),” <http://www.secs.oakland.edu/~llamocca/VHDLforFPGAs.html>
- D. Llamocca, “Unit 2: Concurrent Description.” *VHDL Coding for FPGAs*, slides 7-10.,
<http://www.secs.oakland.edu/~llamocca/Tutorials/VHDLFPGA/Unit%202.pdf>