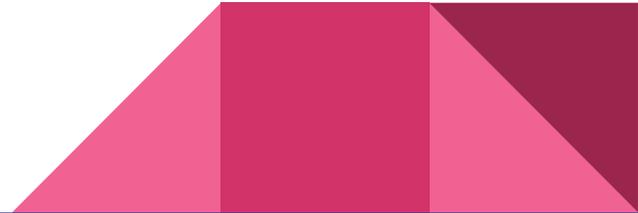


Sound Synthesizer


ECE 4710 - Computer Hardware Design

Matthew Adams, Mohammed Shatit, Thomas Deschutter, Anthony Hamm




The Idea

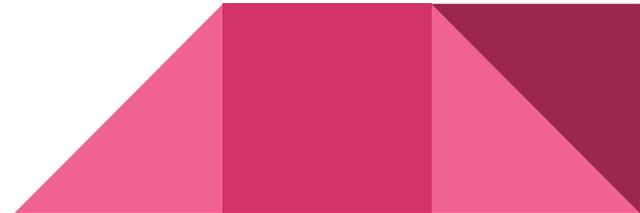- Create a fun tool for musical creativity
- Attempt to emulate a digital keyboard
- Use 16 different keys to produce different notes.
- Features:
 - Notes Display
 - Notes Sustainability
 - Pitch indication




Flowchart

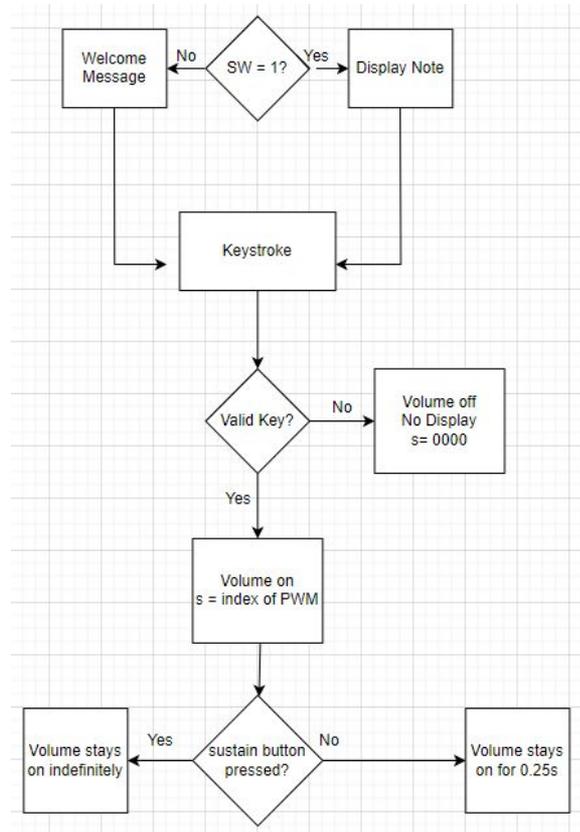


Hardware

- Nexys A7 100-T
- Piezo Buzzer
- Standard USB Keyboard

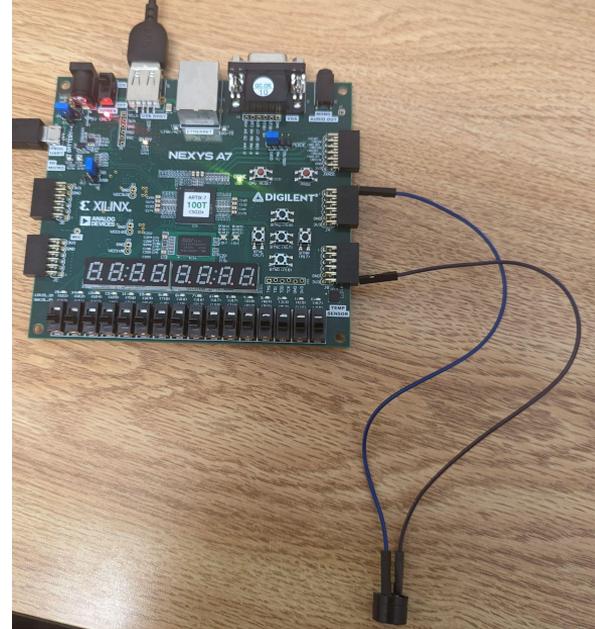– The piezo buzzer has one lead connected to pin **JA1** and the other connected to **ground**




Keyboard Layout

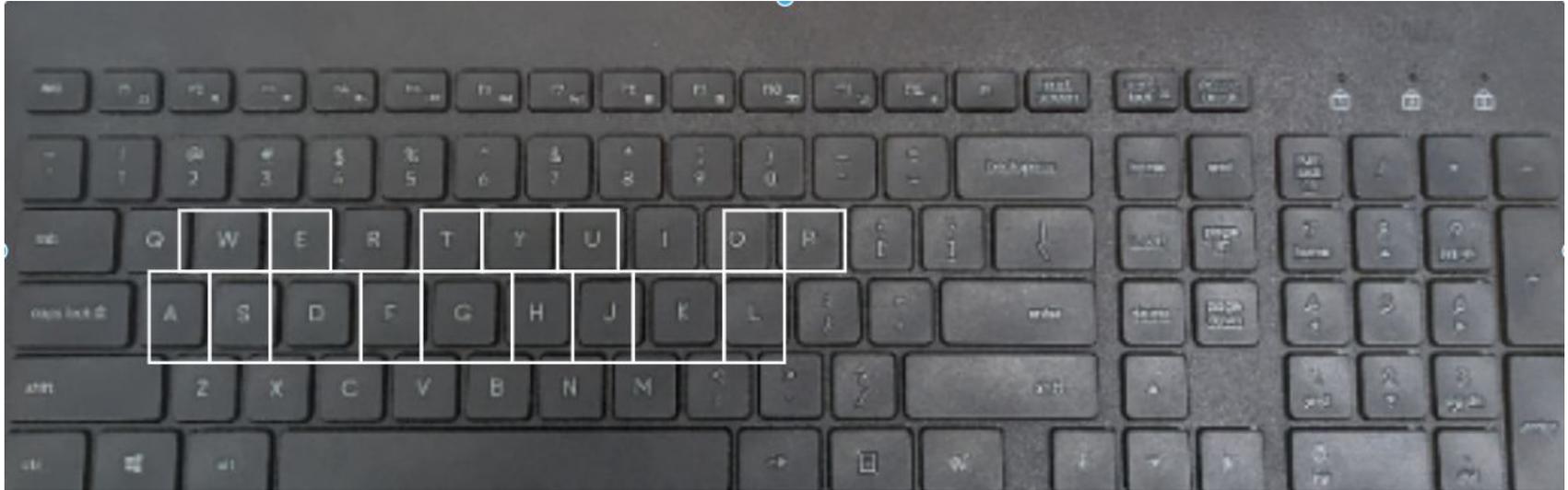


Components

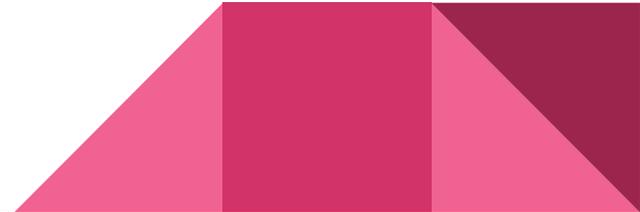- PS/2 Keyboard
- LUT
- MMCM Clock Divider
- 7 Segment Display Module
- 16 PWM Circuits
- 16-to-1 Mux
- FSM




Block Diagram

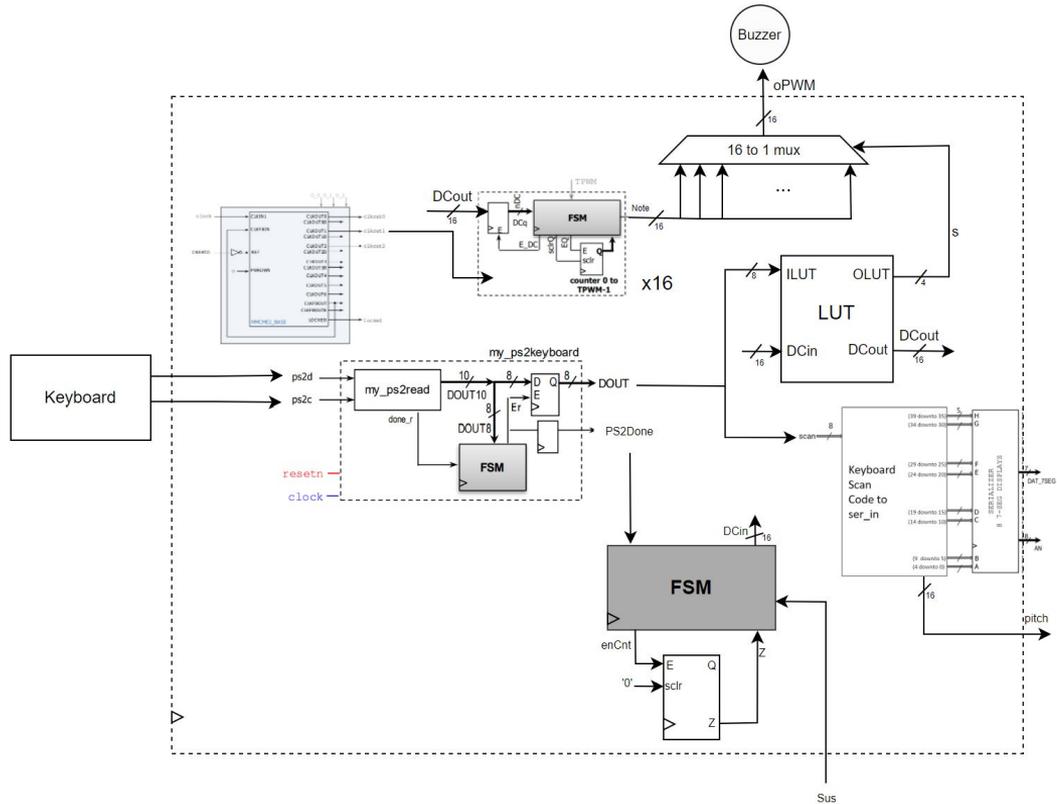


LUT

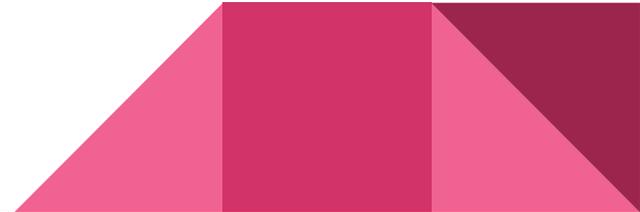- Receives the scancode and duty cycle as inputs
- Outputs the index of the PWM signal the mux should select based on the scancode received
- Outputs the unchanged input duty cycle if one of the 16 keys are pressed
- Outputs a duty cycle of zero if any other key is pressed




LUT

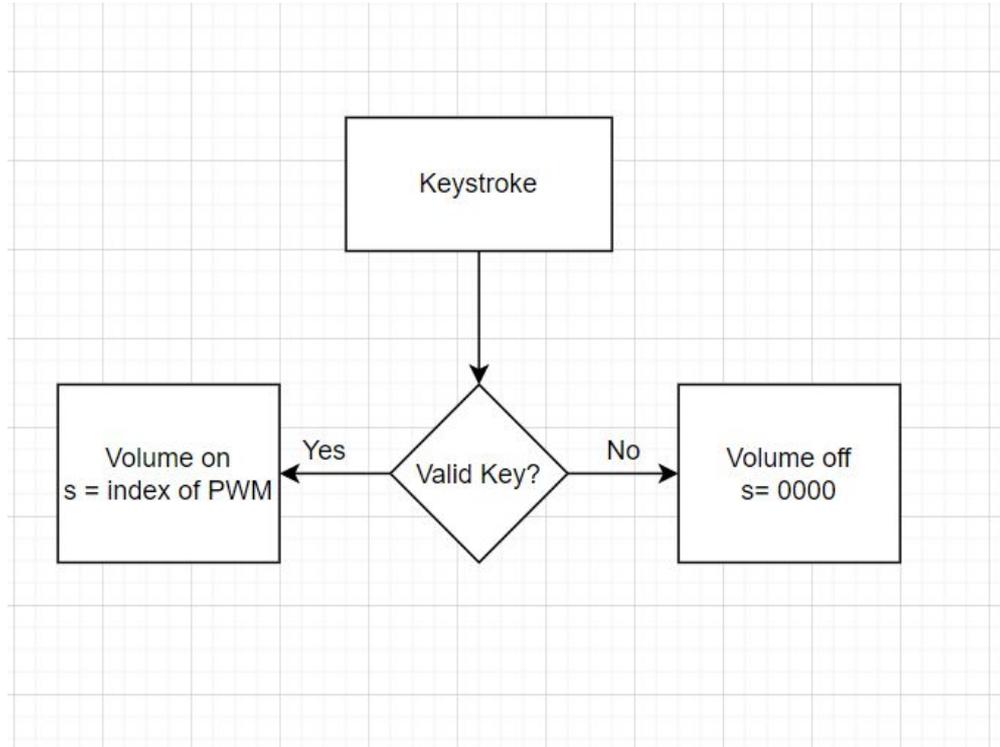


Audio (PWM)

C ₅	523.25	65.93
C [#] ₅ /D ^b ₅	554.37	62.23
D ₅	587.33	58.74
D [#] ₅ /E ^b ₅	622.25	55.44
E ₅	659.25	52.33
F ₅	698.46	49.39
F [#] ₅ /G ^b ₅	739.99	46.62
G ₅	783.99	44.01
G [#] ₅ /A ^b ₅	830.61	41.54
A ₅	880.00	39.20
A [#] ₅ /B ^b ₅	932.33	37.00
B ₅	987.77	34.93
C ₆	1046.50	32.97
C [#] ₆ /D ^b ₆	1108.73	31.12
D ₆	1174.66	29.37
D [#] ₆ /E ^b ₆	1244.51	27.72

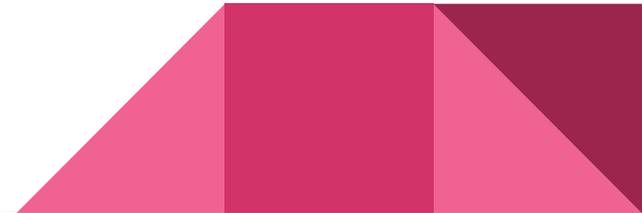


Audio (PWM)

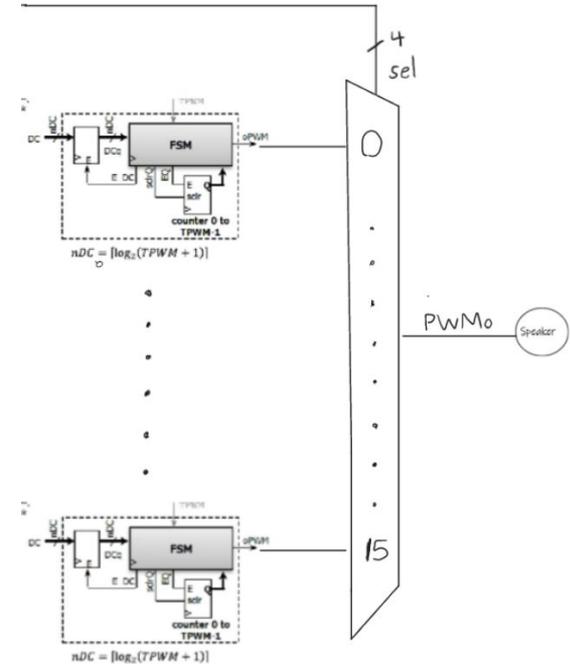- 16 PWM circuits to generate 16 different notes
- Each takes different TPWM for desired frequency
- DCin is the duty cycle signal and it's a constant value (For now)
- The output of these circuits are inputted into a 16-to-1 mux which is controlled by an LUT output.




MMCM Clock Divider

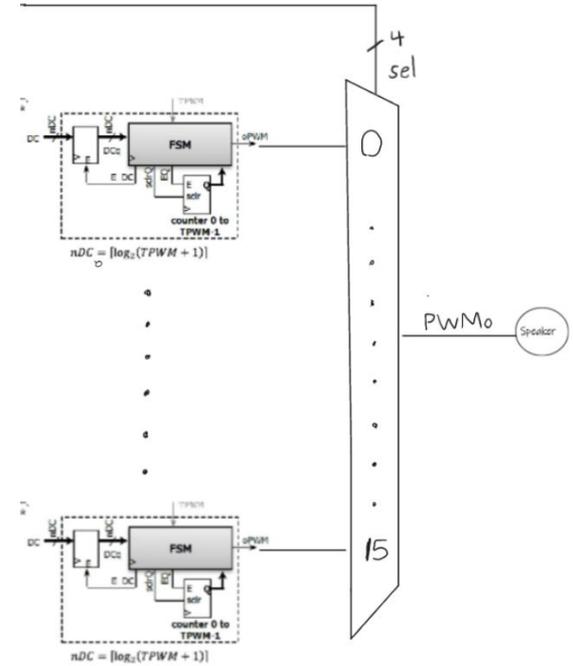- Since on board clock is 100 MHz, the TPWM parameter (integer) cannot go high enough to achieve the desired PWM frequencies.
- We use a clock divider so that the clock of the PWM module is 25 MHz (for lower frequency modules) and 50 MHz (for higher frequency modules)




7 Segment Display Circuit

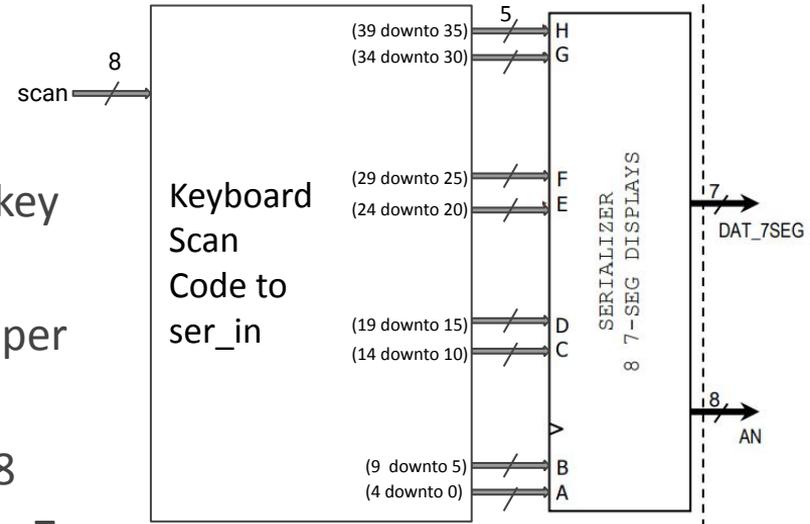
- Controls output to 7 segment display
- Takes 8 bit scan code that identifies the key pressed
- Converts 8 bits to a 40 bit output (5 bits per serializer input)
- Then those 5-bit chunks are sent to the 8 inputs of the serializer which controls the 7 segment displays



FSM

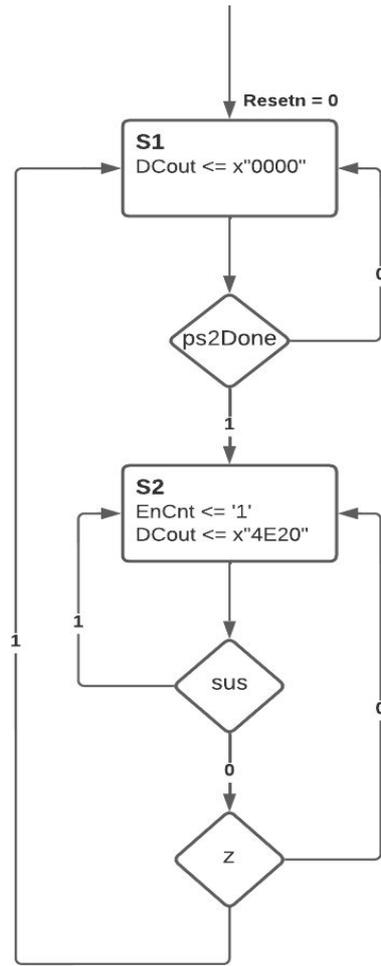

Simulation Results

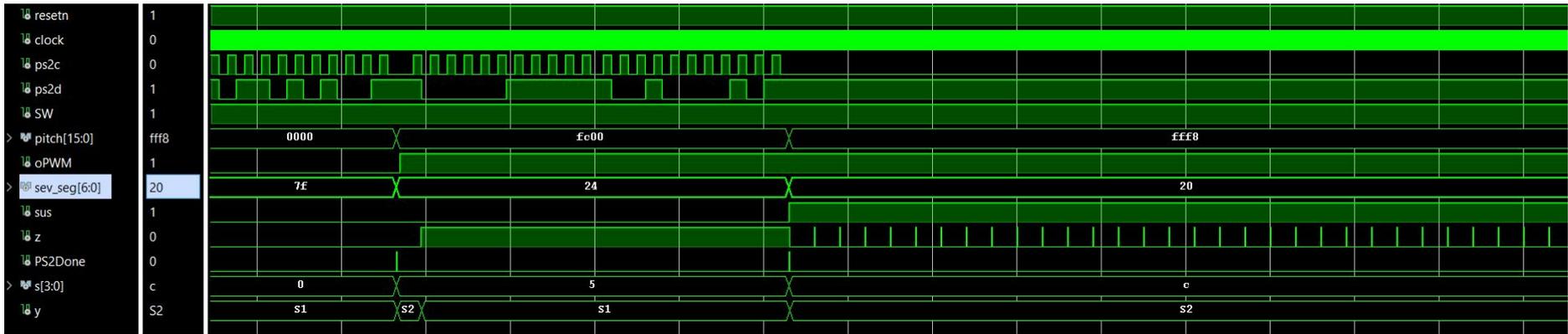

DEMO!