

Laboratory 3

(Due date: **005**: March 6th, **006**: March 7th)

OBJECTIVES


- ✓ Implement a Digital System: Control Unit and Datapath Unit
- ✓ Describe Algorithmic State Machine (ASM) charts in VHDL.
- ✓ Learn interfacing with SPI devices.

VHDL CODING

- ✓ Refer to the [Tutorial: VHDL for FPGAs](#) for parametric code for: Registers, busmux.

FIRST ACTIVITY: ACCELEROMETER DATA RETRIEVER: DESIGN AND SIMULATION (60/100)

- **ACCELEROMETER ADXL362:** This 3-axis MEMS device communicates via a 4-wire SPI and operates as a SPI slave device. We read/write 8-bit data via a register-based interface. ADXL362 parameters (range, resolution, ODR are selectable):
 - ✓ Range: $\pm 2g$ (default at reset), $\pm 4g$, $\pm 8g$.
 - ✓ Resolution: 1mg/LSB (default at reset), 2 mg/LSB, 4 mg/LSB
 - ✓ Output data rate (ODR): 12.5 – 400 Hz. Default at reset: 100 Hz.
 - ✓ Output resolution: 12 bits. Representation: signed.
- **wr_reg_adxl362:** This circuit handles basic SPI communication with the ADXL362. The user provides address, data, and read/write. Then, a read/write transaction is executed via the SPI bus (data structure specified in the ADXL362 datasheet). Use the VHDL code `wr_reg_axl362.vhd` (use all the design .vhd files in [accelerom.zip](#) except `accelerom.vhd`) with `SCLK_T = 105` (cycles of 10 ns in a period of a 1000 Hz SCLK).

 


- **FSMemb:** FSM embedding counters *i* and *j*. It configures 2 ADXL362 registers (`0x1F`, `0x2D`), and then cyclically requests read from 12 8-bit ADXL362 registers containing accelerometer data and places retrieved data on 12 8-bit output registers.
- Data is organized into:
 - ✓ 4 16-bit measurements (X, Y, Z, Temperature). We display this on 16 LEDs (selectable by `sel`). Note that since the actual measurements are only 12-bit wide, the 4 MSBs (of the 16 bits) are sign-extended.
 - ✓ 3 8-bit measurements (low precision X, Y, Z) and 8-bit Status: Shown (as hex) on 8 7-segment displays: `|X|Y|Z|ST|`

- This is the list of registers we deal with in this experiment, which is a basic operation mode. Refer to the ADXL362 datasheet for a full list of registers and operation modes.

Reg. Address	Name	Reg. Address	Name
0x1F	SOFT_RESET	0x0E	XDATA_L
0x2D	POWER_CTL	0x0F	XDATA_H
		0x10	YDATA_L
		0x11	YDATA_H
0x08	XDATA	0x12	ZDATA_L
0x09	YDATA	0x13	ZDATA_H
0x0A	ZDATA	0x14	TEMP_L
0x0B	STATUS	0x15	TEMP_H

 
- 8-display Serializer:** Eight 7-segment displays.



PROCEDURE

- Vivado: Complete the following steps:**

- ✓ Create a new Vivado Project. Select the corresponding Artix-7 FPGA device (e.g.: the XC7A50T-1CSG324 FPGA device for the Nexys A7-50T board).
- ✓ Write the VHDL code for the given circuit. Run Synthesis to clear your circuit of syntax errors as well as to evaluate the warnings.
 - Use the **Structural description**: Create (or re-use) a separate .vhd file for the components and interconnect them all in a top file:
 - Register with enable: my_rege. You need 12 of these units. Use the proper parameters and I/O connections (the input sclr is not used in these registers; however, you still need to assign it a value of '0').
 - Basic AXL362 controller: wr_reg_axl362. Use parameter SCLK_T = 10⁵.
 - 8-display Serializer: It includes its own components (hex-to-7seg decoder, 3-to-8 decoder, counter, BusMUX 8-to-1). You can use the [VHDL code](#) for the 4-display serializer and modify it for 8 displays.
 - Other components: BusMUX 4-to-1, 3-to-8 decoder with enable, 2-to-4 decoder with enable.
- ✓ Write the VHDL testbench (generate a 100 MHz input clock for your simulations).
 - With SCLK_T = 10⁵, we get a SCLK of 1000 Hz. For SPI, this means that a bit is read/written every 1 ms. This is the expected behavior; however, simulating this behavior will take a very long time in our Vivado simulator window. In addition, we need to emulate data coming from the accelerometer (MISO).
 - Thus, for simplicity's sake, and only for simulation purposes we will do the following:
 - Set the parameter SCLK_T=16 for the wr_reg_axl362 block. For SPI, this means that a bit is read/written every 16 clock cycles.
 - In the testbench, set MISO = 1. This means that our accelerometer controller will only read 1's.
 - Input sel. Set it to "00". This way, only the data X_H X_L will be available in ODATA_LEDS.

 

- ✓ Perform Behavioral Simulation of your design. **Demonstrate this to your TA.**
 - To help debug your circuit, add the internal signals to the waveform (e.g.: state, i, j, address, data, odata, done, etc.)
 - Run the simulation for as long as needed to observe the main FSMemb issue the 2 writing commands and 12 reading commands. This is, when the FSMemb goes from S1 to S8, and then returns to S5 for the first time.
 - Here, verify that the signals address, data, w_rd, i, and j behave as expected (see FSMemb ASM diagram).
 - You can observe how the SPI signals (MOSI, MISO, /CS, SCLK) behave for:
 - 2 writing commands.
 - 8 reading commands + 4 reading commands. These reading commands repeat cyclically (S5 to S8).
 - Right after the FSMemb returns to S5 for the first time, verify that data on ODATA_LEDS and on the input to DAT_7SEG is correct (you should see just 1's). You could modify sel in the testbench to select what to display on ODATA_LEDS, but you will just see 1's.
 - DAT_7SEG outputs: It would take a very long time to see changes in the Vivado simulator window (as the transitions in the 8-display serializer occur every 1 ms). Thus, this is better tested in the circuit.

SECOND ACTIVITY: TESTING (40/100)

▪ Vivado: complete the following steps:

- ✓ I/O Assignment: Create the XDC file associated with your board.

- Suggestion (Nexys A7-50T/A7-100T, Nexys 4/DDR):

Board pin names	CLK100MHZ	CPU_RESET	SW1-SW0	LED15-LED0	CA-CG	AN7-AN0
Signal names in code	clock	resetrn	sel1-sel0	ODATA_LEDS[15..0]	DAT7_SEG[6..0]	AN7-AN0
Board pin names	ACL_MISO	ACL_MOSI	ACL_SCLK	ACL_CSN		
Signal names in code	MISO	MOSI	SCLK	/CS		

- ✓ Generate and download the bitstream on the FPGA. Test the circuit. **Demonstrate this to your TA.**
 - **Note:** Do not forget to set the parameter SCLK_T=10⁵ when testing (this is: synthesize, implement, and generate bitstream with this parameter).
 - Low precision data (8-bit XDATA, YDATA, ZDATA) and STATUS should appear on the 7-seg displays.
 - Verify that STATUS is 0x41.
 - High precision data (16-bit X, Y, Z, T): Only one of them appears on the 16 LEDs based on the 2-bit input sel.
 - ODATA_LEDS[15..0]: Verify the 4 MSBs are effectively sign-extended bits. This means that we only need the 12 LSBs: ODATA_LEDS[11..0].
 - Verify that the low precision data (8-bit XDATA, YDATA, ZDATA) on the 7-seg displays match the high precision data (16-bit X, Y, Z) for ODATA_LEDS[11..4]; use sel to select among different high precision measurements.
 - To ensure that you are reading correct data from the accelerometer, check the following:
 - At rest, z should be about 0xC28 (7-seg display: 0xC2). This corresponds to -984mg. When the board is face down, the sign of z should be positive.
 - Feel free to tilt the axes of the FPGA Board to detect changes.

SUBMISSION

- Submit to Moodle (an assignment will be created):
 - ✓ This lab sheet ([as a .pdf](#)) completed (if applicable) and signed off by the TA (or instructor).
 - *Note: The lab assignment has two activities. You get full points of the 1st activity if you demo it by the due date. You can demo the 2nd activity by the due date or late (here, we apply a penalty towards the points of the 2nd activity).*
 - ✓ ([As a .zip file](#)) All the generated files: VHDL code, VHDL testbench, and XDC file. **DO NOT submit the whole Vivado Project.**
 - Your .zip file should only include one folder. Do not include subdirectories.
 - It is strongly recommended that all your design files, testbench, and constraints file be located in a single directory. This will allow for a smooth experience with Vivado.
 - You should only submit your source files AFTER you have demoed your work. Submission of work files without demoing will be assigned NO CREDIT.

TA signature: _____

Date: _____